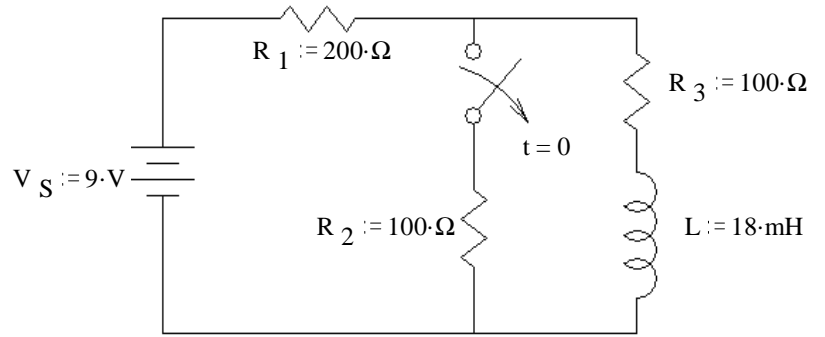


**ECE 2210/00 Exam 2 given: Spring 16** (The space between problems has been removed.)

1. (34 pts) The switch has been closed for a long time and is opened (as shown) at time  $t = 0$ .

a) Find the complete expression for  $i_L(t)$ .




b) What is  $i_L$  when  $t = 1.2\tau$ ?  $i_L(1.2\tau) = ?$

c) At time  $t = 1.2\tau$  the switch is closed again. Find the complete expression for  $i_L(t')$ , where  $t'$  starts at  $t = 1.2\tau$ . Be sure to clearly show the time constant.

2. (18 pts) Find  $Z_{eq}$  in simple polar form (give me numbers).

You must show work and intermediate results.

$f := 1000\text{-Hz}$

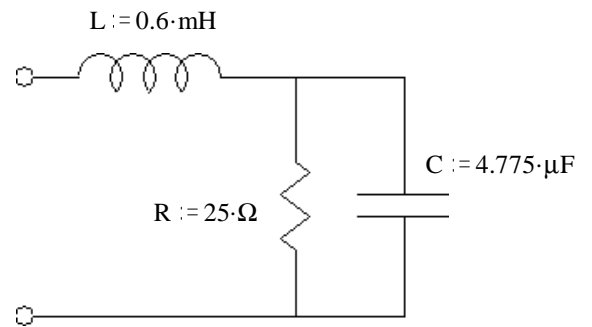


3. (28 pts) For partial credit, you must show work and/or intermediate results.

a) Find  $I_2$

b) Find  $V_S$  in polar form.

c) Find  $I_1$  in polar form.


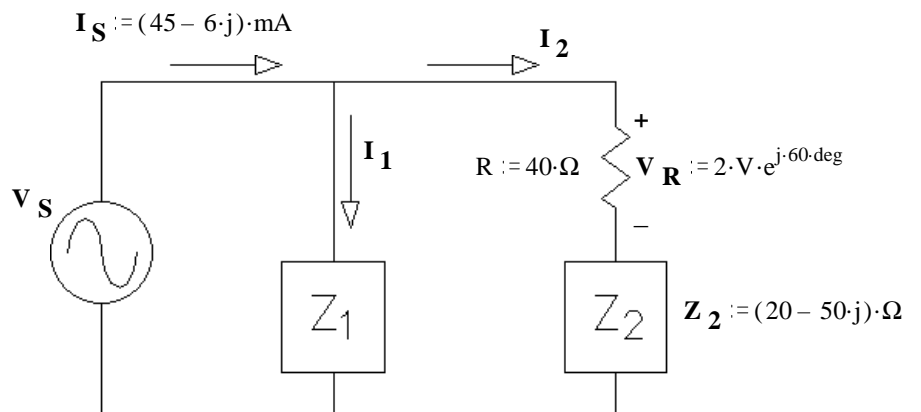


4. 20 pts) The voltage across a capacitor is shown below. Make an accurate drawing of the capacitor current. Make reasonable assumptions where necessary. Label your graph.

Note: You will be graded on the accuracy of your plot at 0, 1, 5 and 8 ms, so calculate those values and plot or label them carefully. Between those points your plot must simply be the correct shape.

You **MUST SHOW** how you calculate your values starting from the original relationships between voltage and current.

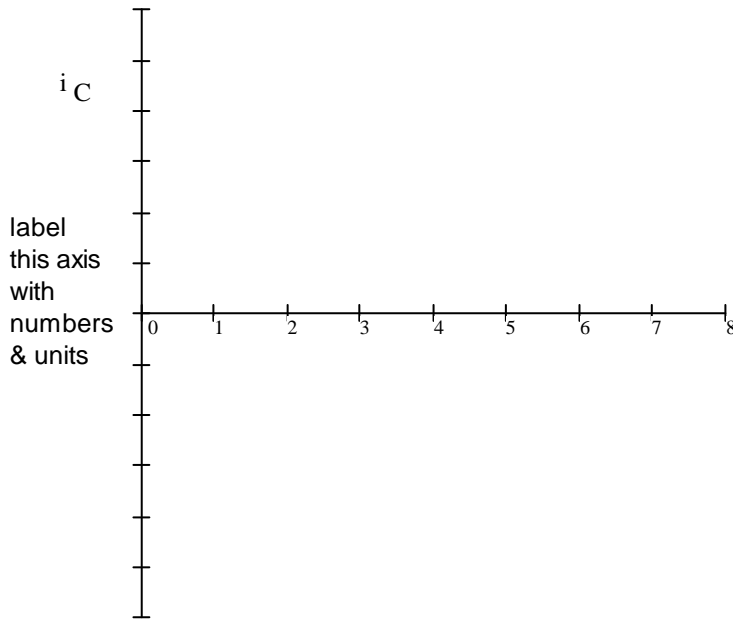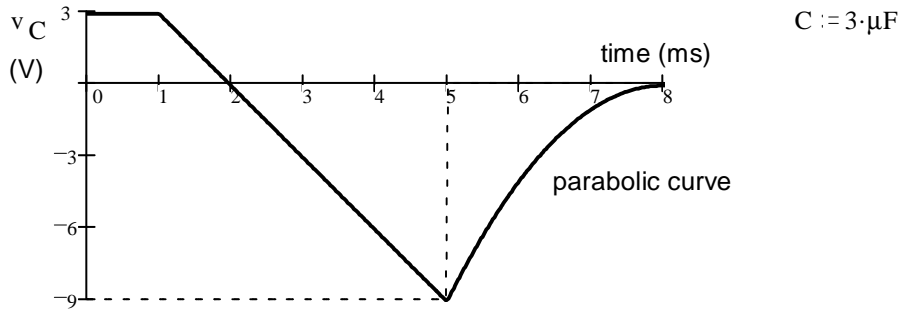That is: **Start with the interger and/or differential equations for the capacitor!**



**Answers**

Folder Number \_\_\_\_\_

1. a)  $30 \cdot \text{mA} - 12 \cdot \text{mA} \cdot e^{\frac{-t}{60 \cdot \mu\text{s}}}$

b)  $26.4 \cdot \text{mA}$

c)  $18 \cdot \text{mA} + 8.4 \cdot \text{mA} \cdot e^{\frac{-t}{108 \cdot \mu\text{s}}}$

2.  $18.0 \Omega \angle -27.2^\circ$

3. a)  $50 \cdot \text{mA} \cdot e^{j \cdot 60 \cdot \text{deg}}$

b)  $53.2 \cdot \text{mA} \cdot e^{-j \cdot 67.9 \cdot \text{deg}}$

b)  $3.905 \cdot \text{V} \cdot e^{j \cdot 20.2 \cdot \text{deg}}$

4.

