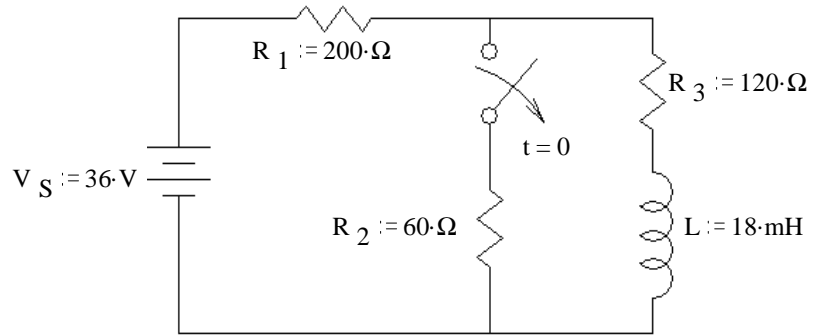


# ECE 2210/00 Exam 2 given: Spring 17

(The space between problems has been removed.)

1. (32 pts) The switch has been closed for a long time and is opened (as shown) at time  $t = 0$ .

a) Find the complete expression for  $i_L(t)$ .




b) Find  $i_L$  at time  $t = 1.5\tau$ .  $i_L(1.5\tau) = ?$

c) At time  $t = 1.5\tau$  the switch is closed again. Find the complete expression for  $i_L(t')$ , where  $t'$  starts when the switch closes. Be sure to clearly show the time constant.

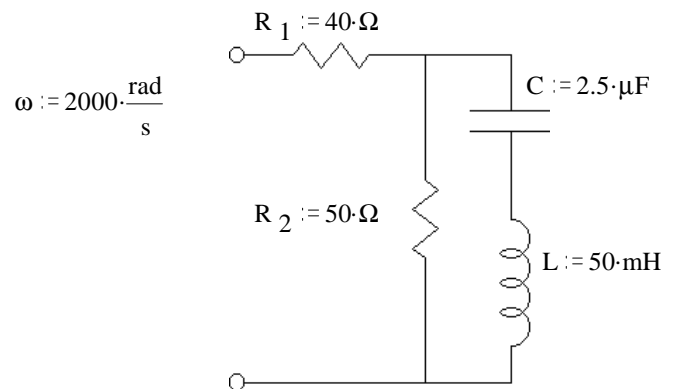3. (21 pts) Find  $Z_{eq}$  in simple polar form (give me numbers).

For partial credit, you must show work and/or intermediate results.




3. (26 pts)

a) Find  $Z_2$

$$I_{Z1} = 63.383 + 46.988j \text{ mA} = 78.9 \text{ mA} \angle 36.55^\circ$$

$$I_{Z2} = 18.794 + 6.84j \text{ mA}$$

$$= 20 \text{ mA} \angle 20^\circ$$

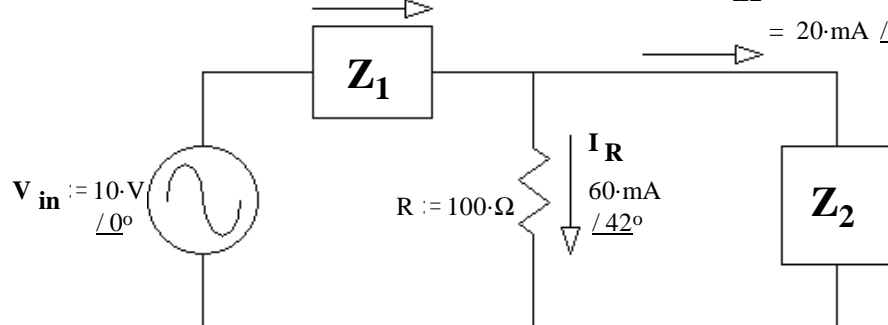

b) Find  $Z_1$  in polar form.

3. c) Circle the best, most comprehensive answer:



- i)  $Z_1$  must contain a capacitor
- ii)  $Z_1$  must contain a resistor and a capacitor
- iii)  $Z_1$  must contain an inductor
- iv)  $Z_1$  must contain a resistor and an inductor

4. 21 pts) The voltage across a capacitor is shown below. Make an accurate drawing of the capacitor current. Make reasonable assumptions where necessary. Label your graph.

Note: You will be graded on the accuracy of your plot at 0, 1, 5 and 8 ms, so calculate those values and plot or label them carefully. Between those points your plot must simply be the correct shape.


You **MUST SHOW** how you calculate your values starting from the original relationships between voltage and current.

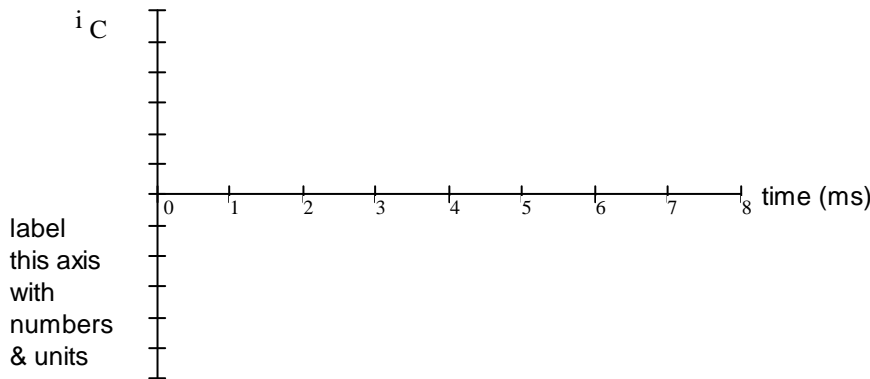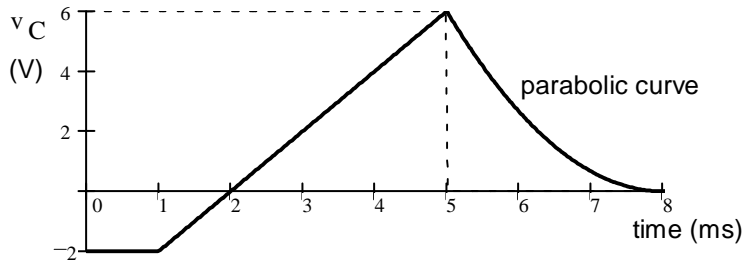That is: **Start with the interger and/or differential equations for the capacitor!**



**Answers** Folder Number \_\_\_\_\_

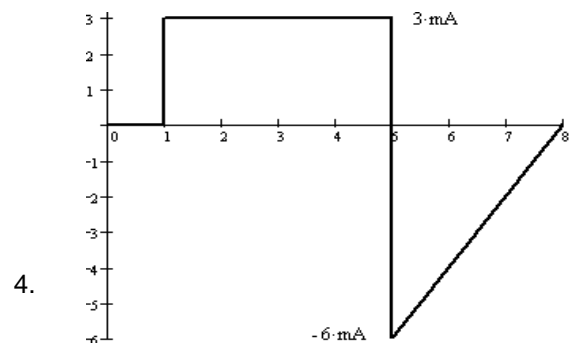- 1. a)  $112.5 \cdot \text{mA} - 62.5 \cdot \text{mA} \cdot e^{\frac{-t}{56.25 \cdot \mu\text{s}}}$
- b)  $98.6 \cdot \text{mA}$
- c)  $50 \cdot \text{mA} + 48.6 \cdot \text{mA} \cdot e^{\frac{-t'}{108.3 \cdot \mu\text{s}}}$
- 2.  $82.5 \Omega / -14.0^\circ$
- 3. a)  $300 \Omega / 22^\circ$     b)  $86.7 \Omega / -72.5^\circ$     c) ii)



4.