

# ECE 2210/00 Exam 2 given: Fall 13

(The space between problems has been removed.)



1. (35 pts) The switch has been closed for a long time and is opened (as shown) at time  $t = 0$ .

a) Find the complete expression for  $i_L(t)$ .

b) Find  $i_L$  at time  $t = 2\tau$ .  $i_L(2\tau) = ?$

c) At time  $t = 2\tau$  the switch is closed again. Find the complete expression for  $i_L(t')$ , where  $t'$  starts when the switch opens. Be sure to clearly show the time constant.

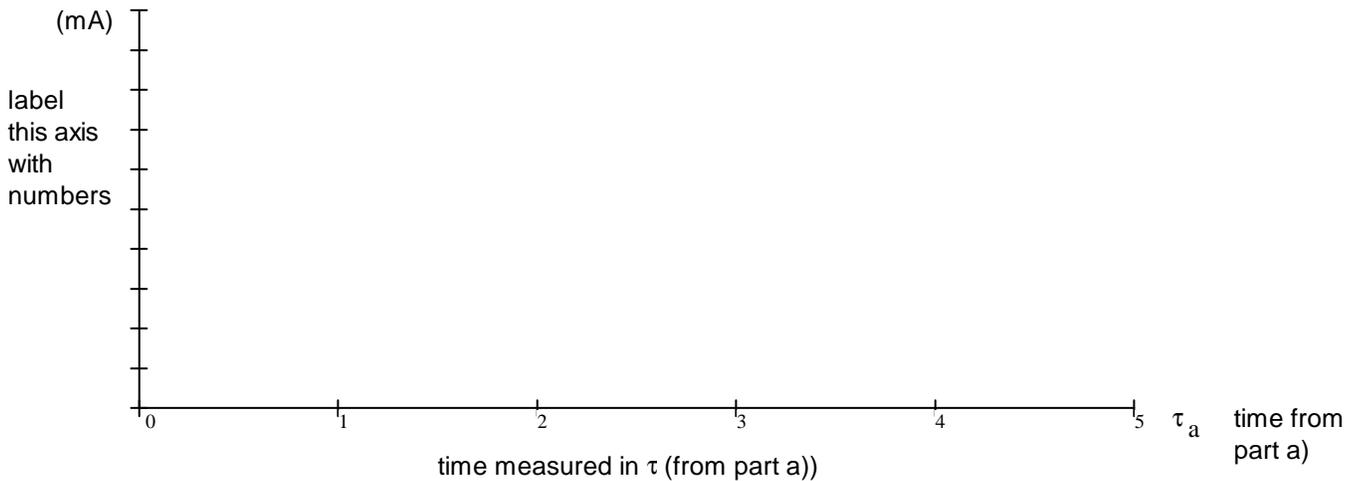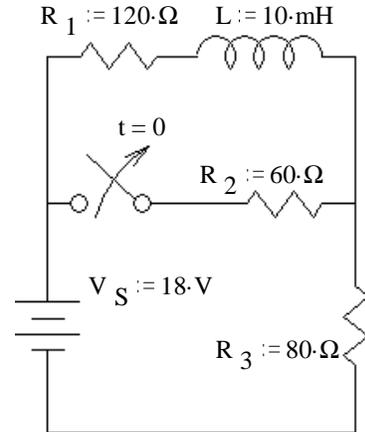
d) Draw a sketch of the inductor current below. Show values on the vertical scale. The horizontal scale is marked in units of  $\tau$  from part a).



2. (22 pts) Find  $Z_{eq}$  in simple polar form (give me numbers).


For partial credit, you must show work and/or intermediate results.

$$f = 636.62 \cdot \text{Hz}$$

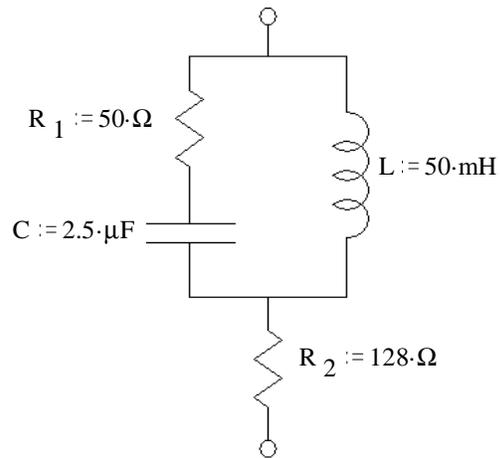


3. (27 pts)  $V_a$  is the nodal voltage at node a and  $V_b$  is the nodal voltage at node b.

a) Find  $Z_2$ .

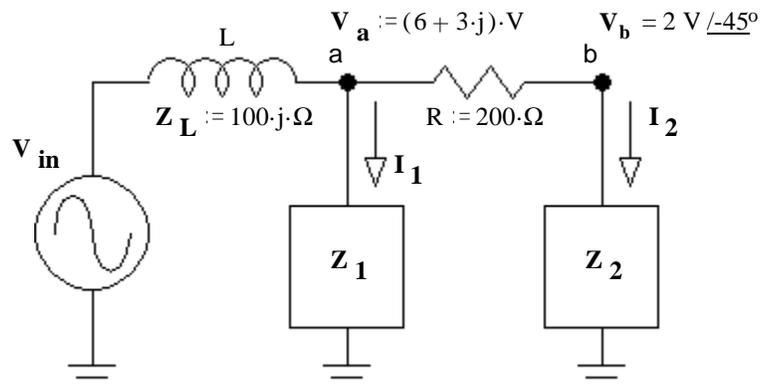

b)  $I_1 := (20 - 30j) \cdot \text{mA}$  Find  $V_{in}$ .

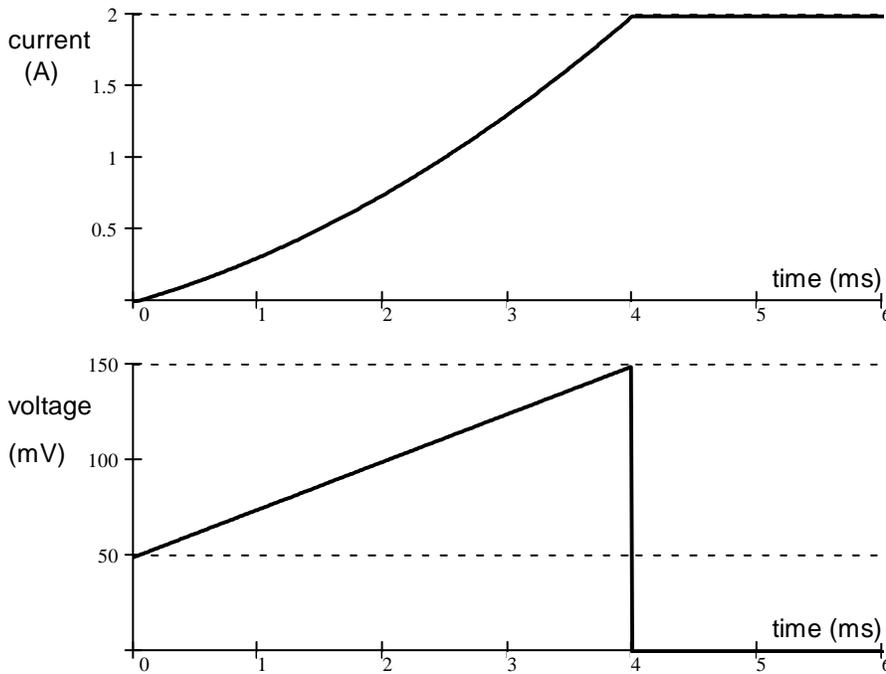4. (16 pts) a) The current through some part and the voltage across the same part are shown below. Tell me what kind of part it is.



b) Find the part's value.

**Answers**

1. a)  $90 \cdot \text{mA} - 40 \cdot \text{mA} \cdot e^{\frac{-t}{50 \cdot \mu\text{s}}}$       b) 84.6 mA

c)  $50 \cdot \text{mA} + 34.6 \cdot \text{mA} \cdot e^{\frac{-t}{64.8 \cdot \mu\text{s}}}$

2.  $312 \Omega \angle -22.6^\circ$

3. a)  $62.8 \Omega \angle -88.9^\circ$       b)  $9.97 \text{ V} \angle 47^\circ$

4. a) inductor      b) 0.2 mH

