

Folder no. _____ Name: _____

ECE 2210 / 00

Spring 2020 Exam 2

Useful Information

$$C = \frac{Q}{V} \quad v_C = \frac{1}{C} \int_{-\infty}^t i_C dt = \frac{1}{C} \int_0^t i_C dt + v_C(0) \quad \Delta v_C = \frac{1}{C} \int_{t_1}^{t_2} i_C dt$$



$$\text{farad} = \frac{\text{coul}}{\text{volt}} = \frac{\text{amp}\cdot\text{sec}}{\text{volt}} \quad i_C = C \cdot \frac{d}{dt} v_C$$

parallel: $C_{eq} = C_1 + C_2 + C_3 + \dots$ **series:** $C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots}$

$W_C = \frac{1}{2} \cdot C \cdot V_C^2$ Capacitor voltage **cannot** change instantaneously

$$\text{henry} = \frac{\text{volt}\cdot\text{sec}}{\text{amp}} \quad i_L = \frac{1}{L} \int_{-\infty}^t v_L dt = \frac{1}{L} \int_0^t v_L dt + i_L(0) \quad \Delta i_L = \frac{1}{L} \int_{t_1}^{t_2} v_L dt$$

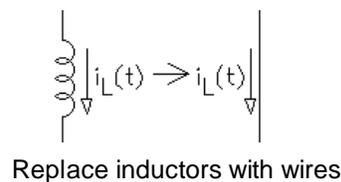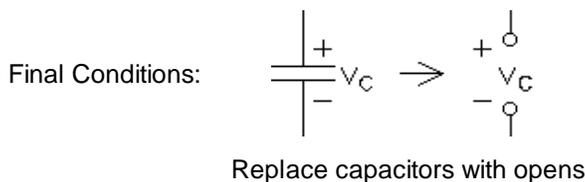$W_L = \frac{1}{2} \cdot L \cdot I_L^2$ $v_L = L \cdot \frac{d}{dt} i_L$ Inductor current **cannot** change instantaneously



For all first order transients: $x(t) = x(\infty) + (x(0) - x(\infty)) \cdot e^{-\frac{t}{\tau}}$ $\tau = R_{Th} \cdot C$ OR $\frac{L}{R_{Th}}$

Resonance: $\omega_0 = \frac{1}{\sqrt{L_{eq} \cdot C_{eq}}}$

Steady-state sinusoidal AC Impedances: $Z_C = \frac{1}{j \cdot \omega \cdot C} = \frac{-j}{\omega \cdot C}$ $Z_L = j \cdot \omega \cdot L$ $\omega = 2 \cdot \pi \cdot f$

$A = |\mathbf{A}| = \sqrt{a^2 + b^2}$ $\theta = \arg(\mathbf{A}) = \text{atan}\left(\frac{b}{a}\right)$ $a = A \cdot \cos(\theta)$ $b = A \cdot \sin(\theta)$

March 4, 2020
 Closed Book, Closed notes, Calculators OK
 Show all work to receive credit
 Circle answers, show units, and round off reasonably


ECE 2210/00 Exam 2 given: Spring 20

(Some space has been removed)

1. (32 pts) The switch has been closed for a long time and is opened (as shown) at time $t = 0$.

a) Find the initial and final conditions and write the full expression for $v_C(t)$, including all the constants that you find.

$$I_S := 30\text{-mA}$$

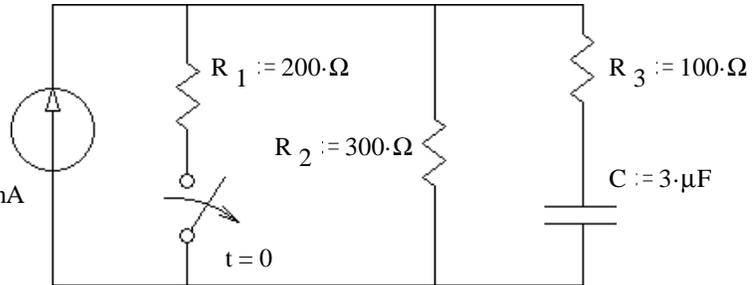

b) What is v_C when $t = 2\tau$?


c) At time $t = 2\tau$ the switch is closed again. Find the complete expression for $v_C(t')$, where t' starts when the switch closes. Be sure to clearly show the time constant.

ECE 2210/00 Exam 2 Spring 20 p2

3. (22 pts) Find Z_{eq} in simple polar form (give me numbers).


For partial credit, you must show work and/or intermediate results.

$$f := 159.155 \cdot \text{Hz}$$

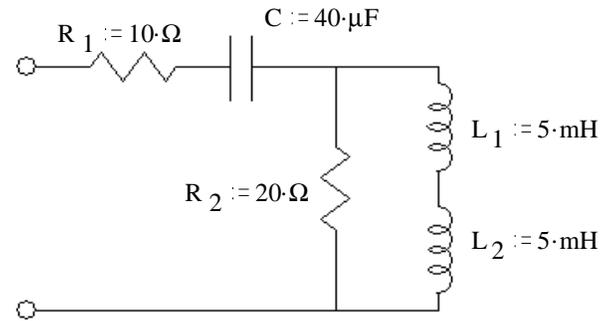

3. (28 pts) V_a is the nodal voltage at node a and V_b is the nodal voltage at node b.

a) Find Z_2 in polar form


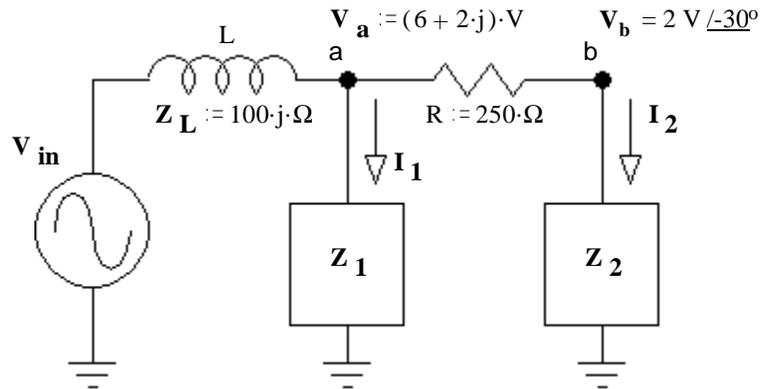


b) $I_1 := (20 - 25j) \cdot \text{mA}$ Find V_{in} .

ECE 2210/00 Exam 2 Spring 20 p3

4. (18 pts) The current through some part and the voltage across the same part are shown below.

a) Tell me what kind of part it is.

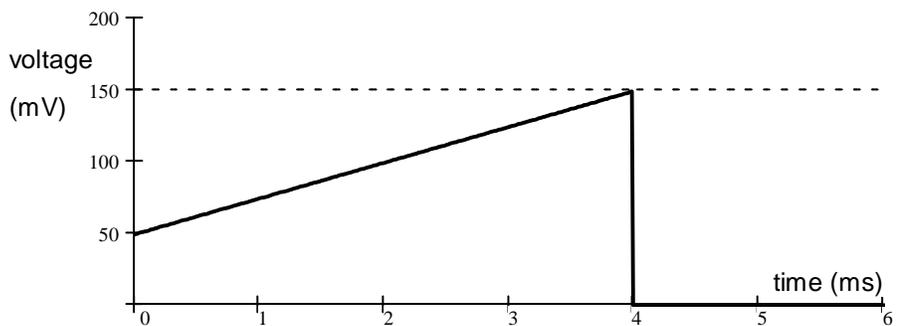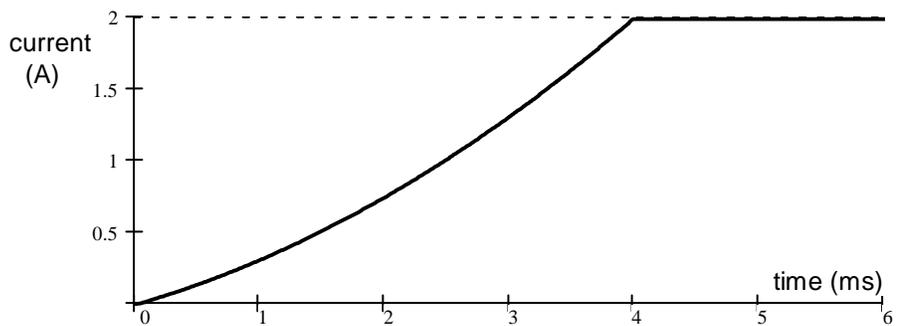

b) Find the part's value.

Answers

1. a) $9 \cdot V - 5.4 \cdot V \cdot e^{\frac{-t}{1.2 \cdot \text{ms}}}$ b) $8.27 \cdot V$ c) $3.6 \cdot V + 4.67 \cdot V \cdot e^{\frac{-t'}{660 \cdot \mu\text{s}}}$ 2. $22.0 \Omega \angle -50.5^\circ$
 3. a) $95.8 \Omega \angle -65.1^\circ$ b) $7.3 + 5.71j \text{ V} = 9.27 \text{ V} \angle 38.0^\circ$ 4. a) inductor b) $0.2 \cdot \text{mH}$