

ECE2210/00 Exam 3 given: Fall 06

1. (18 pts)


a) Find V_{in} in polar form.

b) Find I_T in polar form..

c) Circle 1:

i) The source current leads the source voltage

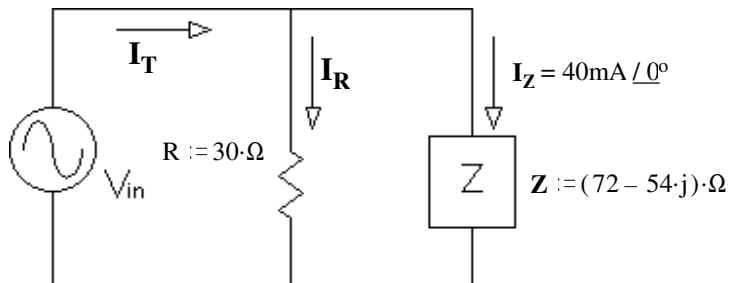ii) The source voltage leads the source current




2. (15 pts) a) Find the s-type transfer function of the circuit shown.

V_i is the input and V_o is the output.

You MUST show work to get credit.

Simplify your expression for $H(s)$ so that the denominator is a simple polynomial beginning with s^2 .

$H(s) = ?$

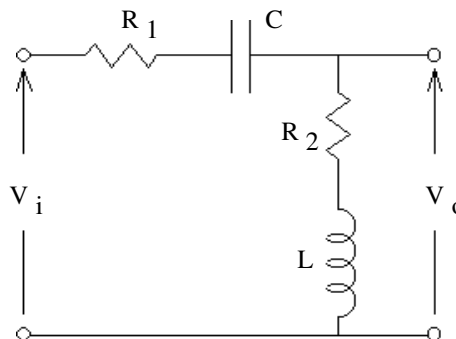

b) Find the characteristic equation of the circuit shown.

c) The solutions to the characteristic equation are called the _____ of the transfer function.

d) Does the transfer function have one or more zeros? If yes, express it (them) in terms of $R_1, R_2, C,$ & L .

3. (20 pts) Analysis of a circuit (not pictured) yields the characteristic equation below.

$$0 = s^2 + 500 \cdot s + 62500$$

$R := 80 \cdot \Omega$ $L := 640 \cdot \text{mH}$ $C := 25 \cdot \mu\text{F}$ $V_{in} := 12 \cdot \text{V}$

Further analysis yields the following initial and final conditions:

$i_L(0) = 50 \cdot \text{mA}$ $v_L(0) = -9 \cdot \text{V}$ $v_C(0) = 4 \cdot \text{V}$ $i_C(0) = 80 \cdot \text{mA}$

$i_L(\infty) = 110 \cdot \text{mA}$ $v_L(\infty) = 0 \cdot \text{V}$ $v_C(\infty) = 12 \cdot \text{V}$ $i_C(\infty) = 0 \cdot \text{mA}$

Write the full expression for $i_L(t)$, including all the constants that you find.


$i_L(t) = ?$

Include **units** in your answer

4. (10 pts) For waveform shown, find:

a) Average DC (V_{DC}) value

b) RMS (effective) value

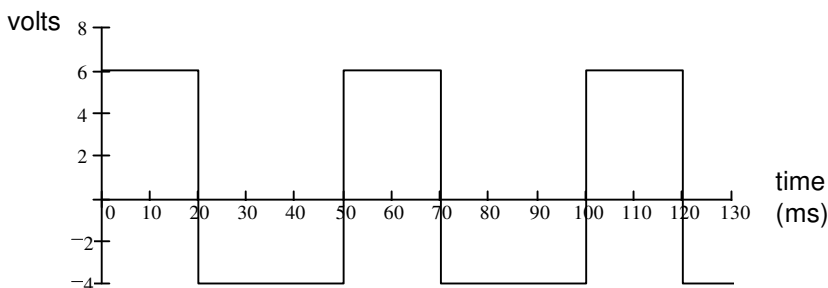


ECE2210/00 Exam 3 Fall 06 p2

5. (13 pts) The transformer shown in the circuit below is ideal. It is rated at 120/12 V, 8 VA, 60 Hz
Find the following:


a) $I_1 = ?$

b) $V_2 = ?$

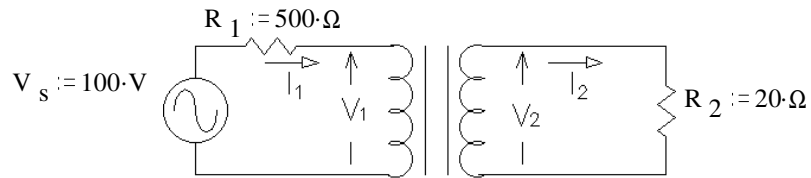

6. (24 pts) Consider the circuit at right. The switch has been in the closed position for a long time and is open (as shown) at time $t = 0$.

$I_S := 300\text{-mA}$

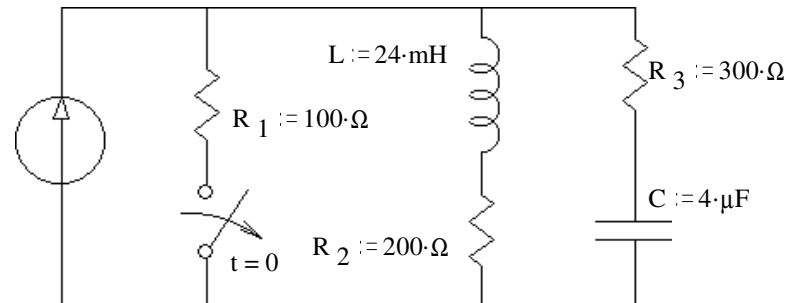

a) What are the final conditions of i_L and the v_C ?

$i_L(\infty) = ? \quad v_C(\infty) = ?$

b) Find the initial condition and initial slope of v_C that you would need to have in order to find all the constants in $v_C(t)$. Don't find $v_C(t)$ or it's constants, just the initial conditions.

c) Find the initial condition and initial slope of i_L that you would need to have in order to find all the constants in $i_L(t)$. Don't find $i_L(t)$ or it's constants, just the initial conditions.

Answers

1. a) $V_{in} = 3.6V \angle -36.9^\circ$ b) $I_T = 154mA \angle -27.9^\circ$ c) i) $-27.9^\circ > -36.9^\circ$

2. a) $\frac{s^2 + \frac{R_2}{L} \cdot s}{s^2 + \left(\frac{R_1 + R_2}{L}\right) \cdot s + \frac{1}{L \cdot C}}$ b) $0 = s^2 + \left(\frac{R_1 + R_2}{L}\right) \cdot s + \frac{1}{L \cdot C}$ c) poles d) 0 and $-\frac{R_2}{L}$

3. $i_L(t) := 110 \cdot mA - 60 \cdot mA \cdot e^{-\frac{250}{sec} \cdot t} - 29 \cdot \frac{A}{sec} \cdot t \cdot e^{-\frac{250}{sec} \cdot t}$

4. a) 0·V b) 4.9·V

5. a) 40·mA b) 8·V

6. a) 300·mA 60·V

b) 20·V $50000 \cdot \frac{V}{sec}$

c) 100·mA $2500 \cdot \frac{A}{sec}$

ECE 2210 Exam #3
Arn Stolp

Name _____

Scores:

Pgs 1&2 _____ of a possible 33 points

Pgs 3&4 _____ of a possible 30 points

Pgs 5&6 _____ of a possible 37 points

Total _____ of a possible 100 points