

ECE2210 Exam 3 given: Fall 08

(The space between problems has been removed.)

1. (20 pts) a) Draw the asymptotic Bode plot (the straight-line approximation) of the transfer function below. Accurately draw it on the graph provided.


$$H(f) := \frac{200 \cdot (100 \cdot \text{Hz} + j \cdot f)}{(30 \cdot \text{kHz} + j \cdot f)}$$

Magnitude plot

$$|H(f)|$$

Straight-line approximation _____


Actual - - - -

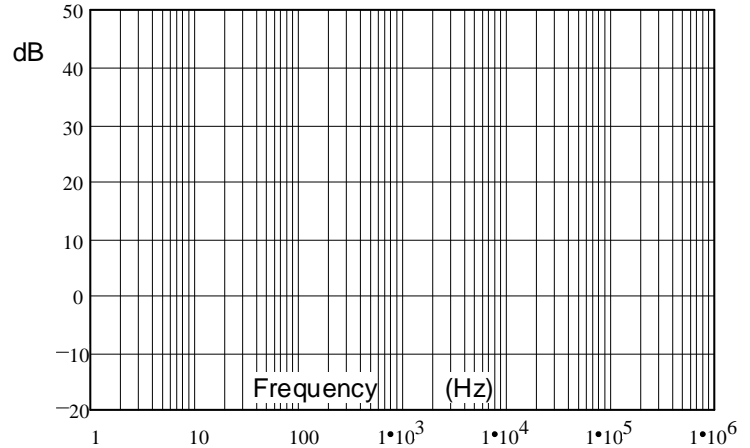

- b) The asymptotic Bode plot is not exact. Using a dotted line, sketch the actual magnitude of the transfer function $|H(f)|$ on the plot above. Indicate the point(s) where the difference between the two lines is the biggest (draw arrow(s) and write down the actual magnitude(s) at that (those) point(s).
- c) If there are any corners in the Bode plot associated with **poles** in the transfer function, list that/those corner frequency(ies) below (f_p).
- d) If there are any corners in the Bode plot associated with **zeroes** in the transfer function, list that/those corner frequency(ies) below (f_z).


2. (12 pts) Find:

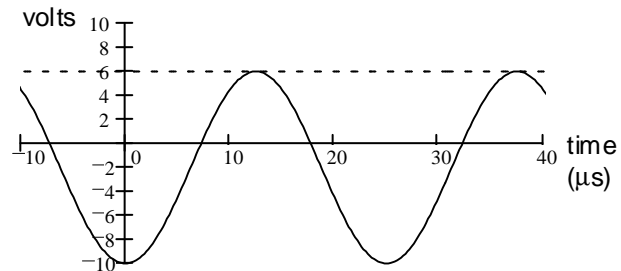- a) The average, DC (V_{DC}) voltage.
- b) The RMS (effective) voltage (show work)



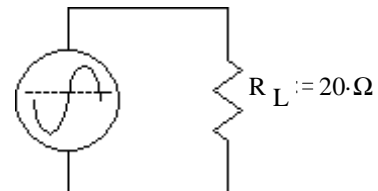- c) The voltage is hooked to a resistor, as shown, for 5 seconds.

How much energy is transferred to the resistor during that 5 seconds?



- d) What happened to that energy?

3. (22 pts) Analysis of a circuit (not pictured) yields the characteristic equation below.

$$0 = s^2 + 50 \cdot s + 400$$

$$R := 10 \cdot \Omega$$

$$L := 80 \cdot \text{mH}$$

$$C := 60 \cdot \mu\text{F}$$

Further analysis yields the following initial and final conditions:

$$i_L(0) = 18 \cdot \text{mA}$$

$$v_L(0) = -6 \cdot \text{V}$$

$$v_C(0) = 12 \cdot \text{V}$$

$$i_C(0) = -9 \cdot \text{mA}$$

$$i_L(\infty) = 10 \cdot \text{mA}$$

$$v_L(\infty) = 0 \cdot \text{V}$$

$$v_C(\infty) = 3 \cdot \text{V}$$

$$i_C(\infty) = 0 \cdot \text{mA}$$


Write the full expression for $v_C(t)$, including all the constants that you find.

$$v_C(t) = ?$$

Include **units** in your answer

ECE2210 Exam 3 Fall 08 p2

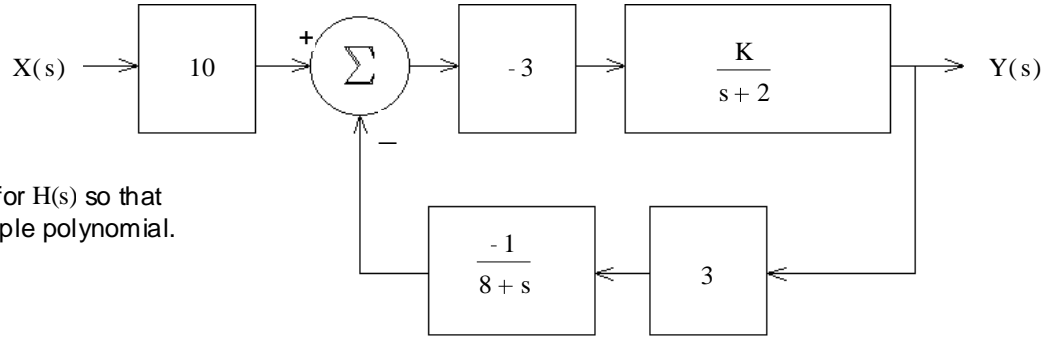4. (22 pts) a) A feedback system is shown in the figure. What is the transfer function of the whole system, with feedback.




$$H(s) = \frac{Y(s)}{X(s)} = ?$$

Simplify your expression for $H(s)$ so that the denominator is a simple polynomial.

- b) Find the value of K to make the transfer function critically damped. Answer may be left as a fraction.
- c) If $K := 5$, find the pole(s) of the transfer function:
- d) If $K := 5$, find the zero(s) of the transfer function:

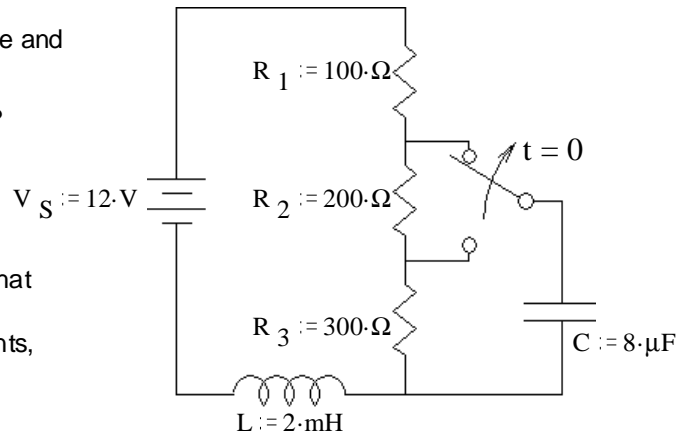5. (24 pts) The switch has been down for a long time and is switched up (as shown) at time $t = 0$.



a) What are the final conditions of i_L and the v_C ?
 $i_L(\infty) = ?$ $v_C(\infty) = ?$

b) Find the initial condition and initial slope of i_L that you would need to have in order to find all the constants in $i_L(t)$. Don't find $i_L(t)$ or it's constants, just the initial conditions.

c) Find the initial condition and initial slope of v_C that you would need to have in order to find all the constants in $v_C(t)$. Don't find $v_C(t)$ or it's constants, just the initial conditions.

Answers


1. a) & b)

Magnitude plot

$$|H(f)|$$

Straight-line approximation ___

Actual - - - -

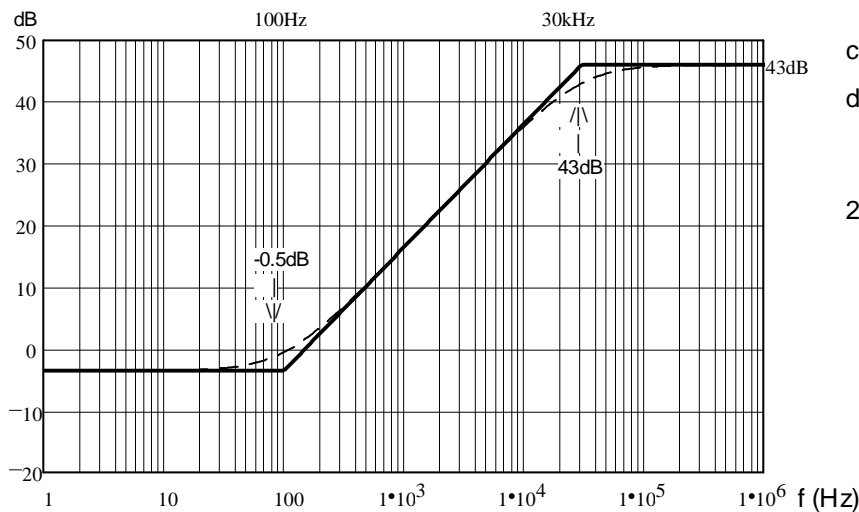

c) $f_{C2} = 30 \cdot \text{kHz}$

d) $f_{C1} = 100 \cdot \text{Hz}$

2. a) $-2 \cdot \text{V}$

b) $6 \cdot \text{V}$

c) $9 \cdot \text{J}$

d) It was converted to heat

3. $v_C(t) := 3 \cdot \text{V} + 7 \cdot \text{V} \cdot e^{-\frac{10}{\text{sec}} \cdot t} + 2 \cdot \text{V} \cdot e^{-\frac{40}{\text{sec}} \cdot t}$

4. a) $\frac{-30 \cdot K \cdot (s + 8)}{s^2 + 10 \cdot s + 16 + 9 \cdot K}$

b) 1

c) $-5 + 6 \cdot j$

d) -8

$-5 - 6 \cdot j$

5. a) $20 \cdot \text{mA}$ $10 \cdot \text{V}$ b) $20 \cdot \text{mA}$ $2000 \cdot \frac{\text{A}}{\text{sec}}$

c) $6 \cdot \text{V}$ $1000 \cdot \frac{\text{V}}{\text{sec}}$