

ECE 2210 Exam 3 given: Fall 13

(The space between problems has been removed.)

1. (20 pts) Analysis of a circuit (not pictured) yields the characteristic equation below.

$$0 = s^2 + 800 \cdot s + 160000 \quad R_1 := 100 \cdot \Omega \quad R_2 := 20 \cdot \Omega \quad L := 200 \cdot \text{mH} \quad C := 40 \cdot \mu\text{F} \quad V_{\text{in}} := 18 \cdot \text{V}$$

Further analysis yields the following initial and final conditions:

$$i_L(0) = 40 \cdot \text{mA} \quad v_L(0) = -12 \cdot \text{V} \quad v_C(0) = 5 \cdot \text{V} \quad i_C(0) = 60 \cdot \text{mA}$$

$$i_L(\infty) = 120 \cdot \text{mA} \quad v_L(\infty) = 0 \cdot \text{V} \quad v_C(\infty) = 15 \cdot \text{V} \quad i_C(\infty) = 0 \cdot \text{mA}$$


Write the full expression for $i_L(t)$, including all the constants that you find.

$$i_L(t) = ?$$

Include **units** in your answer

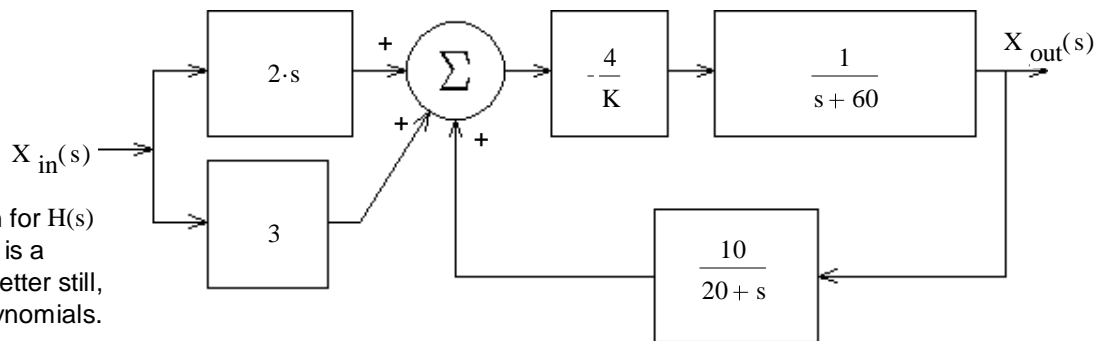2. (24 pts) a) A feedback system is shown in the figure. What is the transfer function of the whole system, with feedback.

$$H(s) = \frac{X_{\text{out}}(s)}{X_{\text{in}}(s)} = ?$$



Simplify your expression for $H(s)$ so that the denominator is a simple polynomial, or, better still, a multiple of simple polynomials.

b) Find the value of K to make the transfer function critically damped.

c) If K is **greater** than this value the system will be: underdamped or overdamped
Circle one


d) Does the transfer function have a zero?
Answer no or find the s value(s) of the zero(s).

ECE 2210/00 Exam 3 Fall 13 p1

3. (36 pts) The switch has been up in position 1 for a long time and is switched down to position 2 (as shown) at time $t = 0$.

SHOW YOUR WORK, no credit for guesses!

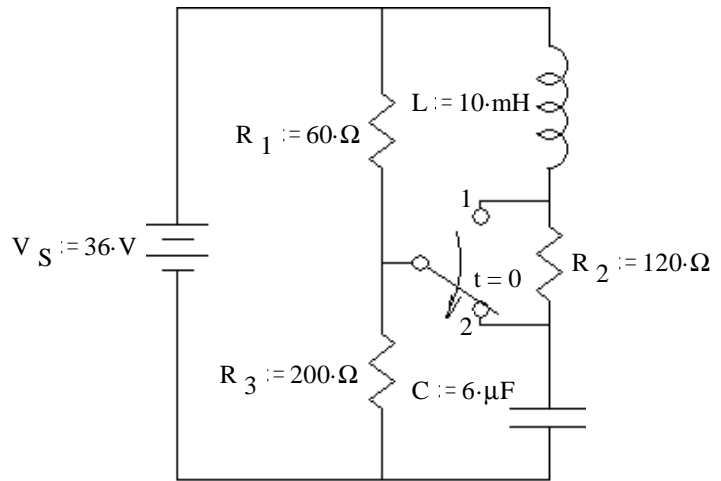a) What are the final conditions of i_L and the v_C ?
 $i_L(\infty) = ? \quad v_C(\infty) = ?$



b) Find the initial condition and initial slope of i_L that you would need to have in order to find all the constants in $i_L(t)$. Don't find $i_L(t)$ or it's constants, just the initial conditions.

c) Find the initial condition and initial slope of v_C that you would need to have in order to find all the constants in $v_C(t)$. Don't find $v_C(t)$ or it's constants, just the initial conditions.

4. (20 pts) The transformer shown in the circuit below is ideal. It is rated at 300/100 V, 1.0 kVA, 60 Hz

All values are RMS unless specified otherwise.

Find the following:

a) The primary current (magnitude).


$$|\mathbf{I}_1| = ?$$

b) The secondary current (magnitude). $|\mathbf{I}_2| = ?$

c) The secondary voltage (magnitude). $|\mathbf{V}_2| = ?$

d) The complex power (P and Q) used by the load. $\mathbf{S}_L = ?$

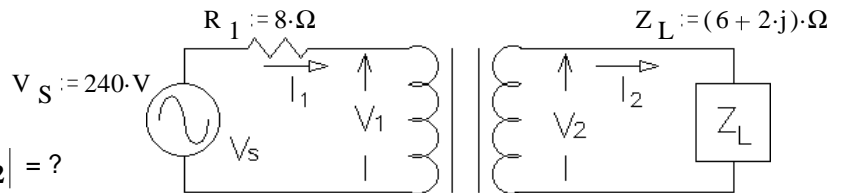e) Is this transformer operating within its ratings? Show your evidence.



Answers

1. $120\ \text{mA} - 80\ \text{mA} \cdot e^{-\frac{400}{\text{sec}}t} - 92 \cdot \frac{\text{A}}{\text{sec}} \cdot t \cdot e^{-\frac{400}{\text{sec}}t}$

3. a) $50\ \text{mA}$ $30\ \text{V}$ b) $180\ \text{mA}$ $-2160 \cdot \frac{\text{A}}{\text{sec}}$

c) $36\ \text{V}$ $0 \cdot \frac{\text{V}}{\text{sec}}$

4. a) $3.72\ \text{A}$ b) $11.15\ \text{A}$ c) $70.5\ \text{V}$

d) $746 + 249j\ \text{VA}$ e) NO $11.15\ \text{A} > 10\ \text{A}$

2. a) $(2 \cdot s + 3) \cdot \frac{-\frac{4}{\text{K}} \cdot (s + 20)}{s^2 + 80 \cdot s + 1200 + \frac{40}{\text{K}}}$

b) 0.1 c) overdamped

d) $-20 - \left(\frac{3}{2}\right)$