

ECE 2210 Exam 3

Useful Information

Bode Plots

Look for places in $|H(s)|$ where a real number and a $j\omega$ or jf term are added.
 Set real = |imaginary| to find poles and zeroes.
 Poles come from denominator of transfer function, zeroes from numerator.
 Divide frequencies into regions & find approx $|H(s)|$ in each region by simplifying each (real + imaginary) to just the largest part.

Slopes: -20, 0, or +20 dB/decade
 dB is $20 \cdot \log_{10}(|H(\omega)|)$
 cut corners by 3·dB

2nd order tran.

Overdamped $b^2 - 4 \cdot k > 0$ s_1 and s_2 are real and negative

$$X(t) = X(\infty) + B \cdot e^{s_1 t} + D \cdot e^{s_2 t} \quad X(0) = X(\infty) + B + D \quad \frac{d}{dt} X(0) = B \cdot s_1 + D \cdot s_2$$

Critically damped $b^2 - 4 \cdot k = 0$ $s_1 = s_2 = -\frac{b}{2} = s$ s_1 and s_2 are real, equal and negative


$$X(t) = X(\infty) + B \cdot e^{s t} + D \cdot t \cdot e^{s t} \quad B = X(0) - X(\infty) \quad D = \frac{d}{dt} X(0) - B \cdot s$$

Underdamped $b^2 - 4 \cdot k < 0$ $s = \alpha \pm j\omega$ complex s_1 and s_2

$$X(t) = X(\infty) + e^{\alpha t} \cdot (B \cdot \cos(\omega t) + D \cdot \sin(\omega t)) \quad B = X(0) - X(\infty) \quad D = \frac{\frac{d}{dt} X(0) - B \cdot \alpha}{\omega}$$


$$\frac{d}{dt} i_L(0) = \frac{v_L(0)}{L} \quad \frac{d}{dt} v_C(0) = \frac{i_C(0)}{C}$$

Final Conditions, or "after a long time"

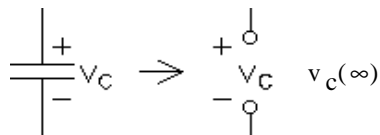

Replace capacitors with opens



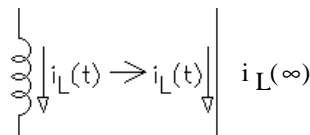
Capacitor voltage **cannot** change instantaneously



Replace inductors with wires

Inductor current **cannot** change instantaneously


System Block Diagrams

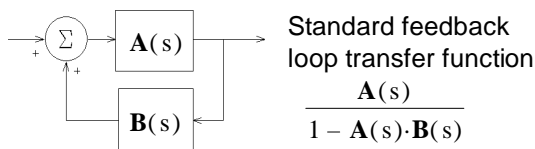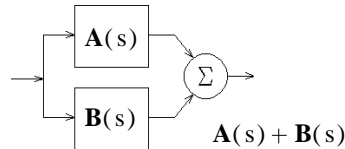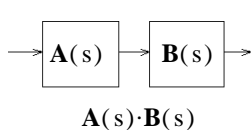


Standard feedback loop transfer function $\frac{A(s)}{1 - A(s) \cdot B(s)}$

Diodes

conducting not conducting

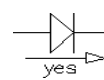


or

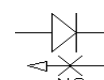

Use these models for the diodes and LEDs on this exam.



current

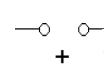

$V_d < 0.7V$ Check

LEDs: 2V

