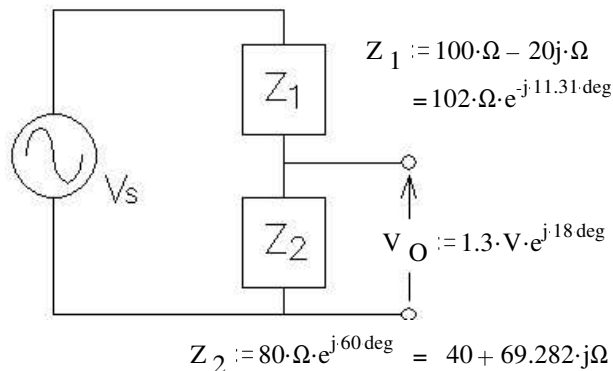


EE1050 Exam 3 given: Spring 2000

(The space between problems has been removed.)


1. (18 pts)

- Find V_S in the circuit below. Express it as a magnitude and phase angle (the way V_O is expressed). Show all the necessary work, not just the results from your calculator.
- Consider Z_2 as the load. What is the power factor of this load?
- How much power is dissipated by Z_2 ?




2. (24 pts) Assume the transformer is ideal and all voltages and currents are RMS. The magnitude of the secondary voltage ($|V_2|$) is 48 V.

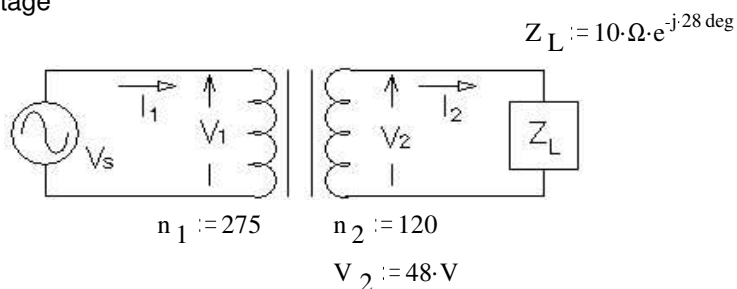- What is the magnitude of I_2 ?
- What is the power factor of the load?
- How much power does the load dissipate?
- What is the turns ratio (N) of this transformer?
- What is the magnitude of I_1 ?
- What is the magnitude of V_S ?
- What is the load as seen by V_S ? (magnitude and angle)
- What is the power factor as seen by V_S ?



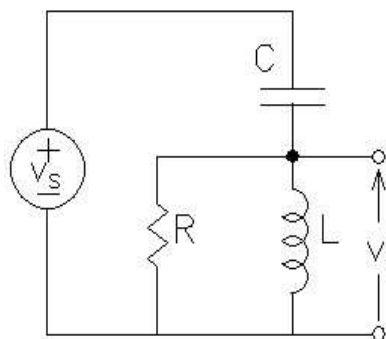3. (12 pts) For the circuit show;

- Find the differential equation for v_L .
- Find the characteristic equation for v_L .



4. (18 pts) Analysis of a circuit for v_X yields the characteristic equation shown.

$$s^2 + 75 \cdot s + 1400 = 0$$

- Write an expression for $v_X(t)$. You don't have initial and final conditions, so you can't find the constants in this expression. Use letters in place of constants that you cannot find


$$v_X(t) =$$

- This circuit is: overdamped critically damped underdamped (circle one)
- Which, if any, of your constants above represents the final condition of v_X ?

EE1050 Exam 3 given: Spring 00 p2

5. (16 pts) Consider the circuit at right. The switch has been in the top position for a long time and is switched down at time $t=0$.

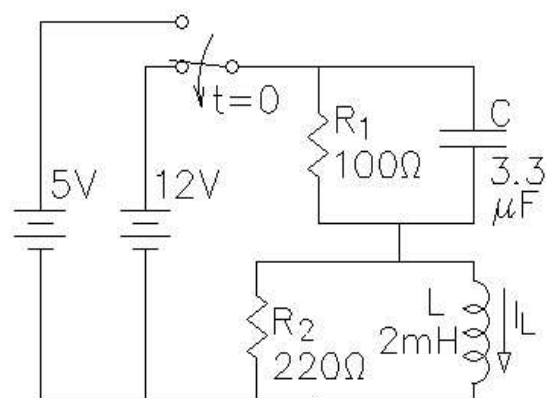
- a) What is the final condition for the current i_L ?
- b) Find the initial condition(s) of i_L that you would need to have in order to find all the constants in $i_L(t)$. Don't find $i_L(t)$ or it's constants, just the initial condition(s).



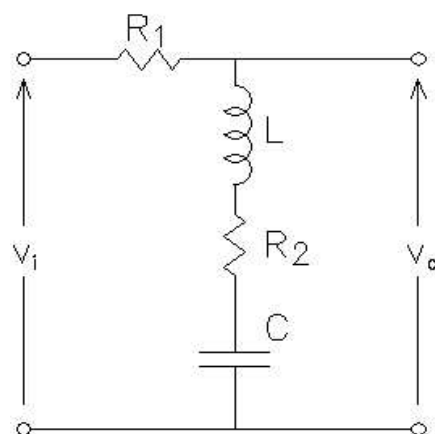6. (10 pts) Find the transfer function $H(s) = \frac{V_o(s)}{V_i(s)}$ for this circuit.

Write $H(s)$ in the normal form, as shown below.

$$H(s) = K \cdot \frac{s^n + k_1 \cdot s^{n-1} + \dots + k_{n-1}}{s^m + c_1 \cdot s^{m-1} + \dots + c_{m-1}}$$



Answers

- 1. a) 2.41V $\angle -22.6^\circ$ b) 0.5 c) 10.6mW
- 2. a) 4.8A b) 0.883 c) 203W d) 0.436 e) 2.1A f) 110V g) 53Ω $\angle -28^\circ$ h) 0.883

3. a) $\frac{d^2}{dt^2} v_L + \frac{1}{C \cdot R} \frac{d}{dt} v_L + \frac{1}{L \cdot C} \cdot v_L = \frac{d^2}{dt^2} v_S$ b) $0 = s^2 + \frac{1}{C \cdot R} \cdot s + \frac{1}{L \cdot C}$

4. a) $v_X(t) = (A + B \cdot e^{-40t} + D \cdot e^{-35t}) \cdot V$ b) overdamped c) A

5. a) 120mA b) $i_L(0) = 50\text{mA}$ $\frac{d}{dt} i_L(0) = 3500 \cdot \frac{A}{\text{sec}}$

6.
$$\frac{s^2 + \frac{R_2}{L} \cdot s + \frac{1}{L \cdot C}}{s^2 + \frac{R_1 + R_2}{L} \cdot s + \frac{1}{L \cdot C}}$$

EE 1050 midterm #3

April 17, 2000
Arn Stolp

Name _____

Scores:
Page 1 _____ of a possible 42 points

Page 2 _____ of a possible 32 points

Page 3 _____ of a possible 26 points

Total _____ of a possible 100 points