

ECE1050 Exam 3 given: Spring 05

(The space between problems has been removed.)

1. (16 pts) Analysis of a circuit (not pictured) yields the characteristic equation below.

$$0 = s^2 + 400 \cdot s + 400000$$

$$R := 80 \cdot \Omega$$

$$L := 20 \cdot \text{mH}$$

$$C := 2 \cdot \mu\text{F}$$

Further analysis yields the following initial and final conditions:

$$i_L(0) = 120 \cdot \text{mA}$$

$$v_L(0) = -3 \cdot \text{V}$$

$$v_C(0) = 7 \cdot \text{V}$$

$$i_C(0) = -80 \cdot \text{mA}$$

$$i_L(\infty) = 800 \cdot \text{mA}$$


$$v_L(\infty) = 0 \cdot \text{V}$$

$$v_C(\infty) = 12 \cdot \text{V}$$

$$i_C(\infty) = 0 \cdot \text{mA}$$

Write the full expression for $i_L(t)$, including all the constants that you find. $i_L(t) = ?$

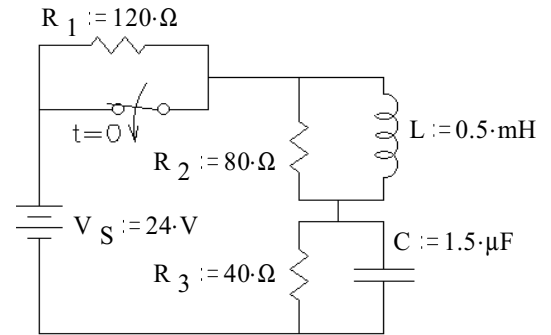2. (20 pts) Consider the circuit at right. The switch has been in the open position for a long time and is closed (as shown) at time $t = 0$.



a) What are the final conditions of i_L and the v_C ?

b) Find the initial condition and initial slope of i_L so that you could find all the constants in $i_L(t)$.

Don't find $i_L(t)$ or its constants, just the initial conditions.

c) Find the initial condition and initial slope of v_C so that you could find all the constants in $v_C(t)$. Don't find $v_C(t)$ or its constants, just the initial conditions.

3. (22 pts) a) Draw the asymptotic Bode plot (the straight-line approximation) of the transfer function below. Accurately draw it on the graph provided. I've done the first section, you do the remainder.

$$H(f) := \frac{10 \cdot (10 \cdot \text{Hz} + j \cdot f)}{(400 \cdot \text{Hz} + j \cdot f) \cdot \left(1 + \frac{0.00002}{\text{Hz}} \cdot j \cdot f\right)}$$

$$10 \cdot \text{Hz} = |j \cdot f C_1|$$

$$f_{C1} := 10 \cdot \text{Hz}$$

$$f < f_{C1}$$


$$|H(f)| \simeq \frac{10 \cdot (10 \cdot \text{Hz})}{(400 \cdot \text{Hz}) \cdot (1)} = 0.25$$

$$20 \cdot \log(0.25) = -12 \cdot \text{dB}$$

I've drawn the first part of the Bode plot, you draw the rest.

From here on the transfer function can be approximated as:

$$|H(f)| \simeq \frac{10 \cdot (j \cdot f)}{(400 \cdot \text{Hz} + j \cdot f) \cdot \left(1 + \frac{0.00002}{\text{Hz}} \cdot j \cdot f\right)}$$

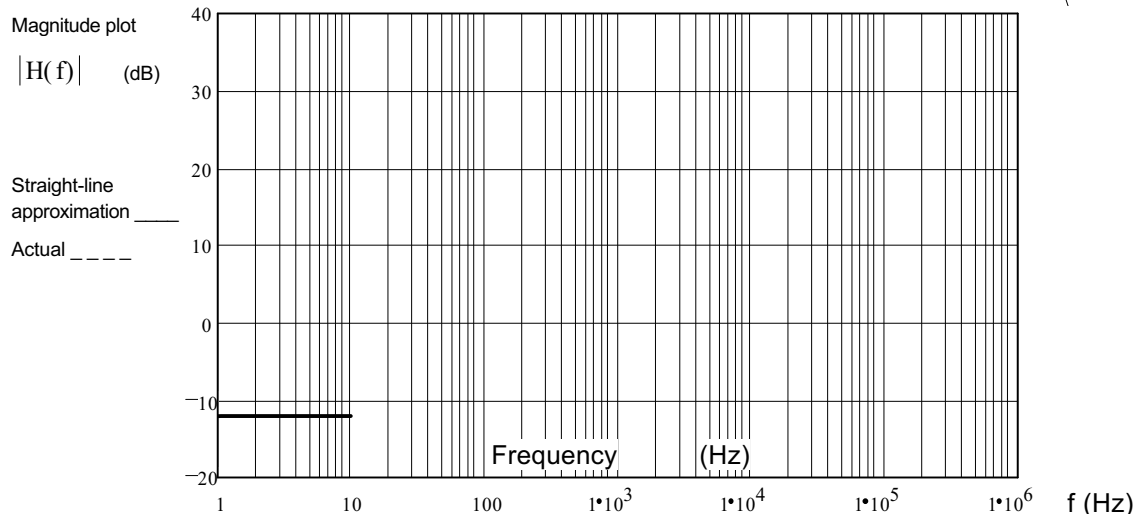


b) If there are any corners in the Bode plot associated with **poles** in the transfer function, list that/those corner frequency(ies) below (f_p).

c) If there are any corners in the Bode plot associated with **zeroes** in the transfer function, list that/those corner frequency(ies) below (f_z).

d) The asymptotic Bode plot is not exact. Using a dotted line, sketch the actual magnitude of the transfer function $|H(f)|$ on the plot above. Indicate the point(s) where the difference between the two lines is the biggest (draw arrow(s)) and write down the actual magnitude(s) at that (those) point(s).


ECE1050 Exam 3 Spring 05 p2

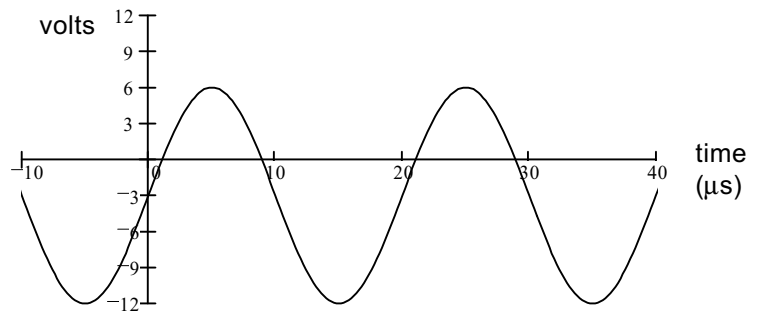4. (8 pts) Find:
 a) The average, DC (V_{DC}) voltage.
 b) The RMS (effective) voltage



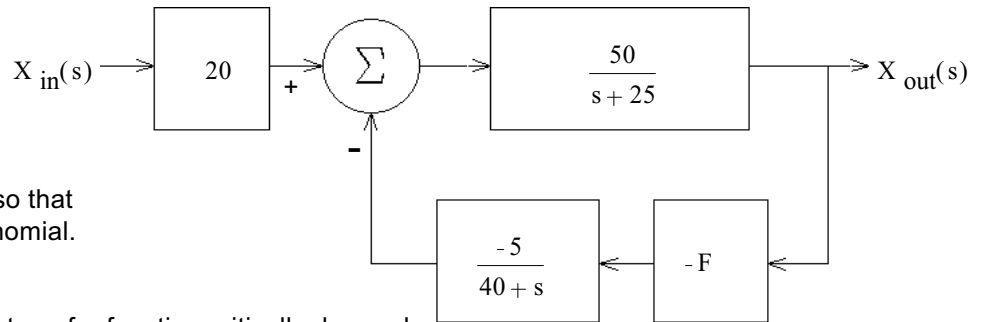5. (20 pts) a) A feedback system is shown in the figure. What is the transfer function of the whole system, with feedback.

$$H(s) = \frac{X_{out}(s)}{X_{in}(s)} = ?$$




Simplify your expression for $H(s)$ so that the denominator is a simple polynomial.

- b) Find the value of F to make the transfer function critically damped.
 c) If F is **Greater** than this value the system will be: underdamped or overdamped Circle one
 d) Does the transfer function have a zero? Answer no or find the s value of that zero.

6. (14 pts) The transformer shown in the circuit below is ideal. It is rated at 120/20 V, 200 VA, 60 Hz Find the following:

- a) $V_1 = ?$
 b) $I_2 = ?$

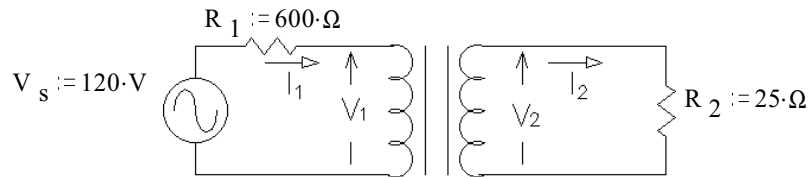


Answers

1. $i_L(t) := 800 \cdot \text{mA} + e^{-200t} \cdot (-680 \cdot \text{mA} \cdot \cos(600 \cdot t) - 477 \cdot \text{mA} \cdot \sin(600 \cdot t))$

2. a) 600 mA 24 V b) 150 mA $36000 \cdot \frac{\text{A}}{\text{sec}}$ c) 6 V $15 \cdot 10^5 \cdot \frac{\text{V}}{\text{sec}}$

3. a) & d)

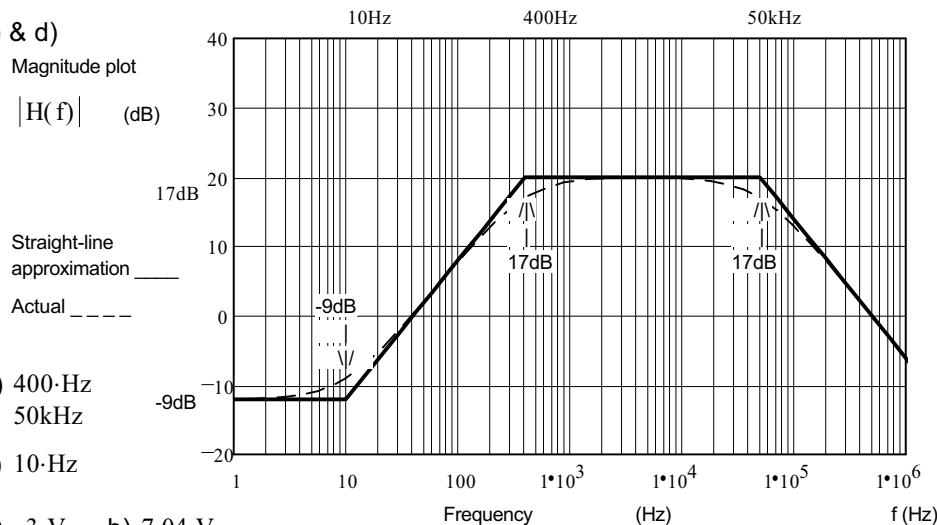

- b) 400 Hz
 50 kHz
 c) 10 Hz

4. a) -3 V b) 7.04 V

5.a) $H(s) = 20 \cdot \frac{50 \cdot s + 2000}{s^2 + 65 \cdot s + 1000 + 250 \cdot F}$

- b) 0.225 c) underdamped d) -40

6. a) 72 V b) 0.48 A

ECE 1050 Exam #3
 Arn Stolp
 Name _____
 Scores:
 Pgs 1&2 _____ of a possible 36 points
 Pgs 3&4 _____ of a possible 30 points
 Pgs 5&6 _____ of a possible 34 points
 Total _____ of a possible 100 points