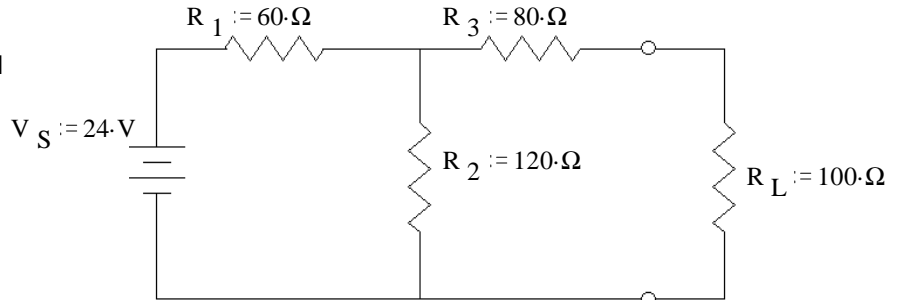


# ECE2210 Final given: Fall 09


1. (19 pts) a) Find and draw the Thévenin equivalent of the circuit shown. The load resistor is  $R_L$ .
- b) Find and draw the Norton equivalent of the same circuit.
- c) Find the load current using your Thévenin equivalent circuit.



2. (12 pts) a) Find the s-type transfer function of the circuit shown. Consider  $I_C$  as the "output".
- You MUST show work to get credit. Simplify your expression for  $H(s)$  so that the denominator is a simple polynomial.


$$H(s) = \frac{I_C(s)}{I_{in}(s)} = ?$$

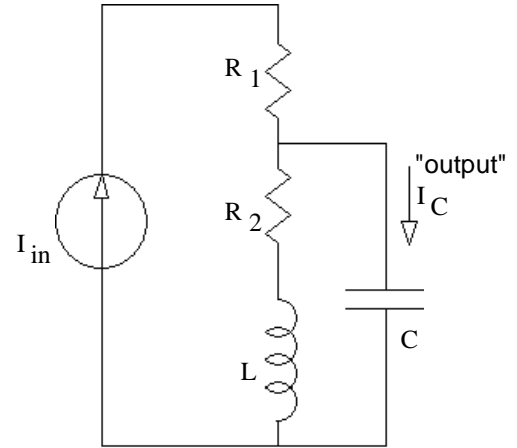- b) How many poles does this transfer function have?
- c) How many zeroes does this transfer function have?
- If it has 1 or more, express them (probably in terms of  $R_1$ ,  $R_2$ ,  $L$  and  $C$ ).



3. (15 pts) a) Find:  $V_1$  &  $I_2$

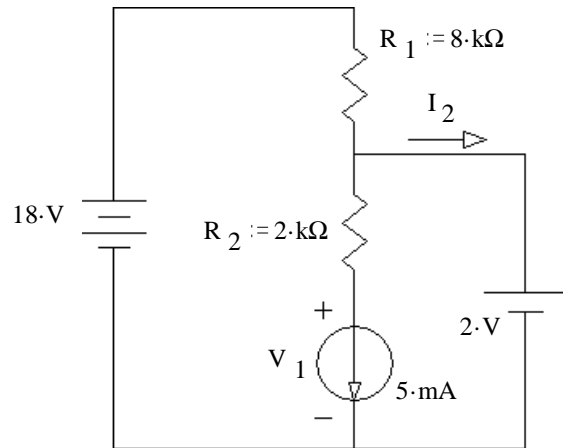- b) How much power does the 2-V battery supply to the circuit?



4. (21 pts) The transformer shown in the circuit below is ideal. It is rated at 220/110 V, 200 VA, 60 Hz
- Find the following:
- All values are RMS unless specified otherwise.

- a) The primary current (magnitude).

$$|I_1| = ?$$

- b) The primary voltage (magnitude).

$$|V_1| = ?$$


- c) The secondary voltage (magnitude).

$$|V_2| = ?$$

- d) The power supplied by the source.

$$P_S = ?$$

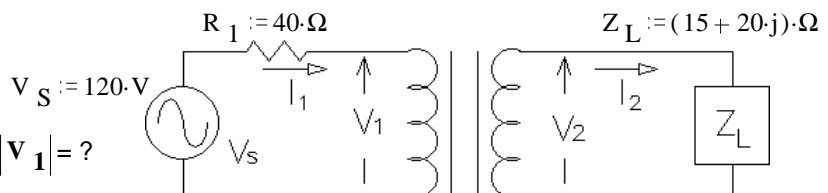- e) Is this transformer operating within its ratings? Show your evidence.



**ECE2210 Final given: Fall 09 p2**

Use constant-voltage-drop models for the diodes and LEDs on this exam.

5. (22 pts) Assume that diode  $D_1$  does **NOT** conduct.

Assume that diodes  $D_2$  and  $D_3$  **DO** conduct.


a) Stick with these assumptions even if your answers come out absurd.

Find the following:

$V_{D1} =$  \_\_\_\_\_

$I_{R3} =$  \_\_\_\_\_

$I_{D2} =$  \_\_\_\_\_

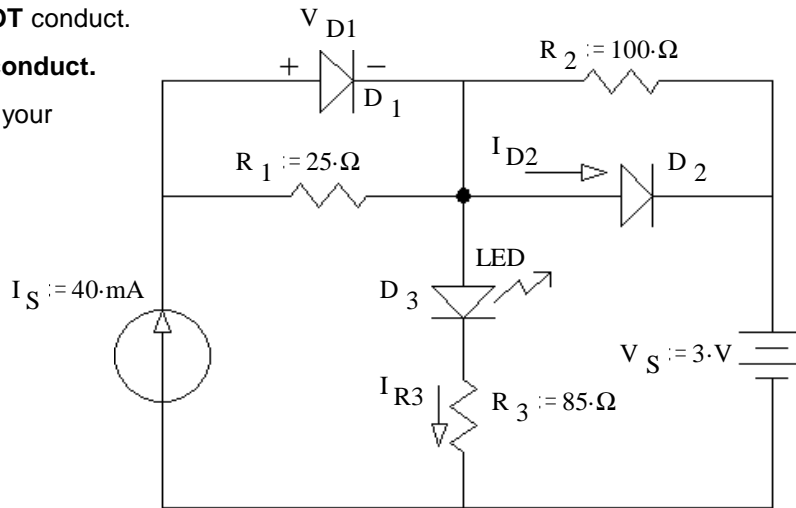

b) Based on the numbers above, was the assumption about  $D_1$  correct? Circle one:    yes    no  
How do you know? (Specifically show a value which is or is not within a correct range.)

c) Based on the numbers above, was the assumption about  $D_2$  correct? Circle one:    yes    no  
How do you know? (Specifically show a value which is or is not within a correct range.)

d) Based on the numbers above, was the assumption about  $D_3$  correct? Circle one:    yes    no  
How do you know? (Specifically show a value which is or is not within a correct range.)

5. continued



i) The **real**  $I_{R3} < I_{R3}$  calculated in part a.

e) Based on your answers to parts b), c) & d), Circle one:

ii) The **real**  $I_{R3} > I_{R3}$  calculated in part a.


iii) The **real**  $I_{R3} = I_{R3}$  calculated in part a.

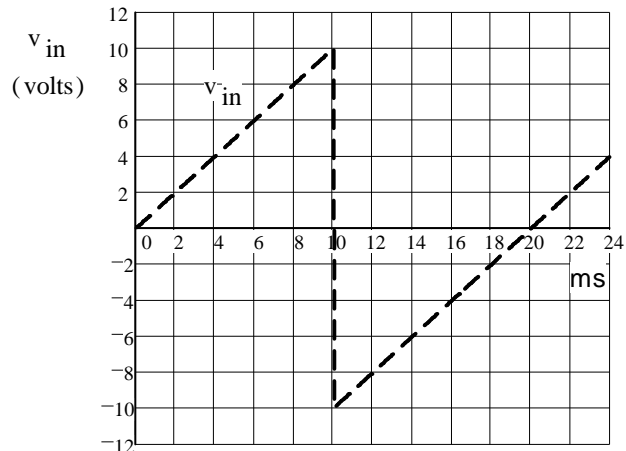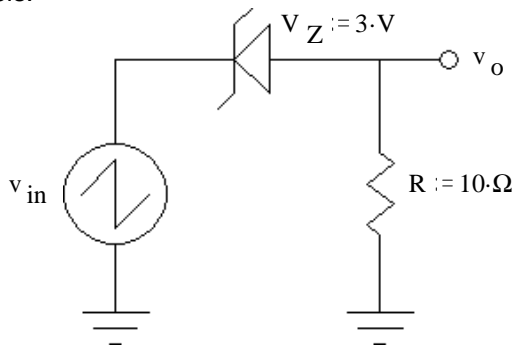6. (16 pts) A voltage waveform (dotted line) is applied to the circuit shown. Accurately draw the output waveform ( $v_o$ ) you expect to see. Label important times **and** voltage levels.




**ECE2210 Final given: Fall 09 p3**

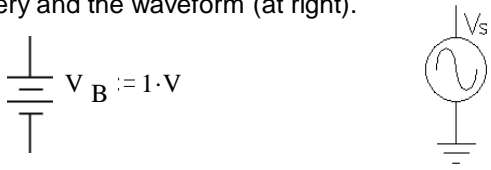
7. (34 pts) You have two input voltages to work with.  
A 1V battery and the waveform (at right).



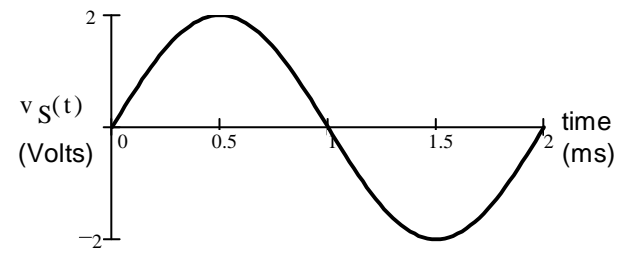
The problems below are op-amp design problems. The answer should be a schematic of a circuit showing the values of all the parts. Use reasonable resistor values (in the  $100\Omega$  to  $1\text{ M}\Omega$  range). Also show how one or both of the sources are hooked up to your circuit. Most circuits won't need both.



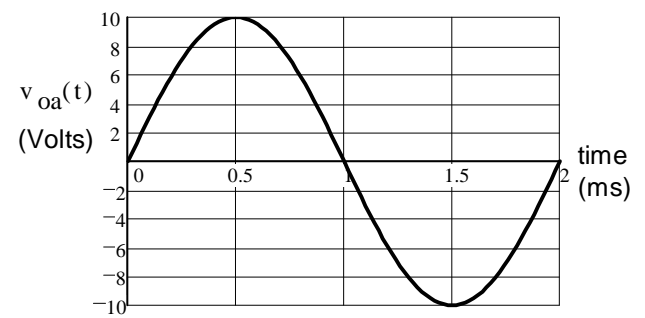a) Design a circuit which will output the waveform at right.




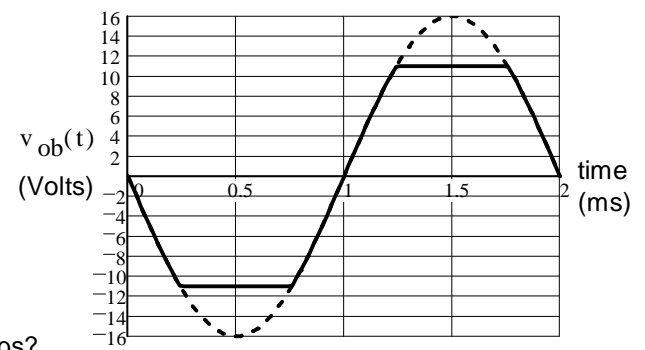b) Design a circuit which will output the waveform at right.




c) What power supply or supplies are being used with your op-amps?

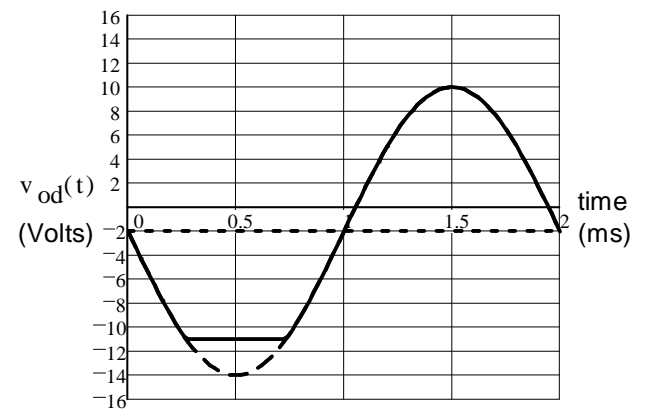d) Design a circuit which will output the waveform at right.



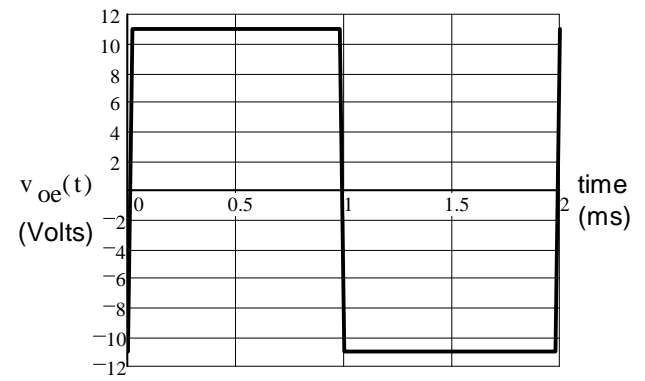e) Design a circuit which will output the waveform at right.  
Hint: Think nonlinear.




**ECE2210 Final given: Fall 09 p4**

8. (31 pts) A couple of transistors are used to control the current flow through an inductive load.

- a) The switch is open, as shown. What is the minimum  $V_2$  needed to insure that transistor  $Q_2$  is in saturation.

$\beta_2 = 25$        $V_2 = ?$

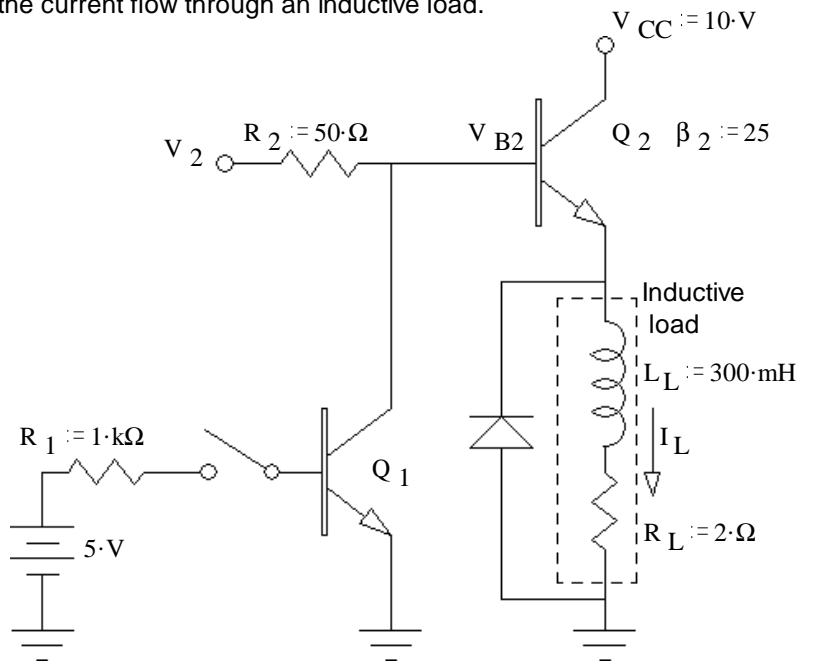

- b) Find the power dissipated in transistor  $Q_2$  with this  $V_2$ .       $P_{Q2} = ?$
- c) What if the voltage  $V_2$  was too low so that the base voltage of transistor  $Q_2$  was only 8V, how much power would be dissipated in transistor  $Q_2$  ?  
 IF  $V_{B2} := 8 \cdot V$        $P_{Q2} = ?$
- d) The transistor  $Q_2$  was selected to be able to handle the power found in part b) (with a 2x factor of safety). What would happen with the  $V_2$  of part c)?

$V_2$  is NOT too low for the remainder of the problem, that is, use the  $V_2$  found in part a).


- e) When the switch is closed, you would like transistor  $Q_1$  to saturate. What minimum  $\beta_1$  would be required to achieve saturation?

Use the  $\beta_1$  for the remainder of the problem.

- f) The diode in this circuit conducts a significant current:      (circle one)
- |                                   |                                 |
|-----------------------------------|---------------------------------|
| A) never.                         | D) always.                      |
| B) when the switch closes.        | E) when the switch opens.       |
| C) whenever the switch is closed. | F) whenever the switch is open. |
- g) What is the maximum diode current you expect when the switch is cycled. (Answer 0 if it never conducts.)
- h) This circuit design is:      A) incredibly fantastic.      C) dumb.      Why?
- B) a very good design.      D) not a good design.

**ECE2210 Final given: Fall 09 p4**

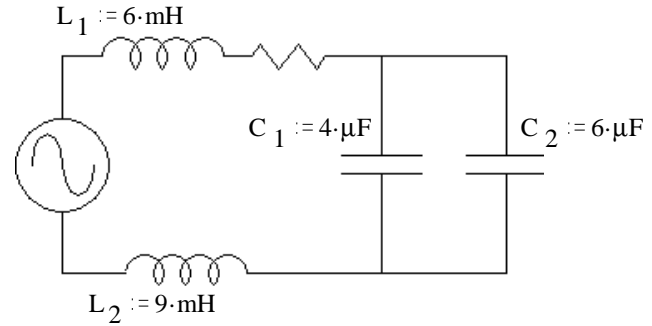9. (10 pts) Find the resonant frequency (or frequencies) of the circuit shown (in cycles/sec or Hz).




10. Do you want your grade and scores posted on my door and on the Internet? If your answer is yes, then provide some sort of password

or alias: \_\_\_\_\_  
otherwise, leave blank

The grades will be posted on my door in alphabetical order under the alias that you provide here. I will not post grades under your real name. The Internet version will be a pdf file which you can download. Both will show the homework, lab, and exam scores of everyone who answers here.

**Answers**

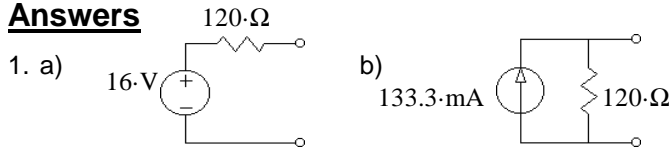

3. a) -8·V    -3·mA    b) 6·mW
4. a) 937·mA    b) 93.7·V    c) 46.85·V  
d) 87.8·W    e) NO     $I_{1max} := 909\text{·mA} < I_1$
5. a) 1·V    20·mA    13·mA    b) no     $V_{D1} = 1\text{·V} > 0.7\text{V}$   
c) yes     $I_{D2} = 13\text{·mA} > 0$     d) yes     $I_{D3} = 20\text{·mA} > 0$     e) iii)
7. a) Non-inverting amp with  $R_f = 4R_1$ .  
b) Inverting amp with  $R_f = 8R_1$ .    c)  $\pm 12\text{V}$
- d) Summer with  $R_f = 6R_1$ , waveform is hooked to  $R_1$  &  $R_f = 2R_2$ , battery + terminal is hooked to  $R_2$  and - to ground.  
e) Comparator, waveform is hooked to noninverting input, other inputs hooked to ground.
8. a) 20.3·V    b) 0.98·W    c) 9.86·W    d)  $Q_2$  will burn out.    e) 93.5    f) B    g) 4.9·A  
h) C D    There are good ways to do this same thing without the extra requirement of  $V_2$ , and this extra voltage makes the transistor  $Q_2$  more vulnerable to failure (see part d)).

9. 411·Hz

c) 72.7·mA    2.a)  $\frac{s^2 + \frac{R_2}{L} \cdot s}{s^2 + \frac{R_2}{L} \cdot s + \frac{1}{L \cdot C}}$     b) 2  
c) 2, 0 &  $-\frac{R_2}{L}$

