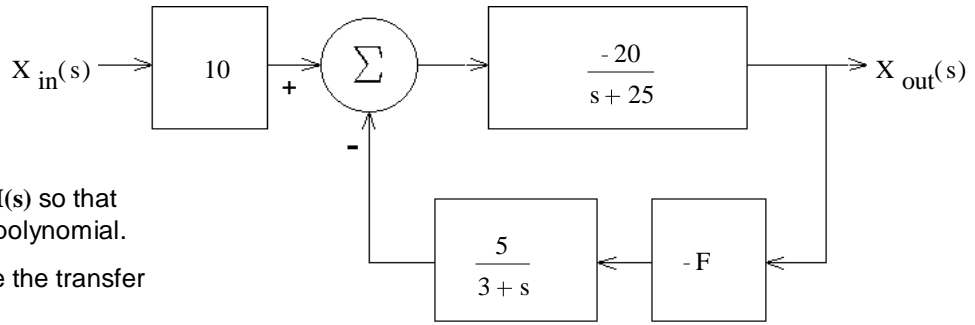


ECE2210 Final given: Fall 10

1. (18 pts) a) A feedback system is shown in the figure. What is the transfer function of the whole system, with feedback.

$$H(s) = \frac{X_{out}(s)}{X_{in}(s)} = ?$$



SHOW YOUR WORK

Simplify your expression for $H(s)$ so that the denominator is a simple polynomial.

- b) Find the value of F to make the transfer function critically damped.


c) If F is **Greater** than this value the system will be: underdamped or overdamped Circle one

d) Does the transfer function have a zero? Answer no or find the s value of that zero.

2. (16 pts) a) Find the s -type transfer function of the circuit shown after time $t = 0$. Consider I_L as the "output".

You **MUST** show work to get credit. Simplify your expression for $H(s)$ so that the denominator is a simple polynomial.

$$H(s) = \frac{I_L(s)}{V_{in}(s)} = ?$$

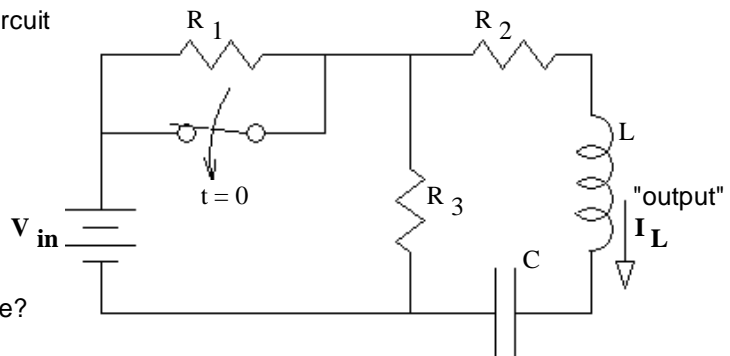

- b) How many zeroes does this transfer function have?

- c) How many poles does this transfer function have?

If it has 1 or more, express them (probably in terms of R_1, R_2, R_3, L and C).

3. (31 pts) A transformer is rated at 360V / 120V, 0.9kVA. Assume the transformer is ideal and all voltages and currents are RMS.


- a) What is the current rating of the primary?

- b) What is the current rating of the secondary?

- c) The secondary has 150 turns of wire. How many turns does the primary have?

- d) The voltage across the load, $V_L := 110 \cdot V$. How big is the source voltage ($|V_s|$)?

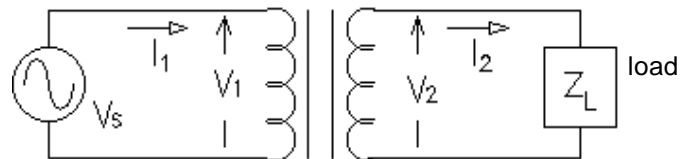- e) The secondary load (Z_L) has a magnitude of 12Ω at a power factor of 80%. Find the secondary current, I_2 (magnitude **and angle**).



$$|Z_L| = 12 \cdot \Omega$$

$$pf := 80\% \text{ lagging}$$

$$V_L := 110 \cdot V \angle 0^\circ$$

$$pf := 80\%$$

- h) How much average power does the load dissipate?

- i) How much average power does the power source (V_s) supply?

- j) Is this transformer operating within its ratings?

How do you know? (Specifically show a values which are or are not within a correct range.)

Within range? yes no (circle one)

- k) Using the given load voltage and power factor, what is the smallest load impedance magnitude that you could hook to this transformer and still operate within its ratings?

$$|Z_{Lmin}| = ?$$

- g) What is the load as seen by V_s ? (magnitude **and angle**)

- l) Using the given load voltage and power factor, what is the maximum power that this transformer can deliver to the load and still operate within its ratings?

ECE2210 Final given: Fall 10 p2

Use constant-voltage-drop models for the diodes and LEDs on this exam.

4. (25 pts) Assume that diodes D_1 and D_2 **DO** conduct.

Assume that diode D_3 does **NOT** conduct.

a) Find I_{R2} , I_{D2} , I_{D1} , & V_{D3} based on these assumptions. Stick with these assumptions even if your answers come out absurd.

$I_{R2} =$ _____
 $I_{D2} =$ _____
 $I_{D1} =$ _____
 $V_{D3} =$ _____

b) Based on the numbers above, was the assumption about D_1 correct? yes no (circle one)


How do you know? (Specifically show a value which is or is not within a correct range.)

c) Was the assumption about D_2 correct? yes no (circle one)
 How do you know? (Show a value & range.)



d) Was the assumption about D_3 correct? yes no (circle one)
 How do you know? (Show a value & range.)

e) Based on your answers to parts b), c) & e), Circle one:
 i) The **real** $I_{D2} < I_{D2}$ calculated in part a.
 ii) The **real** $I_{D2} = I_{D2}$ calculated in part a.
 iii) The **real** $I_{D2} > I_{D2}$ calculated in part a.

You do not need to justify your answer.

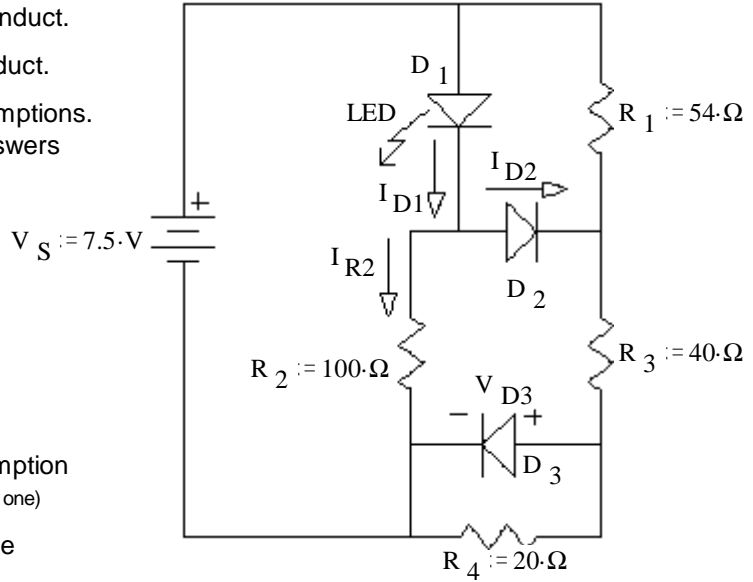

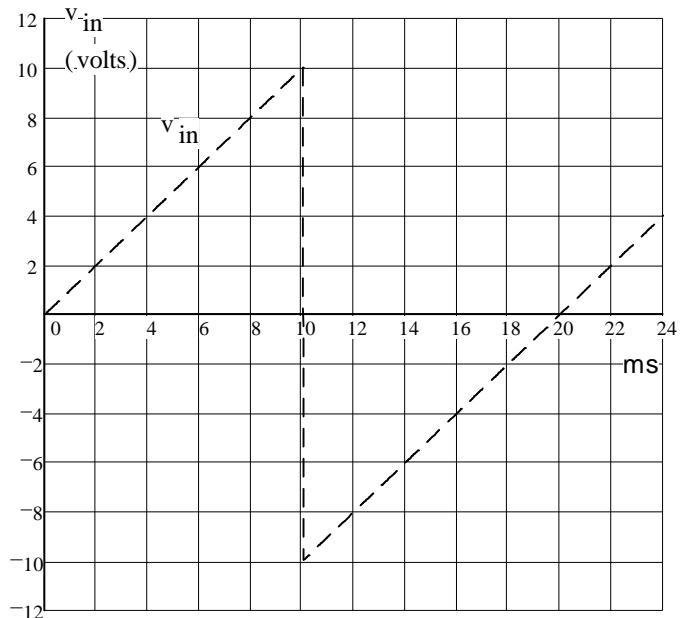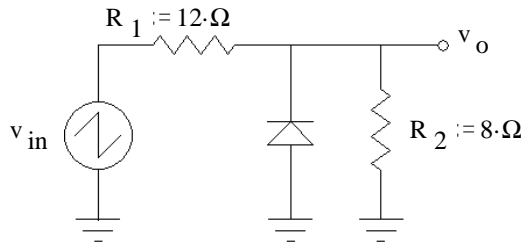5. (18 pts) A voltage waveform (dotted line) is applied to the circuit shown. Accurately draw the output waveform (v_o) you expect to see. Label important times **and** voltage levels.












9. Do you want your grade and scores posted on the Internet? If your answer is yes, then provide some sort of alias.
 _____ otherwise, leave blank

The grades will be posted on line in pdf form in alphabetical order under the alias that you provide here. I will not post grades under your real name. It will show the homework, lab, and exam scores of everyone who answers here.

ECE2210 Final given: Fall 10 p3

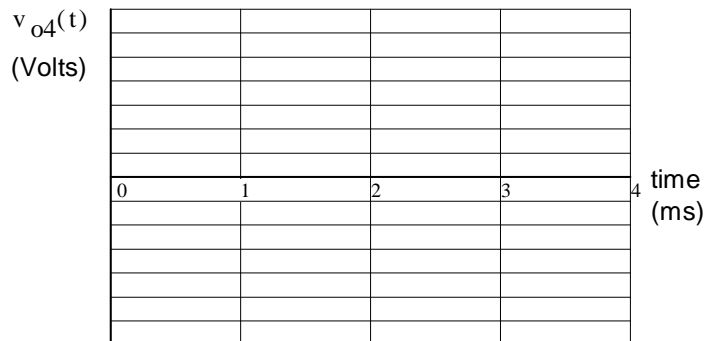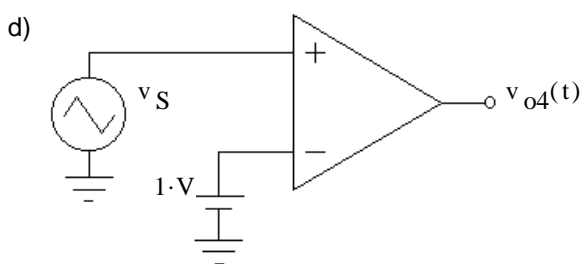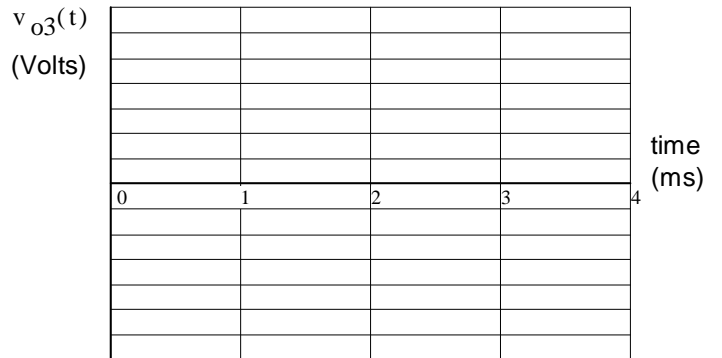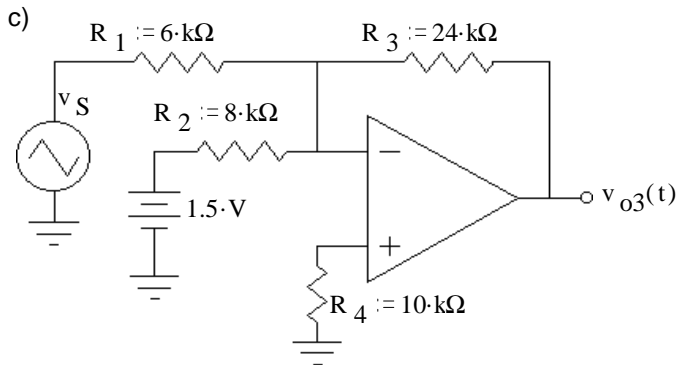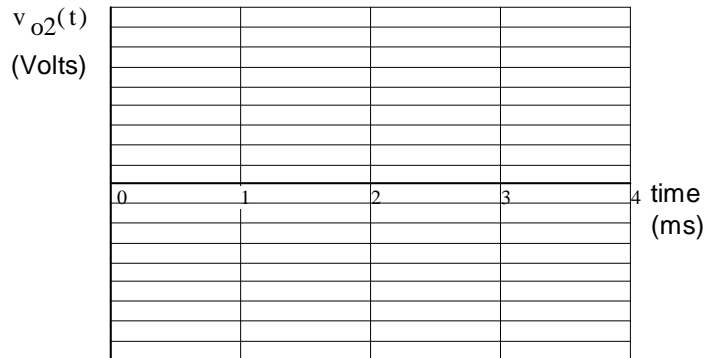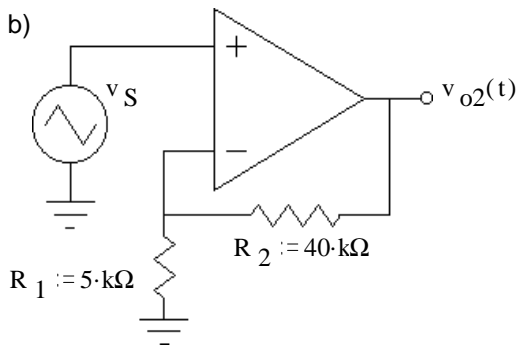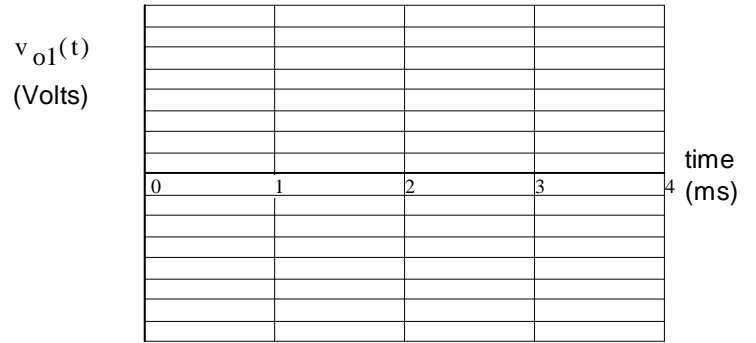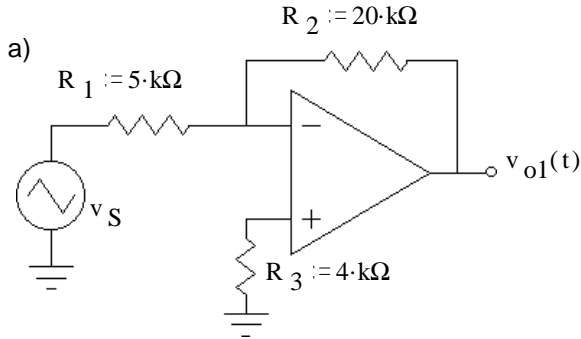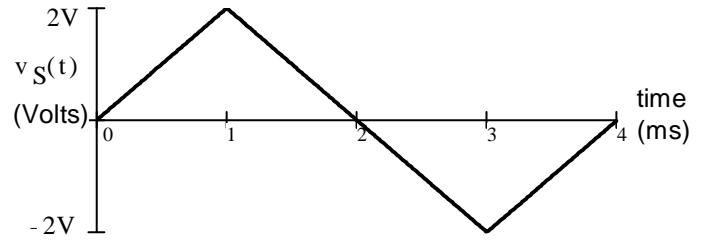
6. (27 pts) The same input signal (at right) is connected to several op-amp circuits below. Sketch the output waveform for each circuit. Clearly label important voltage levels on each output. If I can't easily make out what your peak values are, I'll assume you don't know. Don't forget to show inversions. All op-amps are powered by $\pm 12\text{ V}$ power supplies.



ECE2210 Final given: Fall 10 p4

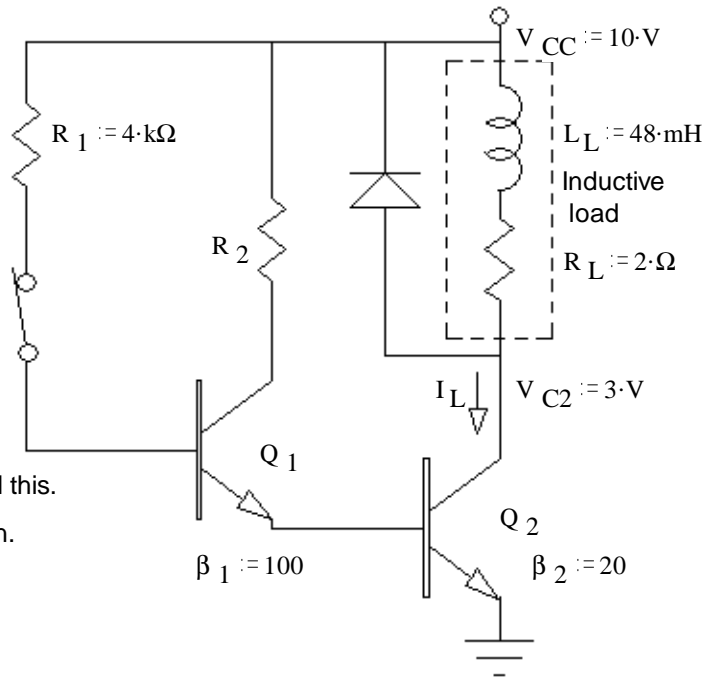
7. (35 pts) A couple of transistors are used to control the current flow through an inductive load.

- The switch has been closed for a long time. You measure the voltage at the collector of Q_2 to be the value shown (referenced to ground). Find the power dissipated in transistor Q_2 . $P_{Q2} = ?$
- Q_1 is in saturation, what is the value of R_2 ? You may assume that the emitter current of Q_1 is approximately equal to the collector current of Q_1 . $R_2 = ?$
- Determine if Q_1 actually is saturated. Show how you find this.
- Find the minimum value β_2 so that Q_2 will be in saturation.
- Find the power dissipated in transistor Q_2 with the β you just calculated (Q_2 in saturation). $P_{Q2} = ?$
- The diode in this circuit conducts a significant current: (circle one)
 - never.
 - when the switch first closes.
 - whenever the switch is closed.
 - always.
 - when the switch first opens.
 - whenever the switch is open.
- What is the maximum diode current you expect when the switch is cycled. (Answer 0 if it never conducts.) Assume the β_2 of part d) (Q_2 in saturation when on).



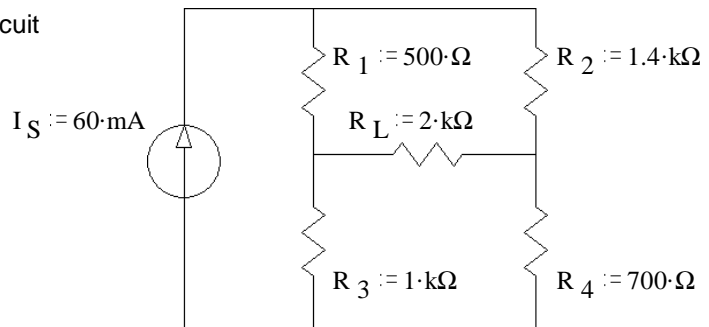8. (10 pts) a) Draw the Thévenin equivalent of the circuit shown and find V_{Th} **only**. The load resistor is R_L .

You don't need to find R_{Th} , but you'll get 6 points extra credit if you do find the correct R_{Th} .



Answers

- $\frac{-200 \cdot (s+3)}{s^2 + 28 \cdot s + 75 + 100 \cdot F}$
 - 1.21
 - underdamped
 - $s = -3$
- $\frac{\frac{1}{L} \cdot s}{s^2 + \frac{R_2}{L} \cdot s + \frac{1}{L \cdot C}}$
 - 1
 - $s = 0$
 - 2 $\frac{-\frac{R_2}{L} + \sqrt{\left(\frac{R_2}{L}\right)^2 - \frac{4}{L \cdot C}}}{2}$ $\frac{-\frac{R_2}{L} - \sqrt{\left(\frac{R_2}{L}\right)^2 - \frac{4}{L \cdot C}}}{2}$
- 2.5·A
 - 7.5·A
 - 450
 - 330·V
 - 9.17A $\angle -36.9^\circ$
 - 3.06A $\angle -36.9^\circ$
 - 108Ω $\angle 36.9^\circ$
 - 807·W
 - 807·W
 - No
 - 9.17·A > 7.5·A
 - 14.7·Ω
 - 660·W
- 55·mA
 - 30·mA
 - 85·mA
 - 1.6·V
 - yes $I_{D1} = 85 \cdot \text{mA} > 0$
 - yes $I_{D2} = 30 \cdot \text{mA} > 0$
 - no $V_{D1} = 1.6 \cdot \text{V} > 0.7 \text{V}$
 - iii
- Starts at 0V, ramps up to 4V at 10ms, then drops instantly to -0.7V where it stays until 18.25ms, Finally it ramps up through 0V at 20ms.
- Inverted triangle wave that peaks at -8 and +8V.
 - Triangle wave that would peak at +18 and -18V but is clipped off at +11 and -11V.
 - Inverted triangle wave centered around -4.5V that would peak at -12.5V but is clipped off at -11V, the positive peak is 3.5V.
 - 11V to 0.5ms, then +11V to 1.5ms, -11V from then on.
- 10.5·W
 - 52·Ω
 - more accurate: 52.5·Ω
 - yes
 - 28
 - 0.98·W
 - E
 - 4.9·A
 - 17.5·V