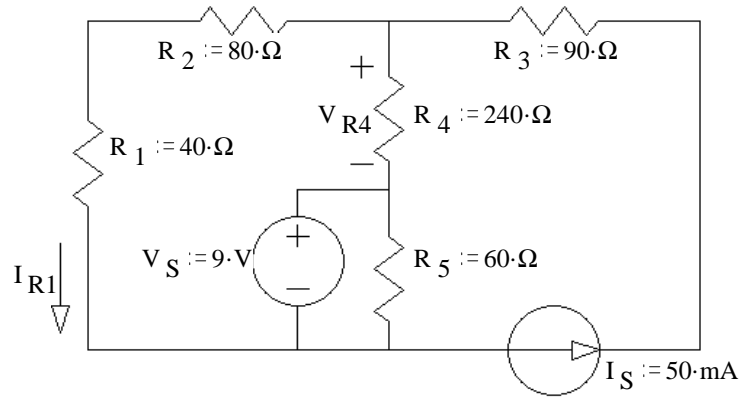


# ECE 2210 Final given: Fall 20

1. (22 pts) Use nodal analysis to find the voltage across  $R_4$  ( $V_{R4}$ ) and the current through  $R_1$  ( $I_{R1}$ ).


You **MUST** show all the steps of nodal analysis work to get credit, including drawing appropriate symbols and labels on the circuit shown.



2. (20 pts) Find  $Z_{eq}$  in simple polar form (give me numbers).

You must show work and intermediate results.

$f := 1.59155 \cdot \text{kHz}$

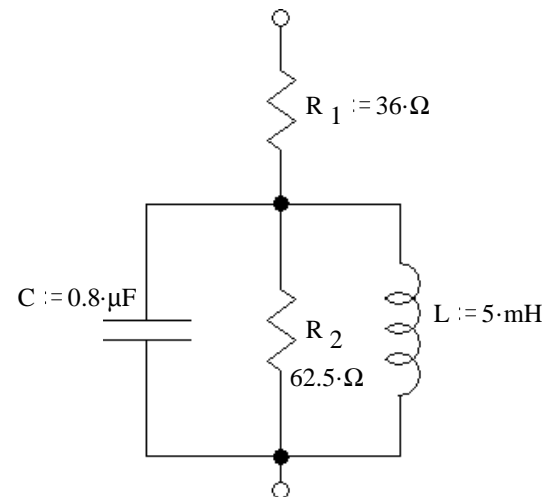

3. (36 pts) A couple of transistors are used to control the current flow through an inductive load.

a) You measure the voltage at each collector (referenced to ground) as shown on the drawing. Find the power dissipated by transistor  $Q_2$ .  
 $P_{Q2} = ?$

b) Find the  $\beta$  of transistor  $Q_2$ .  $\beta_2 = ?$

You may assume that the emitter current of  $Q_1$  is approximately equal to the collector current of  $Q_1$ .

c) Find the  $\beta$  of transistor  $Q_1$ .  $\beta_1 = ?$

d) Find the minimum  $\beta$  for transistor  $Q_1$  to be in saturation.  $\beta_{1min} = ?$


You replace  $Q_1$  with a different transistor so that  $\beta_1 > \beta_{1min}$ . Use this from now on.

e) Find the new load current.  $I_L = ?$  Be sure to explicitly check any assumption you make about the state of  $Q_2$ .






f) Find the power dissipated in transistor  $Q_2$ .  $P_{Q2} = ?$

g) The diode in this circuit conducts a significant current: (circle one)  
 A) never. D) always.  
 B) when the switch first closes. E) when the switch first opens.  
 C) whenever the switch is closed. F) whenever the switch is open.




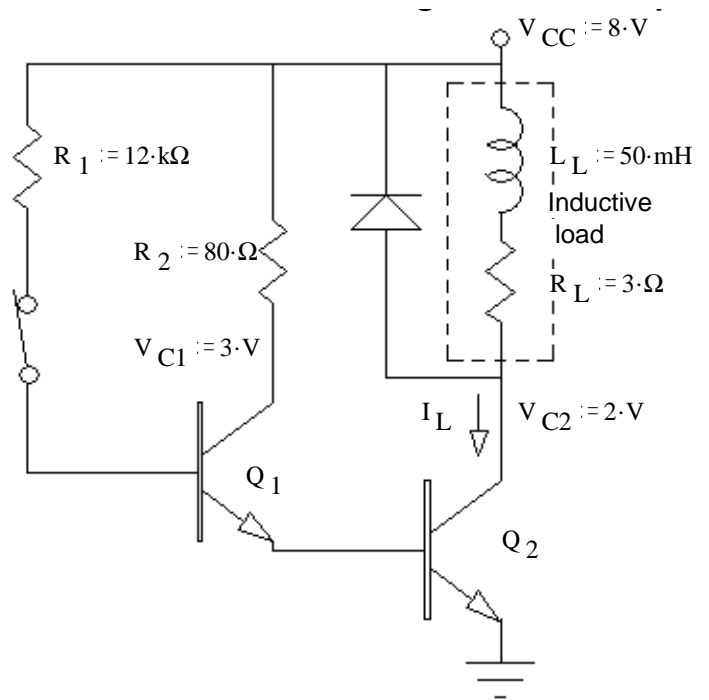
h) What is the maximum diode current you expect when the switch is cycled. (Answer 0 if it never conducts.)



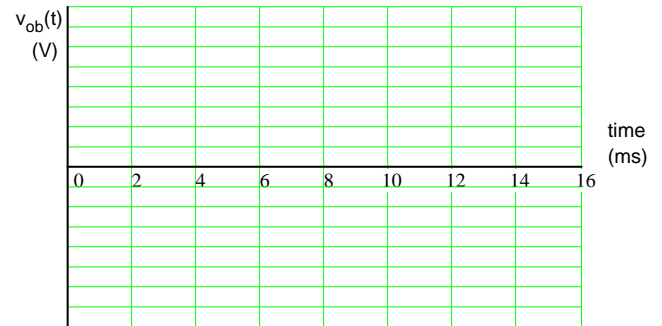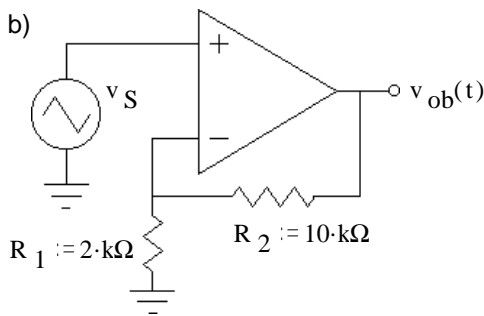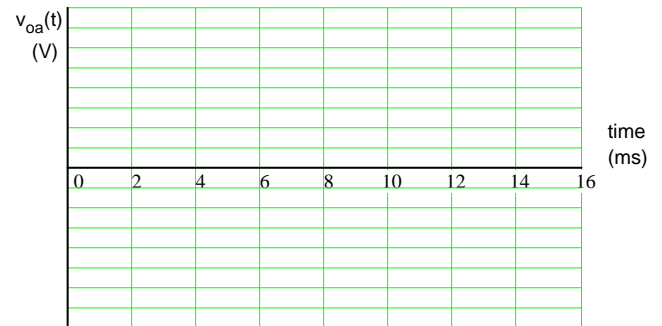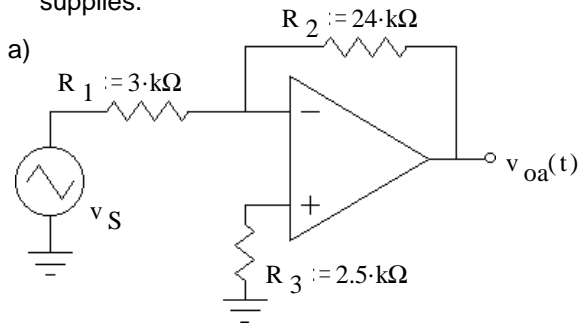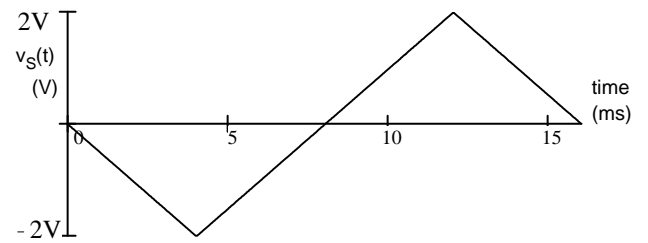4. (32 pts) The same input signal (at right) is connected to several op-amp circuits below. Sketch the output waveform for each circuit. Clearly label important voltage levels on each output. If I can't easily make out what your peak values are, I'll assume you don't know. Don't forget to show inversions. All op-amps are powered by  $\pm 15$  V power supplies.



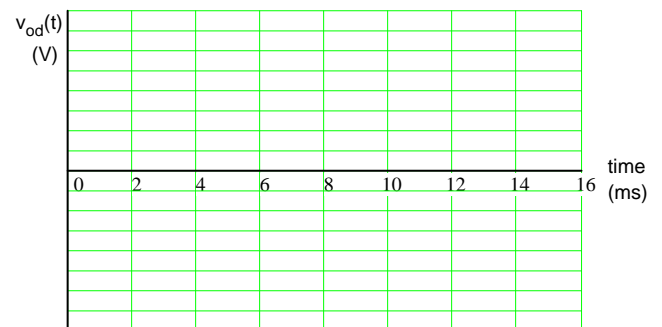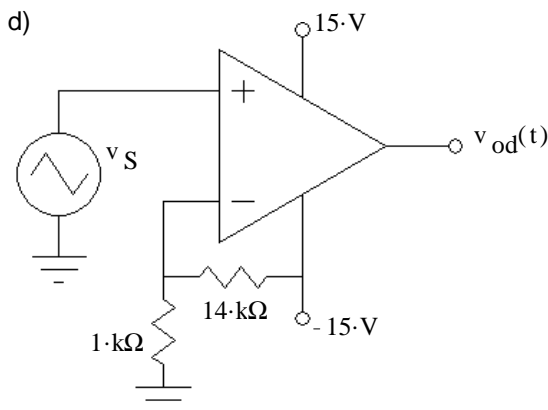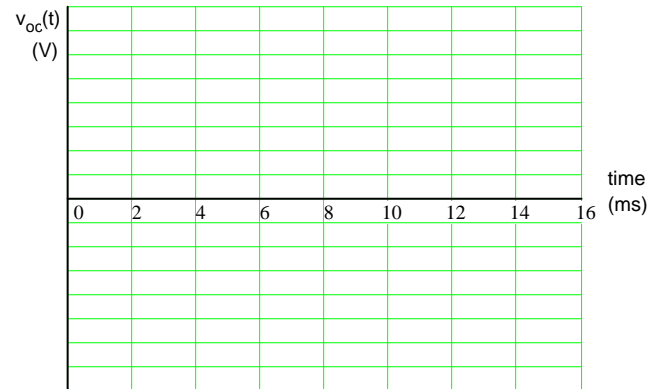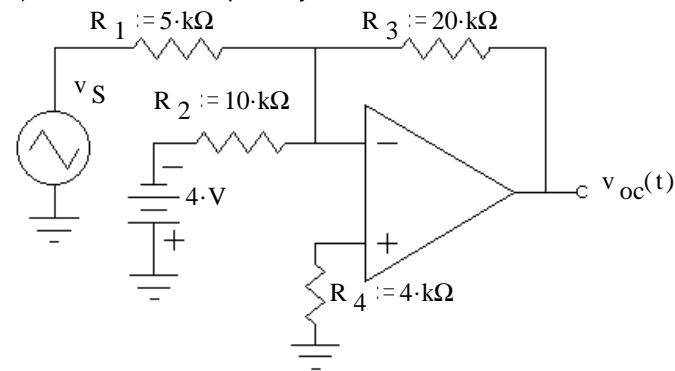
c) Please note the polarity of the 4-V DC source.



5. (42 pts) the Cs, L, & R together are the load in the circuit shown. Find the following: Be sure to show the correct units for each value.

a) The magnitudes of these 3 currents.

$$|I_{R1}| = ? \quad |I_L| = ? \quad |I_C| = ?$$

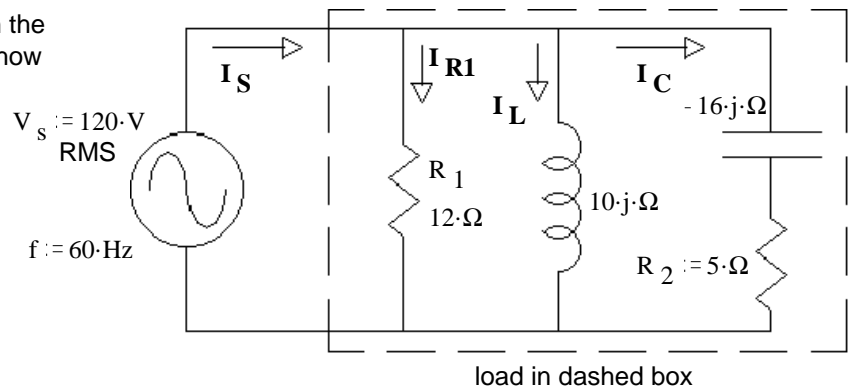

b) The real power.  $P = ?$

c) The reactive power.  $Q = ?$

d) The complex power.  $S = ?$

e) The apparent power.  $|S| = ?$

f) The power factor.  $pf = ?$








g) The power factor is: i) leading ii) lagging (circle one)

h) The magnitude of the source current.  $|I_S| = ?$

i) Remove the inductor and replace it with a new component which makes the power factor the entire load perfect (make  $pf = 1$ ). Determine the type and value of this component.

j) Find the new magnitude of the source current.  $|I_S| = ?$

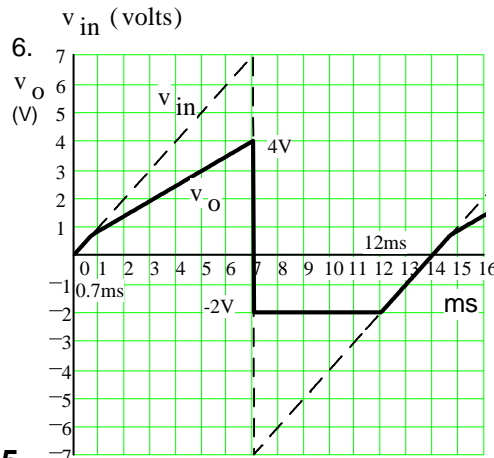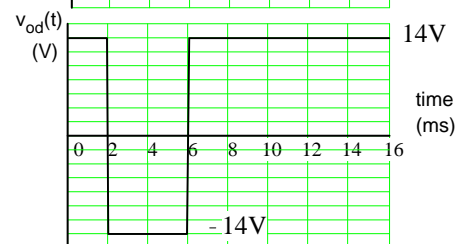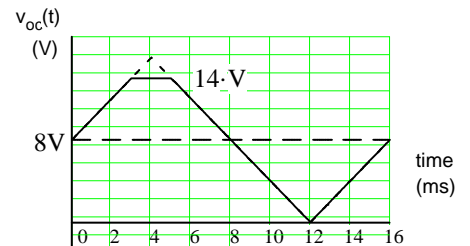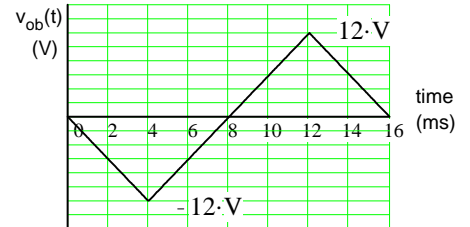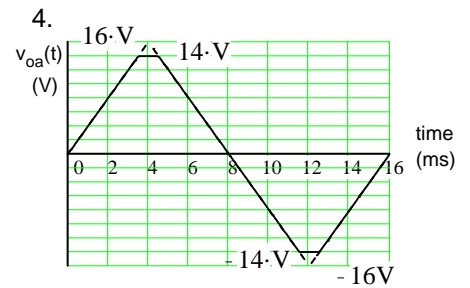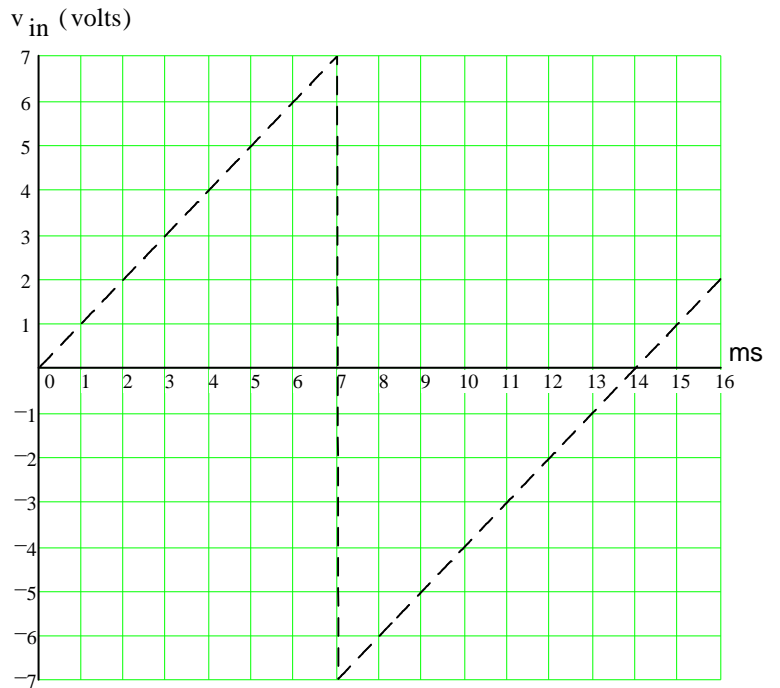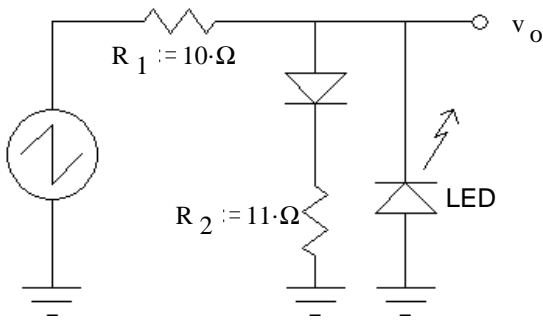6. (24 pts) A voltage waveform (dotted line) is applied to the circuit shown. Accurately draw the output waveform ( $v_o$ ) you expect to see. Label important times and voltage levels.



### Answers

1.  $-2 \cdot V$     $58.3 \cdot mA$    2.  $81.7 \Omega / -21.5^\circ$
3. a)  $4 \cdot W$    b) 32   c) 113.6  
d) 161.4   e)  $2.6 \cdot A$    f)  $0.52 \cdot W$   
g) E)   h)  $2.6 \cdot A$
5. a)  $10 \cdot A$     $12 \cdot A$     $7.16 \cdot A$    b)  $1456 \cdot W$   
c)  $620 \cdot VAR$    d)  $(1456 + 620 \cdot j) \cdot VA$   
e)  $1583 \cdot VA$    f) 0.92   g) ii)  
h)  $13.2 \cdot A$    i) Replace inductor with  
j)  $12.14 \cdot A$    a  $46.6 \text{mH}$  inductor.