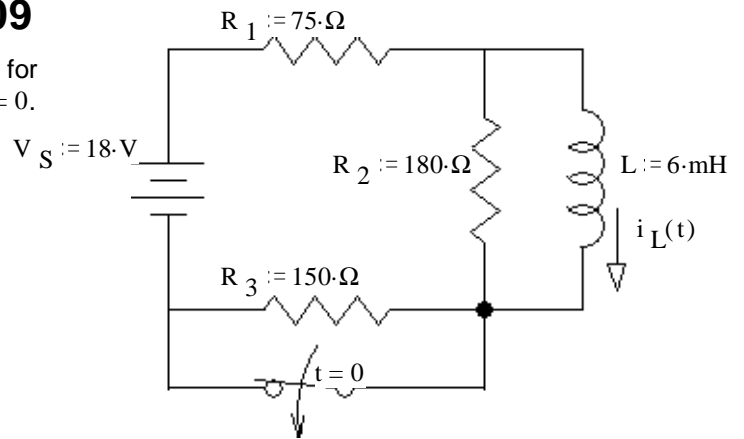


# ECE2210 Final given: Spring 09

1. (22 pts) The switch has been open (not making contact) for a long time and is switched closed (as shown) at time  $t = 0$ .

- Find the complete expression for  $i_L(t)$ .
- Find  $i_L$  at time  $t = 1.2\tau$ .
- At time  $t = 1.2\tau$  the switch is opened again. Will the time constant be different now? If yes, find the new time constant.




2. (12 pts) a) Find the s-type transfer function of the circuit shown.

You **MUST** show work to get credit. Simplify your expression for  $H(s)$  so that the denominator is a simple polynomial.

$H(s) = ?$


b) How many poles does this transfer function have?

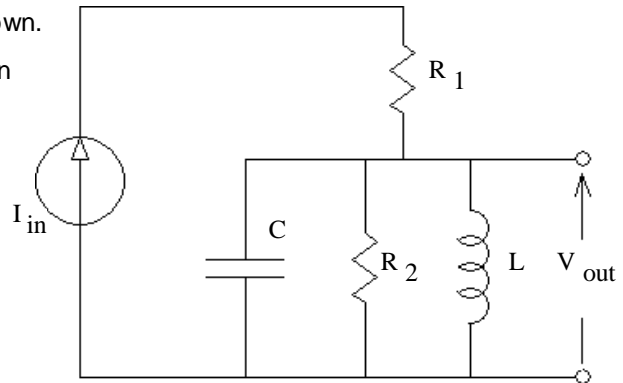c) Does the transfer function have any zeroes? If yes, express them in terms of the circuit parts.



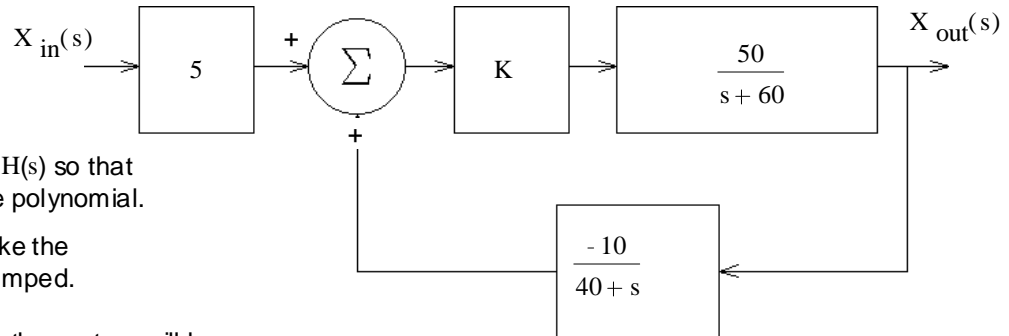3. (17 pts) a) A feedback system is shown in the figure. What is the transfer function of the whole system, with feedback.

$$H(s) = \frac{X_{out}(s)}{X_{in}(s)} = ?$$




Simplify your expression for  $H(s)$  so that the denominator is a simple polynomial.

b) Find the value of  $K$  to make the transfer function critically damped.

c) If  $K$  is **less** than this value the system will be: underdamped or overdamped Circle one

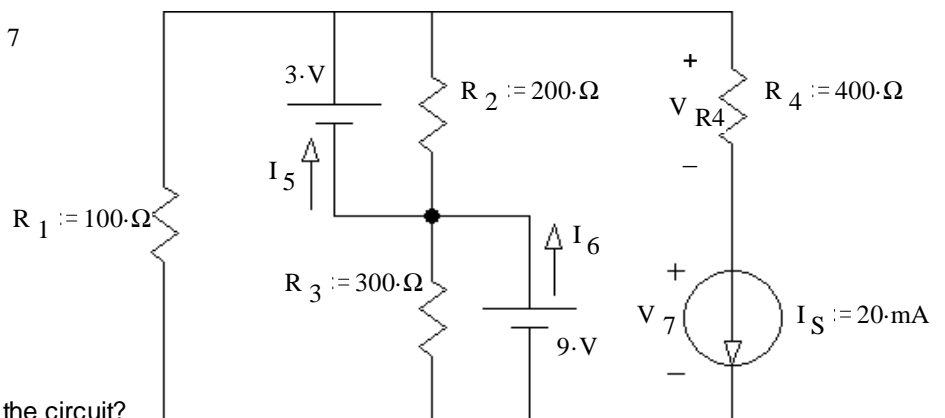4. (18 pts) a) Find:  $I_5$   $I_6$  &  $V_7$



b)  $I_S$  Supplies how much power to the circuit?

**ECE2210 Final given: Spring 09 p2**

Use constant-voltage-drop models for the diodes and LEDs on this exam.

5. (22 pts) Assume that diodes  $D_1$  and  $D_3$  **DO** conduct.

Assume that diode  $D_2$  does **NOT** conduct.


a) Stick with these assumptions even if your answers come out absurd.

Find the following:

$I_{D1} =$  \_\_\_\_\_

$I_{D3} =$  \_\_\_\_\_

$V_{D2} =$  \_\_\_\_\_

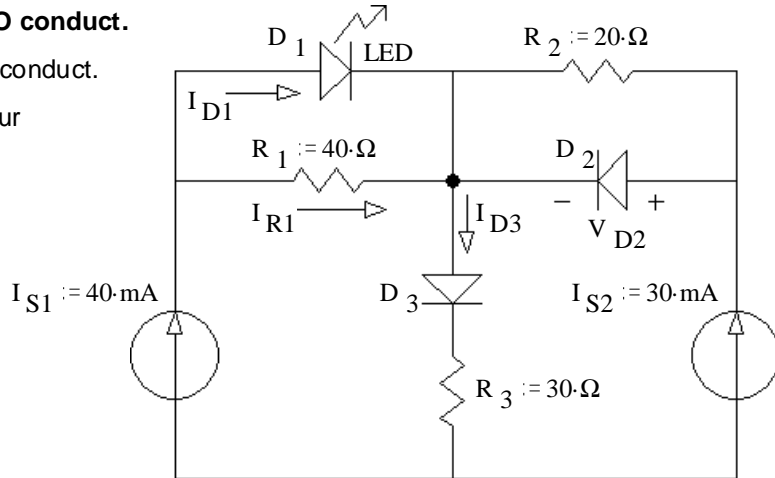

b) Based on the numbers above, was the assumption about  $D_1$  correct? Circle one:    yes    no  
How do you know? (Specifically show a value which is or is not within a correct range.)




c) Based on the numbers above, was the assumption about  $D_2$  correct? Circle one:    yes    no  
How do you know? (Specifically show a value which is or is not within a correct range.)

d) Based on the numbers above, was the assumption about  $D_3$  correct? Circle one:    yes    no  
How do you know? (Specifically show a value which is or is not within a correct range.)

e) Based on your answers to parts b), c) & e), which of the following need to be recalculated:



Circle those answers that that are wrong:     $I_{D1}$      $I_{D3}$      $V_{D2}$

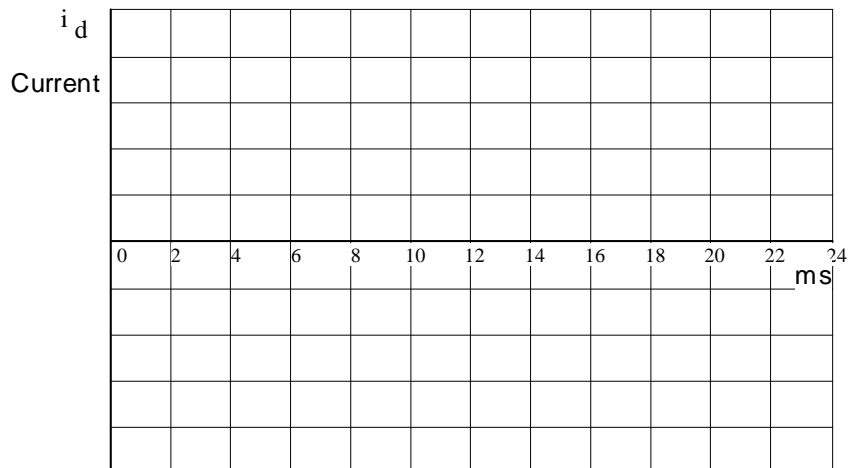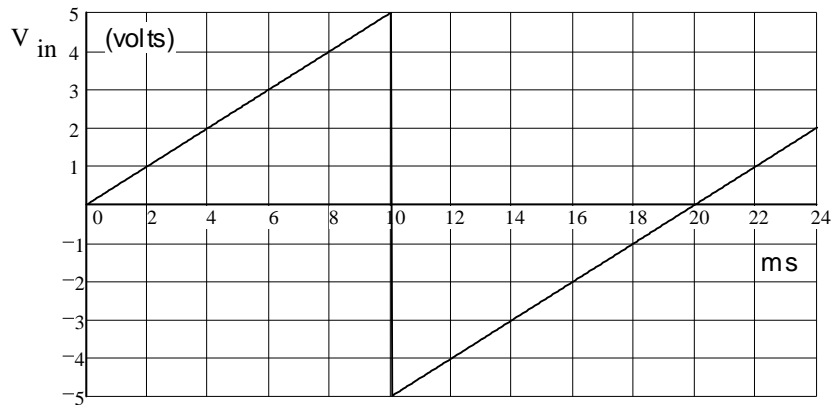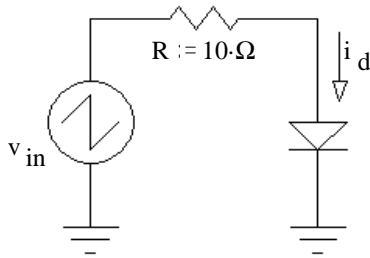6. (12 pts) A voltage waveform is applied to the circuit shown. Accurately draw the diode current waveform ( $i_d$ ) you expect to see. Label important times and current levels.





**ECE2210 Final given: Spring 09 p3**

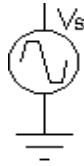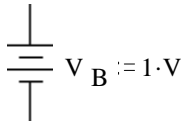7. (34 pts) You have two input voltages to work with. A 1V battery and the waveform (at right).




The problems below are op-amp design problems. The answer should be a schematic of a circuit showing the values of all the parts. Use reasonable resistor values (in the  $100\Omega$  to  $1\text{ M}\Omega$  range). Also show how one or both of the sources are hooked up to your circuit. Most circuits won't need both.

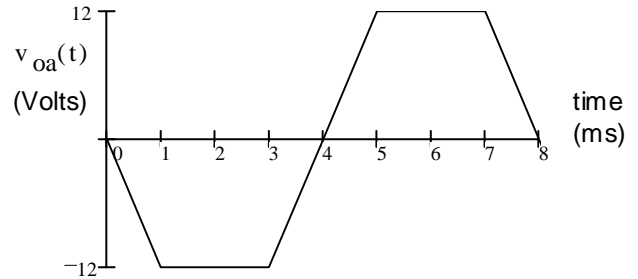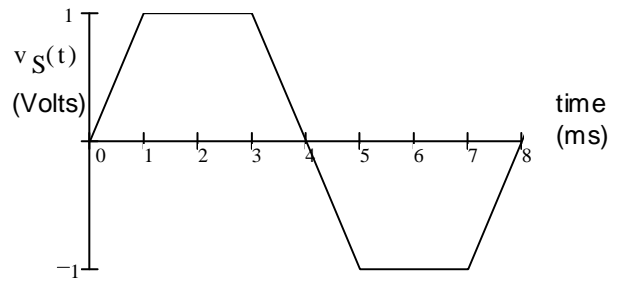
a) Design a circuit which will output the waveform at right.



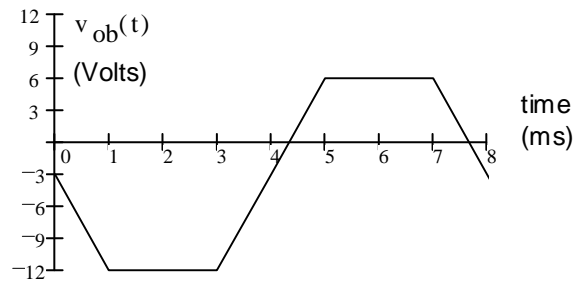
b) Design a circuit which will output the waveform at right.



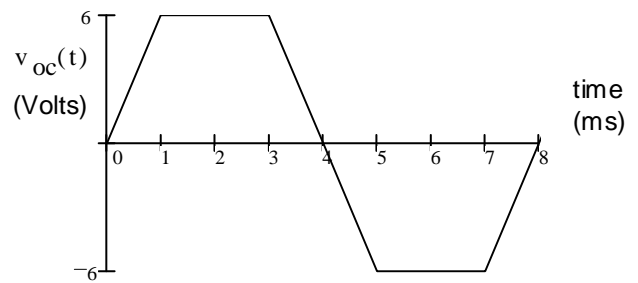c) Design a circuit which will output the waveform at right.



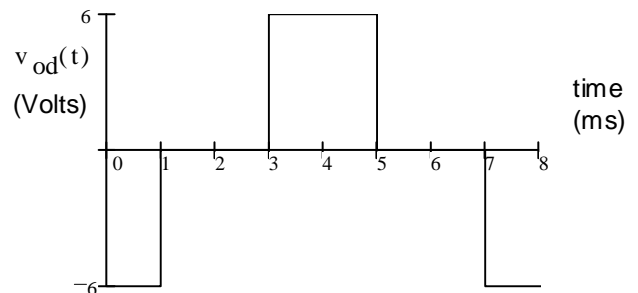d) Design a circuit which will output the waveform at right. Hint: Think differentiation.





10. Do you want your grade and scores posted on my door and on the Internet? If your answer is yes, then provide some sort of password

or alias: \_\_\_\_\_  
 otherwise, leave blank

The grades will be posted on my door in alphabetical order under the alias that you provide here. I will not post grades under your real name. The Internet version will be a pdf file which you can download. Both will show the homework, lab, and exam scores of everyone who answers here.

Name \_\_\_\_\_

Scores:  
 pages 1-2 \_\_\_\_\_ / 34 pts  
 pages 3-4 \_\_\_\_\_ / 35 pts  
 pages 5-6 \_\_\_\_\_ / 34 pts  
 pages 7-8 \_\_\_\_\_ / 34 pts  
 pgs 9-10 \_\_\_\_\_ / 26 pts  
 page 11 \_\_\_\_\_ / 17 pts

Total \_\_\_\_\_ / 180 pts

**Answers**


1. a)  $240 \cdot \text{mA} - 160 \cdot \text{mA} \cdot e^{-\frac{t}{0.113 \cdot \text{ms}}}$       b) 192·mA      c) 60·μs      2. a)  $\frac{1}{C} \cdot s$       b) 2      c) yes, 0

3. a)  $5 \cdot \frac{(50 \cdot \text{K}) \cdot (s + 40)}{s^2 + 100 \cdot s + 500 \cdot \text{K} + 2400}$       b) 0.2      c) overdamped       $\frac{1}{C \cdot R_2} \cdot s + \frac{1}{C \cdot L}$

4. a) 155·mA    170·mA    4·V      b) - 80·mW

5. a) - 10·mA    70·mA    0.6·V  
 b) no  $I_{D1} = -10 \cdot \text{mA} < 0$   
 c) yes  $V_{D2} = 0.6 \cdot \text{V} < 0.7 \text{V}$   
 d) yes  $I_{D3} = 70 \cdot \text{mA} > 0$     e)  $I_{D1}$

6.

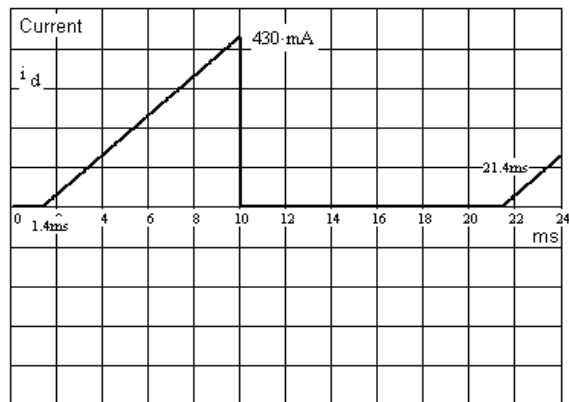

7. a) inverting amp with  $R_f = 12R$   
 b) summer with  $R_f = 9R_1$  waveform is hooked to  $R_1$  &  $R_f = 3R_2$  battery + terminal is hooked to  $R_2$  and - to ground  
 c) non-inverting amp with  $R_f = 5R$   
 d) differentiator with  $R_f = 6V/(C(1000V/s))$ , if  $C = 1\mu\text{F}$  then  $R_f = 6\text{k}\Omega$

8. a) 1.84·A    2.32·V    4.27·W    b) yes  $V_{CE} = 2.32 \cdot \text{V} > 0.2 \cdot \text{V}$     c) 45.7·Ω    d) 97.6    e) D    f) 2.9·A

9. a) 240·W      b) 200·W      c) NO