
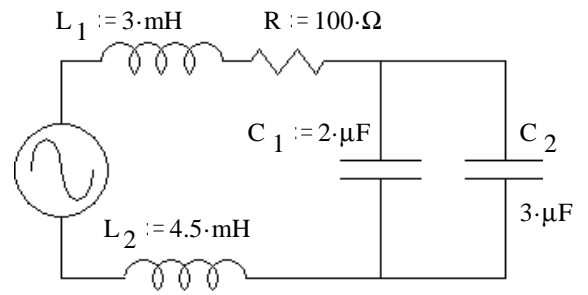


# ECE2210 Final given: Spring 11

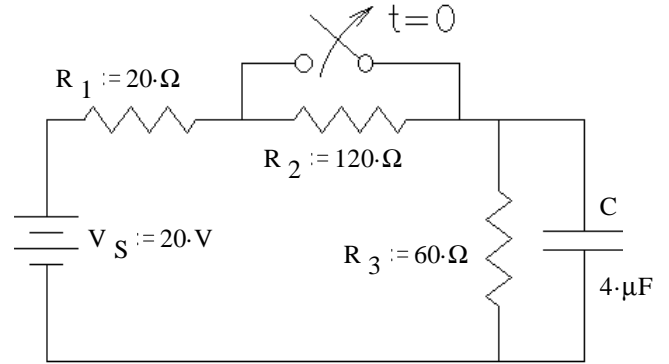1. (10 pts) Find the resonant frequency (or frequencies) of the circuit shown (in cycles/sec or Hz).



2. (25 pts) The switch has been closed (making contact) for a long time and is switched open (as shown) at time  $t = 0$ .



a) Find the complete expression for  $v_C(t)$ .


b) What is  $v_C$  when  $t = \tau$ ?  $v_C(\tau) = ?$

c) At time  $t = \tau$  the switch is closed again. Find the complete expression for  $v_C(t')$ , where  $t'$  starts at  $t = \tau$ . Be sure to clearly show the time constant.

3. 9 pts)  $Z := |Z| \cdot e^{j40\text{-deg}}$  We don't know its magnitude, but its phase angle is  $+40^\circ$ .


$$\omega := 3000 \frac{\text{rad}}{\text{sec}}$$

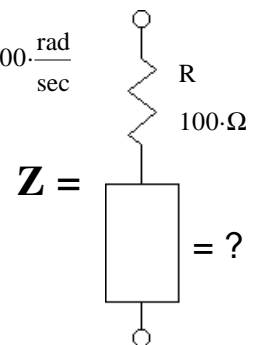$Z$  is made of a  $100\Omega$  resistor in series with one other part. What is the part? Give type and value.



4. (24 pts) An inductor is used to completely correct the power factor of a load. Find the following:

a) The power consumed by the load.  $P_L = ?$   
Hint 1: Since  $L$  corrects the power factor, its  $Q$  must exactly cancel the load's  $Q$  and the source provides only  $P$  and no  $Q$ .

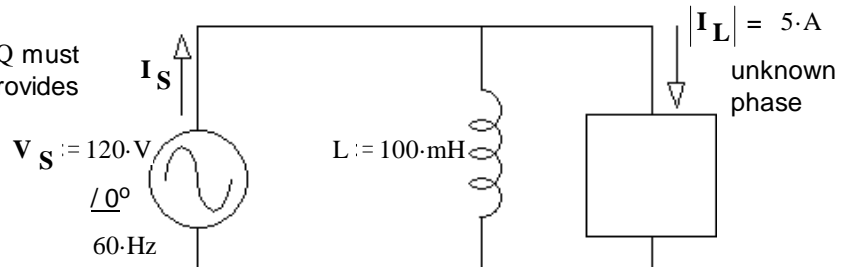

Hint 2: If hint 1 doesn't make sense to you, you don't know AC power well enough to do part a) -- so skip to part b).

If you can't find this power, mark an x here \_\_\_\_\_ and assume  $P_L = 550\text{W}$  for the rest of the problem.

b) The power supplied by the source.  $P_S = ?$

c) The source current (magnitude and phase).  $I_S = ?$

d) The load can be modeled as 2 parts in series. Draw the model and find the values of the parts.

e) The inductor,  $L$ , is replaced with a  $50\text{ mH}$  inductor.


- circle one
- i) The **new** source current  $|I_S|$  is **greater** than that calculated in part c).
  - ii) The **new** source current  $|I_S|$  is **the same** as that calculated in part c).
  - iii) The **new** source current  $|I_S|$  is **less** than that calculated in part c).

**ECE2210 Final given: Spring 11 p2**

5. (15 pts) a) Find the s-type transfer function of the circuit shown after time  $t = 0$ . Consider  $I_2$  as the "output".

You **MUST** show work to get credit. Simplify your expression for  $H(s)$  so that the denominator is a simple polynomial with no coefficient before the highest-order  $s$  term in the denominator.

$$H(s) = \frac{I_2(s)}{I_{in}(s)} = ?$$

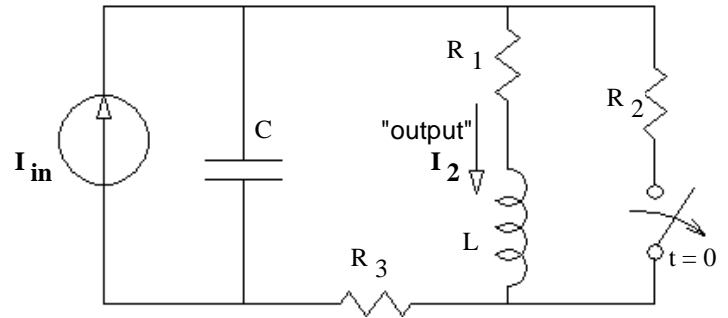



b) How many zeroes does this transfer function have?

If it has 1 or more, express them (probably in terms of  $R_1, R_2, R_3, L$  and  $C$ ).

c) How many poles does this transfer function have?

If it has 1 or more, express them (probably in terms of  $R_1, R_2, R_3, L$  and  $C$ ).

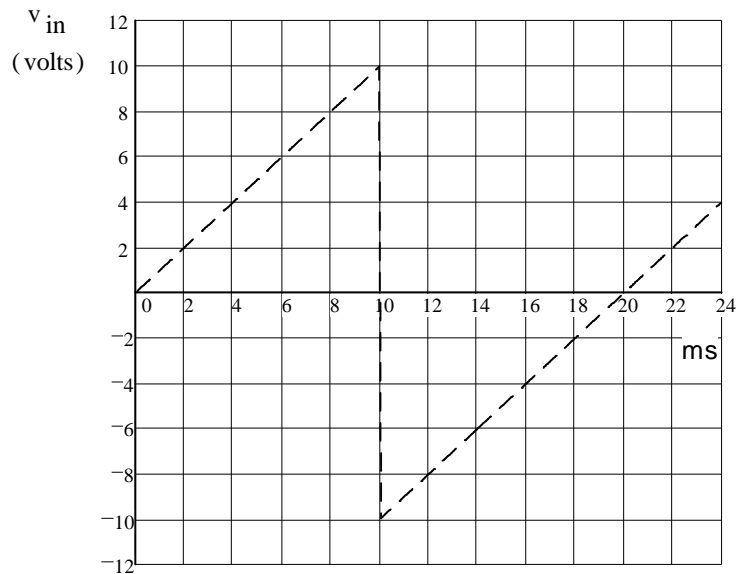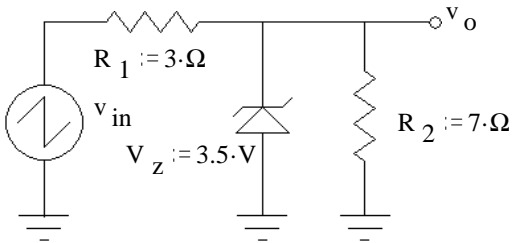6. (22 pts) A voltage waveform (dotted line) is applied to the circuit shown. Accurately draw the output waveform ( $v_o$ ) you expect to see. Label important times **and** voltage levels.



7. (31 pts) A couple of transistors are used to control the current flow through an inductive load.

a) The switch is open, as shown. What is the maximum  $R_2$  can be if transistor  $Q_2$  is in saturation.


$$\beta_2 = 30 \quad R_2 = ?$$

b) Find the power dissipated in transistor  $Q_2$  with this  $R_2$ .  $P_{Q2} = ?$

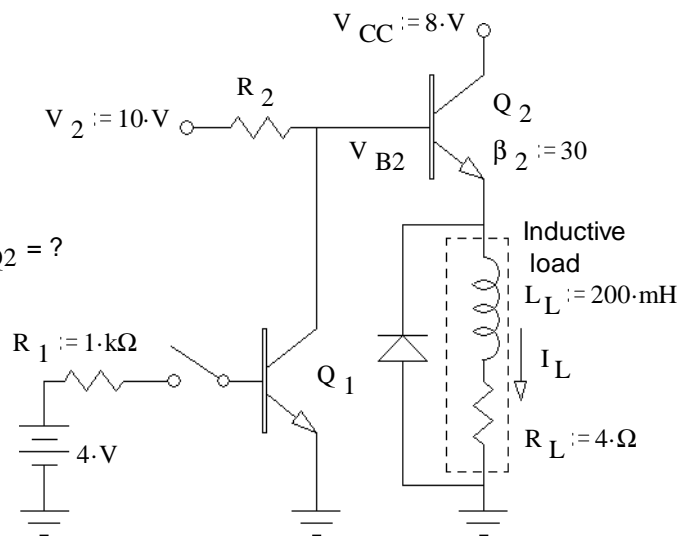c) When the switch is closed, you would like transistor  $Q_1$  to saturate. What minimum  $\beta_1$  would be required to achieve saturation?

$$\beta_{1min} = ?$$

Assume at least this  $\beta_1$  for the remainder of the problem.



d) What if the voltage  $V_2$  was too low so that the base voltage of transistor  $Q_2$  was only 6V, how much power would be dissipated in transistor  $Q_2$ ?

$$\text{IF } V_{B2} := 6\text{-V} \quad P_{Q2} = ?$$

e) The transistor  $Q_2$  was selected to be able to handle the power found in part b) (with a 2x factor of safety).  
 What would happen with the  $V_2$  of part d)?

$V_2$  is NOT too low for the remainder of the problem, that is, use the original  $V_2 = 10 \cdot V$

- f) The diode in this circuit conducts a significant current: (circle one)
- A) never. D) always.
  - B) when the switch closes. E) when the switch opens.
  - C) whenever the switch is closed. F) whenever the switch is open.

g) What is the maximum diode current you expect when the switch is cycled. (Answer 0 if it never conducts.)

h) This circuit design is: (circle as many as apply and don't forget to say **why**)

- A) incredibly fantastic. C) dumb.
- B) a very good design. D) not a good design.

Why?


Use constant-voltage-drop models for the diodes and LEDs on this exam.

8. (24 pts) Assume that diode  $D_1$  does **NOT** conduct.

Assume that diodes  $D_2$  and  $D_3$  **DO** conduct.

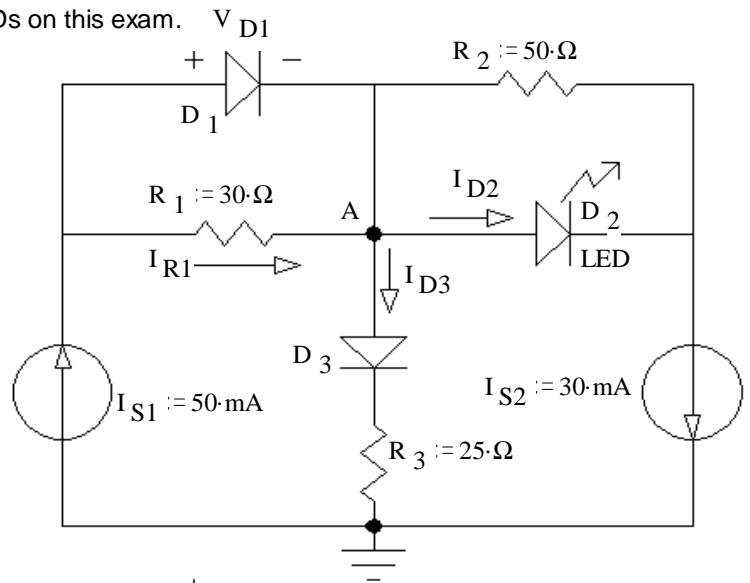a) Stick with these assumptions even if your answers come out absurd.  
 Find the following:

- $V_{D1} =$  \_\_\_\_\_
- $I_{D2} =$  \_\_\_\_\_
- $I_{D3} =$  \_\_\_\_\_
- $V_A =$  \_\_\_\_\_



b) Based on the numbers above, was the assumption about  $D_1$  correct?    yes    no    (circle one)  
 How do you know? (Specifically show a value which is or is not within a correct range.)

c) Was the assumption about  $D_2$  correct?    yes    no  
 How do you know? (Show a value & range.)  
(circle one)






d) Was the assumption about  $D_3$  correct?    yes    no  
 How do you know? (Show a value & range.)

e) Based on your answers to parts b), c) & e), Circle one:  
(circle one)  
 Justify your answer.

- i) The **real**  $I_{R1} < I_{R1}$  calculated in part a.
- ii) The **real**  $I_{R1} = I_{R1}$  calculated in part a.
- iii) The **real**  $I_{R1} > I_{R1}$  calculated in part a.

**ECE2210 Final given: Spring 11 p4**

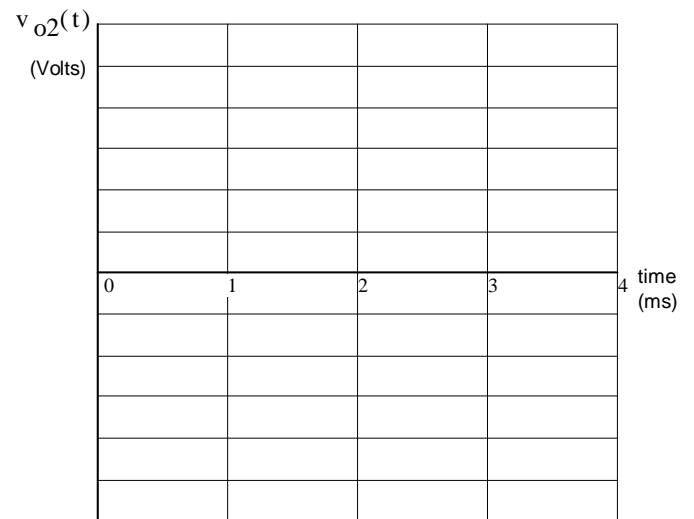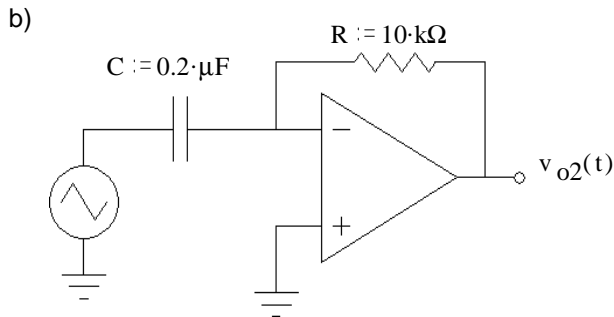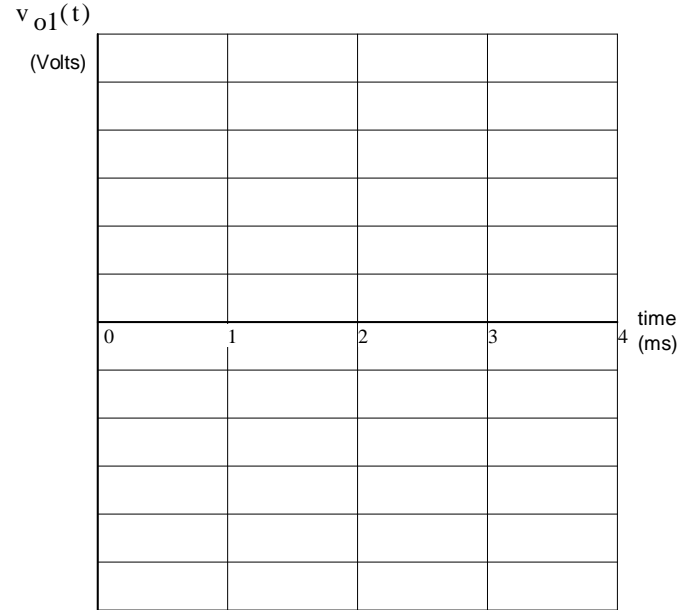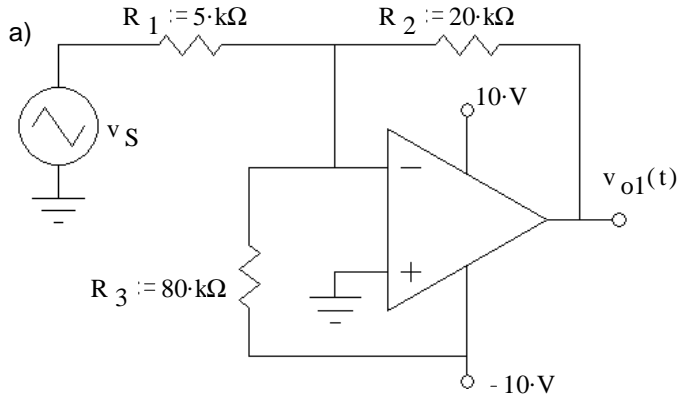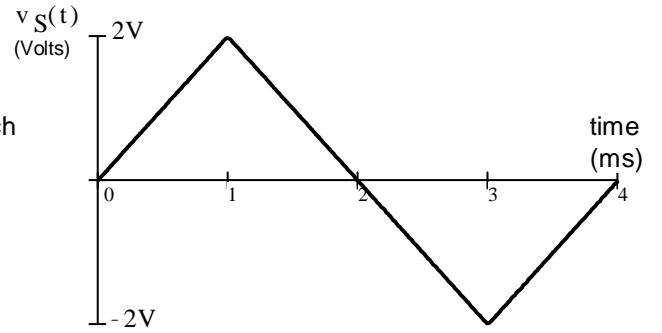10. (18 pts) The same input signal (at right) is connected to several op-amp circuits below. Sketch the output waveform for each circuit. Clearly label important voltage levels on each output. If I can't easily make out what your peak values are, I'll assume you don't know. Don't forget to show inversions. All op-amps are powered by  $\pm 10$  V power supplies.



9. Do you want your grade and scores posted on the Internet?  
 If your answer is yes, then provide some sort of alias. \_\_\_\_\_

otherwise, leave blank

The grades will be posted on line in pdf form in alphabetical order under the alias that you provide here. I will not post grades under your real name. It will show the homework, lab, and exam scores of everyone who answers here.

**Answers**

1. 822·Hz

2. a)  $6 \cdot V + 9 \cdot V \cdot e^{-\frac{t}{168 \cdot \mu s}}$       b) 9.31·V      c)  $15 \cdot V - 5.69 \cdot V \cdot e^{-\frac{t}{60 \cdot \mu s}}$


3. 28·mH Inductor

4. a) 463·W      b) 463·W      c) 3.86·A  $\angle 0^\circ$       d)  $R := 18.5 \cdot \Omega$        $C := 174 \cdot \mu F$       e) i)

5. a)  $\frac{1}{s^2 + \frac{R_1 + R_3}{L} \cdot s + \frac{1}{L \cdot C}}$       b) 0

c)  $2 \cdot \frac{R_1 + R_3}{L} \pm \sqrt{\left(\frac{R_1 + R_3}{L}\right)^2 - \frac{4}{L \cdot C}}$

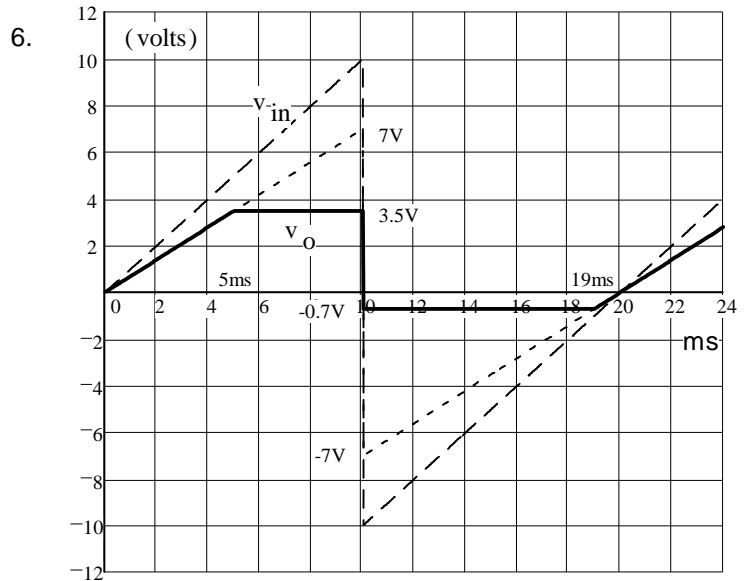7. a) 23.1·Ω or 23.8·Ω (2nd ans is more accurate)      b) 0.39·W  
 c) 129 or 125      d) 3.58·W  
 e) The smoke would get out.      f) B      g) 1.95·A  
 h) C & D There are good ways to do this same thing without the extra requirement of  $V_2$ , and this extra voltage makes the transistor  $Q_2$  more vulnerable to failure (see part d)).



8. a) 1.5·V    -10·mA    20·mA    1.2·V      b) no     $V_{D1} := 1.5 \cdot V > 0.7V$       c) no     $I_{D2} := -10 \cdot mA < 0$   
 d) yes     $I_{D3} := 20 \cdot mA > 0$       e) i)  $V_{R1}$  is actually 0.7·V which is less than 1.5·V

so less current will flow through  $R_1$

9.  $v_{o1}(t)$

