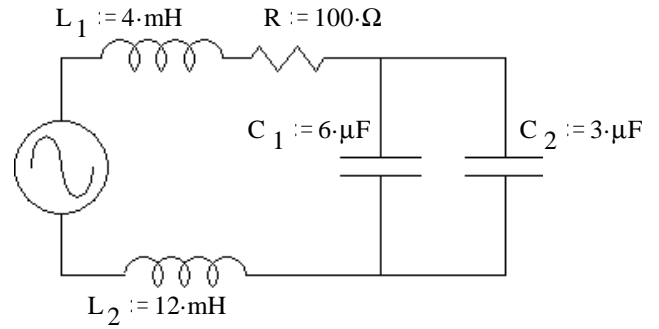



# ECE2210 Final given: Spring 17

1. (10 pts) Find the resonant frequency (or frequencies) of the circuit shown (in cycles/sec or Hz).



2. (25 pts) The switch has been closed (making contact) for a long time and is switched open (as shown) at time  $t = 0$ .

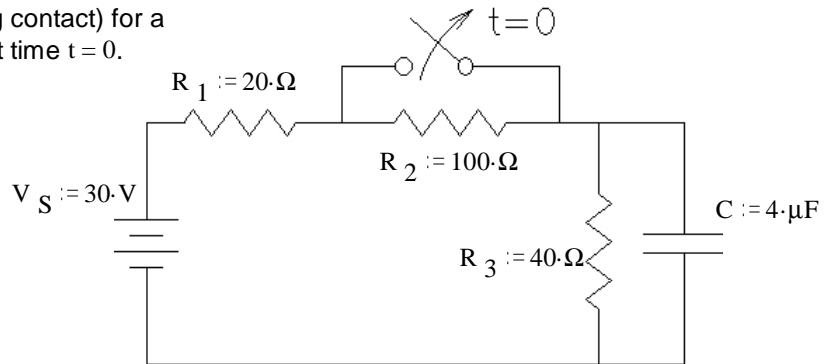
a) Find the complete expression for  $v_C(t)$ .



b) What is  $v_C$  when  $t = \tau$ ?  $v_C(\tau) = ?$


c) At time  $t = \tau$  the switch is closed again. Find the complete expression for  $v_C(t')$ , where  $t'$  starts at  $t = \tau$ . Be sure to clearly show the time constant.

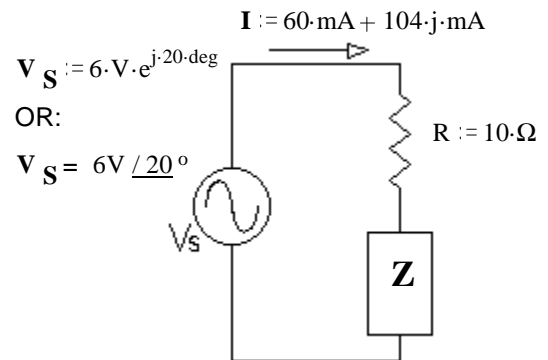3. (14 pts) Find  $Z$ . Express in simplest polar or rectangular form.



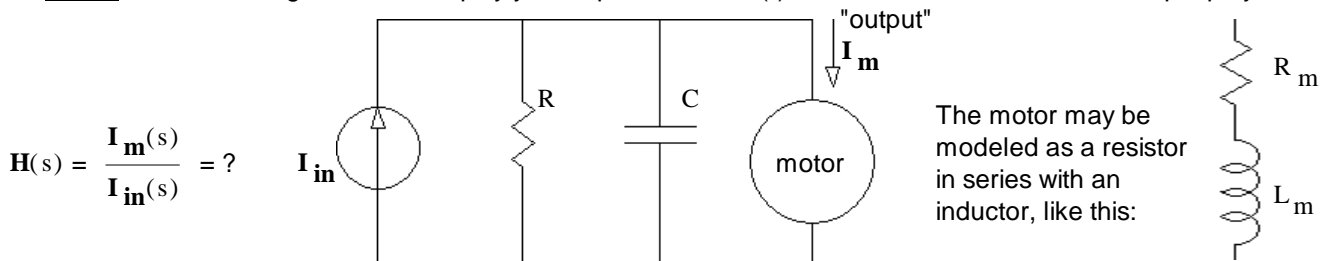4. (15 pts) a) Find the s-type transfer function of the circuit shown. Consider the motor current ( $I_m$ ) as the "output".

You **MUST** show work to get credit. Simplify your expression for  $H(s)$  so that the denominator is a simple polynomial.



$$H(s) = \frac{I_m(s)}{I_{in}(s)} = ?$$

b) How many poles does this transfer function have?

c) How many zeroes does this transfer function have?


If it has 1 or more, express them (probably in terms of  $R_1$ ,  $C$ ,  $R_m$ , and  $L_m$ ).

**ECE2210 Final given: Spring 17 p2**

5. (30 pts) A couple of transistors are used to control the current flow through an inductive load.

- a) The switch has been closed for a long time. You measure the voltage at the collector of  $Q_2$  to be the value shown (referenced to ground). Find the power dissipated in transistor  $Q_2$ .

$P_{Q2} = ?$

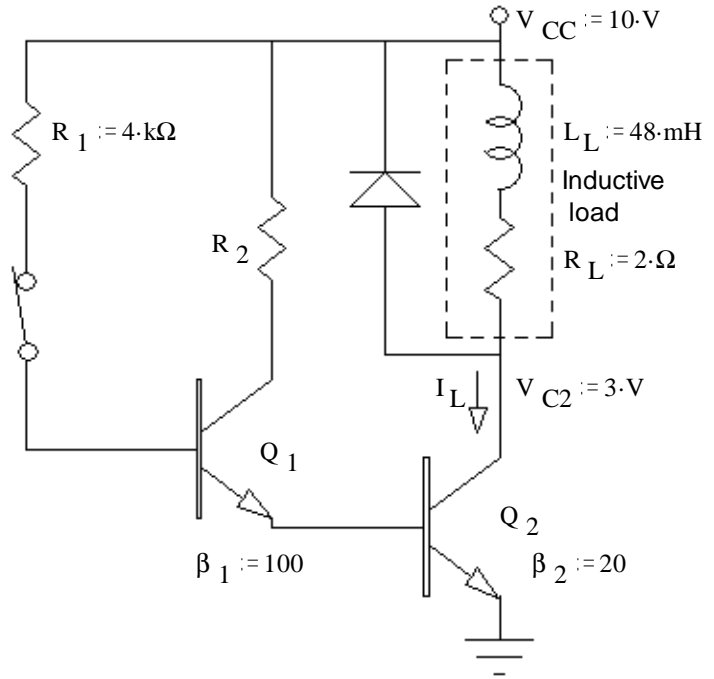

- b)  $Q_1$  is in saturation, what is the value of  $R_2$ ?

You may assume that the emitter current of  $Q_1$  is approximately equal to the collector current of  $Q_1$ .  $R_2 = ?$

- c) Determine if  $Q_1$  actually is saturated. Show how you find this.

Is  $Q_1$  actually saturated? Circle one:    yes    no

- d) Find the minimum value  $\beta_2$  so that  $Q_2$  will be in saturation.     $\beta_{2min} = ?$



- e) Find the power dissipated in transistor  $Q_2$  with the  $\beta$  you just calculated ( $Q_2$  in saturation).     $P_{Q2} = ?$

- f) The diode in this circuit conducts a significant current:    (circle one)  
 A) never.    C) whenever the switch is closed.    E) when the switch first opens.  
 B) when the switch first closes.    D) always.    F) whenever the switch is open.

- g) What is the maximum diode current you expect when the switch is cycled. (Answer 0 if it never conducts.)  
 Assume the  $\beta_2$  of part d ( $Q_2$  in saturation when on).


**ECE2210 Final given: Spring 17 p3**

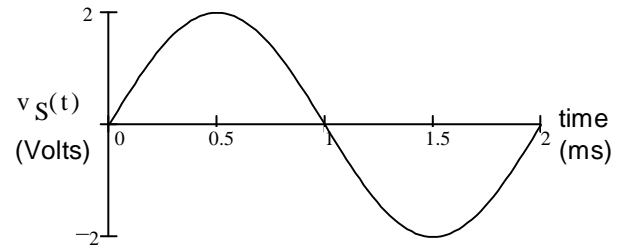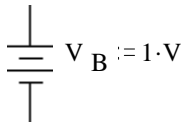6. (34 pts) You have two input voltages to work with.  
A 1V battery and the waveform (at right).




The problems below are op-amp design problems. The answer should be a schematic of a circuit showing the values of all the parts. Use reasonable resistor values (in the 100Ω to 1 MΩ range). Also show how one or both of the sources are hooked up to your circuit. Most circuits won't need both.

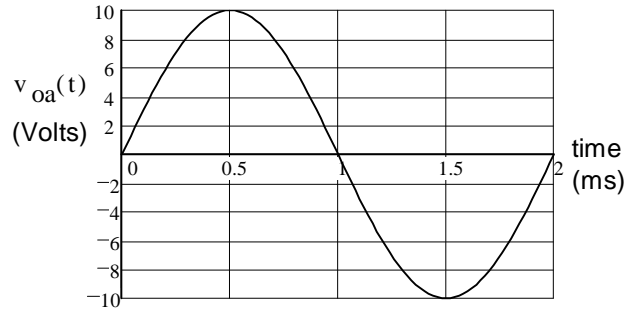a) Design a circuit which will output the waveform at right.




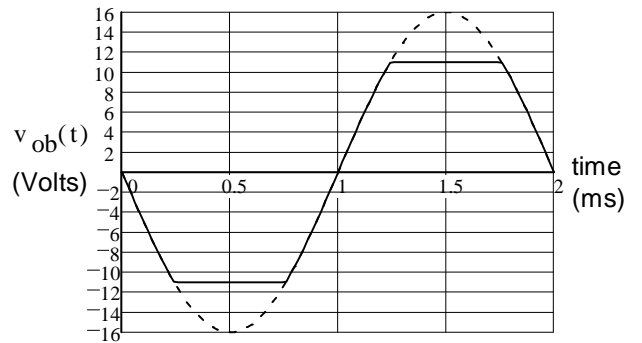b) Design a circuit which will output the waveform at right.




c) What power supply or supplies are being used with your op-amps?

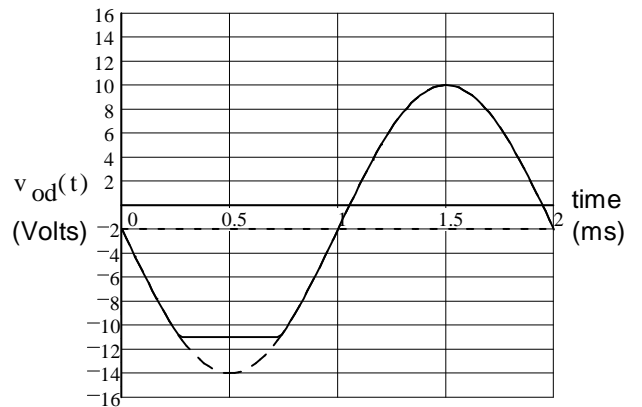d) Design a circuit which will output the waveform at right.




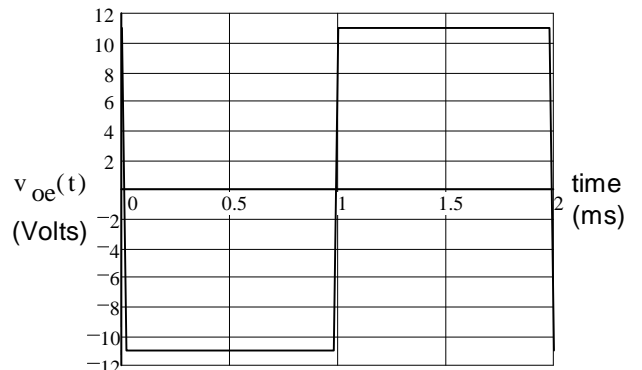e) Design a circuit which will output the waveform at right.  
Hint: Think nonlinear.



**ECE2210 Final given: Spring 17 p4**

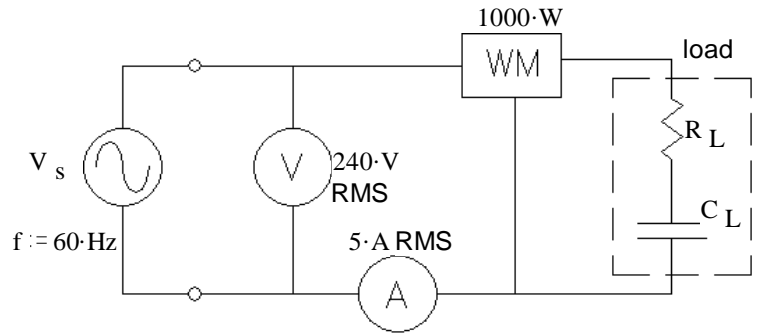7. (20 pts)  $R_L$  &  $C_L$  together are the load in the circuit shown. The voltmeter, ammeter, and wattmeter measurements are shown. Find the following: Include the correct units for each value.



- a) The real power.  $P = ?$
- b) The value of the load resistor.  $R_L = ?$

c) The apparent power.  $|S| = ?$

d) The reactive power.  $Q = ?$

e) The value of the capacitor.  $C_L = ?$


f) The complex power.  $S = ?$

g) The power factor.  $pf = ?$

h) The power factor is: i) leading ii) lagging (circle one)

8. (14 pts) The transformer shown in the circuit below is ideal. It is rated at 120/20 V, 8 VA, 60 Hz. Find the following:



a)  $I_1 = ?$

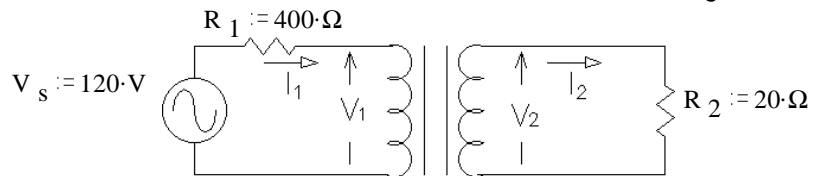

b)  $V_2 = ?$

**ECE2210 Final given: Spring 17 p5**

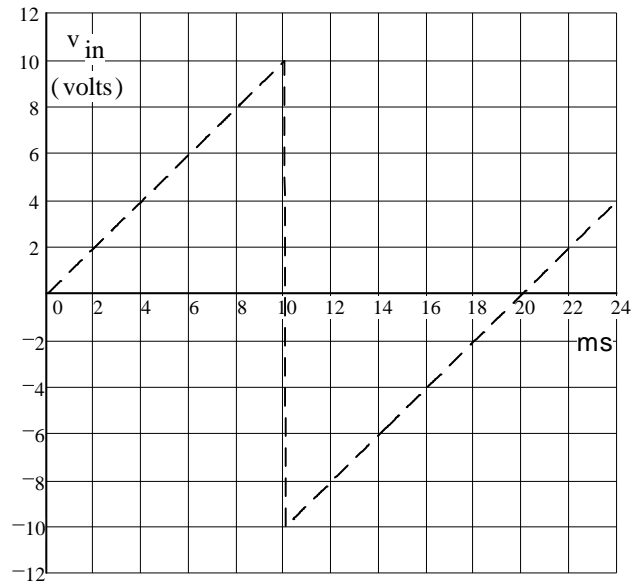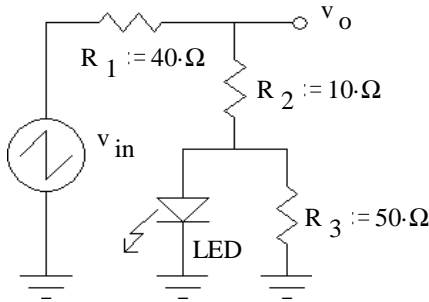9. (18 pts) A voltage waveform (dotted line) is applied to the circuit shown. Accurately draw the output waveform ( $v_o$ ) you expect to see. Label important times and voltage levels.



Folder number \_\_\_\_\_

10. Do you want your grade and scores posted on the Internet?  
If your answer is yes, then provide some sort of alias: \_\_\_\_\_

otherwise, leave blank

The grades will be posted on line in pdf form in alphabetical order under the alias that you provide here. **I will not** post grades under your real name or an alias that looks like a real name or u-number. The pdf spreadsheet will show the homework, lab, and exam scores of everyone who answers here.

**Answers**

1. 419·Hz    2. a)  $7.5 \cdot V + 12.5 \cdot V \cdot e^{-\frac{t}{120 \cdot \mu s}}$     b) 12.1·V    c)  $20 \cdot V - 7.9 \cdot V \cdot e^{-\frac{t}{53.33 \cdot \mu s}}$

3.  $(28.3 - 32.1 \cdot j) \cdot \Omega$      $42.8 \Omega / -48.7^\circ$     4. a)  $\frac{1}{L_m \cdot C}$     b) 2    c) 0

5. a) 10.5·W    b) 52· $\Omega$  OR 52.52· $\Omega$

c)  $\frac{I_{C1}}{I_{B1}} < 100$     YES    d) 28

e) 0.98·W    f) E)    g) 4.9·A

6. a) Non-inverting amp with  $R_f = 4R_1$ .

b) Inverting amp with  $R_f = 8R_1$ .    c)  $\pm 12V$

d) Summer with  $R_f = 6R_1$  &  $R_f = 2R_2$ , waveform is hooked to  $R_1$ , battery + terminal is hooked to  $R_2$  and - to ground.

e) Comparator, waveform is hooked to inverting (-) input, noninverting (+) input is hooked to ground.

7. a) 1000·W    b) 40· $\Omega$     c) 1.2·kVA

d) -663·VAR    e) 100· $\mu F$

f)  $(1 - 0.663 \cdot j) \cdot kVA = 1.2 kVA / -33.6^\circ$     h) i)

8. 107·mA    b) 12.9·V

$$s^2 + \left( \frac{R_m}{L_m} + \frac{1}{R \cdot C} \right) \cdot s + \frac{1}{L_m \cdot C} \cdot \left( 1 + \frac{R_m}{R} \right)$$

