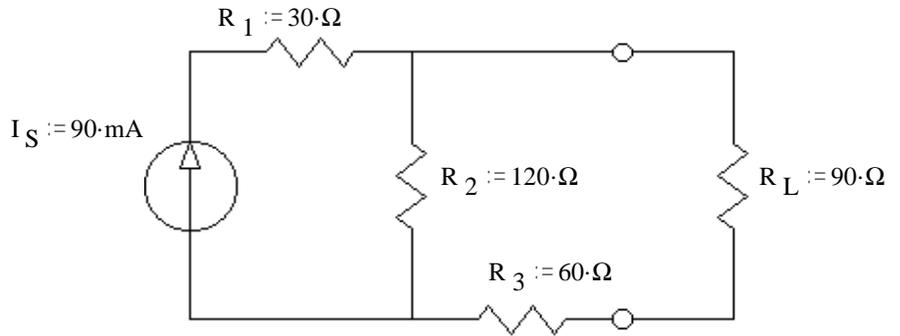


# ECE2210 Final given: Fall 12

1. (15 pts) a) Find and draw the Thévenin equivalent of the circuit shown. The load resistor is  $R_L$ .




b) Find and draw the Norton equivalent of the same circuit.

c) Find the load current using your Thévenin equivalent circuit.

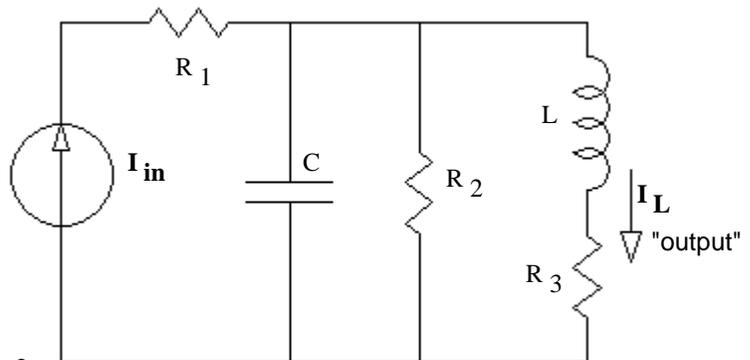2. (15 pts) a) Find the s-type transfer function of the circuit shown. Consider  $I_{in}$  as the input and  $I_L$  as the "output".

You **MUST** show work to get credit. Simplify your expression for  $H(s)$  so that the denominator is a simple polynomial with no coefficient before the highest-order  $s$  term in the denominator.



$H(s) = ?$

b) How many zeroes does this transfer function have?

If it has 1 or more, express them (probably in terms of  $R_1, R_2, R_3, L$  and  $C$ ).

c) How many poles does this transfer function have?

3. (22 pts) A generator produces 300-V, 60-Hz power. It is connected through an extension cord to a single load which consumes 1.2 kW with a 80% lagging power factor. The total resistance of the wires in the extension cord is  $R_{line}$ . The system efficiency is 96%.

Source end: 300-V      wires:  $R_{line}$       Efficiency:  $96\% = \frac{P_{out}}{P_{in}}$       Load end: 1.2 kW, 80% pf, lagging

a) Find the complex power ( $P$  and  $Q$ ) provided by the source.


b) Find the current flowing in each wire of the extension cord.

c) What is the value of the line resistance?  $R_{line} = ?$

d) What is the line voltage at the load? Just magnitude.

4. (12 pts) The transformer shown in the circuit below is ideal. It is rated at 220/55 V, 100 VA, 60 Hz. Find the following:

a)  $V_2 = ?$



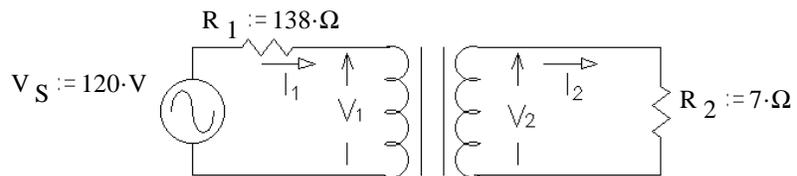


b) Is this transformer operating within its ratings? Show your evidence.

**ECE2210 Final given: Fall 12 p2**

5. (18 pts) The same input signal (at right) is connected to several op-amp circuits.

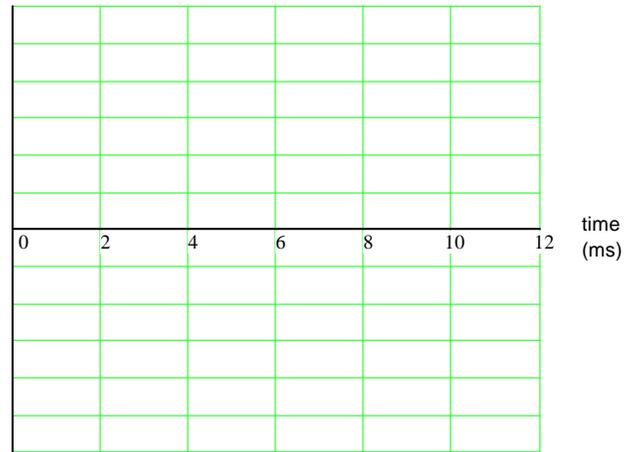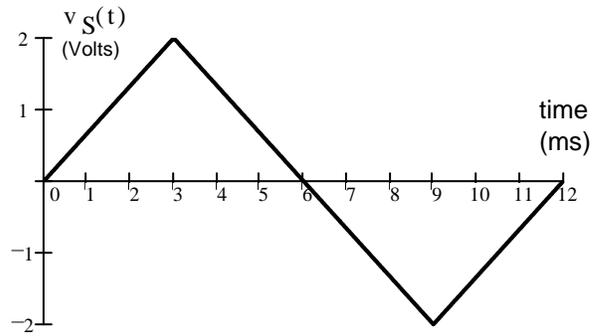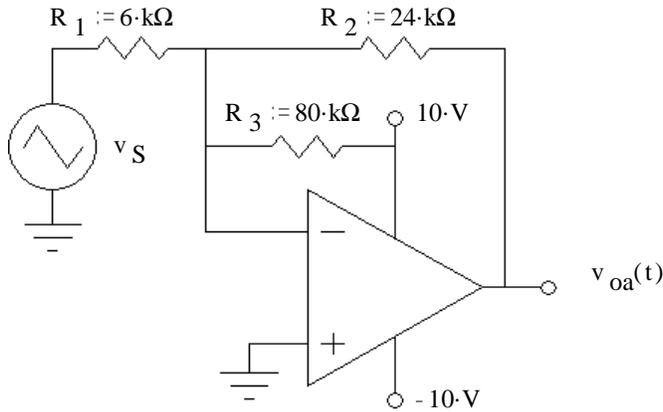a) Sketch the output waveform for this circuit. Clearly label important voltage levels on the output. If I can't easily make out what your peak values are, I'll assume you don't know. Don't forget to show inversions.





b) Devise an op-amp circuit which will output the waveform shown below given the input waveform shown at right. Choose the power supplies and use whatever passive parts you need.

You **may not** use any other batteries, input signals, or power supplies beyond the two that power the op amp.

output

$v_{ob}(t)$   
(Volts)

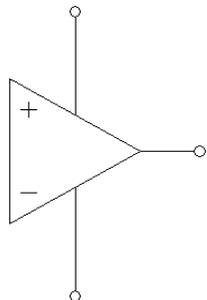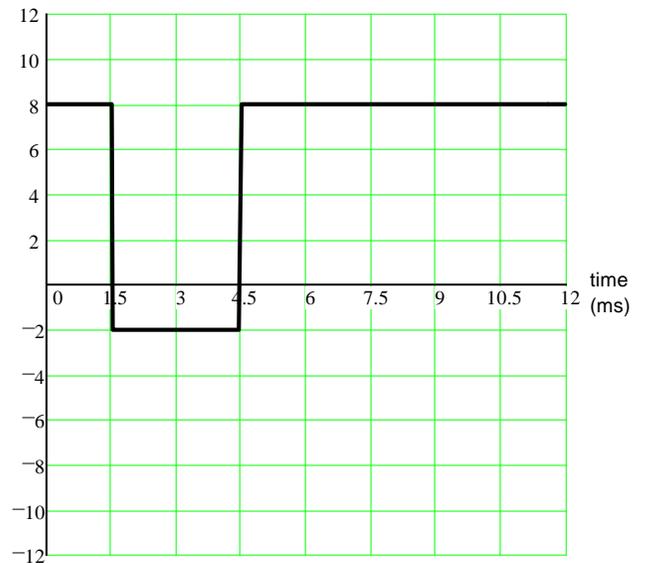

**ECE2210 Final given: Fall 12 p3**

6. (34 pts) A couple of transistors are used to control the current flow through an inductive load. The switch has been closed, as shown, for a long time.


a) You measure the voltage at each collector (referenced to ground) as shown on the drawing. Find the power dissipated by transistor  $Q_2$ .

b) Find the  $\beta$  of transistor  $Q_2$ .

c) Find the  $\beta$  of transistor  $Q_1$ .

d) Find the minimum  $\beta$  for transistor  $Q_1$  to be in saturation.

$\beta_{1min} = ?$

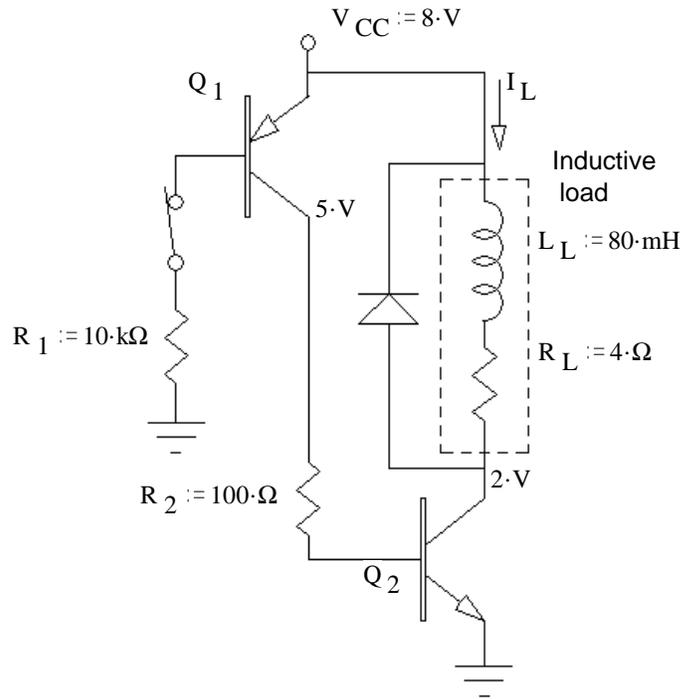

You replace  $Q_1$  with a different transistor so that now:  $\beta_1 := 200$  Use this from now on.

e) Find the new load current ( $I_L$ ) assuming transistor  $Q_2$  is in the active region.

f) Check the assumption that  $Q_2$  is in the active region and recalculate  $I_L$  if necessary.

g) The diode in this circuit conducts a significant current: (circle one)

- A) never.
- B) when the switch closes.
- C) whenever the switch is closed.
- D) always.
- E) when the switch opens.
- F) whenever the switch is open.

h) What is the maximum diode current you expect when the switch is cycled. (Answer 0 if it never conducts.)


7. (16 pts) Find the values below. Show your work.

Note: feel free to show work & answers right on the schematic

a)  $V_{I_S} = ?$

b)  $I_{V_2} = ?$

c)  $P_S = ?$


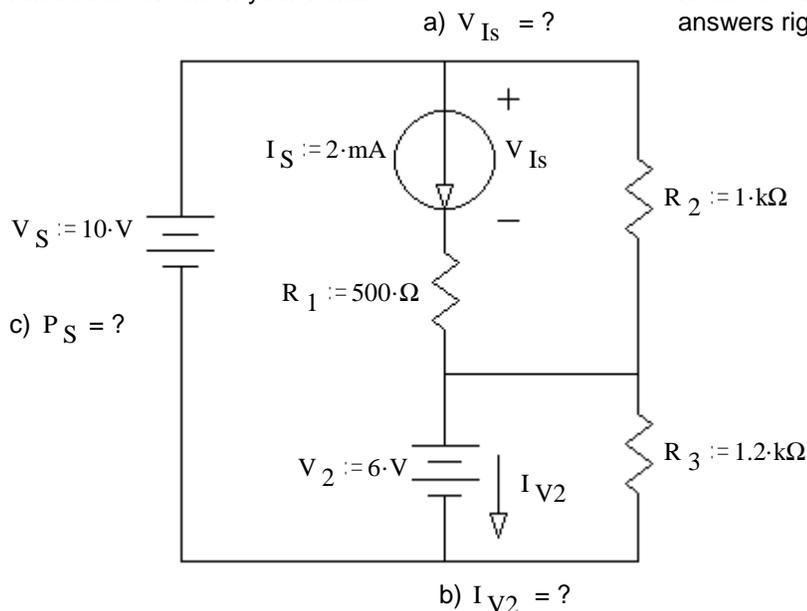


b)  $I_{V_2} = ?$

**ECE2210 Final given: Fall 12 p4**

Use constant-voltage-drop models for the diodes and LEDs on this exam.

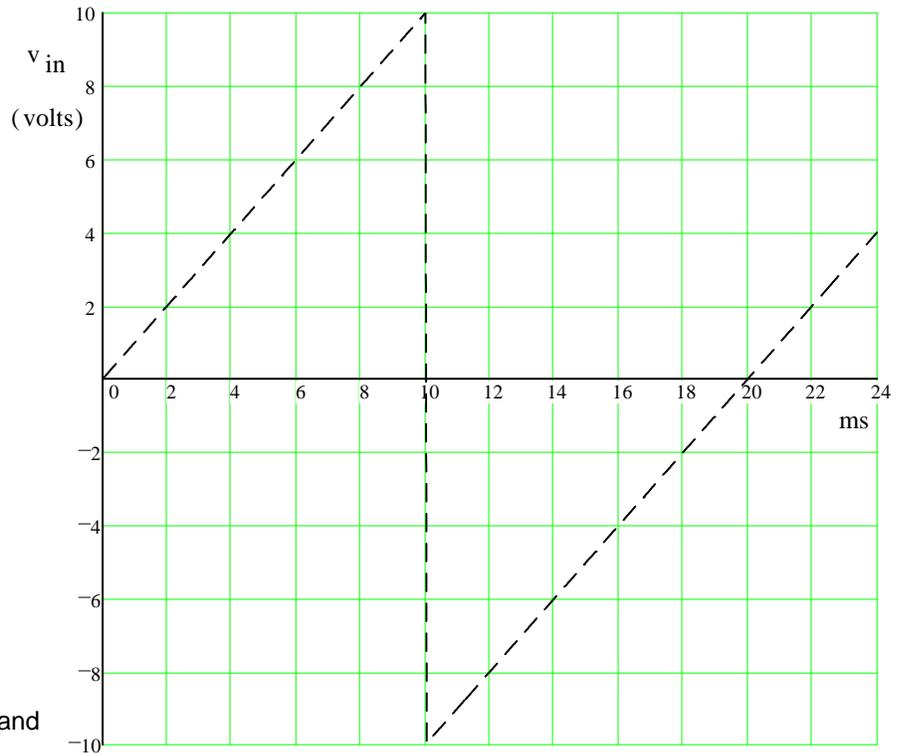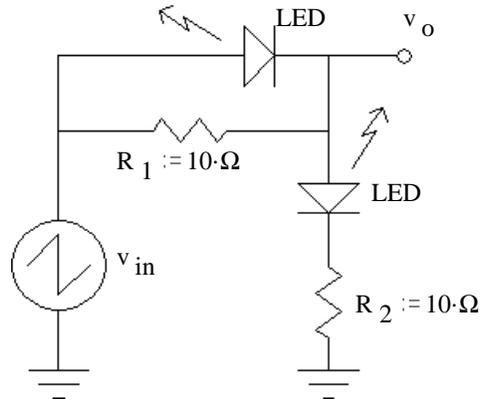8. (18 pts) A voltage waveform (dotted line) is applied to the circuit shown. Accurately draw the output waveform ( $v_o$ ) you expect to see. Label important times and voltage levels.




If you're not specific about your times and voltages, I'll assume you don't know !

9. (30 pts) Assume that diodes  $D_1$ ,  $D_3$  and  $D_4$  **DO** conduct.

Assume that diode  $D_2$  does **NOT** conduct.

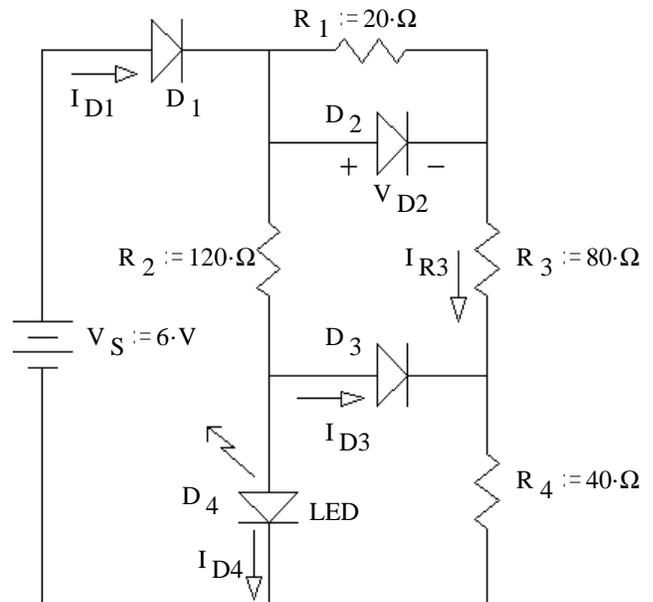- a) Stick with these assumptions even if your answers come out absurd. Find the following and anything else you need in order to check the assumptions:

- $I_{R3} =$  \_\_\_\_\_
- $I_{D3} =$  \_\_\_\_\_
- $V_{D2} =$  \_\_\_\_\_
- $I_{D4} =$  \_\_\_\_\_
- $I_{D1} =$  \_\_\_\_\_



**ECE2210 Final given: Fall 12 p5**

b) Based on the numbers above, was the assumption about  $D_1$  correct?    yes    no    (circle one)  
 How do you know? (Specifically show a value which is or is not within a correct range.)

c) Was the assumption about  $D_2$  correct?    yes    no  
 How do you know? (Show a value & range.)    (circle one)

d) Was the assumption about  $D_3$  correct?    yes    no  
 How do you know? (Show a value & range.)

e) Was the assumption about  $D_4$  correct?    yes    no  
 How do you know? (Show a value & range.)

f) Based on your answers to parts b), c), d) & e), Circle one:    (circle one)



Justify your answer.

- i) The **real**  $I_{D4} < I_{D4}$  calculated in part a.
- ii) The **real**  $I_{D4} = I_{D4}$  calculated in part a.
- iii) The **real**  $I_{D4} > I_{D4}$  calculated in part a.

10. Do you want your grade and scores posted on the Internet?    \_\_\_\_\_ otherwise, leave blank \_\_\_\_\_  
 If your answer is yes, then provide some sort of alias:

The grades will be posted on line in pdf form in alphabetical order under the alias that you provide here. I will not post grades under your real name. It will show the homework, lab, and exam scores of everyone who answers here.

**Answers**

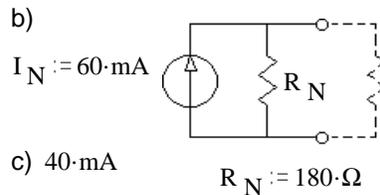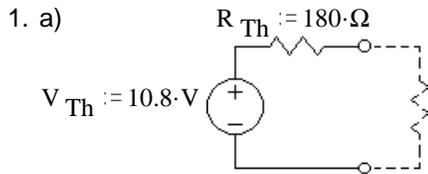



2. a) 
$$\frac{1}{L \cdot C} \cdot \frac{1}{s^2 + \left( \frac{1}{R_2 \cdot C} + \frac{R_3}{L} \right) \cdot s + \frac{1}{L \cdot C} \cdot \left( \frac{R_3}{R_2} + 1 \right)}$$

b) 0    c) 2


3. a)  $1.25 + 0.9 \cdot j$  kVA    b) 5.134 A

c)  $1.90 \cdot \Omega$     d) 292 V

4. a) 13.4 V    b) 1.92 A

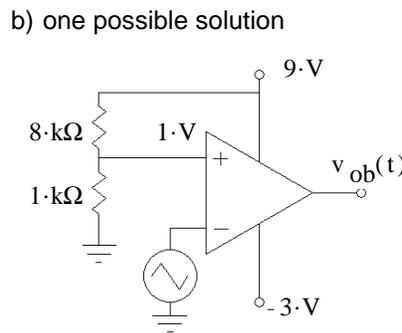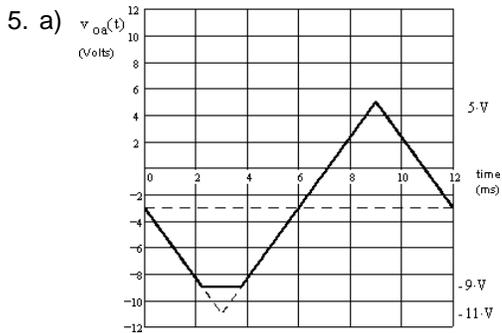

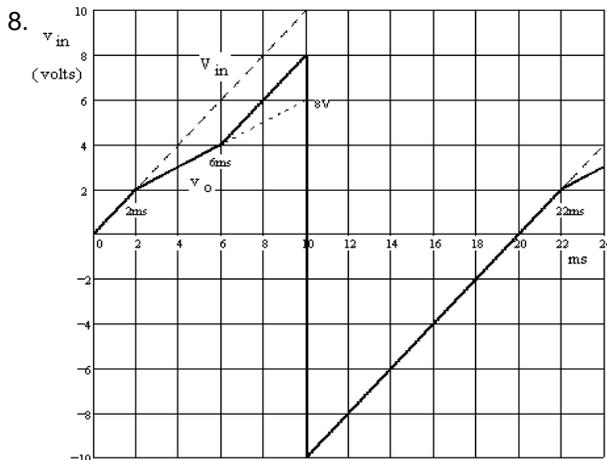6. a) 3 W    b) 34.9    c) 58.9  
 d) 97.3    e) 2.48 A    f) 1.95 A  
 g) E    h) 1.95 A
7. a) 3 V    b) 1 mA    c) 60 mW



9. a) 40 mA    -7.5 mA    0.8 V    35 mA    67.5 mA
- b) yes     $I_{D1} = 67.5 \text{ mA} > 0$
- c) no     $V_{D2} = 0.8 \text{ V} > 0.7 \text{ V}$
- d) no     $I_{D3} = -7.5 \text{ mA} < 0$
- e) yes     $I_{D4} = 35 \text{ mA} > 0$
- f) i) The additional current from  $D_3$  doesn't really flow.