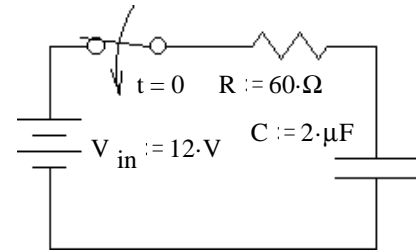


Name \_\_\_\_\_

1. A 10-microfarad capacitor has been charged to a potential of 150 volts. A resistor of  $25\ \Omega$  is then connected across the capacitor through a switch. When the switch has been closed for 10 time constants the total energy dissipated by the resistor is most nearly (An FE style problem)

- (A)  $1.0 \times 10^{-7}$  joules
- (B)  $1.1 \times 10^{-1}$  joules
- (C)  $9.0 \times 10^1$  joules
- (D)  $1.1 \times 10^3$  joules
- (E)  $9.0 \times 10^3$  joules


2. a) The switch is closed at time  $t = 0$  and  $v_C(0) = 0V$ , find  $v_C(t)$ .



- b) What is the value of the voltage across C at  $t = 40\ \mu s$

3. In the circuit shown, the switch has been in the upper position for a long time and is switched down at time  $t = 0$ .  
a) Find the initial and final capacitor voltages.

$$v_C(0) = ? \quad v_C(\infty) = ?$$

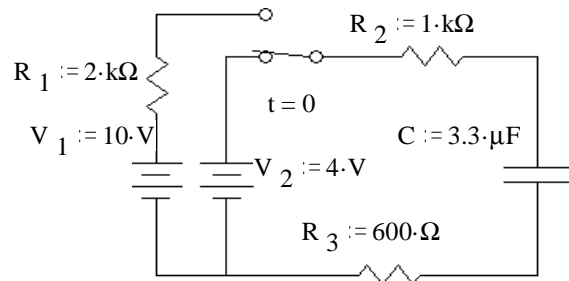


- b) Find the time constant.  
(after  $t = 0$ )

3. continued c) Find  $v_C(t)$ . (always after  $t = 0$ )

d) At what time is  $v_C = 5$  V?

4. a) What will be the final value of  $v_C$ ?  $v_C(\infty) = ?$

Hint: Use a Thevenin equivalent circuit.

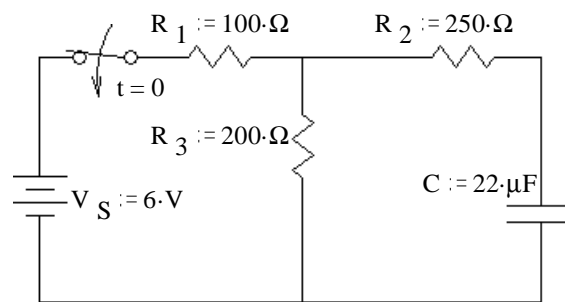

b) What is the time constant of this circuit?

c) Find  $v_C(t)$ . The switch had been open for a long time before  $t = 0$ .


**Answers**

1. B 2.a)  $12 \cdot V - 12 \cdot V \cdot e^{-\frac{t}{0.12 \cdot \text{ms}}}$  b) 3.4 V 3. a) 10 V 4 V b) 5.28 ms c)  $4 \cdot V + 6 \cdot V \cdot e^{-\frac{t}{5.28 \cdot \text{ms}}}$  d) 9.46 ms

4. a) 4 V b) 6.97 ms c)  $4 \cdot V - 4 \cdot V \cdot e^{-\frac{t}{6.97 \cdot \text{ms}}}$  5. a)  $36 \cdot V - 20 \cdot V \cdot e^{-\frac{t}{138 \cdot \mu\text{s}}}$  b) 27 V c)  $16 \cdot V + 11 \cdot V \cdot e^{-\frac{t}{78 \cdot \mu\text{s}}}$

6.a)  $\tau = R \cdot \frac{1}{\left(\frac{1}{C_1} + \frac{1}{C_2}\right)}$  b)  $i(t) = 45 \cdot \text{mA} \cdot e^{-\frac{t}{3.2 \cdot \text{ms}}}$  c)  $12 \cdot V - 12 \cdot V \cdot e^{-\frac{t}{3.2 \cdot \text{ms}}}$  d) 1.3 mJ dissipated in resistor **1stTr1 p2**

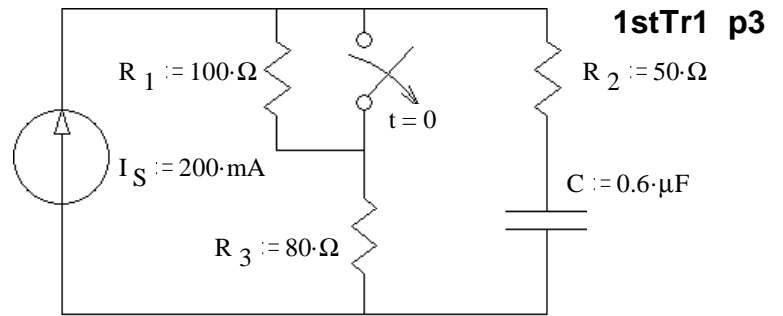5. The switch has been closed for a long time and is opened (as shown) at time  $t = 0$ .
- a) Find the initial and final conditions and write the full expression for  $v_C(t)$ , including all the constants that you find.



b) What is  $v_C$  when  $t = 0.8\tau$ ?  $v_C(0.8\tau) = ?$


c) At time  $t = 0.8\tau$  the switch is closed again. Find the complete expression for  $v_C(t')$ , where  $t'$  starts when the switch closes. Be sure to clearly show the time constant.

6. In a circuit with two capacitors, the left capacitor ( $C_1$ ) has an initial charge and the right capacitor ( $C_2$ ) does not. When the switch is closed at time  $t = 0$ , current  $i(t)$  flows, discharging  $C_1$  and charging  $C_2$ .

a) Derive the differential equation for  $i(t)$ . Hint: write an equation in terms of  $i$  and integrals of  $i$ , then differentiate the whole equation.

Write your DE in this form:  $\text{Constant} = x(t) + \tau \frac{d}{dt}x(t)$

What is the time constant ( $\tau$ )?

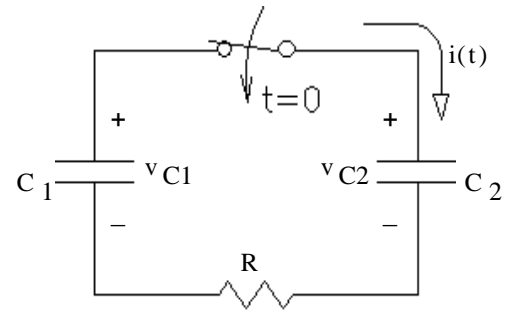

b) Find  $i(t)$  given  $C_1 := 24 \cdot \mu\text{F}$        $C_2 := 12 \cdot \mu\text{F}$        $R := 400 \cdot \Omega$        $v_{C1}(0) = 18 \cdot \text{V}$        $v_{C2}(0) = 0 \cdot \text{V}$

c) Find  $v_{C2}(t)$  for the same values. Hint: The trick here will be finding the final condition. Realize that charge will be conserved. If  $C_1$  discharges  $x$  coulombs, then  $C_2$  will charge  $x$  coulombs. Charges will stop flowing when  $v_{C1} = v_{C2}$ . It may help to think of two water tanks, one with half the cross-sectional area of the other.

$$v = \frac{Q}{C}$$

d) Find the initial and final stored energy of the system ( $W_{C1} + W_{C2}$ ) to find the total "loss".  
What happened to that energy?