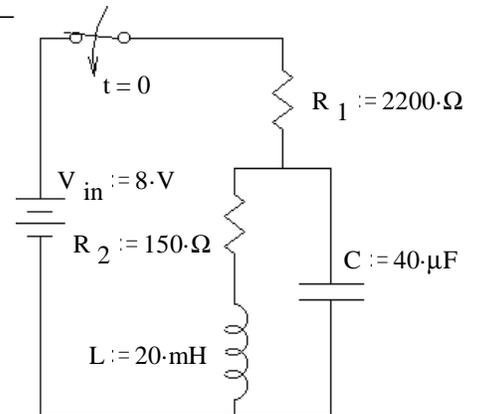


ECE 2210 Homework 2ndTr3

2nd - Order Transients Name _____

A.Stolp
d

1. a) Find the characteristic equation of the circuit at right.



b) Find the solutions to the characteristic equation.

c) Is this circuit over, under, or critically damped?

1. continued d) Find the final conditions:

e) The switch has been open for a long time and is switched down at time $t = 0$. Find the initial conditions:


f) Write the full expression for $v_C(t)$, including all the constants.

ECE 2210 homework 2ndTr3 p3

2. The transfer function of the circuit shown is:

$$\mathbf{H}(s) = \frac{\mathbf{I}_L(s)}{\mathbf{I}_{in}(s)} = \frac{\frac{R_2}{L} \cdot s}{s^2 + \frac{R_2}{L} \cdot s + \frac{1}{L \cdot C}}$$

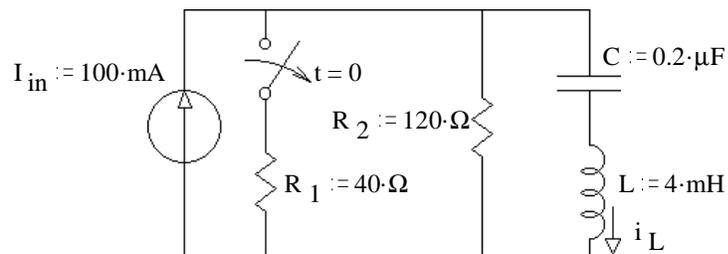a) Find the solutions to the characteristic equation.



b) Is this circuit over, under, or critically damped?

c) The switch is opened at time $t = 0$. Find the final and initial conditions of i_L .

d) Write the full expression for $i_L(t)$, including all the constants that you find.

Answers

1.a) $0 = s^2 + \left(\frac{R_2}{L} + \frac{1}{R_1 \cdot C}\right) \cdot s + \left(\frac{1}{L \cdot C} + \frac{R_2}{R_1 \cdot L \cdot C}\right)$ b) $s_1 := -182.2 \cdot \frac{1}{\text{sec}}$, $s_2 := -7329 \cdot \frac{1}{\text{sec}}$ c) overdamped

d) $0.511 \cdot V$ $3.404 \cdot \text{mA}$ e) $0 \cdot V$ $0 \cdot \text{mA}$ $90.91 \cdot \frac{V}{\text{sec}}$ $0 \cdot \frac{A}{\text{sec}}$

f) $v_C(t) = 0.511 \cdot V - 0.511 \cdot V \cdot e^{-182.2 \cdot t} + 0.000295 \cdot V \cdot e^{-7329 \cdot t}$

2. a) $-15000 \pm 32016j \text{ 1/sec}$ c) $12 \cdot V$ $0 \cdot \text{mA}$ $0 \cdot \text{mA}$ $2250 \cdot \frac{A}{\text{sec}}$ d) $i_L(t) := 0 \cdot \text{mA} + e^{\frac{-15000}{\text{sec}} \cdot t} \cdot \left(70.3 \cdot \sin\left(\frac{32016}{\text{sec}} \cdot t\right)\right) \cdot \text{mA}$
 b) underdamped

