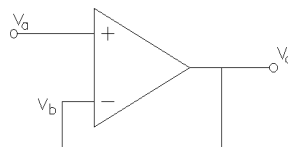



7. Design a differentiator using an op-amp, a resistor, and an inductor. You do not need to show parts values, but you need to show that the circuit will differentiate by showing a derivation similar to the ones in my handout.
8. Design a comparator whose output will be high (about 8 or 9 V) when the input is greater than 5 V and whose output will be low (about 1 V or so) when the input is less than 5 V.

Answers


- 1.) Draw a voltage follower.



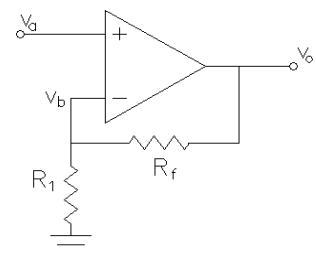
- 2.) Draw a noninverting amplifier. Choose an R_1 and an R_f which is 11 times bigger than R_1 . Say $R_1 = 10 \text{ k}\Omega$ and $R_f = 110 \text{ k}\Omega$.



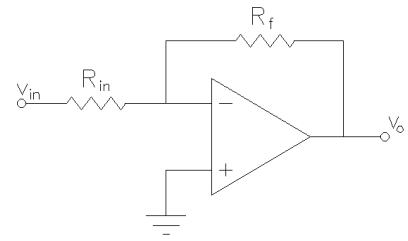
- 3.) Draw an inverting amplifier. $R_{in} = 10\text{ k}\Omega$, $R_f = 250\text{ k}\Omega$.



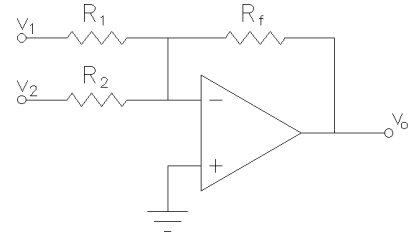
- 4.) Draw a two-input summer. Choose a value for R_f . Choose a value for R_1 which is $R_f/10$ and a value for R_2 which is $R_f/4$. Say $100\text{ k}\Omega$, $10\text{ k}\Omega$ and $25\text{ k}\Omega$.



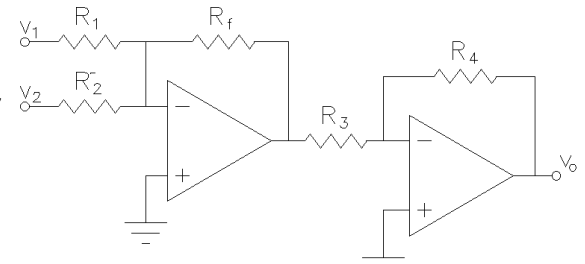- 5.) Redraw the same circuit as problem 4, only now follow it with an inverting amp with a gain of 1. Say $R_3 = R_4 = 10\text{ k}\Omega$ for the second op-amp.



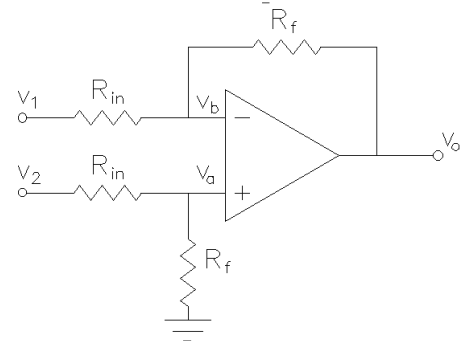
- 6.) Draw a differential amplifier. Choose an R_{in} value. Make R_f 12 times bigger than R_{in} . Say $R_{in} = 10\text{ k}\Omega$ and $R_f = 120\text{ k}\Omega$.



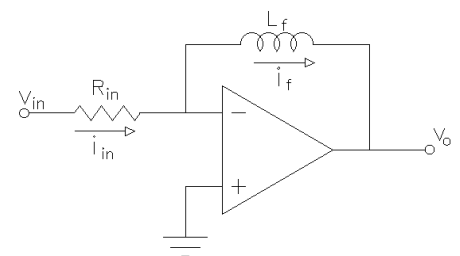- 7.) Design a differentiator using an op-amp, a resistor, and an inductor. You do not need to show parts values, but you need to show that the circuit will differentiate by showing a derivation similar to the ones in my handout.

$$i_{in} = \frac{v_{in}}{R_{in}} = i_L = -\frac{1}{L} \int v_o dt$$

$$v_o = -\frac{L}{R_{in}} \frac{dv_{in}}{dt}$$



- 8.) Just choose the two resistor values to be equal, so the voltage at the inverting input pin will be 5 V. Now, anytime the voltage on the noninverting pin is above 5 V the output will be high ($\sim 8\text{ V}$) and anytime the voltage on the noninverting pin is below 5 V the output will be low ($\sim 2\text{ V}$).

