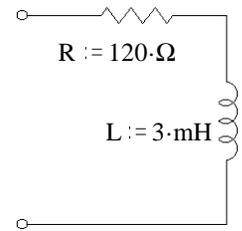


Name \_\_\_\_\_

**Warning: This homework is longer than normal -- DO NOT put it off until the last minute.**  
In the week of the exam, lab will be replaced by a video lecture


1. For the circuit shown, find the following:

a) At what frequency would the magnitude of the total impedance be  $240\Omega$ ?



b) At this frequency, what is the phase angle of the impedance?

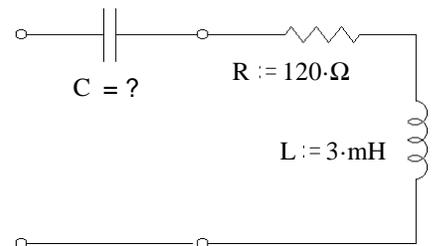
c) At this frequency, you want to add a capacitor in series to make the circuit appear purely resistive (the impedance has no imaginary component). Find the value of the capacitor.



2. You need to design a circuit in which the current  $i(t)$  leads the voltage  $v_S(t)$  by  $36^\circ$  of phase.



a) What should go in the box: R, L, C?

b) Find its value.

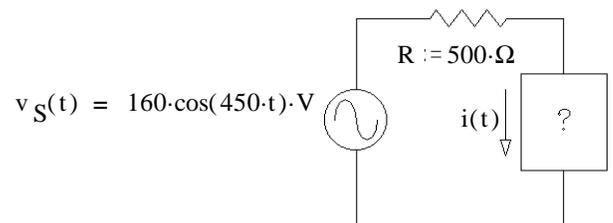



### ECE 2210 homework Ph3 p2

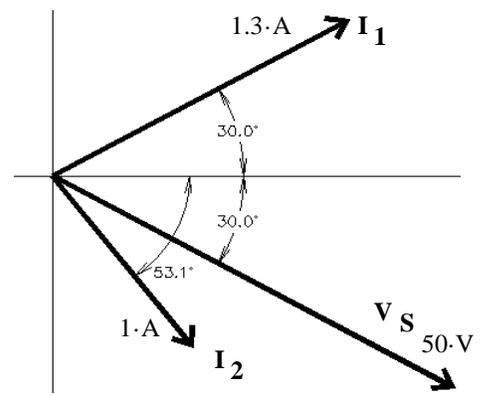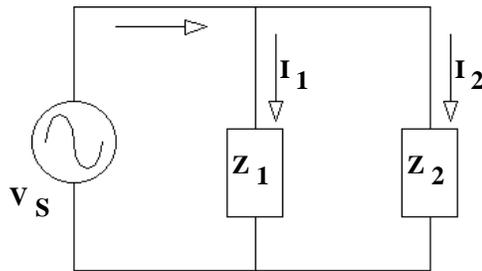3. The phasor diagram at right shows the source voltage and two branch currents of a parallel circuit. Find the impedance of each of the two branches.



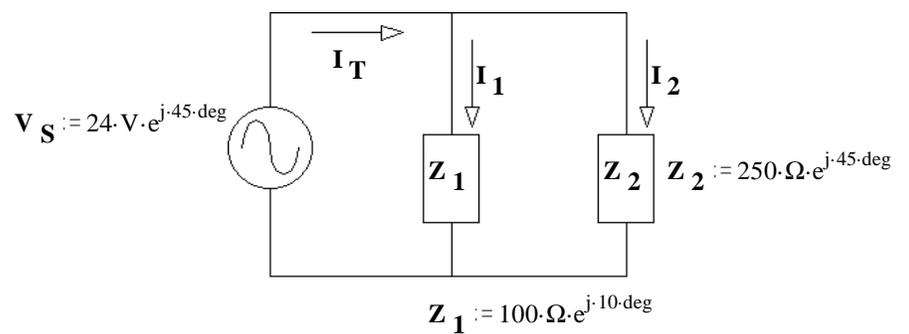
4. a) Find all the currents,  $I_1$ ,  $I_2$ , and  $I_T$ .



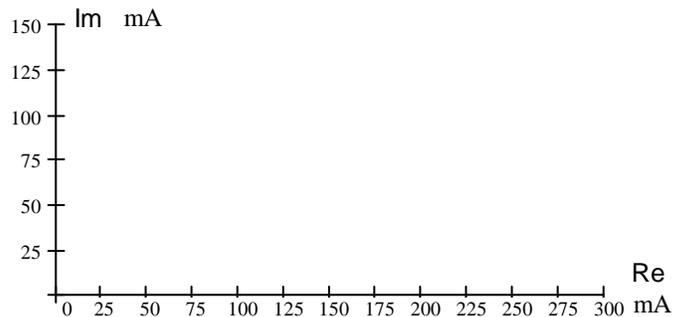

b) Draw a phasor diagram showing  $I_1$ ,  $I_2$ , and  $I_T$  to scale so that you can show that they obey KCL.

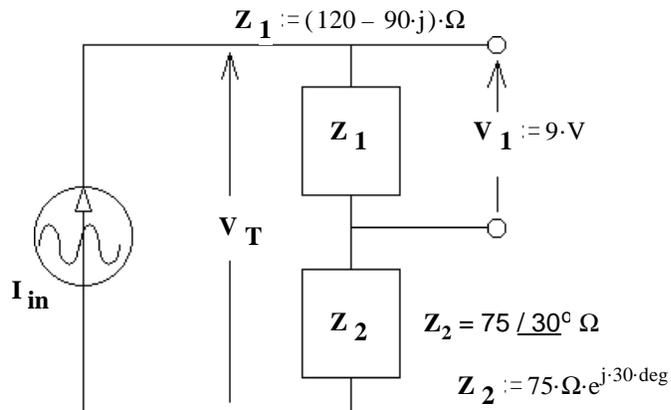5. a) Find the AC current source,  $I_{in}$  in polar form.




b) Find  $V_T$ .

- c) Choose one: i) The source current leads the source voltage.  
 ii) The source current lags the source voltage.

ECE 2210 homework Ph3 p4

6. a) Find  $Z_1$ .

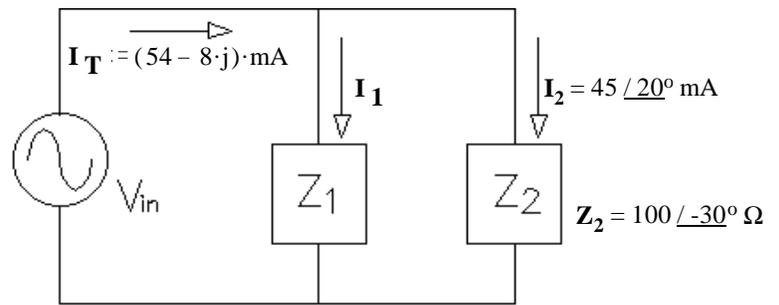

b) To make  $Z_1$  in the simplest way, what part(s) would you need? Just determine the needed part(s) from the list below and state why you made that choice, don't find the values.


- |                   |                   |           |              |                |
|-------------------|-------------------|-----------|--------------|----------------|
| resistor          | capacitor         | inductor  | power supply | current source |
| Thevenin resistor | Ideal transformer | voltmeter | ammeter      | scope          |

c) Choose one: i)  $I_2$  leads the source voltage ( $V_{in}$ )      ii)  $I_2$  lags the source voltage ( $V_{in}$ )

d) Choose one: i)  $I_1$  leads  $I_2$       ii)  $I_1$  lags  $I_2$


ECE 2210 homework Ph3 p5

7. Find Z.

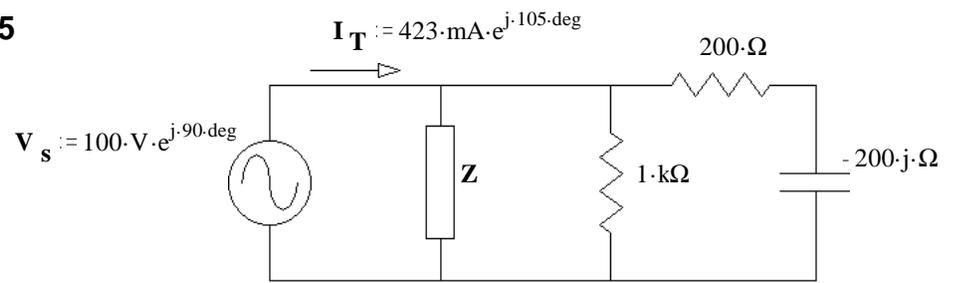

ECE 2210 homework Ph3 p6

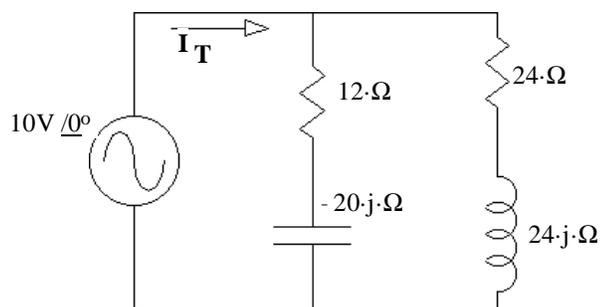8. a) Find the total impedance of the circuit.




b) Find  $I_T$ .

## ECE 2210 homework Ph3 p7

9. Find  $Z_{eq}$  in simple polar form.

$$f := 8000 \cdot \text{Hz}$$

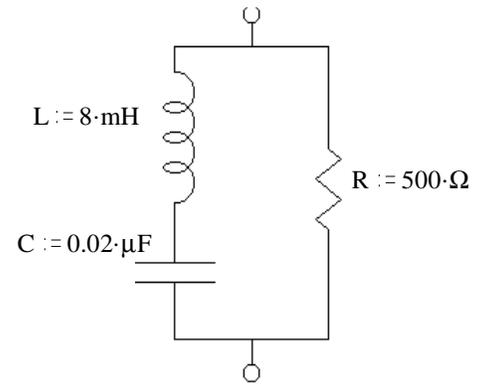

### Answers

1. a) 11·kHz      b)  $60^\circ$       c)  $0.0694 \cdot \mu\text{F}$
2. a) C      b)  $6.12 \cdot \mu\text{F}$
3.  $Z_1 = (19.2 - 33.3j) \cdot \Omega$        $Z_2 = (46.0 + 19.6j) \cdot \Omega$
4. a)  $(0.197 + 0.138j) \cdot \text{A} + 0.096 \cdot \text{A} = 0.293 + 0.138j \cdot \text{A}$
5. a)  $60 / \underline{36.87^\circ} \text{ mA}$       b)  $11.54 / \underline{21^\circ} \text{ V}$       c) i)
6. a)  $172 / \underline{53.4^\circ} \Omega$       b) phase angle  $> 0$ , resistor and inductor  
c) i)      d) ii)
7.  $657 \Omega / \underline{67.4^\circ}$       8. a)  $21.86 \Omega / \underline{-20.38^\circ}$       b)  $0.457 \text{ A} / \underline{20.38^\circ}$
9.  $382 \Omega / \underline{-40.2^\circ}$

