

Ohm's law (resistors)


$$V = I \cdot R$$



$$I = \frac{V}{R}$$

$$R = \frac{V}{I}$$

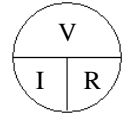definition of resistance and the unit " Ω "




Power


flow $\frac{m^3}{sec}$ pressure $\frac{N}{m^3}$ flow x pressure: $\frac{m^3}{sec} \cdot \frac{N}{m^3} = \frac{m \cdot N}{sec \cdot 1} = \frac{N \cdot m}{sec} = \frac{Joule}{sec} = W = power$

same for electricity power $P = I \cdot V$

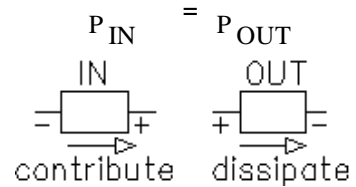
Power dissipated by resistors: $P = V \cdot I = \frac{V^2}{R} = I^2 \cdot R$



Series Resistors

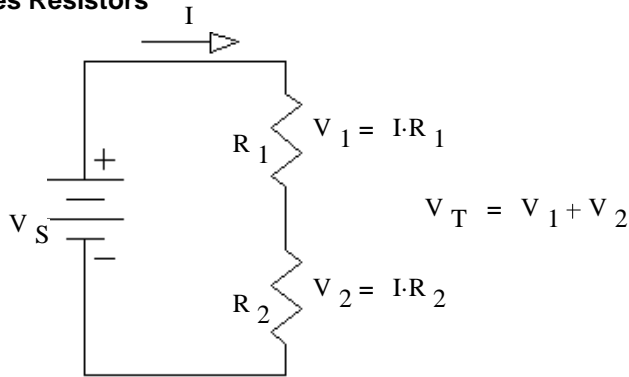

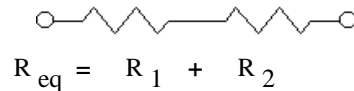
$$R_{eq} = \frac{V_T}{I} = \frac{V_1 + V_2}{I} = \frac{V_1}{I} + \frac{V_2}{I} = R_1 + R_2$$




Resistors are in series if and only if exactly the **same current** flows through each resistor.

Parallel Resistors

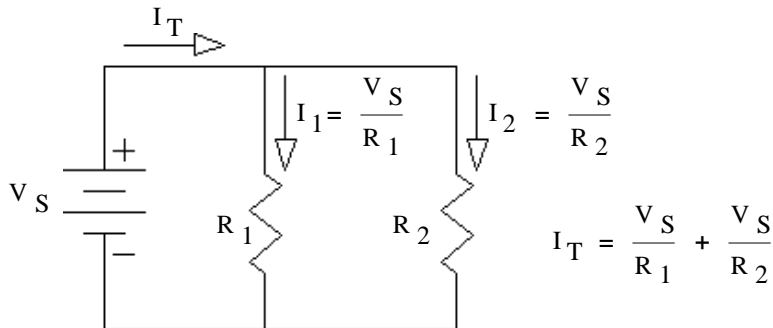

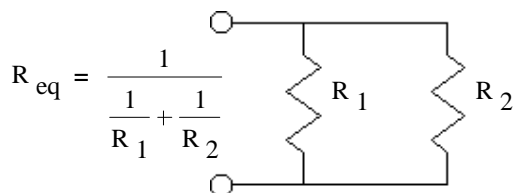
$$R_{eq} = \frac{V_S}{I_T} = \frac{V_S}{\frac{V_S}{R_1} + \frac{V_S}{R_2}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$



Resistors are in parallel if and only if the **same voltage** is across each resistor.

Series and Parallel

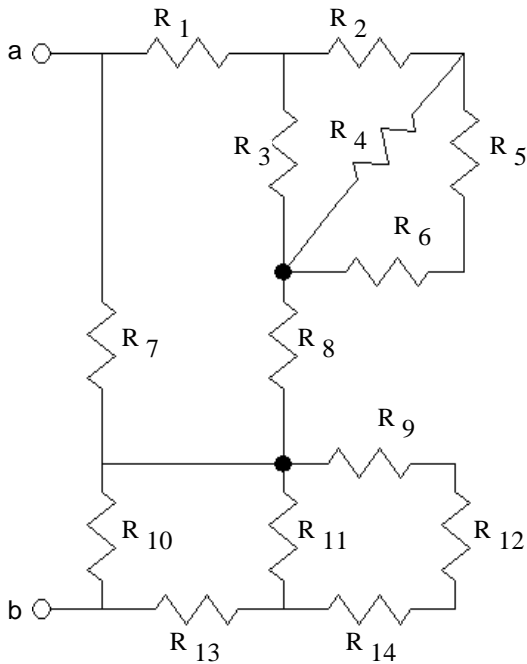

All resistor-only networks can be reduced to a single equivalent, but not always by means of series and parallel concepts.

Voltage Divider

series: $R_{eq} = R_1 + R_2 + R_3 + \dots$

Exactly the **same current** through each resistor

Voltage divider:

$$V_{Rn} = V_{total} \cdot \frac{R_n}{R_1 + R_2 + R_3 + \dots}$$

Current Divider


parallel: $R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots}$

Exactly the **same voltage** across each resistor

current divider:

$$I_{Rn} = I_{total} \cdot \frac{\frac{1}{R_n}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots}$$

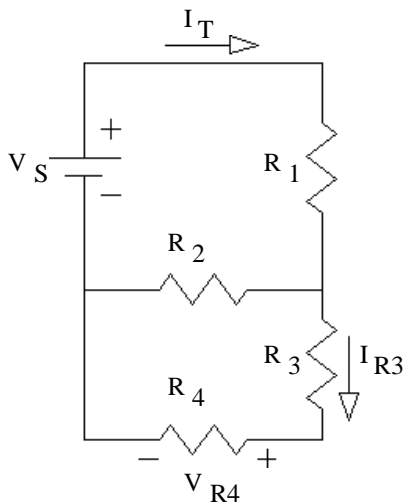May have to combine some resistors first to get series and parallel resistors to use with divider expressions.





$V_{R4} =$

$I_T =$



$I_{R3} =$

Resistors


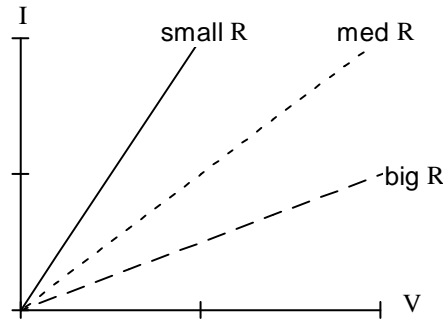
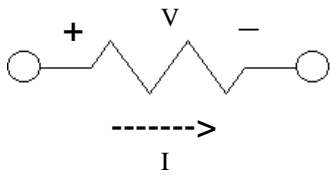


$$R = \frac{1}{\text{slope}} = \frac{\Delta V}{\Delta I}$$


Sources

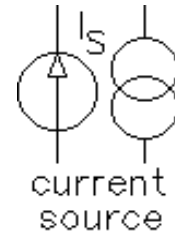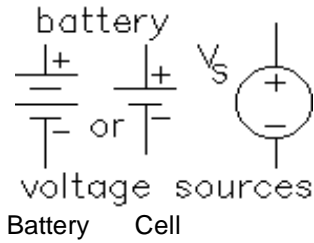

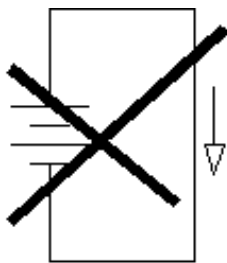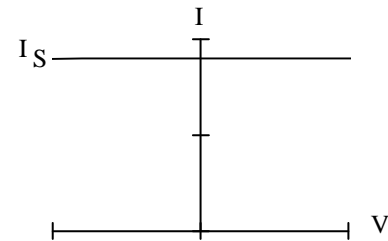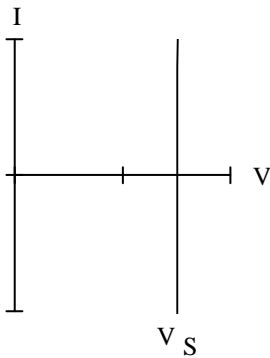
Less intuitive, less like sources we are used to seeing.



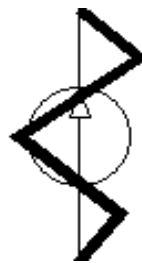Doesn't make sense with for ideal voltage sources and ideal wires




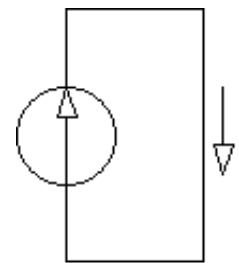Doesn't make sense for ideal current sources




Must have a path for the current to flow

Ground

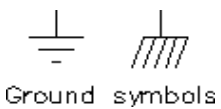


Ground symbols

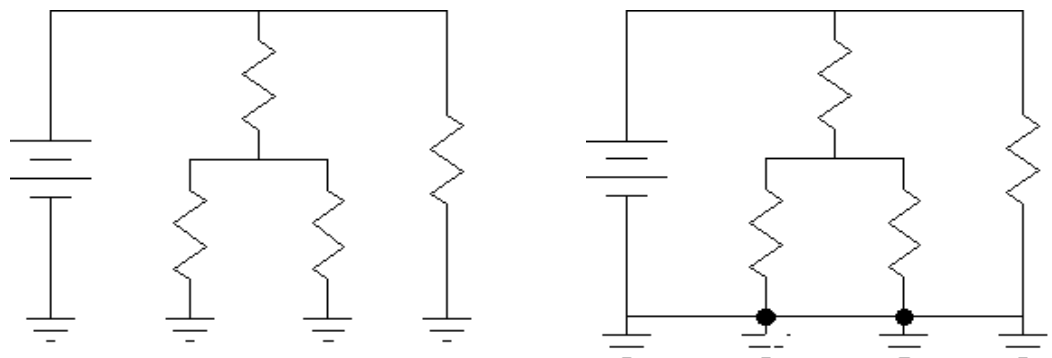


Ground is considered zero volts and is a reference for other voltages.

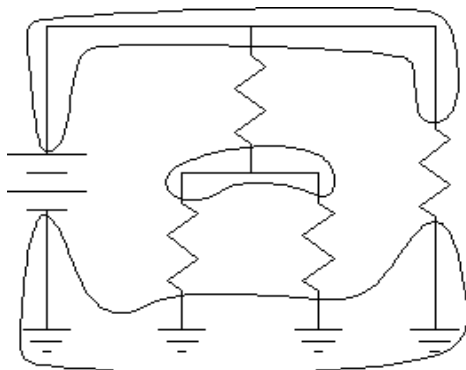Node = all points connected by wire, all at same voltage (potential)





ground is a node





Branch = all parts with the same current

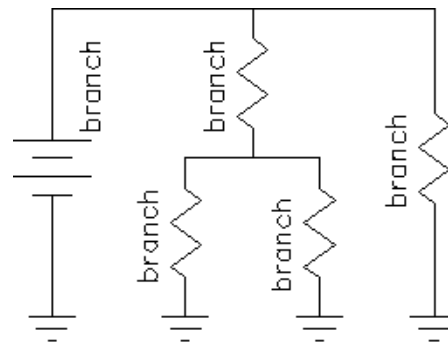

Meters

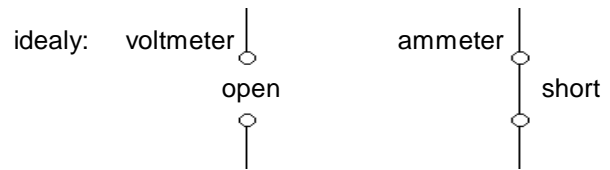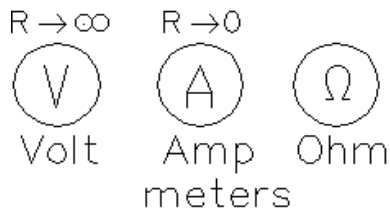

Analog meters

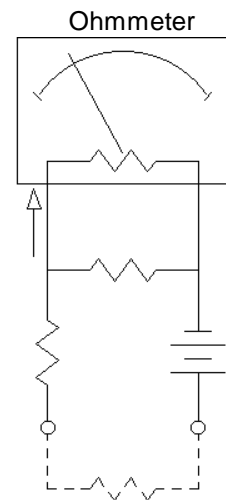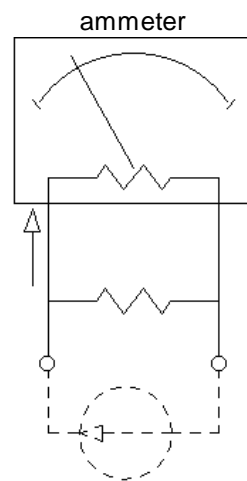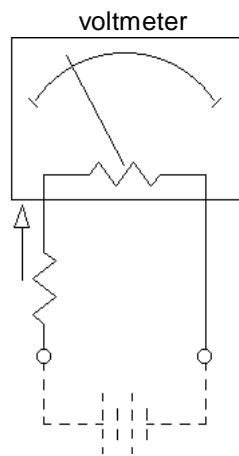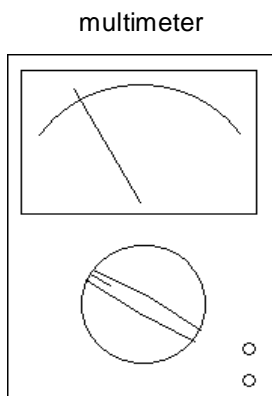

Digital meter

