

General Network Analysis

In many cases you have multiple unknowns in a circuit, say the voltages across multiple resistors. Network analysis is a systematic way to generate multiple equations which can be solved to find the multiple unknowns. These equations are based on basic Kirchoff's and Ohm's laws.

Loop or Mesh Analysis You may have used these methods in previous classes, particularly in Physics. The best thing to do now is to forget all that. Loop analysis is rarely the easiest way to analyze a circuit and is inherently confusing. Hopefully I've brought you to a stage where you have some intuitive feeling for how currents flow in circuits. I don't want to ruin that now by screwing around with loop currents that don't really exist.

Nodal analysis This is a much better method. It's just as powerful, usually easier, and helps you develop your intuitive feeling for how circuits work.

Nodal Analysis

Node = all points connected by wire, all at same voltage (potential)

Ground: One node in the circuit which will be our reference node. Ground, by definition, will be the zero voltage node. All other node voltages will be referenced to ground and may be positive or negative. Think of gage pressure in a fluid system. In that case atmospheric pressure is considered zero. If there is no ground in the circuit, define one for yourself. Try to choose a node which is hooked to one side of a voltage source.

Nodal Voltage: The voltage of a node referenced to ground. The objective of nodal analysis is to find all the nodal voltages. If you know the voltage at a node then it's a "known" node. Ground is a known node (duh, it's zero). If one end of a known voltage source hooked to ground, then the node on the other end is also known (another duh).


Method: Label all the unknown nodes as; "a", "b", "c", etc. Then the unknown nodal voltages become; V_a , V_b , V_c , etc. Write a KCL equation for each unknown node, defining currents as necessary. Replace each unknown current with an Ohm's law relationship using the nodal voltages. Now you have just as many equations as unknowns. Solve.

Nodal Analysis Steps

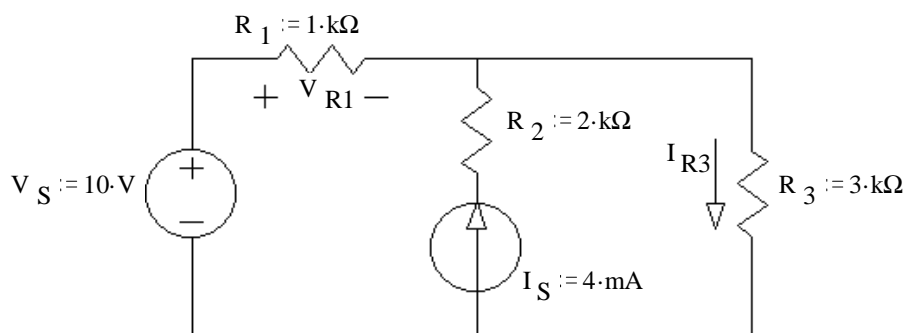- 1) If the circuit doesn't already have a ground, label one node as ground (zero voltage).
If the ground can be defined as one side of a voltage source, that will make the following steps easier.
Label the remaining node, either with known voltages or with letters, a, b,
- 2) Label unknown node voltages as V_a , V_b , ... and label the current in each resistor as I_1 , I_2 ,
- 3) Write Kirchoff's current equations for each unknown node.
- 4) Replace the currents in your **KCL** equations with expressions like this. $\frac{V_a - V_b}{R_1}$ Ohm's law relationship using the nodal voltages.
- 5) Solve the multiple equations for the multiple unknown voltages.

Nodal Analysis Examples

Ex 1 Use nodal analysis to find the voltage across R_1 (V_{R1}).



- 1) See next page
Label one node as ground (zero voltage). By choosing the negative side of a voltage source as ground, the upper-left node is known (10V). Label the remaining nodes, either with known voltages or with letters, a, b,

2) Label unknown node voltages as V_a, V_b, \dots
and label the current in each resistor as I_1, I_2, \dots

3) Write Kirchoff's current equations for node a.

$$I_1 + I_S = I_{R3}$$

4) Replace the currents in the **KCL** equations with Ohm's law relationships.

$$\frac{V_S - V_a}{R_1} + I_S = \frac{V_a - 0}{R_3}$$


$$\frac{V_S}{R_1} - \frac{V_a}{R_1} + I_S = \frac{V_a}{R_3}$$

5) Solve:

$$\frac{V_S}{R_1} + I_S = \frac{V_a}{R_3} + \frac{V_a}{R_1}$$

$$\frac{V_S}{R_1} + I_S = V_a \cdot \left(\frac{1}{R_1} + \frac{1}{R_3} \right)$$
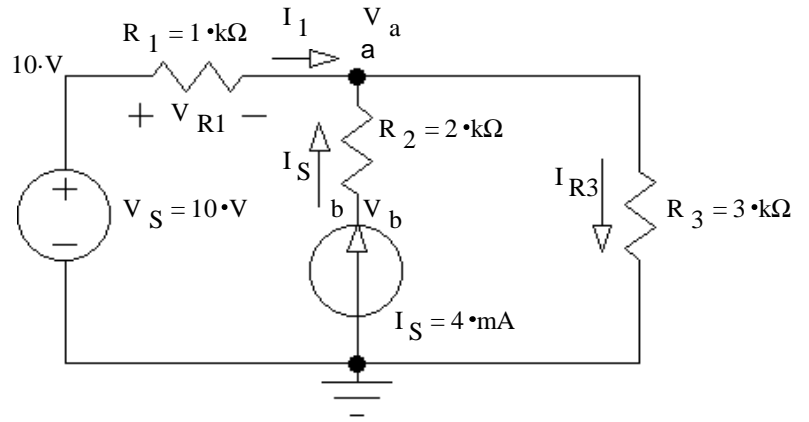
$$V_a := \frac{\frac{V_S}{R_1} + I_S}{\left(\frac{1}{R_1} + \frac{1}{R_3} \right)} \quad V_a = 10.5 \cdot V$$



Usually it's easier to put in the numbers at this point

$$\frac{10 \cdot V}{1 \cdot k\Omega} + 4 \cdot mA = \frac{V_a}{3 \cdot k\Omega} + \frac{V_a}{1 \cdot k\Omega}$$

Multiply both sides by a value that will clear the denominators.

$$3 \cdot k\Omega \cdot \left(\frac{10 \cdot V}{1 \cdot k\Omega} + 4 \cdot mA \right) = \left(\frac{V_a}{3 \cdot k\Omega} + \frac{V_a}{1 \cdot k\Omega} \right) \cdot 3 \cdot k\Omega$$

$$30 \cdot V + 3 \cdot k\Omega \cdot 4 \cdot mA = V_a + 3 \cdot V_a$$

$$30 \cdot V + 12 \cdot V = 4 \cdot V_a$$

$$V_a = \frac{42 \cdot V}{4} = 10.5 \cdot V$$

Either way, you still have to find V_{R1} from V_a .


$$V_{R1} := V_S - V_a$$

$$V_{R1} = -0.5 \cdot V$$


V_b doesn't matter in this case

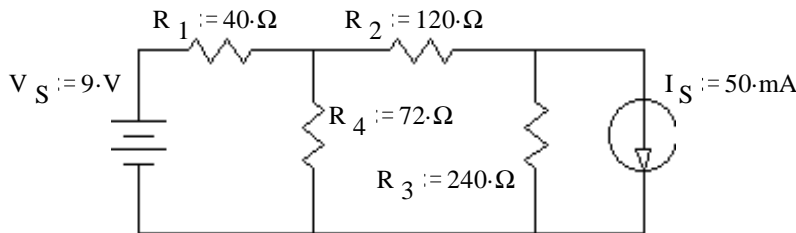b) Find the current through R_3 (I_{R3}). $I_{R3} = \frac{V_a}{R_3} = 3.5 \cdot mA$

Ex 2 Same circuit used in Thévenin example, where R_4 was R_L .




1) Define ground and nodes:

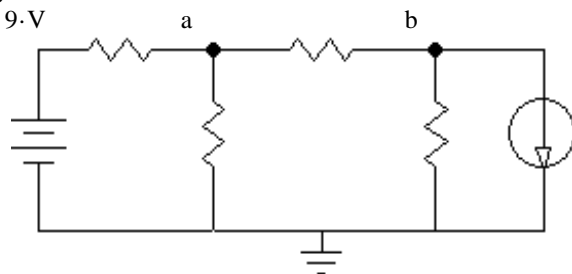

2 unknown nodes ---> will need 2 equations

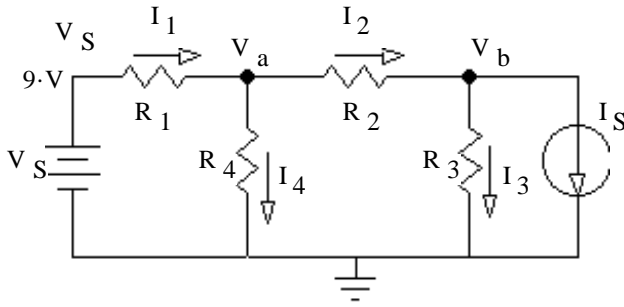2) Label unknown node voltages as V_a, V_b, \dots and label the current in each resistor as I_1, I_2, \dots

It doesn't matter if these currents are in the correct directions.



3) Write Kirchoff's current equations for each unknown node.

$$\text{node a} \quad I_1 = I_2 + I_4$$

$$\text{node b} \quad I_2 = I_3 + I_S$$

4) Replace the currents in your **KCL** equations with expressions like this. $\frac{V_a - V_b}{R_1}$

$$\text{node a} \quad I_1 = I_2 + I_4$$

$$\frac{V_S - V_a}{R_1} = \frac{V_a - V_b}{R_2} + \frac{V_a - 0 \cdot V}{R_4}$$

$$\text{node b} \quad I_2 = I_3 + I_S$$

$$\frac{V_a - V_b}{R_2} = \frac{V_b - 0 \cdot V}{R_3} + I_S$$

Now you have just as many equations as unknowns.

5) Solve the multiple equations for the multiple unknown voltages. Solve by any method you like:

$$\frac{V_S}{R_1} - \frac{V_a}{R_1} = \frac{V_a}{R_2} - \frac{V_b}{R_2} + \frac{V_a}{R_4}$$

$$\frac{V_a}{R_2} - \frac{V_b}{R_2} = \frac{V_b}{R_3} + I_S$$

$$V_b = \frac{\frac{V_a}{R_2} - I_S}{\frac{1}{R_2} + \frac{1}{R_3}}$$

$$\frac{V_S}{R_1} - \frac{V_a}{R_1} = \frac{V_a}{R_2} - \frac{\frac{V_a}{R_2} - I_S}{R_2 \cdot \left(\frac{1}{R_2} + \frac{1}{R_3}\right)} + \frac{V_a}{R_4}$$

$$V_a = \frac{\left[\frac{V_S}{R_1} - \frac{1}{R_2 \cdot \left(\frac{1}{R_2} + \frac{1}{R_3}\right)} \cdot I_S \right]}{\left[\frac{1}{R_1} + \frac{1}{R_2} - \frac{1}{R_2^2 \cdot \left(\frac{1}{R_2} + \frac{1}{R_3}\right)} + \frac{1}{R_4} \right]}$$

$$V_a = 4.6 \cdot V$$

$$V_b = \frac{\frac{V_a}{R_2} - I_S}{\frac{1}{R_2} + \frac{1}{R_3}}$$

$$V_b = -0.933 \cdot V$$

Or, with numbers

$$\text{node a} \quad 360 \cdot \Omega \cdot \left(\frac{9 \cdot V - V_a}{40 \cdot \Omega} \right) = \left(\frac{V_a - V_b}{120 \cdot \Omega} + \frac{V_a}{72 \cdot \Omega} \right) \cdot 360 \cdot \Omega$$

$$\text{node b} \quad 240 \cdot \Omega \cdot \frac{V_a - V_b}{120 \cdot \Omega} = \left(\frac{V_b - 0 \cdot V}{240 \cdot \Omega} + 50 \cdot \text{mA} \right) \cdot 240 \cdot \Omega$$

$$81 \cdot V - 9 \cdot V_a = 3 \cdot V_a - 3 \cdot V_b + 5 \cdot V_a$$

$$2 \cdot V_a - 2 \cdot V_b = V_b + 48 \cdot \text{mA} \cdot 240 \cdot \Omega$$

$$81 \cdot V - 9 \cdot (1.5 \cdot V_b + 6 \cdot V) = 3 \cdot (1.5 \cdot V_b + 6 \cdot V) - 3 \cdot V_b + 5 \cdot (1.5 \cdot V_b + 6 \cdot V)$$

$$V_a = \frac{2 \cdot V_b + V_b + 12 \cdot V}{2} = 1.5 \cdot V_b + 6 \cdot V$$

<-- substitute for V_a

$$81 \cdot V - 13.5 \cdot V_b - 54 \cdot V = 4.5 \cdot V_b + 18 \cdot V - 3 \cdot V_b + 7.5 \cdot V_b + 30 \cdot V$$

$$81 \cdot V - 54 \cdot V - 18 \cdot V - 30 \cdot V = -21 \cdot V = 4.5 \cdot V_b - 3 \cdot V_b + 7.5 \cdot V_b + 13.5 \cdot V_b = 22.5 \cdot V_b$$

$$V_b = \frac{-21 \cdot V}{22.5} = -0.933 \cdot V$$

$$V_a = 1.5 \cdot V_b + 6 \cdot V = 4.6 \cdot V$$



ECE 2210 Lecture 7 notes p4

Ex 3 Like Superposition Ex.2

a) Use nodal analysis to find the voltage across R_2 (V_{R2}).

You **MUST** show all the steps of nodal analysis work to get credit, including drawing appropriate symbols and labels on the circuit shown.

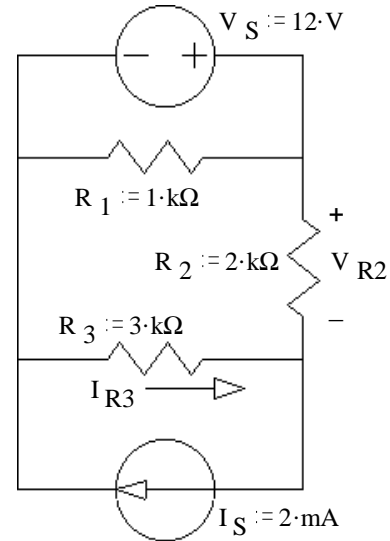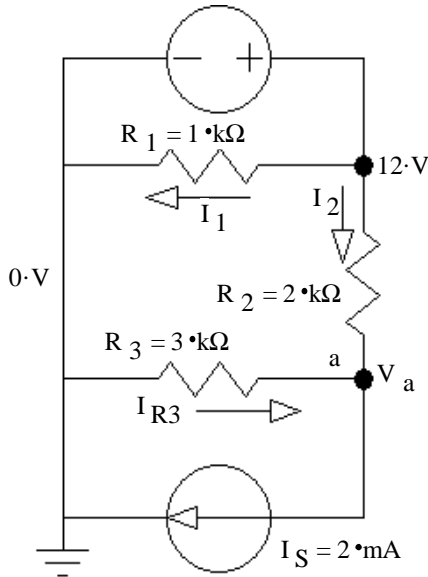- 1) Define ground and nodes:
- 2) Label unknown node voltages as V_a, V_b, \dots and label the current in each resistor as I_1, I_2, \dots



3) Write Kirchoff's current equations for each unknown node.

$$\text{node a: } I_2 + I_{R3} = I_S$$

4) Replace the currents in the **KCL** equations with Ohm's law relationships.

$$\frac{V_S - V_a}{R_2} + \frac{0 - V_a}{R_3} = I_S$$

5) Solve the equation for the unknown voltage.

$$\frac{V_S}{R_2} - \frac{V_a}{R_2} - \frac{V_a}{R_3} = I_S$$

$$\frac{V_S}{R_2} = \frac{V_a}{R_2} + \frac{V_a}{R_3} + I_S$$

$$\frac{V_S}{R_2} - I_S = V_a \cdot \left(\frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$V_a := \frac{\frac{V_S}{R_2} - I_S}{\left(\frac{1}{R_2} + \frac{1}{R_3} \right)} \quad V_a = 4.8 \text{ V}$$

Usually it's easier to put in the numbers at this point

$$\frac{12 \text{ V} - V_a}{2 \text{ k}\Omega} + \frac{0 - V_a}{3 \text{ k}\Omega} = 2 \text{ mA}$$

Multiply both sides by a value that will clear the denominators.

$$6 \text{ k}\Omega \cdot \left(\frac{12 \text{ V} - V_a}{2 \text{ k}\Omega} + \frac{0 - V_a}{3 \text{ k}\Omega} \right) = 2 \text{ mA} \cdot 6 \text{ k}\Omega$$

$$36 \text{ V} - 3 \cdot V_a - 2 \cdot V_a = 12 \text{ V}$$

$$-5 \cdot V_a = -24 \text{ V}$$

$$V_a = \frac{-24 \text{ V}}{-5} = 4.8 \text{ V}$$

Remember, we needed to find the voltage across R_2 (V_{R2}).

$$V_{R2} = V_S - V_a = 7.2 \text{ V}$$



b) Find the current through R_3 (I_{R3}).

$$I_{R3} = \frac{0 - V_a}{R_3} = -1.6 \text{ mA} \quad \text{actually flows the other way}$$

ECE 2210 Lecture 7 notes p5

Ex 4 Use nodal analysis to find the voltage across R_5 (V_{R5}) and the current through R_1 (I_{R1}). From exam 1, F09

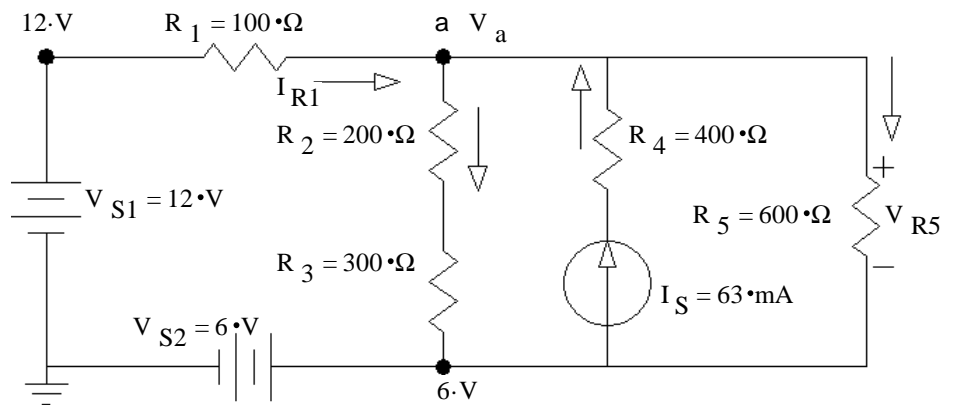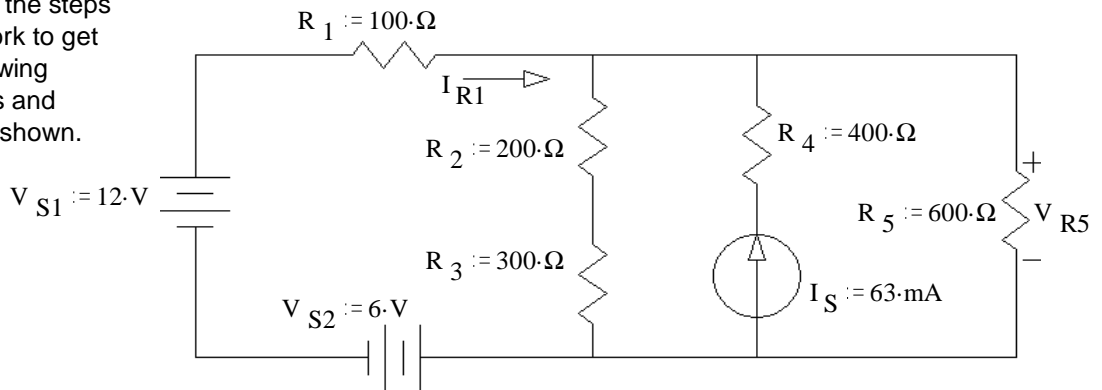You **MUST** show all the steps of nodal analysis work to get credit, including drawing appropriate symbols and labels on the circuit shown.



node a:

$$\begin{aligned}
 I_{R1} + I_S &= I_R + I_5 \\
 R_3 = 300 \cdot \Omega \cdot \frac{V_{S1} - V_a}{R_1} + I_S &= \frac{V_a - V_{S2}}{R_2 + R_3} + \frac{V_a - V_{S2}}{R_5} \\
 \frac{12 \cdot V}{100 \cdot \Omega} - \frac{V_a}{100 \cdot \Omega} + 63 \cdot \text{mA} &= \frac{V_a}{500 \cdot \Omega} - \frac{6 \cdot V}{500} + \frac{V_a}{600 \cdot \Omega} - \frac{6 \cdot V}{600} && \text{multiply both sides by } 3000 \Omega \\
 3000 \cdot \Omega \cdot \left(\frac{12 \cdot V}{100 \cdot \Omega} - \frac{V_a}{100 \cdot \Omega} + 63 \cdot \text{mA} \right) &= \left(\frac{V_a}{500 \cdot \Omega} - \frac{6 \cdot V}{500} + \frac{V_a}{600 \cdot \Omega} - \frac{6 \cdot V}{600} \right) \cdot 3000 \cdot \Omega \\
 360 \cdot V - 30 \cdot V_a + 189 \cdot V &= 6 \cdot V_a - 36 \cdot V + 5 \cdot V_a - 30 \cdot V \\
 360 \cdot V + 189 \cdot V + 36 \cdot V + 30 \cdot V &= 6 \cdot V_a + 5 \cdot V_a + 30 \cdot V_a \\
 615 \cdot V &= 41 \cdot V_a \\
 V_a &:= \frac{615 \cdot V}{41} && V_a = 15 \cdot V \\
 V_{R5} &= V_a - V_{S2} = 9 \cdot V \\
 I_{R1} &= \frac{V_{S1} - V_a}{R_1} = -30 \cdot \text{mA}
 \end{aligned}$$

ECE 2210 Lecture 7 notes p6

What if one side of a voltage source isn't ground?

$$I_1 + I_{VS2} = I_3$$

$$\frac{V_{S1} - V_a}{R_1} + ? = I_S$$

What do you put in for I_{VS2} ??


Go to the other side of V_{S2} .

$$\frac{V_{S1} - V_a}{R_1} + \frac{0 - V_b}{R_2} = I_S$$

Only problem is that you get the same equation at node b!


Where does the second equation come from?

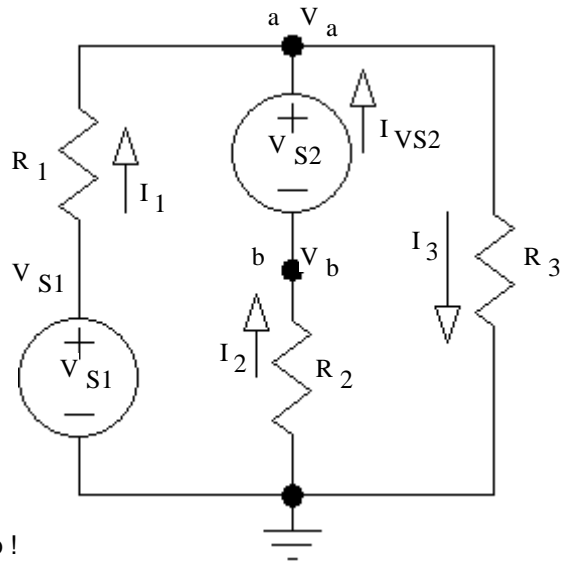Use something like this: $V_a = V_b + V_{S2}$



Similar Circuit, but no V_{S1} .

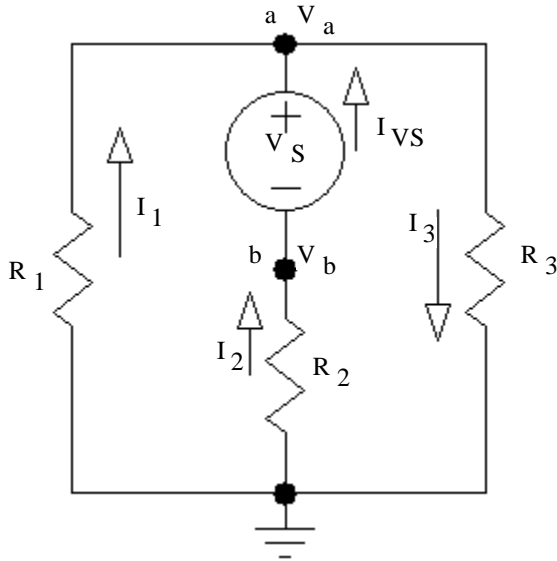If the ground is already at the bottom, use the same method as above.



If you can choose your ground, you can make life a little simpler.

