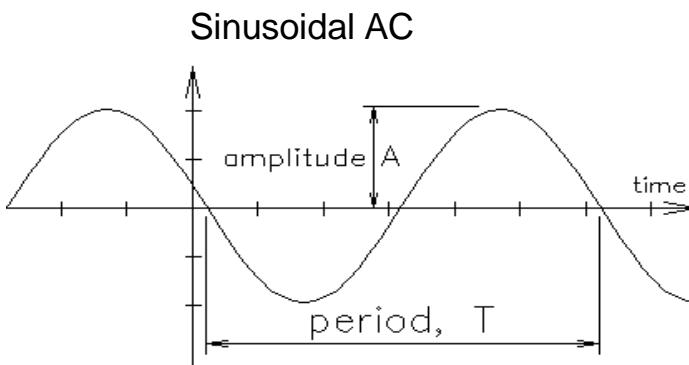


## Phasor analysis with impedances, For steady-state sinusoidal response ONLY

 $T = \text{Period} = \text{repeat time}$ 

$f = \text{frequency, cycles / second} \quad f = \frac{1}{T} = \frac{\omega}{2\pi}$


$\omega = \text{radian frequency, radians/sec} \quad \omega = 2\pi f$

 $A = \text{amplitude}$ 

Phase:  $\phi = -\frac{\Delta t}{T} \cdot 360\text{-deg}$

or:  $\phi = -\frac{\Delta t}{T} \cdot 2\pi \cdot \text{rad}$

$y(t) = A \cdot \cos(\omega \cdot t + \theta)$

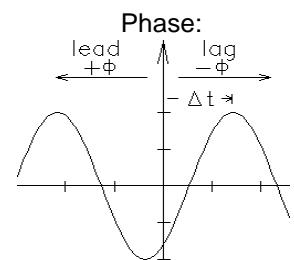**Phasor analysis**

The math is all based on the Euler's equation

**Euler's equation**

$e^{j\alpha} = \cos(\alpha) + j \cdot \sin(\alpha)$

OR:

$\cos(\alpha) = \frac{e^{j\alpha} + e^{-j\alpha}}{2}$


$\sin(\theta) = \frac{e^{j\alpha} - e^{-j\alpha}}{2j}$

$e^{j(\omega t + \theta)} = \cos(\omega t + \theta) + j \cdot \sin(\omega t + \theta)$

$\text{Re}[e^{j(\omega t + \theta)}] = \cos(\omega t + \theta)$

If we freeze this at time  $t=0$ , then we can represent  $\cos(\omega t + \theta)$  by  $e^{j\theta}$ 

That's the phasor

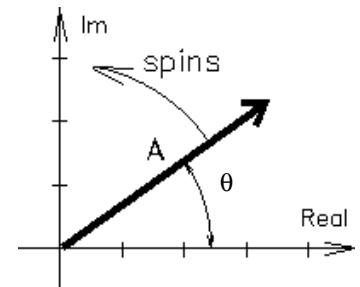Phasor

voltage:  $v(t) = V_p \cdot \cos(\omega \cdot t + \phi)$

$V(\omega) = V_p \cdot e^{j\phi}$

current:  $i(t) = I_p \cdot \cos(\omega \cdot t + \phi)$

$I(\omega) = I_p \cdot e^{j\phi}$

Phasors are drawn on a complex plane.

Phasors are used for adding and subtracting sinusoidal waveforms.

Ex1. Add the sinusoidal voltages  $v_1(t) = 4.5 \cdot V \cdot \cos(\omega \cdot t - 30\text{-deg})$   
and  $v_2(t) = 3.2 \cdot V \cdot \cos(\omega \cdot t + 15\text{-deg})$

using phasor notation, draw a phasor diagram of the three phasors, then convert back to time domain form.

$v_1(t) = 4.5 \cdot V \cdot \cos(\omega \cdot t - 30\text{-deg})$

$V_1(\omega) = 4.5V \underline{-30^\circ} \quad \text{or: } V_1(\omega) = 4.5 \cdot V \cdot e^{-j30\text{-deg}}$

and



$v_2(t) = 3.2 \cdot V \cdot \cos(\omega \cdot t + 15\text{-deg})$

$V_2(\omega) = 3.2V \underline{15^\circ} \quad \text{or: } V_2(\omega) = 3.2 \cdot V \cdot e^{j15\text{-deg}}$

I'm going to drop the  $(\omega)$  notation from the phasor notation, it gets cumbersome, but remember that phasors are in the frequency domain..

$V_1 = 4.5V \underline{-30^\circ} \quad \text{or: } V_1 := 4.5 \cdot V \cdot e^{-j30\text{-deg}}$

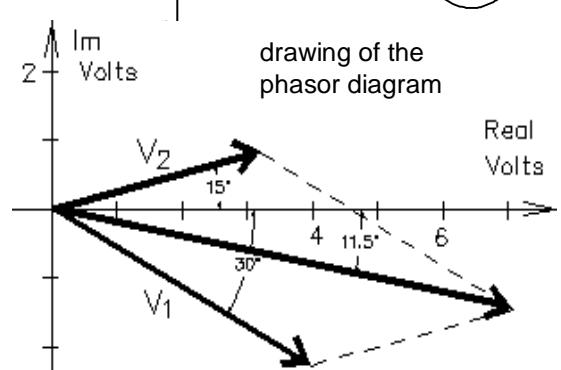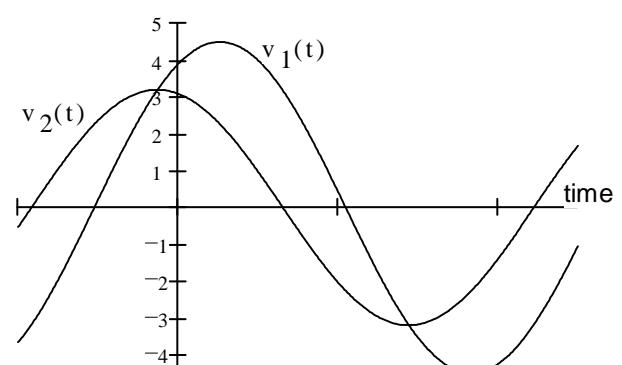$V_2 = 3.2V \underline{15^\circ} \quad \text{or: } V_2 := 3.2 \cdot V \cdot e^{j15\text{-deg}}$



## ECE 2210 / 00 Intro to Phasors p2

Add like vectors, first change to the rectangular form

$$\mathbf{V}_1 = 4.5 \text{ V } \angle -30^\circ$$

$$4.5 \cdot \text{V} \cdot \cos(-30^\circ) = 3.897 \text{ V}$$

$$4.5 \cdot \text{V} \cdot \sin(-30^\circ) = -2.25 \text{ V}$$

$$\mathbf{V}_1 = 3.897 - 2.25j \text{ V} \quad \} \text{ add}$$

$$\mathbf{V}_2 = 3.2 \text{ V } \angle 15^\circ$$

$$3.2 \cdot \text{V} \cdot \cos(15^\circ) = 3.091 \text{ V}$$

$$3.2 \cdot \text{V} \cdot \sin(15^\circ) = 0.828 \text{ V}$$

$$\mathbf{V}_2 = 3.091 + 0.828j \text{ V} \quad /$$

Add real parts:

$$3.897 + 3.091 = 6.988$$

Add imaginary parts:

$$-2.25 + 0.828 = -1.422$$

$$\mathbf{V}_3 := \mathbf{V}_1 + \mathbf{V}_2$$

$$\mathbf{V}_3 = 6.988 - 1.422j \text{ V} \quad \text{sum}$$

Change  $\mathbf{V}_3$  back to polar coordinates:

$$\sqrt{6.988^2 + 1.422^2} = 7.131$$

$$\text{atan}\left(\frac{-1.422}{6.988}\right) = -11.502^\circ$$

OR, in Mathcad notation (you'll see these in future solutions):

$$|\mathbf{V}_3| = 7.131 \text{ V}$$

$$\arg(\mathbf{V}_3) = -11.5^\circ$$

Change  $\mathbf{V}_3$  back to the time domain:

$$v_3(t) = v_1(t) + v_2(t) = 7.13 \cdot \cos(\omega t - 11.5^\circ) \text{ V}$$

Ex 2. Two sinusoidal voltages:  $v_1(t) = 5 \cdot \text{V} \cdot \cos(\omega t + 36.87^\circ)$  and  $v_2(t) = 3.162 \cdot \text{V} \cdot \cos(\omega t - 18.44^\circ)$

a) using phasor notation, find  $v_3 = v_1 - v_2$

$$\mathbf{V}_1 := 5 \cdot \text{V} \cdot e^{j(36.87^\circ)}$$

$$5 \cdot \text{V} \cdot \cos(36.87^\circ) = 4 \text{ V}$$

$$5 \cdot \text{V} \cdot \sin(36.87^\circ) = 3 \text{ V}$$

$$\mathbf{V}_1 = 4 + 3j \text{ V}$$

$$\mathbf{V}_2 := 3.162 \cdot \text{V} \cdot e^{j(-18.44^\circ)}$$

$$3.162 \cdot \text{V} \cdot \cos(-18.44^\circ) = 3 \text{ V}$$

$$3.162 \cdot \text{V} \cdot \sin(-18.44^\circ) = -1 \text{ V}$$

$$\mathbf{V}_2 = 3 - j \text{ V}$$

$$\text{Subtract real parts: } 4 \cdot \text{V} - 3 \cdot \text{V} = 1 \text{ V}$$

$$\text{Subtract imaginary parts: } 3 \cdot \text{V} - (-1 \cdot \text{V}) = 4 \text{ V}$$

$$\mathbf{V}_3 := \mathbf{V}_1 - \mathbf{V}_2 \quad \mathbf{V}_3 = 1 + 4j \text{ V}$$

$$\text{Magnitude: } \sqrt{(1 \cdot \text{V})^2 + (4 \cdot \text{V})^2} = 4.123 \text{ V}$$



OR:

$$|\mathbf{V}_3| = 4.123 \text{ V}$$

$$\text{Angle: } \text{atan}\left(\frac{4 \cdot \text{V}}{1 \cdot \text{V}}\right) = 75.96^\circ$$

$$\arg(\mathbf{V}_3) = 75.96^\circ$$
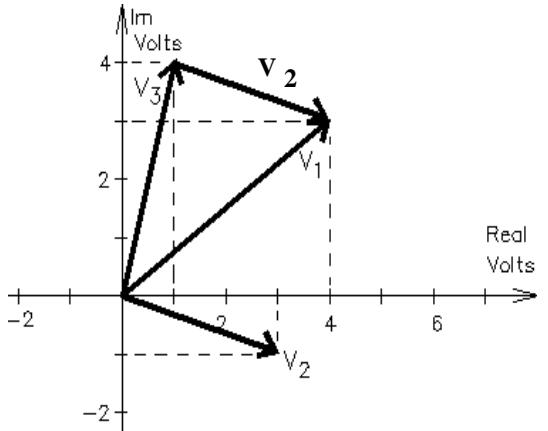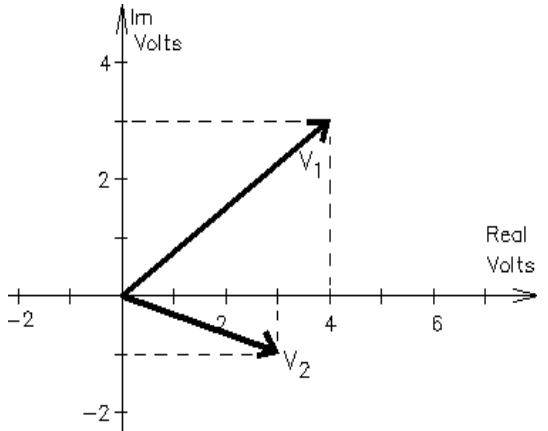
$$\text{So: } v_3(t) = v_1(t) - v_2(t) = 4.123 \cdot \text{V} \cdot \cos(\omega t + 75.96^\circ) \text{ V}$$



### What about Capacitors and Inductors?

Capacitors and Inductors in AC circuits cause  $90^\circ$  phase shifts between voltages and currents because they integrate and differentiate. But... integration and differentiation is a piece-of-cake in phasors.

## ECE 2210 / 00 Intro to Phasors p2

# ECE 2210 / 00 Intro to Phasors p3

**Calculus**


$$\frac{d}{dt} \left[ A \cdot e^{j(\omega t + \theta)} \right] = j \cdot \omega \cdot A \cdot e^{j(\omega t + \theta)} = \omega \cdot A \cdot e^{j(\omega t + \theta + 90^\circ)} = \omega \cdot A \cdot e^{j(\theta + 90^\circ)}$$

$$\int A \cdot e^{j(\omega t + \theta)} dt = \frac{1}{j \cdot \omega} \cdot A \cdot e^{j(\omega t + \theta)} = \frac{1}{\omega} \cdot A \cdot e^{j(\omega t + \theta - 90^\circ)} = \frac{1}{\omega} \cdot A \cdot e^{j(\theta - 90^\circ)}$$

Drop the  $\omega t$  ( $t=0$ ) to get:

## Impedance (like resistance)

Inductor

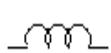

$$v_L = L \frac{d}{dt} i_L = L \frac{d}{dt} I_p \cdot e^{j(\omega t + \theta)} = j \cdot \omega \cdot L \left[ I_p \cdot e^{j(\omega t + \theta)} \right]$$

in phasor notation ---->  $V_L(\omega) = j \cdot \omega \cdot L \cdot I(\omega)$

**AC impedance**

$$Z_L = j \cdot \omega \cdot L$$

Capacitor



$$i_C = C \frac{d}{dt} v_C = C \frac{d}{dt} V_p \cdot e^{j(\omega t + \theta)} = j \cdot \omega \cdot C \left[ V_p \cdot e^{j(\omega t + \theta)} \right]$$

in phasor notation ---->  $I_C(\omega) = j \cdot \omega \cdot C \cdot V(\omega)$

$$V_C(\omega) = \frac{1}{j \cdot \omega \cdot C} \cdot I(\omega)$$

$$Z_C = \frac{1}{j \cdot \omega \cdot C} = \frac{-j}{\omega \cdot C}$$

Resistor




$$v_R = i_R \cdot R$$

$V_R(\omega) = R \cdot I(\omega)$

$Z_R = R$

You can use impedances just like resistances as long as you deal with the complex arithmetic.  
ALL the DC circuit analysis techniques will work with AC.

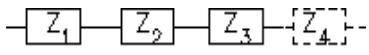
**series:** 

$$Z_{eq} = Z_1 + Z_2 + Z_3 + \dots$$

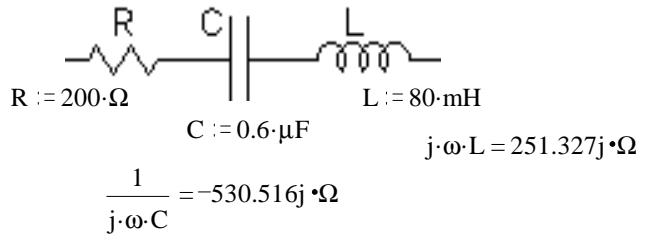Example:

$$f := 500 \cdot Hz$$

$$\omega := 2 \cdot \pi \cdot f = \omega = 3141.6 \frac{rad}{sec}$$



$$Z_{eq} := R + \frac{1}{j \cdot \omega \cdot C} + j \cdot \omega \cdot L = 200 \cdot \Omega - 530.5 \cdot j \cdot \Omega + 251.3 \cdot j \cdot \Omega = 200 - 279.2j \cdot \Omega \quad \text{rectangular form}$$

$$\sqrt{(200 \cdot \Omega)^2 + (279.2 \cdot \Omega)^2} = 343.4 \cdot \Omega \quad \text{atan} \left( \frac{-279.2 \cdot \Omega}{200 \cdot \Omega} \right) = -54.38 \cdot deg$$

$$Z_{eq} = 343.4 \Omega / -54.4^\circ \quad \text{polar form}$$

If:  $V := 12 \cdot V \cdot e^{j0^\circ}$

$$I := \frac{V}{Z_{eq}} = \frac{12 \cdot V}{343.4 \cdot \Omega} = 34.945 \cdot mA \quad \angle 0^\circ - -54.4^\circ = 54.4^\circ \quad deg$$

$$I = 34.95mA / 54.4^\circ = I = 20.348 + 28.405j \cdot mA$$

**Voltage divider:**


$$V_{Zn} = V_{total} \frac{Z_n}{Z_1 + Z_2 + Z_3 + \dots}$$

Note:  $\frac{1}{j} = -j = 1 / -90^\circ$

Eg:  $V_C := V \cdot \frac{j \cdot \omega \cdot C}{Z_{eq}} = 12 \cdot V \cdot e^{j0^\circ} \cdot \frac{530.516 \cdot e^{-j90^\circ} \cdot \Omega}{343.4 \cdot e^{-j54.38^\circ} \cdot \Omega}$

$$12 \cdot V \cdot \frac{530.516 \cdot \Omega}{343.4 \cdot \Omega} = 18.539 \cdot V \quad \angle 0^\circ + -90^\circ - -54.4^\circ = -35.6^\circ \quad deg$$


parallel:

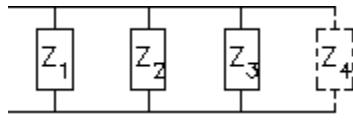

$$Z_{\text{eq}} = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots}$$

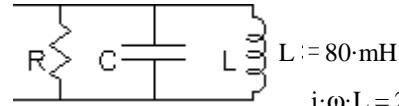Example:

$$f := 500 \cdot \text{Hz} \quad \omega := 2 \cdot \pi \cdot f \quad \omega = 3141.6 \cdot \frac{\text{rad}}{\text{sec}}$$



$$R := 200 \cdot \Omega \quad C := 0.6 \cdot \mu\text{F} \quad L := 80 \cdot \text{mH} \quad j \cdot \omega \cdot L = 251.327j \cdot \Omega$$

$$\frac{1}{\omega \cdot L} = 3.979 \cdot 10^{-3} \cdot \frac{1}{\Omega}$$

$$\frac{1}{j \cdot \omega \cdot C} = -530.516j \cdot \Omega$$

$$\omega \cdot C = 1.885 \cdot 10^{-3} \cdot \frac{1}{\Omega}$$

$$\begin{aligned} Z_{\text{eq}} &:= \frac{1}{\frac{1}{R} + \frac{1}{\left(\frac{1}{j \cdot \omega \cdot C}\right)} + \frac{1}{j \cdot \omega \cdot L}} = \frac{1}{\frac{1}{R} + j \cdot \omega \cdot C - \frac{j}{\omega \cdot L}} = \frac{1}{\frac{1}{200 \cdot \Omega} + 1.885 \cdot 10^{-3} \cdot j \cdot \frac{1}{\Omega} - 3.979 \cdot 10^{-3} \cdot j \cdot \frac{1}{\Omega}} = \frac{1}{(5 \cdot 10^{-3} - 2.094 \cdot 10^{-3} \cdot j) \cdot \frac{1}{\Omega}} \\ &= \frac{1}{(5 \cdot 10^{-3} - 2.094 \cdot 10^{-3} \cdot j) \cdot \frac{1}{\Omega} \cdot \frac{5 \cdot 10^{-3} + 2.094 \cdot 10^{-3} \cdot j}{5 \cdot 10^{-3} + 2.094 \cdot 10^{-3} \cdot j}} = \frac{1}{2.93848 \cdot 10^{-5}} = 170.156 + 71.261j \cdot \Omega \end{aligned}$$

If you want the answer in polar form, it's easier to convert the denominator first.

$$\sqrt{\left(5 \cdot 10^{-3} \cdot \frac{1}{\Omega}\right)^2 + \left(2.094 \cdot 10^{-3} \cdot \frac{1}{\Omega}\right)^2} = 5.4 \cdot 10^{-3} \cdot \frac{1}{\Omega} \quad \text{atan}\left(\frac{-2.094 \cdot 10^{-3} \cdot \Omega}{5 \cdot 10^{-3} \cdot \Omega}\right) = -22.72 \cdot \text{deg}$$

$$\frac{1}{5.4 \cdot 10^{-3} \cdot \frac{1}{\Omega}} = 185.185 \cdot \Omega \angle 0 - -22.7 = 22.7 \text{ deg}$$

$$Z_{\text{eq}} = 185.2 / 22.7^\circ$$

$$\text{If: } V := 12 \cdot \text{V} \cdot e^{j \cdot 0 \cdot \text{deg}} \quad I := \frac{V}{Z_{\text{eq}}} = \frac{12 \cdot \text{V}}{185.2 \cdot \Omega} = 64.795 \cdot \text{mA} \angle 0 - 22.7 = -22.7 \text{ deg}$$

$$I = 60 - 25.127j \cdot \text{mA}$$

Current divider:

$$I_{Zn} = I_{\text{total}} \cdot \frac{\frac{1}{Z_n}}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots}$$

$$\text{Eg: } I_L := I \cdot \frac{\frac{1}{j \cdot \omega \cdot L}}{\frac{1}{R} + j \cdot \omega \cdot C + \frac{1}{j \cdot \omega \cdot L}} = I \cdot \frac{\frac{1}{j \cdot \omega \cdot L}}{\left(\frac{1}{Z_{\text{eq}}}\right)} = I \cdot \frac{Z_{\text{eq}}}{j \cdot \omega \cdot L}$$

$$= 64.795 \cdot \text{mA} \cdot e^{-j \cdot 22.7 \cdot \text{deg}} \cdot \frac{185.2 \cdot e^{j \cdot 22.7 \cdot \text{deg}} \cdot \Omega}{251.327 \cdot e^{j \cdot 90 \cdot \text{deg}} \cdot \Omega}$$

$$= 64.795 \cdot \text{mA} \cdot \frac{185.2 \cdot \Omega}{251.327 \cdot \Omega} = 47.747 \cdot \text{mA} \angle -22.7 + 22.7 - 90 = -90 \text{ deg} \quad I_L = -47.746j \cdot \text{mA}$$