## ECE 2210 Lecture 18 notes Second order Transient examples



b) Find the characteristic equation for this circuit.



Just the denominator set to zero. The solutions of the characteristic equation are the poles of the transfer function.

c) Find the differential equation for  $v_1$ .

Cross-multiply the transfer function

$$s^{2} \cdot \mathbf{V}_{\mathbf{S}}(s) = \left(s^{2} + \frac{1}{C \cdot R} \cdot s + \frac{1}{L \cdot C}\right) \cdot \mathbf{V}_{\mathbf{L}}(s)$$

$$s^{2} \cdot \mathbf{V}_{\mathbf{S}}(s) = s^{2} \cdot \mathbf{V}_{\mathbf{L}}(s) + \frac{1}{C \cdot R} \cdot s \cdot \mathbf{V}_{\mathbf{L}}(s) + \frac{1}{L \cdot C} \cdot \mathbf{V}_{\mathbf{L}}(s)$$

$$\frac{d^{2}}{dt^{2}} \cdot v_{\mathbf{S}}(t) = \frac{d^{2}}{dt^{2}} \cdot v_{\mathbf{L}}(t) + \frac{1}{C \cdot R} \cdot \frac{d}{dt} \cdot v_{\mathbf{L}}(t) + \frac{1}{L \cdot C} \cdot v_{\mathbf{L}}(t)$$

$$\frac{d^{2}}{dt^{2}} \cdot v_{\mathbf{S}}(t) = \frac{d^{2}}{dt^{2}} \cdot v_{\mathbf{L}}(t) + \frac{3.788 \cdot 10^{4}}{\sec} \cdot \frac{d}{dt} \cdot v_{\mathbf{L}}(t) + \frac{9.091 \cdot 10^{9}}{\sec^{2}} \cdot v_{\mathbf{L}}(t)$$

d) What are the solutions to the characteristic equation?

$$s_{1} = \frac{-3.788 \cdot 10^{4}}{2} + \frac{1}{2} \cdot \sqrt{(3.788 \cdot 10^{4})^{2} - 4 \cdot (9.091 \cdot 10^{9})} = -1.894 \cdot 10^{4} + 9.345 \cdot 10^{4} j$$
  

$$s_{2} = \frac{-3.788 \cdot 10^{4}}{2} - \frac{1}{2} \cdot \sqrt{(3.788 \cdot 10^{4})^{2} - 4 \cdot (9.091 \cdot 10^{9})} = -1.894 \cdot 10^{4} - 9.345 \cdot 10^{4} j$$

e) What type of response do you expect from this circuit?

The solutions to the characteristic equation are complex so the response will be **underdamped**.

ECE 2210 Lecture 18 notes p1

## ECE 2210 Lecture 18 notes p2

2. Analysis of the circuit shown yields the characteristic equation below. The switch has been in the open position for a long time and is closed (as shown) at time t = 0. Find the initial and final conditions and write the full expression for  $i_{I}(t)$ , including all the constants that you find.

$$s^{2} + \left(\frac{1}{C \cdot R_{1}}\right) \cdot s + \left(\frac{1}{L \cdot C}\right) = 0$$

$$\left(\frac{1}{C \cdot R_{1}}\right) = 2.273 \cdot 10^{4} \cdot \sec^{-1} \qquad \left(\frac{1}{L \cdot C}\right) = 9.091 \cdot 10^{9} \cdot \sec^{-2}$$

$$s^{2} + 10000 \cdot \frac{1}{\sec} \cdot s + 2 \cdot 10^{7} \cdot \frac{1}{\sec^{2}} = 0$$

$$s_{1} := \left[\frac{-10000}{2} + \frac{1}{2} \cdot \sqrt{(10000)^{2} - 4 \cdot (2 \cdot 10^{7})}\right] \cdot \sec^{-1}$$
  
$$s_{1} = -2764 \cdot \sec^{-1}$$



$$2 := \left[\frac{-10000}{2} - \frac{1}{2} \cdot \sqrt{(10000)^2 - 4 \cdot (2 \cdot 10^7)}\right] \cdot \sec^{-1}$$

$$2 = -7236 \cdot \sec^{-1}$$
s<sub>1</sub> and s<sub>2</sub> are both real and distinct overdamped

Find the initial conditions:

Before the switch closed, the inductor current was:  $\frac{15 \cdot V}{R_1 + R_2} = 30 \cdot mA = i_L(0)$ Before the switch closed, the capacitor voltage was:  $v_C(0) = \frac{R_2}{R_1 + R_2} \cdot (15 \cdot V) = 9 \cdot V$  so:  $v_{C0} := 9 \cdot V$ 

S

s



When the switch is opened, the new voltage across the inductor is:  $v_{L0} = v_{C0}$ 

$$\frac{d}{dt}i_{L}(0) = \frac{1}{L}v_{L0} = \frac{1}{L}v_{C0} = 90 \cdot \frac{1}{5}$$

ECE 2210

Find the final condition:  $i_L(0)$   $v_L(0)$   $v_L(0)$   $i_L(\infty) =$  $\frac{15 \cdot V}{P} = 75 \cdot mA$   $i_L(\infty)$ 



General solution for the overdamped condition:  $i_{L}(t) = i_{L}(\infty) + B \cdot e^{s_{1} \cdot t} + D \cdot e^{s_{2} \cdot t}$ Initial conditions:  $i_{L0} = \frac{15 \cdot V}{R_1 + R_2} = i_{L}(\infty) + B + D$ , so  $B = i_{L0} - i_{L}(\infty) - D = 30 \cdot mA - 75 \cdot mA - D$ = -45·mA – D

$$\frac{d}{dt}i_{L}(0) = 90 \cdot \frac{A}{sec} = s_{1} \cdot B + s_{2} \cdot D = s_{1} \cdot (-45 \cdot mA - D) + s_{2} \cdot D = s_{1} \cdot (-45 \cdot mA) - s_{1} \cdot D + s_{2} \cdot D$$

$$90 \cdot \frac{A}{sec} - s_{1} \cdot (-45 \cdot mA)$$

solve for D & B:  $D := \frac{56 \text{ sec}^{-8} 1^{(-45) \text{ mA}}}{\frac{-8}{1+8}2}$  D = 7.69 mA B := -45 mA - D B = -52.7 mA

Plug numbers back in:  $i_{L}(t) := 75 \cdot mA - 52.7 \cdot mA \cdot e^{-2764t} + 7.69 \cdot mA \cdot e^{-7236t}$ 



## ECE 2210 Lecture 18 notes p3

 $\alpha := -250 \cdot \frac{1}{\sec}$ 

4. Analysis of the circuit shown yields the characteristic equation and s values below. The switch has been in the closed position for a long time and is opened (as shown) at time t = 0. Find the initial and final conditions and write the full expression for  $v_{C}(t)$ , including all the constants.

$$0 = s^{2} + \frac{R_{1}}{L} \cdot s + \frac{1}{L \cdot C}$$
  
s<sub>1</sub> :=  $(-250 + 10^{4} \cdot j) \cdot \frac{1}{sec}$ , s<sub>2</sub> :=  $(-250 - 10^{4} \cdot j) \cdot \frac{1}{sec}$ 

Solution:

$$\omega := 10000 \cdot \frac{1}{\sec}$$

Initial conditions:



Just after switch opens



$$\frac{d}{dt} v_{C}(0) = \alpha \cdot B + D \cdot \omega \qquad D := \frac{8 \cdot 10^{5} \cdot \frac{V}{sec} - \alpha \cdot B}{\omega} \qquad D = 79.9 \cdot V$$

Write the full expression for  $v_{C}(t)$ , including all the constants that you find.  $v_{C}(t) = e^{\omega t} (B \cdot \cos(\omega \cdot t) + D \cdot \sin(\omega \cdot t)) + v_{C}(\infty)$  $\mathbf{v}_{\mathbf{C}}(t) := e^{-250t} \cdot \left(-4 \cdot \mathbf{V} \cdot \cos\left(10^4 \cdot t\right) + 79.9 \cdot \mathbf{V} \cdot \sin\left(10^4 \cdot t\right)\right) + 10 \cdot \mathbf{V}$ 

is not required



ECE 2210 Lecture 18 notes p3