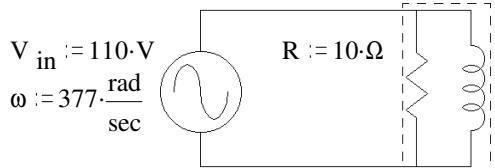


Ex. 1 R & L together are the load. Find the real power P, the reactive power Q, the complex power S, the apparent power |S|, & the power factor pf. Draw phasor diagram for the power.



$$Z = 4.704 + 4.991j \cdot \Omega \quad |Z| = 6.859 \cdot \Omega$$

$$L := 25 \cdot mH$$

$$Z := \frac{1}{\left(\frac{1}{R} + \frac{1}{j \cdot \omega \cdot L} \right)} = \frac{1}{0.1458 \cdot \frac{1}{\Omega} \cdot e^{-j \cdot 46.7 \cdot \text{deg}}}$$

$$\theta := \arg(Z)$$

$$\theta = 46.7 \cdot \text{deg}$$

$$pf := \cos(\theta)$$

$$pf = 0.686$$

$$I := \frac{V_{in}}{Z}$$

$$I = 11 - 11.671j \cdot A$$

$$|I| = 16.038 \cdot A$$

$$\arg(I) = -46.7 \cdot \text{deg}$$

$$P := |V_{in}| \cdot |I| \cdot pf$$

$$P = 1.21 \cdot kW$$

$$Q := |V_{in}| \cdot |I| \cdot \sin(\theta)$$

$$Q = 1.284 \cdot kVAR$$

$$\text{OR...} \quad Q := |V_{in}| \cdot |I| \cdot \sqrt{1^2 - pf^2}$$

$$Q = 1.284 \cdot kVAR$$

$$S := V_{in} \cdot I \quad \text{OR..} \quad S := P + j \cdot Q$$

$$S = 1.21 + 1.284j \cdot kVA$$

$$S := \sqrt{\text{Re}(S)^2 + \text{Im}(S)^2} = |S| = 1.764 \cdot kVA$$

$$\text{atan}\left(\frac{\text{Im}(S)}{\text{Re}(S)}\right) = 46.696 \cdot \text{deg}$$

$$S = 1.764 \text{ kVA } /46.7^\circ$$

OR, since we know that the voltage across each element of the load is V_{in} ...

Real power is dissipated only by resistors

$$P := \frac{(|V_{in}|)^2}{R}$$

$$P = 1.21 \cdot kW$$

$$Q := \frac{(|V_{in}|)^2}{\omega \cdot L}$$

$$Q = 1.284 \cdot kVAR$$

$$S := P + j \cdot Q$$

$$S = |S| = \sqrt{P^2 + Q^2} = 1.764 \cdot kVA$$


$$pf = \frac{P}{|S|} = 0.686$$

What value of C in parallel with R & L would make pf = 1 (Q = 0) ?

$$\text{Im}(I) = -11.671 \cdot A$$

$$X_C := \frac{V_{in}}{\text{Im}(I)}$$

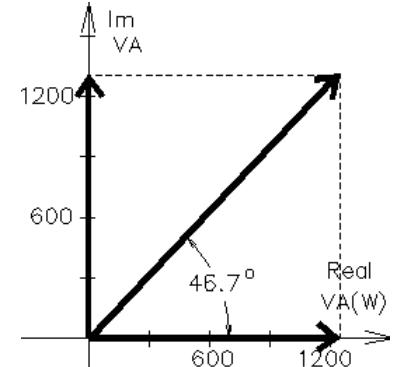
$$X_C = -9.425 \cdot \Omega = \frac{-1}{\omega \cdot C}$$



$$\frac{1}{|X_C| \cdot \omega} = 281 \cdot \mu F \quad \text{OR..} \quad \omega = \frac{1}{\sqrt{L \cdot C}} \quad C := \frac{1}{L \cdot \omega^2} \quad C = 281 \cdot \mu F$$

Ex. 2 R & L together are the load. Find the real power P, the reactive power Q, the complex power S, the apparent power |S|, & the power factor pf. Draw phasor diagram for the power.

Series R & L

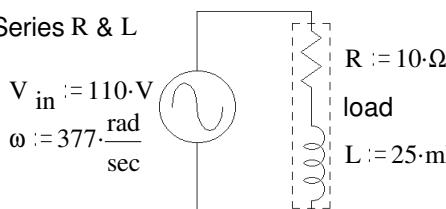

$$Z := R + j \cdot \omega \cdot L$$

$$Z = 10 + 9.425j \cdot \Omega \quad |Z| = 13.742 \cdot \Omega$$

$$|Z| = 13.742 \cdot \Omega$$

$$\theta = 46.696 \cdot \text{deg}$$

$$pf := \cos(\theta)$$

$$pf = 0.686$$

$$I := \frac{V_{in}}{Z}$$

$$I = 11 - 11.671j \cdot \text{sec}^{-1} \cdot \text{coul}$$

$$|I| = 8.005 \cdot A$$

$$\arg(I) = -46.696 \cdot \text{deg}$$

$$P := |V_{in}| \cdot |I| \cdot pf$$

$$P = 0.604 \cdot kW$$

$$Q := |V_{in}| \cdot |I| \cdot \sin(\theta)$$

$$Q = 0.641 \cdot kVAR$$


$$S := V_{in} \cdot I$$

$$S = 0.641 + 0.604j \cdot kVA$$

$$|S| = 0.881 \cdot kVA$$

$$\arg(S) = 43.304 \cdot \text{deg}$$

$$S = 0.881 \text{ kVA } /43.3^\circ$$

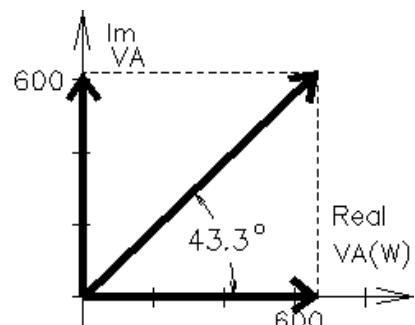

ECE 2210 AC Power Examples, p.2

OR, if we first find the magnitude of the current which flows through each element of the load...

$$|I| = \frac{V_{in}}{\sqrt{R^2 + (\omega L)^2}} = 8.005 \cdot A$$

$$P := (|I|)^2 \cdot R$$

$$P = 0.641 \cdot kW$$

$$Q := (|I|)^2 \cdot (\omega \cdot L)$$

$$Q = 0.604 \cdot kVAR$$

$$S := P + j \cdot Q$$

$$|S| = \sqrt{P^2 + Q^2} = 0.881 \cdot kVA$$

$$pf = \frac{P}{|S|} = 0.728$$

What value of C in parallel with R & L would make pf = 1 (Q = 0) ?

$$Q = 603.9 \cdot VAR \quad \text{so we need: } Q_C := -Q \quad Q_C = -603.9 \cdot VAR = \frac{V_{in}^2}{X_C}$$

$$X_C := \frac{V_{in}^2}{Q_C} \quad X_C = -20.035 \cdot \Omega = \frac{-1}{\omega \cdot C} \quad C := \frac{1}{|X_C| \cdot \omega} \quad C = 132 \cdot \mu F$$

$$\text{Check: } \frac{1}{\frac{1}{R + j \cdot \omega \cdot L} + j \cdot \omega \cdot C} = 18.883 \cdot \Omega \quad \text{No j term, so } \theta = 0^\circ$$

Ex. 3

A step-down transformer has an output voltage of 220 V (rms) when the primary is connected across a 560 V (rms) source.

a) If there are 280 turns on the primary winding, how many turns are required on the secondary?

$$280 \cdot \frac{220 \cdot \text{volt}}{560 \cdot \text{volt}} = 110 \text{ turns}$$

b) If the current in the primary is 2.4 A, what current flows in the load connected to the secondary?

$$2.4 \cdot \text{amp} \cdot \frac{280}{110} = 6.11 \cdot A$$


c) If the transformer is rated at 700/275 V, 2.1 kVA, what are the rated primary and secondary currents?

$$\text{pri: } \frac{2.1 \cdot \text{kVA}}{700 \cdot \text{V}} = 3 \cdot A \quad \text{sec: } \frac{2.1 \cdot \text{kVA}}{275 \cdot \text{V}} = 7.636 \cdot A$$


Ex. 4

The transformer shown in the circuit below is ideal. Find the following:

a) $I_1 = ?$

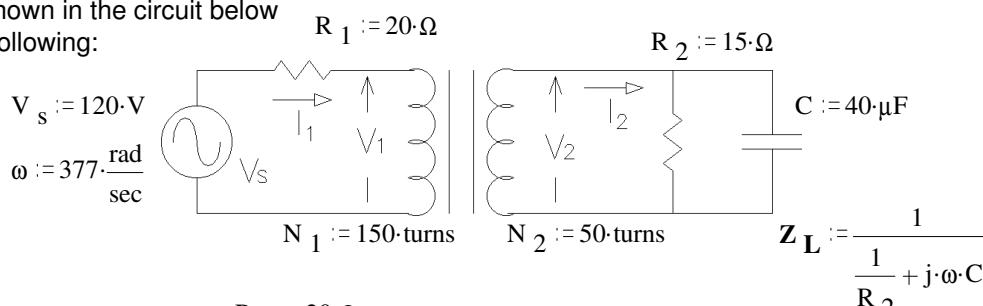

Make an equivalent circuit:

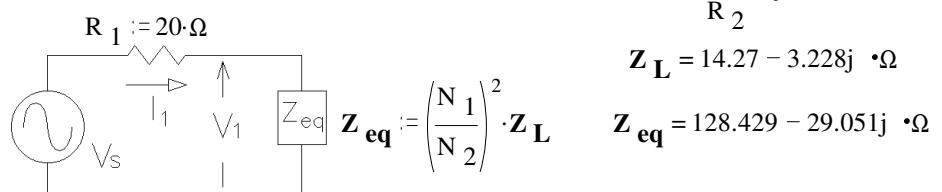

$$I_1 := \frac{V_s}{R_1 + Z_{eq}} \quad I_1 = 0.779 + 0.152j \cdot A$$

$$b) I_2 = ? \quad I_2 := \left(\frac{N_1}{N_2}\right) \cdot I_1 \quad I_2 = 2.336 + 0.457j \cdot A$$

$$c) V_2 = ? \quad V_1 := V_s \cdot \frac{Z_{eq}}{R_1 + Z_{eq}} \quad V_2 = \left(\frac{N_2}{N_1}\right) \cdot V_1 = 34.809 - 1.016j \cdot V$$

$$\text{OR.. } V_2 = I_2 \cdot Z_L = 34.809 - 1.016j \cdot V$$

ECE 2210 AC Power Examples, p.2