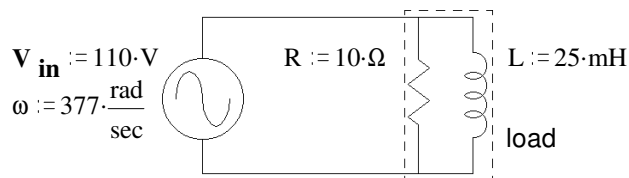


**Ex. 1** R & L together are the load. Find the real power P, the reactive power Q, the complex power S, the apparent power |S|, & the power factor pf. Draw phasor diagram for the power.



$$\mathbf{Z} := \frac{1}{\left(\frac{1}{R} + \frac{1}{j\omega L}\right)} = \frac{1}{0.1458 \cdot \frac{1}{\Omega} \cdot e^{-j46.7\text{-deg}}}$$

$$\mathbf{Z} = 4.704 + 4.991j \cdot \Omega \quad |\mathbf{Z}| = 6.859 \cdot \Omega \quad \theta := \arg(\mathbf{Z}) \quad \theta = 46.7 \cdot \text{deg} \quad \text{pf} := \cos(\theta) \quad \text{pf} = 0.686$$

$$\mathbf{I} := \frac{\mathbf{V}_{in}}{\mathbf{Z}} \quad \mathbf{I} = 11 - 11.671j \cdot \text{A} \quad |\mathbf{I}| = 16.038 \cdot \text{A} \quad \arg(\mathbf{I}) = -46.7 \cdot \text{deg}$$

$$P := |\mathbf{V}_{in}| \cdot |\mathbf{I}| \cdot \text{pf} \quad P = 1.21 \cdot \text{kW}$$

$$Q := |\mathbf{V}_{in}| \cdot |\mathbf{I}| \cdot \sin(\theta) \quad Q = 1.284 \cdot \text{kVAR} \quad \text{OR...} \quad Q := |\mathbf{V}_{in}| \cdot |\mathbf{I}| \cdot \sqrt{1 - \text{pf}^2} \quad Q = 1.284 \cdot \text{kVAR}$$

$$\mathbf{S} := \mathbf{V}_{in} \cdot \bar{\mathbf{I}} \quad \text{OR..} \quad \mathbf{S} := P + j \cdot Q \quad \mathbf{S} = 1.21 + 1.284j \cdot \text{kVA} \quad \mathbf{S} := \sqrt{\text{Re}(\mathbf{S})^2 + \text{Im}(\mathbf{S})^2} = |\mathbf{S}| = 1.764 \cdot \text{kVA}$$

$$\text{atan}\left(\frac{\text{Im}(\mathbf{S})}{\text{Re}(\mathbf{S})}\right) = 46.696 \cdot \text{deg}$$

$$\mathbf{S} = 1.764 \text{kVA} / 46.7^\circ$$

OR, since we know that the voltage across each element of the load is  $V_{in}$  ...

Real power is dissipated only by resistors

$$P := \frac{(|\mathbf{V}_{in}|)^2}{R} \quad P = 1.21 \cdot \text{kW} \quad Q := \frac{(|\mathbf{V}_{in}|)^2}{\omega L} \quad Q = 1.284 \cdot \text{kVAR}$$


$$\mathbf{S} := P + j \cdot Q$$

$$S = |\mathbf{S}| = \sqrt{P^2 + Q^2} = 1.764 \cdot \text{kVA} \quad \text{pf} = \frac{P}{|\mathbf{S}|} = 0.686$$

What value of C in parallel with R & L would make pf = 1 (Q = 0) ?


$$\text{Im}(\mathbf{I}) = -11.671 \cdot \text{A} \quad X_C := \frac{\mathbf{V}_{in}}{\text{Im}(\mathbf{I})} \quad X_C = -9.425 \cdot \Omega = \frac{-1}{\omega \cdot C}$$

$$\frac{1}{|X_C| \cdot \omega} = 281 \cdot \mu\text{F} \quad \text{OR..} \quad \omega = \frac{1}{\sqrt{L \cdot C}} \quad C := \frac{1}{L \cdot \omega^2} \quad C = 281 \cdot \mu\text{F}$$

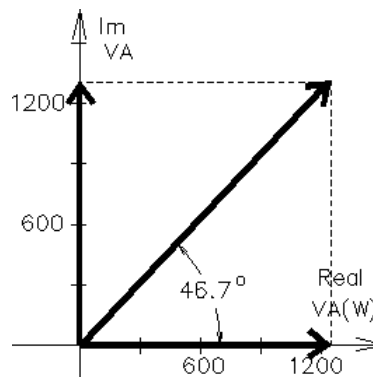

**Ex. 2** R & L together are the load. Find the real power P, the reactive power Q, the complex power S, the apparent power |S|, & the power factor pf. Draw phasor diagram for the power.

Series R & L

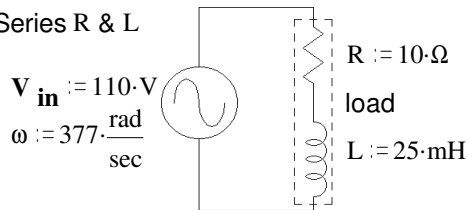

$$\mathbf{Z} := R + j\omega L$$

$$\mathbf{Z} = 10 + 9.425j \cdot \Omega \quad |\mathbf{Z}| = 13.742 \cdot \Omega$$

$$\theta := \arg(\mathbf{Z}) \quad \theta = 43.304 \cdot \text{deg} \quad \text{pf} := \cos(\theta) \quad \text{pf} = 0.728$$

$$\mathbf{I} := \frac{\mathbf{V}_{in}}{\mathbf{Z}} \quad \mathbf{I} = 5.825 - 5.49j \cdot \text{A}$$


$$|\mathbf{I}| = 8.005 \cdot \text{A} \quad \arg(\mathbf{I}) = -43.304 \cdot \text{deg}$$

$$P := |\mathbf{V}_{in}| \cdot |\mathbf{I}| \cdot \text{pf} \quad P = 0.641 \cdot \text{kW}$$

$$Q := |\mathbf{V}_{in}| \cdot |\mathbf{I}| \cdot \sin(\theta) \quad Q = 0.604 \cdot \text{kVAR}$$

$$\mathbf{S} := \mathbf{V}_{in} \cdot \bar{\mathbf{I}} \quad \mathbf{S} = 0.641 + 0.604j \cdot \text{kVA}$$

$$|\mathbf{S}| = 0.881 \cdot \text{kVA} \quad \arg(\mathbf{S}) = 43.304 \cdot \text{deg} \quad \mathbf{S} = 881 \text{VA} / 43.3^\circ$$

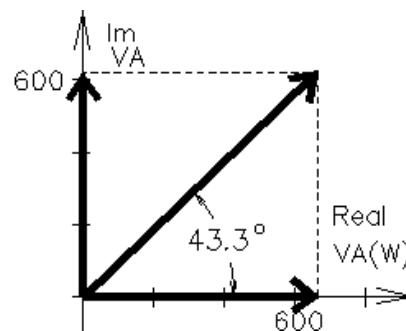

## ECE 2210 AC Power Examples, p.2

OR, if we first find the magnitude of the current which flows through each element of the load...

$$|\mathbf{I}| = \frac{V_{in}}{\sqrt{R^2 + (\omega \cdot L)^2}} = 8.005 \cdot A$$

$$P := (|\mathbf{I}|)^2 \cdot R$$

$$P = 0.641 \cdot kW$$

$$Q := (|\mathbf{I}|)^2 \cdot (\omega \cdot L)$$

$$Q = 0.604 \cdot kVAR$$

$$\mathbf{S} := P + j \cdot Q$$

$$|\mathbf{S}| = \sqrt{P^2 + Q^2} = 0.881 \cdot kVA$$

$$pf = \frac{P}{|\mathbf{S}|} = 0.728$$


What value of C in parallel with R & L would make pf = 1 (Q = 0) ?

$$Q = 603.9 \cdot VAR \quad \text{so we need: } Q_C := -Q \quad Q_C = -603.9 \cdot VAR = \frac{V_{in}^2}{X_C}$$

$$X_C := \frac{V_{in}^2}{Q_C} \quad X_C = -20.035 \cdot \Omega = \frac{-1}{\omega \cdot C} \quad C := \frac{1}{|X_C| \cdot \omega} \quad C = 132 \cdot \mu F$$

$$\text{Check: } \frac{1}{\frac{1}{R + j \cdot \omega \cdot L} + j \cdot \omega \cdot C} = 18.883 \cdot \Omega \quad \text{No } j \text{ term, so } \theta = 0^\circ$$

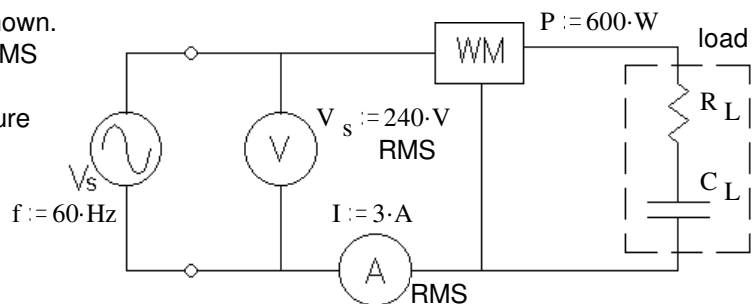**Ex. 3** R, & C together are the load in the circuit shown. The RMS voltmeter measures 240 V, the RMS ammeter measures 3 A, and the wattmeter measures 600 W. Find the following: Be sure to show the correct units for each value.



a) The value of the load resistor.  $R_L = ?$

$$P = I^2 \cdot R_L$$

$$R_L := \frac{P}{I^2} \quad R_L = 66.7 \cdot \Omega$$

b) The apparent power.  $|\mathbf{S}| = ?$

$$\mathbf{S} := V_s \cdot \mathbf{I}$$

$$S = 720 \cdot VA$$

c) The reactive power.  $Q = ?$

$$Q := -\sqrt{S^2 - P^2}$$

$$Q = -398 \cdot VAR$$

d) The complex power.  $\mathbf{S} = ?$

$$\mathbf{S} := P + j \cdot Q$$

$$\mathbf{S} = 600 - 398j \cdot VA$$

e) The power factor.  $pf = ?$

$$pf := \frac{P}{V_s \cdot I}$$

$$pf = 0.833$$

f) The power factor is leading or lagging? leading (load is capacitive, Q is negative)

g) The two components of the load are in a box which cannot be opened. Add (draw it) another component to the circuit above which can correct the power factor (make pf = 1). Show the correct component in the correct place and find its value. This component should not affect the real power consumption of the load.

Add an inductor in parallel with load

$$f = 60 \cdot Hz \quad \omega := 377 \cdot \frac{rad}{sec}$$

$$Q = -398 \cdot VAR \quad \text{so we need: } Q_L := -Q \quad Q_L = 398 \cdot VAR$$

$$Q_L = 398 \cdot VAR = \frac{V_s^2}{X_L}$$



$$X_L := \frac{V_s^2}{Q_L}$$

$$X_L = 144.725 \cdot \Omega = \omega \cdot L$$

$$L := \frac{|X_L|}{\omega}$$

$$L = 384 \cdot mH$$

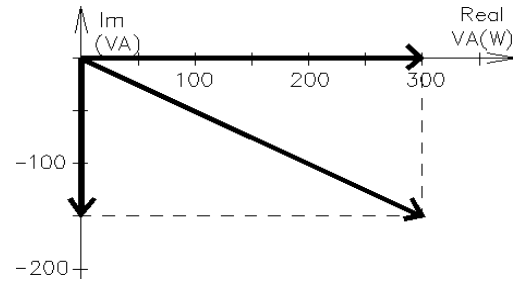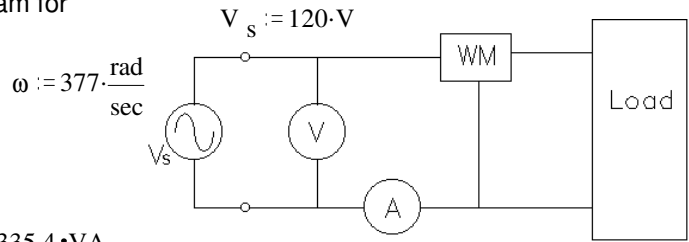**Ex. 4** For the 60 Hz load shown in the figure, the RMS voltmeter measures 120 V. The phasor diagram for the power is also shown. Find the following:



a) The complex power.  $S = ?$

$$P := 300 \cdot \text{W} \quad Q := -150 \cdot \text{VA}$$

$$S := P + j \cdot Q \quad S = 300 - 150j \cdot \text{VA}$$

b) The apparent power.  $|S| = ? \quad |S| = \sqrt{P^2 + Q^2} = 335.4 \cdot \text{VA}$

c) The power factor.  $\text{pf} = ? \quad \text{pf} := \frac{P}{|S|} \quad \text{pf} = 0.894$

d) The item marked "WM" in the figure is a wattmeter, what does it read? (give a number)  $P = 300 \cdot \text{W}$

e) The item marked "A" in the figure is an RMS ammeter, what does it read? (give a number)

$$I := \frac{|S|}{V_s} \quad I = 2.795 \cdot \text{A} \quad I = 2.8 \cdot \text{A}$$

f) The power factor is leading or lagging? leading (Q is negative)

g) The 3 components of the load are in a box which cannot be opened. Add another component to the circuit above which can correct the power factor (make  $\text{pf} = 1$ ). Show the correct component in the correct place and find its value. This component should not affect the real power consumption of the load.

Add an inductor in parallel with load

$$Q = -150 \cdot \text{VAR} \quad \text{need: } Q_L := -Q \quad Q_L = 150 \cdot \text{VAR} = \frac{V_s^2}{\omega \cdot L} \quad L := \frac{V_s^2}{\omega \cdot Q_L} \quad L = 255 \cdot \text{mH}$$


**Ex. 5** R, L, & C together are the load in the circuit shown

The RMS voltmeter measures 120 V.  $V_s := 120 \cdot \text{V}$

The wattmeter measures 270 W.  $P := 270 \cdot \text{W}$

The RMS ammeter measures 3.75 A.  $I := 3.75 \cdot \text{A}$

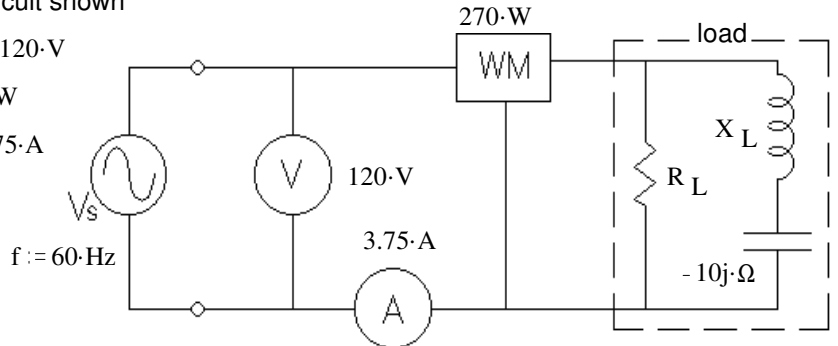Find the following: Be sure to show the correct units for each value.



a) The value of the load resistor.  $R_L = ?$

$$P = \frac{V_s^2}{R_L} \quad R_L := \frac{V_s^2}{P} \quad R_L = 53.3 \cdot \Omega$$

b) The magnitude of the impedance of the load inductor (reactance).  $|Z_L| = X_L = ?$

$$I_R := \frac{V_s}{R_L} \quad I_R = 2.25 \cdot \text{A} \quad I_L := \sqrt{I^2 - I_R^2} \quad I_L = 3 \cdot \text{A} \quad X := \frac{V_s}{I_L} \quad X = 40 \cdot \Omega$$

$$X_C := -10 \cdot \Omega \quad X_L := X - X_C \quad X_L = 50 \cdot \Omega$$

c) The reactive power.  $Q = ? \quad Q := \sqrt{(V_s \cdot I)^2 - P^2} \quad Q = 360 \cdot \text{VAR} \quad \text{positive, because the load is primarily inductive}$

d) The power factor is leading or lagging? lagging (load is inductive, Q is positive)

## ECE 2210 AC Power Examples, p.4

- e) The 3 components of the load are in a box which cannot be opened. Add another component to the circuit above which can correct the power factor (make  $pf = 1$ ). Show the correct component in the correct place and find its value. This component should not affect the real power consumption of the load.

Add a capacitor in parallel with load

$$f = 60 \cdot \text{Hz} \quad \omega := 377 \cdot \frac{\text{rad}}{\text{sec}}$$

$$Q = 360 \cdot \text{VAR} \quad \text{so we need: } Q_C := -Q \quad Q_C = -360 \cdot \text{VAR} = -\frac{V_s^2}{\omega \cdot C} = -\omega \cdot C \cdot V_s^2$$

$$C := \frac{Q_C}{-\omega \cdot V_s^2} \quad C = 66.3 \cdot \mu\text{F}$$

**Ex. 6** A step-down transformer has an output voltage of 220 V (rms) when the primary is connected across a 560 V (rms) source.

- a) If there are 280 turns on the primary winding, how many turns are required on the secondary?

$$280 \cdot \frac{220 \cdot \text{volt}}{560 \cdot \text{volt}} = 110 \text{ turns}$$

- b) If the current in the primary is 2.4 A, what current flows in the load connected to the secondary?


$$2.4 \cdot \text{amp} \cdot \frac{280}{110} = 6.11 \cdot \text{A}$$

- c) If the transformer is rated at 700/275 V, 2.1 kVA, what are the rated primary and secondary currents?

$$\text{pri: } \frac{2.1 \cdot \text{kVA}}{700 \cdot \text{V}} = 3 \cdot \text{A} \quad \text{sec: } \frac{2.1 \cdot \text{kVA}}{275 \cdot \text{V}} = 7.636 \cdot \text{A}$$


**Ex. 7** The transformer shown in the circuit below is ideal. Find the following:

- a)  $|I_1| = ?$

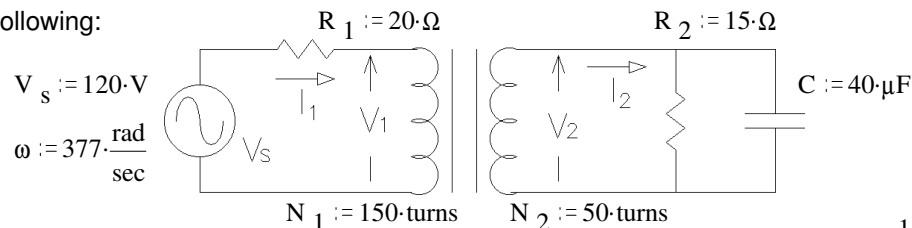

$$Z_L := \frac{1}{\frac{1}{R_2} + j \cdot \omega \cdot C}$$

Make an equivalent circuit:

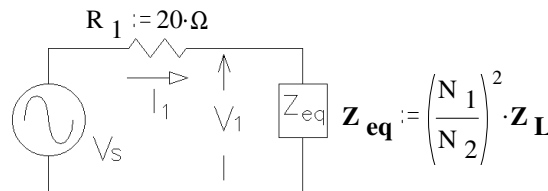

$$Z_L = 14.27 - 3.228j \cdot \Omega$$

$$Z_{eq} := \left(\frac{N_1}{N_2}\right)^2 \cdot Z_L \quad Z_{eq} = 128.429 - 29.051j \cdot \Omega$$

$$R_1 + Z_{eq} = 148.429 - 29.051j \cdot \Omega \quad \sqrt{148.429^2 + 29.051^2} = 151.245$$

$$|I_1| = \frac{V_s}{|R_1 + Z_{eq}|} = \frac{V_s}{151.245 \cdot \Omega} = 0.793 \cdot \text{A}$$

b)  $|I_2| = ? = \left(\frac{N_1}{N_2}\right) \cdot |I_1| = \frac{150}{50} \cdot 0.793 \cdot \text{A} = 2.379 \cdot \text{A}$

c)  $|V_1| = ? = V_s \cdot \left| \frac{Z_{eq}}{R_1 + Z_{eq}} \right|$  OR..  $|V_1| = |I_1| \cdot |Z_{eq}| = 0.793 \cdot \text{A} \cdot \sqrt{128.429^2 + 29.051^2} \cdot \Omega = 104.417 \cdot \text{V}$