

DC Notes

ECE 2210 / 00


A. Stolp
2/8/00, rev 1/28/06

Basic electrical quantities

Quantity	Unit
Charge, actually moves Q	Coulomb (C)
Current, like fluid flow $I = \frac{Q}{s}$	Amp (A, mA, μ A,...)
Voltage, like pressure V	volt (V, mV, kV,...)
Resistance $R = \frac{V}{I}$	Ohm (Ω , k Ω , M Ω ,...)
Conductance $G = \frac{1}{R}$	Siemens (S, old unit mho)
Power energy/time $P = V \cdot I$	Watt (W, mW, kW, MW,...)



KCL, Kirchoff's Current Law

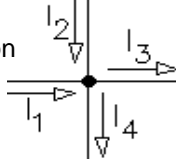$I_{in} = I_{out}$ of any point, part, or section



KVL, Kirchoff's Voltage Law

$V_{gains} = V_{drops}$ around any loop

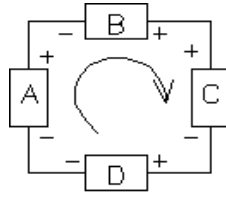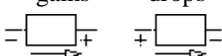

Node = all points connected by wire, all at same voltage (potential)

Ohm's law (resistors)

$$V = I \cdot R$$

$$I = \frac{V}{R}$$


$$R = \frac{V}{I}$$



Power $P_{IN} = P_{OUT}$ for resistor circuits

$$P = V \cdot I \text{ for everything}$$
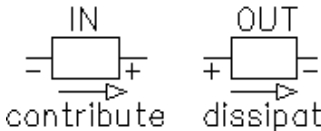
$$= I^2 \cdot R = \frac{V^2}{R} \text{ for resistors}$$




Resistors

series: $R_{eq} = R_1 + R_2 + R_3 + \dots$

Exactly the **same current** through each resistor

parallel: $R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots}$

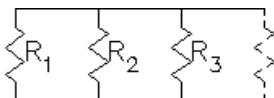
Exactly the **same voltage** across each resistor



Multiple unknowns:

1. Combine resistors into equivalents where possible.
2. Use superposition if there are multiple sources and you know all the resistors.
3. Use KCL, KVL, & Ohm's laws to write multiple equations and solve.

Schematic symbols

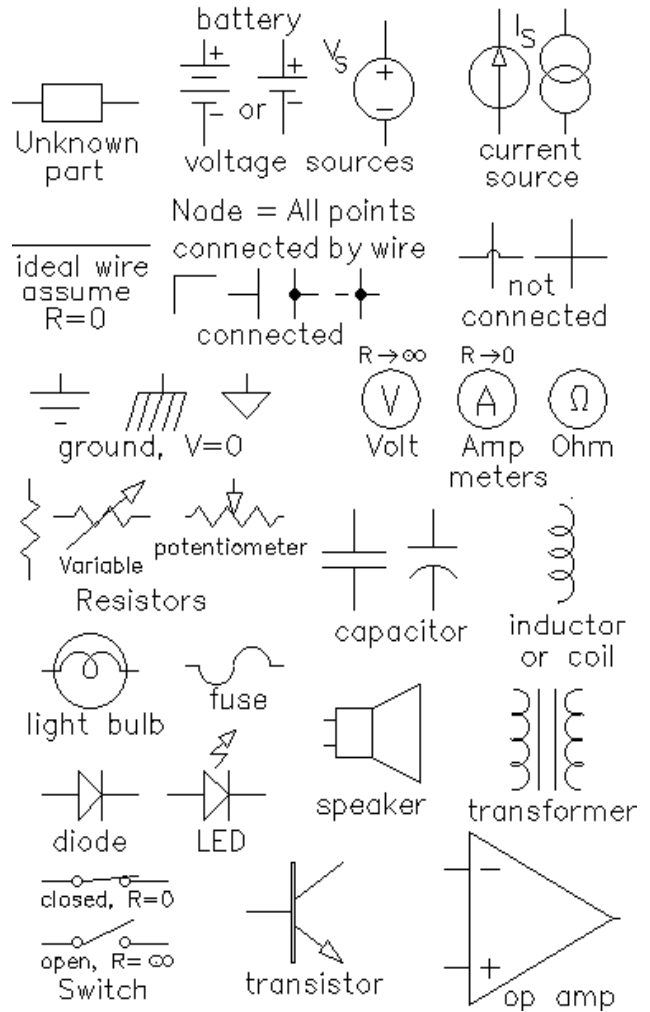

Maximum power transfer: $R_L = R_{Th}$
Load = Thevenin's

Voltage divider:

$$V_{Rn} = V_{total} \cdot \frac{R_n}{R_1 + R_2 + R_3 + \dots}$$

current divider:


$$I_{Rn} = I_{total} \cdot \frac{\frac{1}{R_n}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots}$$

DC Notes

Thévenin equivalent

To calculate a circuit's Thévenin equivalent:

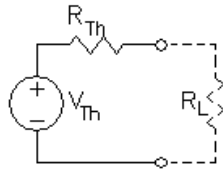
- 1) Remove the load and calculate the open-circuit voltage where the load used to be. This is the Thévenin voltage (V_{Th}).
- 2) Zero all the sources. (To zero a voltage source, replace it with a short. To zero a current source, replace it with an open.)
- 3) Compute the total resistance between the load terminals. (DO NOT include the load in this resistance.) This is the Thévenin source resistance (R_{Th}).
- 4) Draw the Thévenin equivalent circuit and add your values.



Norton equivalent

To calculate a circuit's Norton equivalent:

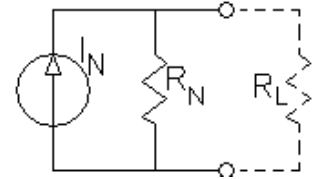- 1) Replace the load with a short (a wire) and calculate the short-circuit current in this wire. This is the Norton current (I_N). Remove the short.
- 2) Zero all the sources. (To zero a voltage source, replace it with a short. To zero a current source, replace it with an open.)
- 3) Compute the total resistance between the load terminals. (DO NOT include the load in this resistance.) This is the Norton source resistance (R_N). (Exactly the same as the Thévenin source resistance (R_{Th})).
- 4) Draw the Norton equivalent circuit and add your values.




OR (the more common way)...

- 1) Find the Thévenin equivalent circuit.
- 2) Convert to Norton circuit, $R_N = R_{Th}$ and $I_N = V_{Th}/R_{Th}$.

Nodal Analysis

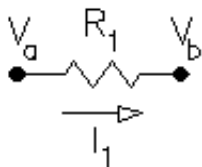- 1) If the circuit doesn't already have a ground, label one node as ground (zero voltage). If the ground can be defined as one side of a voltage source, that will make the following steps easier.
- 2) Label unknown node voltages as V_a , V_b , ... and label the current in each resistor as I_1 , I_2 ,
- 3) Write Kirchoff's current equations for each unknown node.
- 4) Replace the currents in your KCL equations with expressions like the one below.



$$I_1 = \frac{V_a - V_b}{R_1}$$

- 5) Solve the multiple equations for the multiple unknown voltages

Superposition

For circuits with **more than 1 source**.

- 1) Zero all but one source. (To zero a voltage source, replace it with a short. To zero a current source, replace it with an open.)
- 2) Compute your wanted voltage or current due to the remaining source. Careful, some may be negative.
- 3) Repeat the first two steps for all the sources.
- 4) Sum all the contributions from all the sources to find the actual voltage or current. **Watch your signs!**