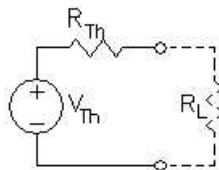


DC Notes

Thévenin equivalent

To calculate a circuit's Thévenin equivalent:


- 1) Remove the load and calculate the open-circuit voltage where the load used to be. This is the Thévenin voltage (V_{Th}).
- 2) Zero all the sources. (To zero a voltage source, replace it with a short. To zero a current source, replace it with an open.)
- 3) Compute the total resistance between the load terminals. (DO NOT include the load in this resistance.) This is the Thévenin source resistance (R_{Th}).
- 4) Draw the Thévenin equivalent circuit and add your values.



Norton equivalent

To calculate a circuit's Norton equivalent:

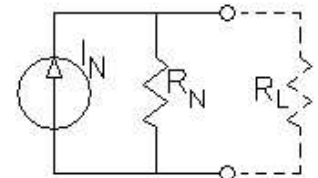- 1) Replace the load with a short (a wire) and calculate the short-circuit current in this wire. This is the Norton current (I_N). Remove the short.
- 2) Zero all the sources. (To zero a voltage source, replace it with a short. To zero a current source, replace it with an open.)
- 3) Compute the total resistance between the load terminals. (DO NOT include the load in this resistance.) This is the Norton source resistance (R_N). (Exactly the same as the Thévenin source resistance (R_{Th})).
- 4) Draw the Norton equivalent circuit and add your values.




OR (the more common way)...

- 1) Find the Thévenin equivalent circuit.
- 2) Convert to Norton circuit, $R_N = R_{Th}$ and $I_N = V_{Th}/R_{Th}$.

Nodal Analysis

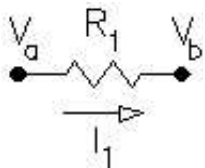- 1) If the circuit doesn't already have a ground, label one node as ground (zero voltage). If the ground can be defined as one side of a voltage source, that will make the following steps easier.
- 2) Label unknown node voltages as V_a, V_b, \dots and label the current in each resistor as I_1, I_2, \dots
- 3) Write Kirchoff's current equations for each unknown node.
- 4) Replace the currents in your KCL equations with expressions like the one below.



$$I_1 = \frac{V_a - V_b}{R_1}$$

- 5) Solve the multiple equations for the multiple unknown voltages

Superposition

For circuits with **more than 1 source**.

- 1) Zero all but one source. (To zero a voltage source, replace it with a short. To zero a current source, replace it with an open.)
- 2) Compute your wanted voltage or current due to the remaining source. Careful, some may be negative.
- 3) Repeat the first two steps for all the sources.
- 4) Sum all the contributions from all the sources to find the actual voltage or current. **Watch your signs!**