

DC Notes


ECE 2210 / 00

A.Stolp
2/8/00, rev 1/28/06

Basic electrical quantities


Quantity	Unit
Charge, actually moves Q	Coulomb (C)
Current, like fluid flow $I = \frac{Q}{s}$	Amp (A, mA, μ A,...)
Voltage, like pressure V	volt (V, mV, kV,...)
Resistance $R = \frac{V}{I}$	Ohm (Ω , k Ω , M Ω ,...)
Conductance $G = \frac{1}{R}$	Siemens (S, old unit mho)
Power energy/time $P = V \cdot I$	Watt (W, mW, kW, MW,...)

Schematic symbols

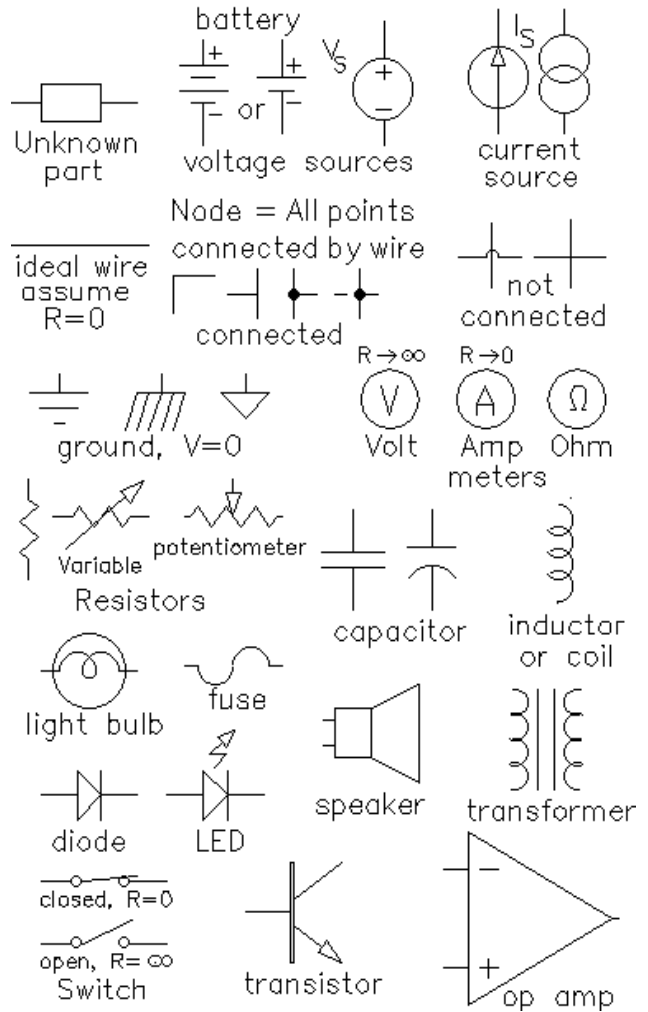

KCL, Kirchoff's Current Law

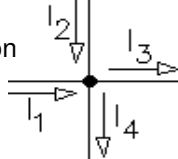$I_{in} = I_{out}$ of any point, part, or section



KVL, Kirchoff's Voltage Law

$V_{gains} = V_{drops}$ around any loop



Node = all points connected by wire, all at same voltage (potential)

Ohm's law (resistors)

$$V = I \cdot R$$

$$I = \frac{V}{R}$$

$$R = \frac{V}{I}$$

Power $P_{IN} = P_{OUT}$ for resistor circuits

$$P = V \cdot I \text{ for everything}$$

$$= I^2 \cdot R = \frac{V^2}{R} \text{ for resistors}$$

Maximum power transfer: $R_L = R_{Th}$
Load = Thevenin's


Resistors

series: $R_{eq} = R_1 + R_2 + R_3 + \dots$

Exactly the **same current** through each resistor

parallel: $R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots}$

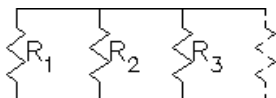Exactly the **same voltage** across each resistor



Voltage divider:

$$V_{Rn} = V_{total} \cdot \frac{R_n}{R_1 + R_2 + R_3 + \dots}$$

current divider:

$$I_{Rn} = I_{total} \cdot \frac{\frac{1}{R_n}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots}$$

Multiple unknowns:

1. Combine resistors into equivalents where possible.
2. Use superposition if there are multiple sources and you know all the resistors.
3. Use KCL, KVL, & Ohm's laws to write multiple equations and solve.