

Exam-type Diode Circuit Examples

On an exam, I usually tell you what assumptions to make about the diodes, then you can show that you know how to analyze the circuit and test those assumptions. Since everyone starts with the same assumptions, everyone should do the same work.

Assume that diode D_1 is conducting and that diode D_2 is not conducting.

- a) Find V_{R1} , I_{R1} , I_{R3} , I_{D1} , V_{R2} based on these assumptions.
Do not recalculate if you find the assumptions are wrong.


$$V_{R1} = \underline{\hspace{2cm}}$$

$$I_{R1} = \underline{\hspace{2cm}}$$

$$I_{R3} = \underline{\hspace{2cm}}$$

$$I_{D1} = \underline{\hspace{2cm}}$$

$$V_{R2} = \underline{\hspace{2cm}}$$

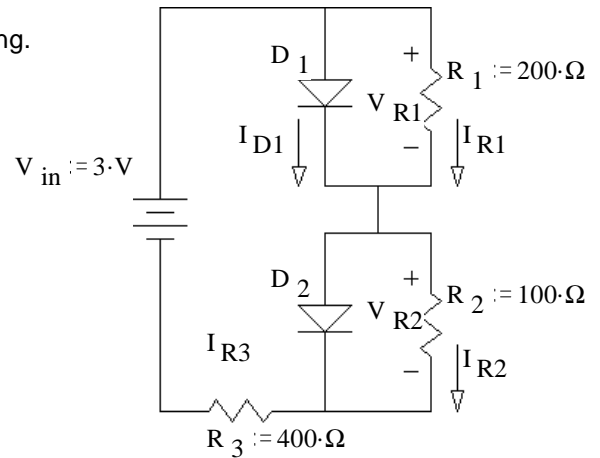

Solution:

$$V_{R1} := 0.7 \cdot V$$


$$I_{R1} := \frac{V_{R1}}{R_1} \quad I_{R1} = 3.5 \cdot \text{mA}$$

$$I_{R3} := \frac{V_{in} - 0.7 \cdot V}{R_2 + R_3} \quad I_{R3} = 4.6 \cdot \text{mA}$$

$$I_{D1} := I_{R3} - I_{R1} \quad I_{D1} = 1.1 \cdot \text{mA}$$

$$I_{R2} := I_{R3}$$
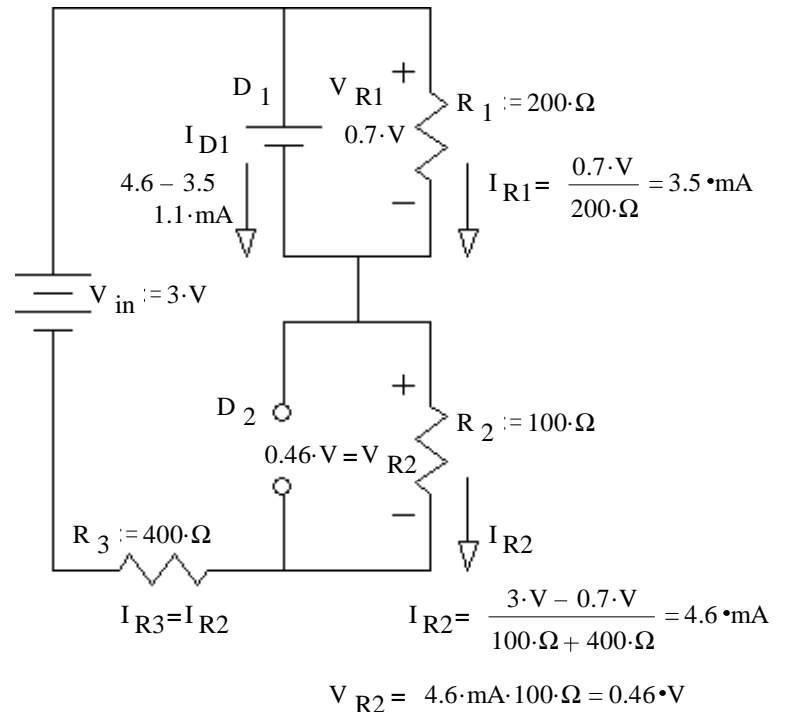
$$V_{R2} := I_{R2} \cdot R_2 \quad V_{R2} = 0.46 \cdot V$$



- b) Was the assumption about D_1 correct? (circle one)
yes no
 How do you know? (Specifically show a value which is or is not within a correct range.)

yes $I_{D1} = 1.1 \cdot \text{mA} > 0$

- c) Was the assumption about D_2 correct? (circle one)
yes no
 How do you know?

yes $V_{D2} = V_{R2} = 0.46 \cdot V < 0.7V$

- d) Based on your answers to b) and c), which (if any) of the following was not correctly calculated in part a.

V_{R1} I_{R1} I_{R3} I_{D2} V_{R2}

(circle any number of answers)

Circle none in this case

ECE 2210 Diode Circuit Examples p2

Assume that diode D_1 does **NOT** conduct.

Assume that diodes D_2 and D_3 **DO** conduct.

a) Stick with these assumptions even if your answers come out absurd.


Find the following:

$V_{D1} =$ _____


$I_{D2} =$ _____

$I_{D3} =$ _____

$I_{Vs} =$ _____

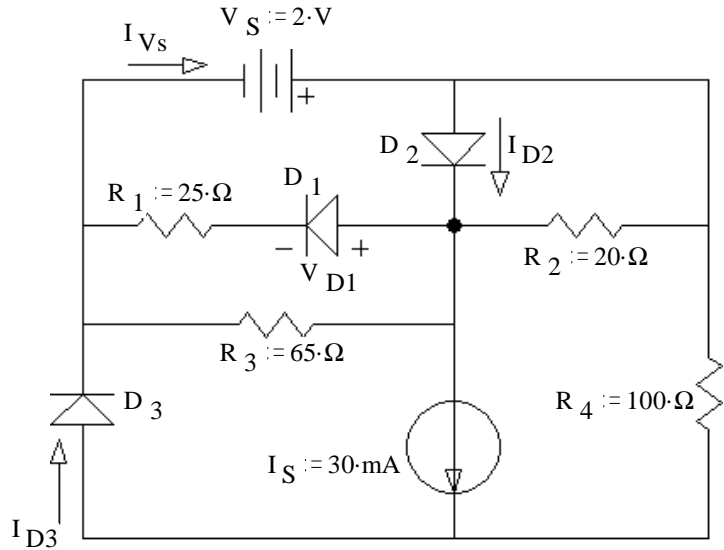

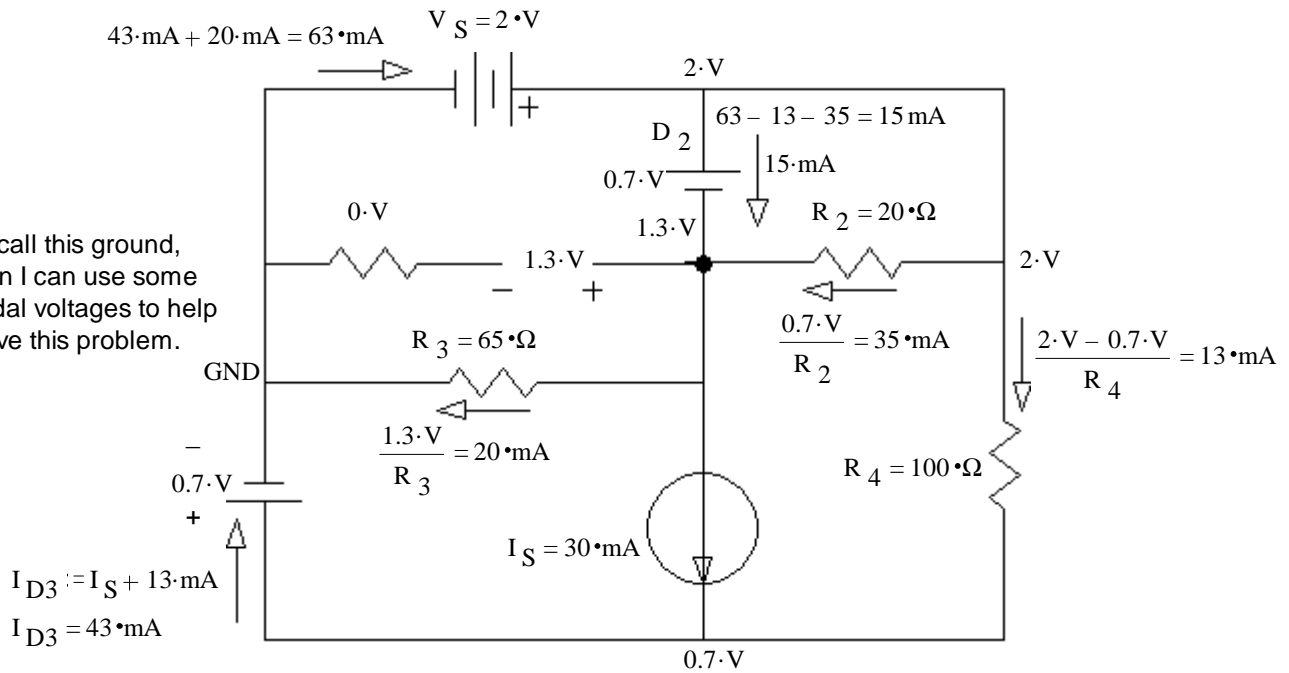If I call this ground, then I can use some nodal voltages to help solve this problem.



Alternate way to find: $I_{D2} := 20\text{mA} + I_S - \frac{0.7\text{V}}{R_2}$ $I_{D2} = 15\text{mA}$

b) Based on the numbers above, was the assumption about D_1 correct? Circle one: yes no
 How do you know? (Specifically show a value which is or is not within a correct range.) $V_{D1} = 1.3 > 0.7\text{V}$ no

c) Based on the numbers above, was the assumption about D_2 correct? Circle one: yes no
 How do you know? (Show a value & range.) $I_{D2} = 15\text{mA} > 0$ yes



d) Based on the numbers above, was the assumption about D_3 correct? Circle one: yes no
 How do you know? (Show a value & range.) $I_{D3} = 43\text{mA} > 0$ yes

ECE 2210 Diode Circuit Examples p2

ECE 2210 Diode Circuit Examples p3

A voltage waveform (dotted line) is applied to the circuit shown.
Accurately draw the output waveform (v_o) you expect to see.
 Label important times **and** voltage levels.


If diode doesn't conduct:

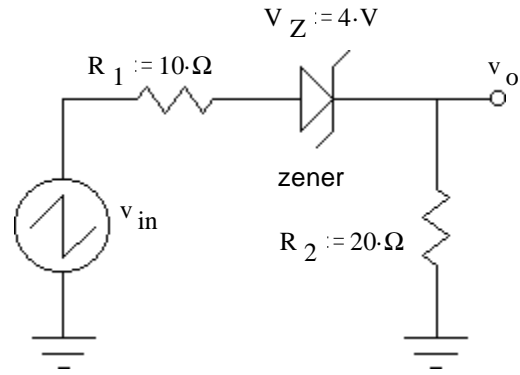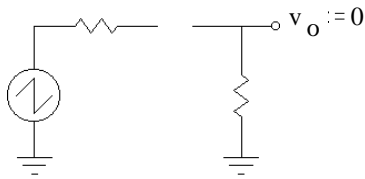

Positive half

Diode conducts at: 0.7 V input at time: $\frac{0.7\text{ V}}{10\text{ V}} \cdot 10\text{ ms} = 0.7\text{ ms}$



Maximum:

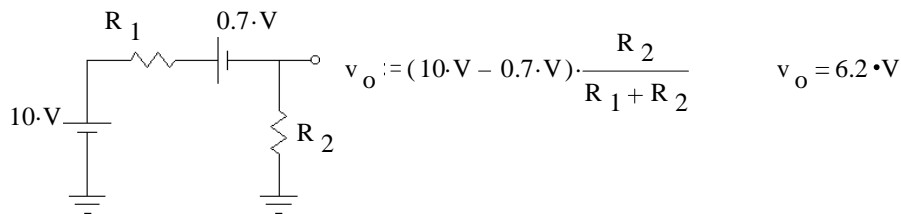


Negative half

Diode conducts at: -4 V input at time: $20\text{ ms} - \frac{4\text{ V}}{10\text{ V}} \cdot 10\text{ ms} = 16\text{ ms}$


Maximum:

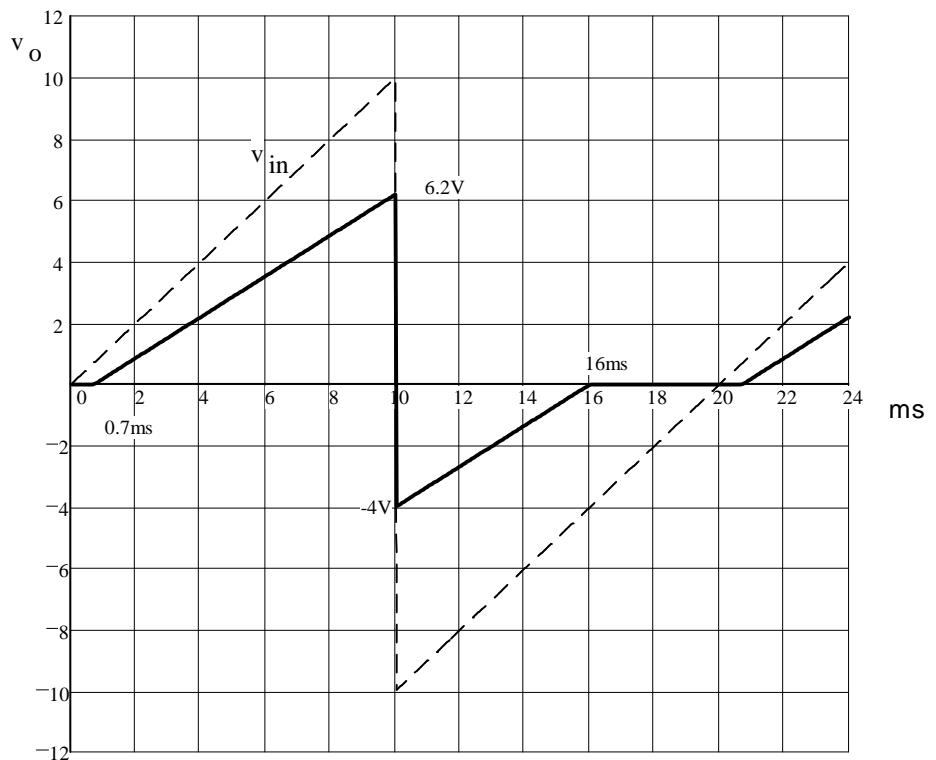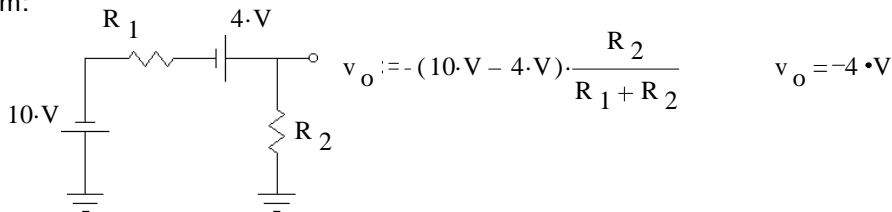

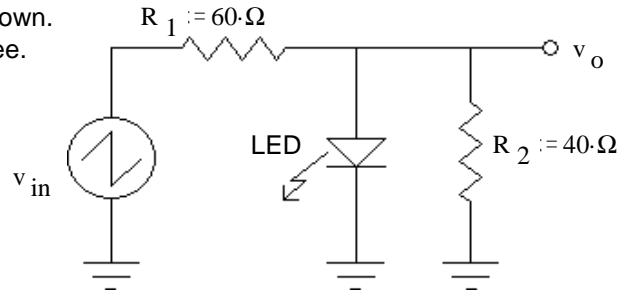A voltage waveform (dotted line) is applied to the circuit shown. Accurately draw the output waveform (v_o) you expect to see. Label important times and voltage levels.



If diode doesn't conduct:

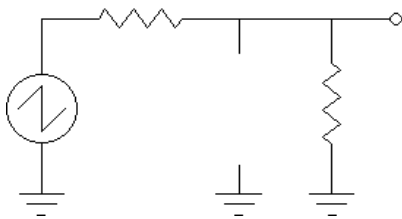

$$v_o = \frac{R_2}{R_1 + R_2} \cdot v_{in}$$

$$\frac{R_2}{R_1 + R_2} \cdot 10 \cdot V = 4 \cdot V$$

When: $v_{in} := \frac{R_1 + R_2}{R_2} \cdot 2 \cdot V$ $v_{in} = 5 \cdot V$ at: 5-ms Diode begins to conduct

When diode conducts:

