

ECE 2210 / 00 Phasor Examples

1. Add the sinusoidal voltages $v_1(t) = 4.5 \cdot V \cdot \cos(\omega \cdot t - 30^\circ)$
and $v_2(t) = 3.2 \cdot V \cdot \cos(\omega \cdot t + 15^\circ)$

using phasor notation, draw a phasor diagram of the three phasors, then convert back to time domain form.

$$v_1(t) = 4.5 \cdot V \cdot \cos(\omega \cdot t - 30^\circ)$$

$$\mathbf{V}_1(\omega) = 4.5V \angle -30^\circ \quad \text{or: } \mathbf{V}_1(\omega) = 4.5 \cdot V \cdot e^{-j30^\circ}$$

and

$$v_2(t) = 3.2 \cdot V \cdot \cos(\omega \cdot t + 15^\circ)$$

$$\mathbf{V}_2(\omega) = 3.2V \angle 15^\circ \quad \text{or: } \mathbf{V}_2(\omega) = 3.2 \cdot V \cdot e^{j15^\circ}$$

I'm going to drop the (ω) notation from the phasor notation, it gets cumbersome, but remember that phasors are in the frequency domain..

$$\mathbf{V}_1 = 4.5V \angle -30^\circ \quad \text{or: } \mathbf{V}_1 := 4.5 \cdot V \cdot e^{-j30^\circ}$$

$$\mathbf{V}_2 = 3.2V \angle 15^\circ \quad \text{or: } \mathbf{V}_2 := 3.2 \cdot V \cdot e^{j15^\circ}$$

$$4.5 \cdot V \cdot \cos(-30^\circ) = 3.897 \cdot V$$

$$4.5 \cdot V \cdot \sin(-30^\circ) = -2.25 \cdot V$$

$$3.2 \cdot V \cdot \cos(15^\circ) = 3.091 \cdot V$$

$$3.2 \cdot V \cdot \sin(15^\circ) = 0.828 \cdot V$$

$$\text{Add real parts: } 3.897 + 3.091 = 6.988$$

$$\text{Add imaginary parts: } -2.25 + 0.828 = -1.422$$

$$\mathbf{V}_1 = 3.897 - 2.25j \cdot V$$

$$\mathbf{V}_2 = 3.091 + 0.828j \cdot V$$

$$\mathbf{V}_3 := \mathbf{V}_1 + \mathbf{V}_2$$

$$\mathbf{V}_3 = 6.988 - 1.422j \cdot V$$

Change \mathbf{V}_3 back to polar coordinates:

$$\sqrt{6.988^2 + 1.422^2} = 7.131$$

$$\text{atan}\left(\frac{-1.422}{6.988}\right) = -11.502^\circ$$


OR, in Mathcad notation (you'll see these in future solutions):

$$|\mathbf{V}_3| = 7.131 \cdot V$$

$$\arg(\mathbf{V}_3) = -11.5^\circ$$

Change \mathbf{V}_3 back to the time domain:
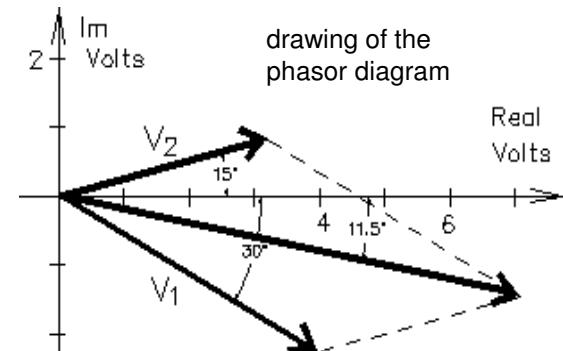
$$v_3(t) = v_1(t) + v_2(t) = 7.13 \cdot \cos(\omega \cdot t - 11.5^\circ) \cdot V$$



2. Two sinusoidal voltages: $v_1(t) = 5 \cdot V \cdot \cos(\omega \cdot t + 36.87^\circ)$ and $v_2(t) = 3.162 \cdot V \cdot \cos(\omega \cdot t - 18.44^\circ)$

a) using phasor notation, find $v_3 = v_1 - v_2$

$$\mathbf{V}_1 := 5 \cdot V \cdot e^{j(36.87^\circ)}$$

$$5 \cdot V \cdot \cos(36.87^\circ) = 4 \cdot V$$

$$5 \cdot V \cdot \sin(36.87^\circ) = 3 \cdot V$$

$$\mathbf{V}_2 := 3.162 \cdot V \cdot e^{j(-18.44^\circ)}$$

$$3.162 \cdot V \cdot \cos(-18.44^\circ) = 3 \cdot V$$

$$3.162 \cdot V \cdot \sin(-18.44^\circ) = -1 \cdot V$$

$$\text{Subtract real parts: } 4 \cdot V - 3 \cdot V = 1 \cdot V$$

$$\text{Subtract imaginary parts: } 3 \cdot V - (-1 \cdot V) = 4 \cdot V$$

$$v_1(t) - v_2(t) = (1 + 4j) \cdot V$$

$$\text{Magnitude: } \sqrt{(1 \cdot V)^2 + (4 \cdot V)^2} = 4.123 \cdot V$$

OR:


$$\text{Angle: } \text{atan}\left(\frac{4 \cdot V}{1 \cdot V}\right) = 75.96^\circ$$

$$|\mathbf{V}_3| = 4.123 \cdot V$$

$$\arg(\mathbf{V}_3) = 75.96^\circ$$

$$\text{So: } v_3(t) = v_1(t) - v_2(t) = 4.123 \cdot V \cdot \cos(\omega \cdot t + 75.96^\circ) \cdot V$$

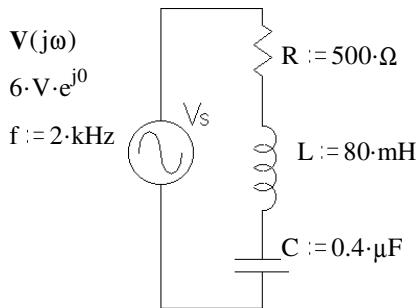3 Find V_R , V_L , and V_C in polar phasor form. $f := 2\text{ kHz}$



$$\omega := 2\pi f$$

$$\omega = 1.257 \cdot 10^4 \frac{\text{rad}}{\text{sec}}$$

$$Z_L := j\omega L$$

$$Z_L = 1.005j \text{ k}\Omega$$

$$Z_C := \frac{1}{j\omega C}$$

$$Z_C = -0.199j \text{ k}\Omega$$

$$Z_{\text{eq}} := R + j\omega L + \frac{1}{j\omega C}$$

$$Z_{\text{eq}} = 500 + 806.366j \text{ }\Omega$$

$$\sqrt{500^2 + 806^2} = 948.491$$

$$\text{atan}\left(\frac{806}{500}\right) = 58.187^\circ$$

$$Z_{\text{eq}} = 948.5 \Omega / 58.2^\circ$$

$$\text{find the current: } I := \frac{6 \cdot V \cdot e^{j0}}{Z_{\text{eq}}}$$

$$\text{magnitude: } \frac{6 \cdot V}{948.5 \cdot \Omega} = 6.326 \text{ mA}$$

$$\text{angle: } 0^\circ - 58.2^\circ = -58.2^\circ$$

$$I = 6.326 \text{ mA } / -58.2^\circ$$

find the magnitude

$$V_R := I \cdot R$$

$$6.326 \text{ mA} \cdot 500 \cdot \Omega = 3.163 \text{ V}$$

$$-58.2^\circ \text{ deg} + 0^\circ = -58.2^\circ$$

$$V_R = 3.163 \text{ V } / -58.2^\circ$$

$$V_L := I \cdot Z_L$$

$$6.326 \text{ mA} \cdot 1005 \cdot \Omega = 6.358 \text{ V}$$

$$-58.2^\circ \text{ deg} + 90^\circ = 31.8^\circ$$

$$V_L = 6.358 \text{ V } / 31.8^\circ$$

$$V_C := I \cdot Z_C$$

$$6.326 \text{ mA} \cdot (-199) \cdot \Omega = -1.259 \text{ V}$$

$$-58.2^\circ \text{ deg} + (90^\circ) = 31.8^\circ$$

$$V_C = -1.259 \text{ V } / 31.8^\circ$$

$$\text{OR: } 6.326 \text{ mA} \cdot (199) \cdot \Omega = 1.259 \text{ V}$$

$$-58.2^\circ \text{ deg} + (-90^\circ) = -148.2^\circ$$

$$V_C = 1.259 \text{ V } / -148.2^\circ$$

OR, you can also find these voltages directly, using a voltage divider. I.E. to find V_C directly:

$$\begin{aligned} V_C &:= \frac{\frac{1}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}} \cdot 6 \cdot V = \frac{1}{R \cdot (j\omega C) + j\omega L \cdot (j\omega C) + 1} \cdot 6 \cdot V = \frac{1}{R \cdot (j\omega C) - \omega^2 \cdot L \cdot C + 1} \cdot 6 \cdot V \\ &= \frac{1}{(1 - \omega^2 \cdot L \cdot C) + j\omega \cdot R \cdot C} \cdot 6 \cdot V \quad (1 - \omega^2 \cdot L \cdot C) = -4.053 \quad j\omega \cdot R \cdot C = 2.513j \\ &= \frac{6 \cdot V}{-4.053 + 2.513j} \cdot \frac{(-4.053 - 2.513j)}{(-4.053 - 2.513j)} = \frac{6 \cdot V \cdot (-4.053 - 2.513j)}{(-4.053)^2 + 2.513^2} \\ &\quad 6 \cdot V \cdot (-4.053 - 2.513j) = -24.318 - 15.078j \text{ V} \\ &\quad (-4.053)^2 + 2.513^2 = 22.742 \\ &= \left(\frac{-24.318}{22.742} - \frac{15.078j}{22.742} \right) \cdot V = -1.069 - 0.663j \text{ V} \end{aligned}$$



$$\text{magnitude: } \sqrt{1.069^2 + 0.663^2} = 1.258$$

$$\text{angle: } \text{atan}\left(\frac{-0.663}{-1.069}\right) = 31.81^\circ$$

but this is actually in the third quadrant,
so modify your calculator's results:

$$31.81^\circ \text{ deg} - 180^\circ = -148.19^\circ$$

$$= 1.258 \text{ V } / -148.2^\circ$$

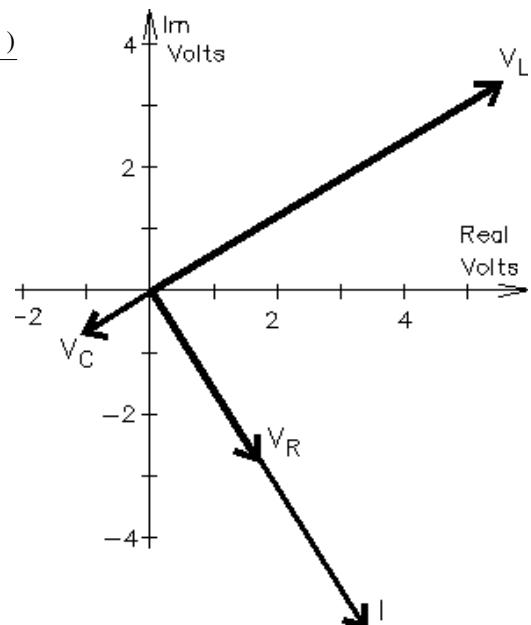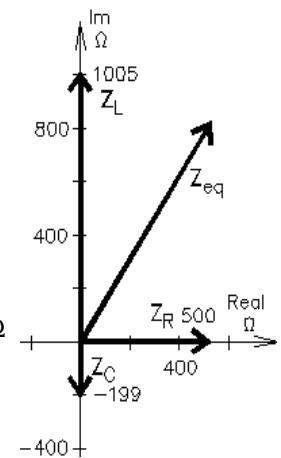

ECE 2210 / 00 Phasor Examples p3

4. a) Find Z_{eq} . $f := 2.5 \cdot kHz$ $\omega := 2 \cdot \pi \cdot f$ $\omega = 1.571 \cdot 10^4 \frac{rad}{sec}$

Left branch

$$Z_L := \frac{1}{j \cdot \omega \cdot C}$$


$$Z_L = -63.662j \Omega$$

Right branch

$$Z_R := j \cdot \omega \cdot L_2 + R$$

$$Z_R = 200 + 125.664j \Omega$$
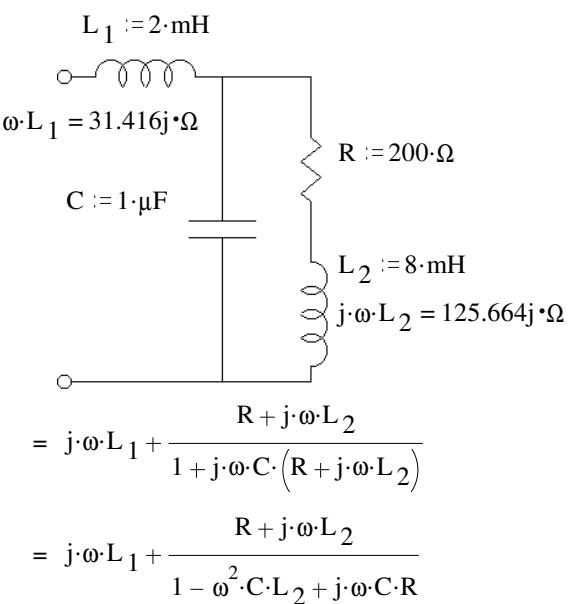
$$Z_{eq} := j \cdot \omega \cdot L_1 + \frac{1}{\frac{1}{R + j \cdot \omega \cdot L_2} + \frac{1}{\frac{1}{j \cdot \omega \cdot C}}} = j \cdot \omega \cdot L_1 + \frac{1}{\frac{1}{R + j \cdot \omega \cdot L_2} + j \cdot \omega \cdot C}$$



Sometimes it's worth simplifying a little before putting in numbers.

$$\begin{aligned} Z_{eq} &= 31.416 \cdot j \Omega + \frac{(200 + 125.664 \cdot j) \cdot \Omega \cdot (-0.974 - 3.142 \cdot j)}{-0.974 + 3.142 \cdot j} = 31.416 \cdot j \Omega + \frac{(200 + 125.664 \cdot j) \cdot (-0.974 - 3.142 \cdot j)}{0.974^2 + 3.142^2} \\ &= 31.416 \cdot j \Omega + \frac{((200 \cdot (-0.974) - 125.664 \cdot (-3.142)) + (125.664 \cdot (-0.974) - 200 \cdot 3.142) \cdot j) \cdot \Omega}{0.974^2 + 3.142^2} \\ &= 31.416 \cdot j \Omega + \frac{(200.036288 - 750.796736 \cdot j) \cdot \Omega}{10.82084} = 31.416 \cdot j \Omega + 18.486 \cdot \Omega - 69.384 \cdot j \Omega = 18.486 - 37.968j \Omega \end{aligned}$$

$$\sqrt{18.49^2 + 37.97^2} = 42.233 \quad \text{atan}\left(\frac{-37.97}{18.49}\right) = -64.036 \cdot \text{deg} \quad Z_{eq} = 42.24 \Omega / -64.04^\circ$$

b) $V_{in} := 12 \cdot V \cdot e^{j20 \cdot \text{deg}}$ Find I_{L1} , V_C $I_{L1} := \frac{V_{in}}{Z_{eq}}$ $\frac{12 \cdot V}{42.24 \cdot \Omega} = 284.091 \cdot \text{mA}$ $20 \cdot \text{deg} - (-64.04) \cdot \text{deg} = 84.04 \cdot \text{deg}$

$$I_{L1} = 284 \cdot \text{mA} / 84.04^\circ = 284 \cdot \text{mA} \cdot e^{j84.04 \cdot \text{deg}} \quad I_{L1} = 29.485 + 282.569j \cdot \text{mA}$$

$$V_C := I_{L1} \cdot (18.486 - 69.384 \cdot j) \Omega = 284 \cdot \text{mA} \cdot \sqrt{18.486^2 + 69.384^2} \cdot \Omega = 20.392 \cdot V$$

$$84.04 \cdot \text{deg} + \text{atan}\left(\frac{-69.384}{18.486}\right) = 8.959 \cdot \text{deg} \quad V_C = 20.4V / 8.96^\circ$$

To find V_C

$$\text{directly: } \frac{1}{\frac{1}{R + j \cdot \omega \cdot L_2} + j \cdot \omega \cdot C}$$

You could then use another voltage divider to find V_R or V_{L2} .

$$\begin{aligned} V_C &:= \frac{\frac{1}{j \cdot \omega \cdot L_1 + \frac{1}{\frac{1}{R + j \cdot \omega \cdot L_2} + j \cdot \omega \cdot C}} \cdot V_{in}}{\frac{1}{R + j \cdot \omega \cdot L_2}} = \frac{1}{j \cdot \omega \cdot L_1 \cdot \left(\frac{1}{R + j \cdot \omega \cdot L_2} + j \cdot \omega \cdot C \right) + 1} \cdot V_{in} = \frac{1}{\frac{j \cdot \omega \cdot L_1}{R + j \cdot \omega \cdot L_2} - \omega^2 \cdot L_1 \cdot C + 1} \\ &= \frac{1}{\frac{j \cdot \omega \cdot L_1}{R + j \cdot \omega \cdot L_2} - \omega^2 \cdot L_1 \cdot C + 1} \cdot V_{in} = \frac{1}{\frac{j \cdot \omega \cdot L_1 \cdot (R - j \cdot \omega \cdot L_2)}{R^2 + (\omega \cdot L_2)^2} - \omega^2 \cdot L_1 \cdot C + 1} \cdot V_{in} \\ &= \frac{1}{\left[\frac{\omega^2 \cdot L_1 \cdot L_2}{R^2 + (\omega \cdot L_2)^2} - \omega^2 \cdot L_1 \cdot C + 1 \right] + j \cdot \frac{\omega \cdot L_1 \cdot R}{R^2 + (\omega \cdot L_2)^2}} \cdot V_{in} = \frac{12 \cdot V \cdot e^{j20 \cdot \text{deg}}}{0.58816 \cdot e^{j11.039 \cdot \text{deg}}} = \frac{12 \cdot V}{0.58816} / 20 - 11.039^\circ \\ &= 20.4V / 8.96^\circ \quad \text{Same} \\ V_C &= 20.153 + 3.178j \cdot V \end{aligned}$$

ECE 2210 / 00 Phasor Examples p4

4. Continued Let's find I_{L2} .

$$Z_r := j\omega L_2 + R \\ Z_r = 200 + 125.664j \cdot \Omega \quad \sqrt{200^2 + 125.664^2} = 236.202 \quad \text{atan}\left(\frac{125.664}{200}\right) = 32.142^\circ$$

$$I_{L2} = \frac{20.4 \cdot V \cdot e^{j8.96^\circ}}{236.202 \cdot \Omega \cdot e^{j32.142^\circ}} = \frac{20.4 \cdot V}{236.202 \cdot \Omega} / 8.96 - 32.142^\circ = 86.4 \text{mA } / -23.18^\circ$$

Or, directly by

$$\text{Current divider: } I_{L2} := \frac{\frac{1}{R + j\omega L_2}}{\frac{j\omega C + \frac{1}{R + j\omega L_2}}{1}} \cdot I_{L1} = \frac{1}{j\omega C(R + j\omega L_2) + 1} \cdot I_{L1} = \frac{I_{L1}}{1 - \omega^2 C L_2 + j\omega C R}$$

$$\text{denominator: } \sqrt{(1 - \omega^2 C L_2)^2 + (\omega C R)^2} = 3.289 \quad \text{atan}\left(\frac{\omega C R}{1 - \omega^2 C L_2}\right) + 180^\circ = 107.224^\circ$$

$$I_{L2} = \frac{284 \cdot \text{mA} \cdot e^{j84.04^\circ}}{3.289 \cdot e^{j107.224^\circ}} = \frac{284 \cdot \text{mA}}{3.289} / 84.04 - 107.224^\circ = 86.4 \text{mA } / -23.18^\circ$$

$$I_{L2} = 79.404 - 34.001j \cdot \text{mA}$$

$$\text{How about } I_C? \quad I_C := \frac{V_C}{\left(\frac{1}{j\omega C}\right)} = V_C \cdot j\omega C = 20.4V / 8.96^\circ \cdot 0.015708 / 90^\circ \cdot \frac{1}{\Omega} = 320 \text{mA } / 98.96^\circ$$

Or, directly by

$$\text{Current divider: } I_C := \frac{\frac{j\omega C}{R + j\omega L_2}}{\frac{j\omega C + \frac{1}{R + j\omega L_2}}{1}} \cdot I_{L1} = \frac{j\omega C(R + j\omega L_2)}{j\omega C(R + j\omega L_2) + 1} \cdot I_{L1} = \frac{-\omega^2 C L_2 + j\omega C R}{1 - \omega^2 C L_2 + j\omega C R} \cdot I_{L1}$$

$$\text{numerator: } \sqrt{(\omega^2 C L_2)^2 + (\omega C R)^2} = 3.71 \quad \text{atan}\left(\frac{\omega C R}{-\omega^2 C L_2}\right) + 180^\circ = 122.142^\circ$$

denominator is the same as above.

$$I_C = \frac{3.71 \cdot e^{j122.14^\circ}}{3.289 \cdot e^{j107.224^\circ}} \cdot 284 \cdot \text{mA} \cdot e^{j84.04^\circ} = \frac{3.71}{3.289} \cdot 284 \cdot \text{mA} / 122.14 - 107.224 + 84.04^\circ = 320 \text{mA } / 98.96^\circ$$

This current is greater than the input current. What's going on?

The angle between I_C & I_{L2} is big enough that they somewhat cancel each other out.

Check Kirchoff's Current Law: $I_C + I_{L2} = 29.485 + 282.569j \cdot \text{mA} = I_{L1} = 29.485 + 282.569j \cdot \text{mA}$


5. a) Find Z_2 . For partial credit, you must show work and/or intermediate results.

$$I := 25 \cdot \text{mA} \cdot e^{j10^\circ}$$

$$V_{in} := 10 \cdot V / -20^\circ$$

$$Z_T := \frac{V_{in}}{I} = \frac{10 \cdot V}{25 \cdot \text{mA}} / -20 - 10^\circ = 400 \Omega / -30^\circ$$

$$Z_T = 346.41 - 200j \cdot \Omega$$

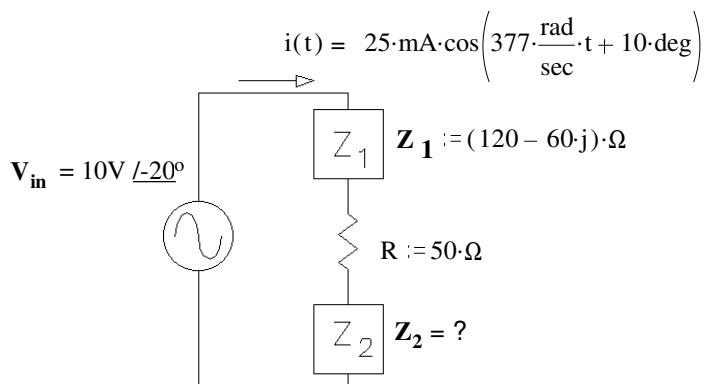

$$Z_2 := Z_T - R - Z_1 = (346.41 - 200j) \cdot \Omega - 50 \cdot \Omega - (120 - 60j) \cdot \Omega = 176.41 - 140j \cdot \Omega$$

b) Circle 1: i) The source current leads the source voltage

<--- answer, because $10^\circ > -20^\circ$.

ii) The source voltage leads the source current

ECE 2210 / 00 Phasor Examples p5

6. a) Find \mathbf{V}_{in} in polar form.

$$\mathbf{I}_Z := 100 \cdot \text{mA}$$

$$\mathbf{Z} := (80 - 60j) \cdot \Omega$$


$$\mathbf{V}_{in} := \mathbf{I}_Z \cdot \mathbf{Z}$$

$$\mathbf{V}_{in} = 8 - 6j \cdot \text{V}$$

$$\sqrt{8^2 + 6^2} = 10$$

$$\text{atan}\left(\frac{-6}{8}\right) = -36.87 \cdot \text{deg}$$
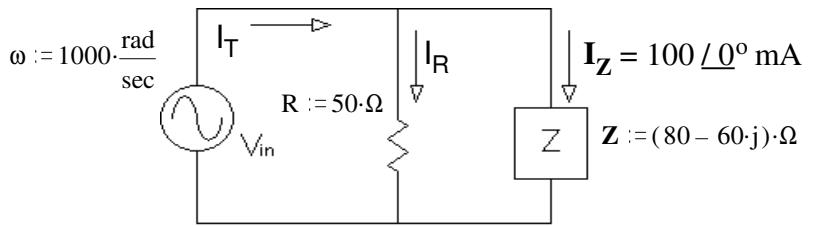
$$\mathbf{V}_{in} = 10 \text{V } \angle -36.9^\circ$$



b) Find \mathbf{I}_T in polar form.

$$\mathbf{I}_R := \frac{\mathbf{V}_{in}}{R} = \frac{10 \cdot \text{V}}{50 \cdot \Omega} \angle -36.9^\circ = \frac{10 \cdot \text{V}}{50 \cdot \Omega} \cdot \cos(-36.9^\circ \cdot \text{deg}) + j \cdot \frac{10 \cdot \text{V}}{50 \cdot \Omega} \cdot \sin(-36.9^\circ \cdot \text{deg}) = 160 - 120j \cdot \text{mA}$$

$$\mathbf{I}_T := \mathbf{I}_R + \mathbf{I}_Z = (160 - 120j) \cdot \text{mA} + 100 \cdot \text{mA} = 260 - 120j \cdot \text{mA}$$

$$\sqrt{260^2 + 120^2} = 286.356 \quad \text{atan}\left(\frac{-120}{260}\right) = -24.78 \cdot \text{deg} \quad \mathbf{I}_T = 286 \text{mA } \angle -24.8^\circ$$

c) Circle 1: i) The source current leads the source voltage ii) The source voltage leads the source current

answer i), $-24.8^\circ > -36.9^\circ$


7. d) The impedance \mathbf{Z} is made of two components in series. What are they and what are their values?

$$\mathbf{Z} = 80 - 60j \cdot \Omega$$

Must have a resistor because there is a real part.

$$R := \text{Re}(\mathbf{Z})$$

$$R = 80 \cdot \Omega$$

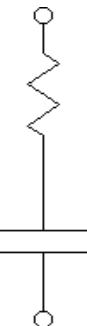

Must have a capacitor because the imaginary part is negative.

$$\text{Im}(\mathbf{Z}) = -60 \cdot \Omega = \frac{-1}{\omega \cdot C}$$

$$C := \frac{-1}{\omega \cdot \text{Im}(\mathbf{Z})}$$

$$C = 16.667 \cdot \mu\text{F}$$



e) The impedance \mathbf{Z} is made of two components in parallel. What are they and what are their values?

$$\mathbf{Z} = 80 - 60j \cdot \Omega$$

Must have a resistor because there is a real part.

Must have a capacitor because the imaginary part is negative.

$$\mathbf{Z} = \frac{1}{\frac{1}{R} + j \cdot \omega \cdot C} \quad \frac{1}{\mathbf{Z}} = \frac{1}{(80 - 60j) \cdot \Omega} \cdot \frac{(80 + 60j)}{(80 + 60j)} = \frac{80 + 60j}{80^2 + 60^2} = \frac{80 + 60j}{10,000} \cdot \frac{1}{\Omega}$$

$$\frac{1}{\mathbf{Z}} = 8 \cdot 10^{-3} + 6 \cdot 10^{-3}j \cdot \Omega^{-1} = \frac{1}{R} + j \cdot \omega \cdot C$$

$$\frac{1}{R} = .008 \cdot \frac{1}{\Omega}$$

$$R := \frac{1}{.008 \cdot \frac{1}{\Omega}}$$



$$R = 125 \cdot \Omega$$

$$\omega \cdot C = .006 \cdot \frac{1}{\Omega}$$

$$C := \frac{.006}{\omega}$$

$$C = 6 \cdot \mu\text{F}$$

$$R = 125 \cdot \Omega$$

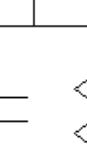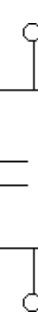

ECE 2210 / 00 Phasor Examples p6


8. You need to design a circuit in which the the "output" voltage leads the input voltage ($v_S(t)$) by 40° of phase.

a) What should go in the box: R, L, C?

$$V_o = \frac{Z_{\text{box}}}{R + Z_{\text{box}}} \cdot V_S$$

$$\text{angle of } \frac{Z_{\text{box}}}{R + Z_{\text{box}}} \text{ is } 40^\circ.$$

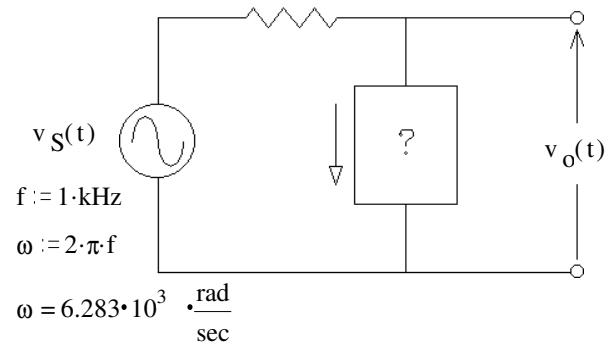This can only happen if the angle of Z_{box} is positive,
so Z_{box} is a inductor



b) Find its value. $V_o = V_o = \frac{j \cdot \omega \cdot L}{R + j \cdot \omega \cdot L} \cdot V_S$ angle $\frac{j \cdot \omega \cdot L}{R + j \cdot \omega \cdot L}$ is $90 - \text{atan}\left(\frac{\omega \cdot L}{R}\right) = 40^\circ$.

$$\text{atan}\left(\frac{\omega \cdot L}{R}\right) = 60^\circ.$$

$$\frac{\omega \cdot L}{R} = \tan(60 \cdot \text{deg}) = 1.732$$

$$L := \frac{R \cdot 1.732}{\omega} \quad L = 34.5 \cdot \text{mH}$$


9. You need to design a circuit in which the the "output" voltage lags the input voltage ($v_S(t)$) by -40° of phase.

a) What should go in the box: R, L, C?

$$V_o = \frac{Z_{\text{box}}}{R + Z_{\text{box}}} \cdot V_S$$

$$\text{angle of } \frac{Z_{\text{box}}}{R + Z_{\text{box}}} \text{ is } -40^\circ.$$

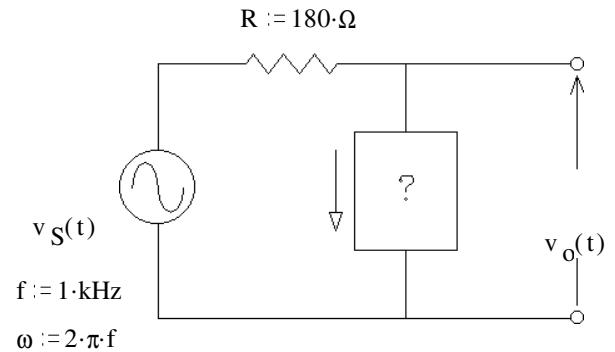This can only happen if the angle of Z_{box} is negative,
so Z_{box} is a capacitor



b) Find its value. $V_o = \frac{\frac{1}{j \cdot \omega \cdot C}}{R + \frac{1}{j \cdot \omega \cdot C}} \cdot V_S$ angle $\frac{\frac{1}{j \cdot \omega \cdot C}}{R + \frac{1}{j \cdot \omega \cdot C}}$ is $-90 - \text{atan}\left(-\frac{1}{\omega \cdot C \cdot R}\right) = -90 - \text{atan}\left(-\frac{1}{\omega \cdot C \cdot R}\right)$
 $\text{atan}\left(-\frac{1}{\omega \cdot C \cdot R}\right) = -60^\circ.$

$$-\frac{1}{\omega \cdot C \cdot R} = \tan(-60 \cdot \text{deg}) = -1.732$$

$$C := \frac{1}{\omega \cdot R \cdot 1.732} \quad C = 0.511 \cdot \mu\text{F}$$