

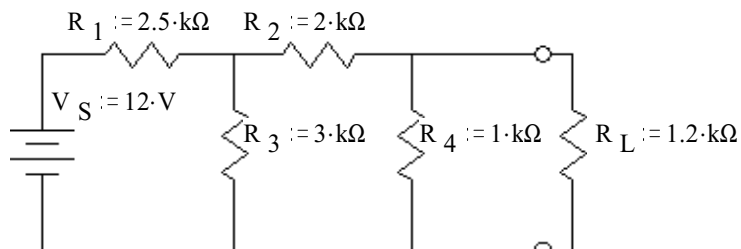


Ex 1 a) Find and draw the Thevenin equivalent circuit.

Find the open circuit voltage:

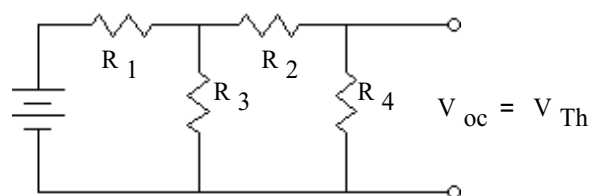


First do some simplification:

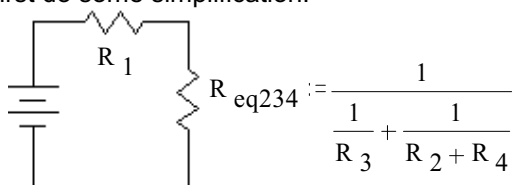

$$R_{eq234} = 1.5 \cdot \text{k}\Omega$$

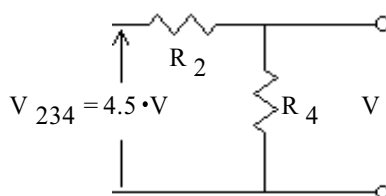
$$V_{234} := \frac{R_{eq234}}{R_1 + R_{eq234}} \cdot V_S$$



$$V_{Th} := \frac{R_4}{R_2 + R_4} \cdot V_{234}$$

$$V_{Th} = 1.5 \cdot \text{V}$$


Find the Thevenin resistance:

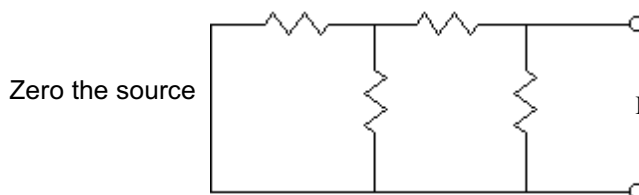


$$R_{Th} := \frac{1}{\frac{1}{R_4} + \frac{1}{R_2 + \left(\frac{1}{\frac{1}{R_1} + \frac{1}{R_3}} \right)}}$$

$$R_{Th} = 770.8 \cdot \Omega$$


Thevenin equivalent circuit:

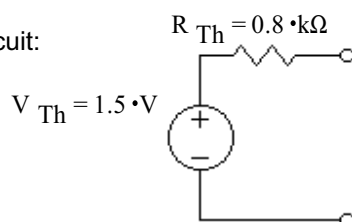

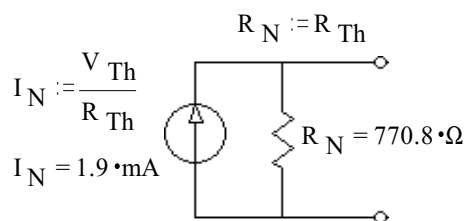b) Find and draw the Norton equivalent circuit.



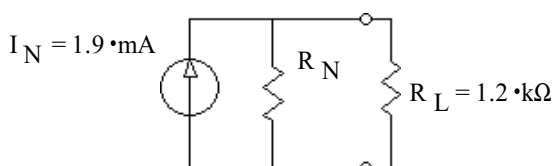c) Use your Norton equivalent circuit to find the current through the load.




$$I_L := \frac{\frac{1}{R_L}}{\left(\frac{1}{R_N} + \frac{1}{R_L} \right)} \cdot I_N$$


$$I_L = 0.761 \cdot \text{mA}$$

ECE 2210 / 00 Thevenin & Norton Examples p.2

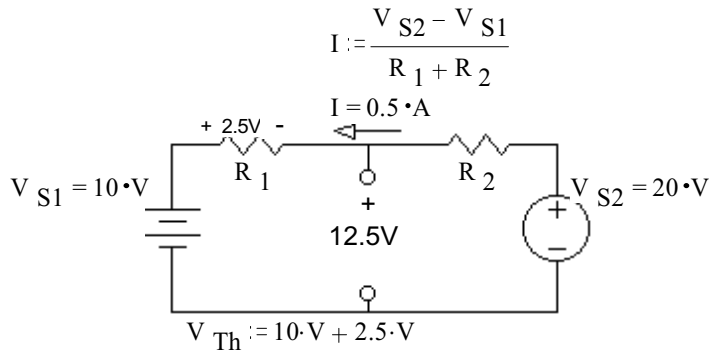
Ex 2 a) Find and draw the Thevenin & Norton equivalent circuits.




Thevenin equivalent circuit:

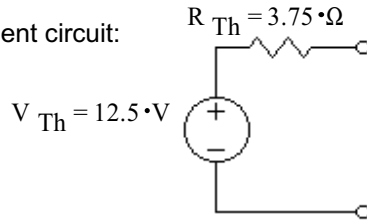

Norton equivalent circuit:

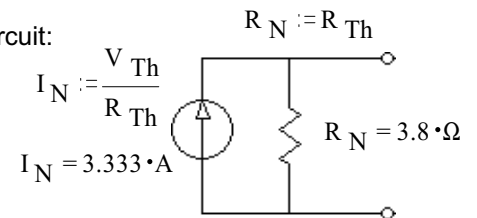

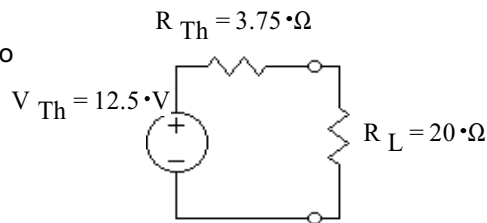
b) Use your Thevenin equivalent circuit to find the voltage across the load.




$$V_L = \frac{R_L}{R_{Th} + R_L} \cdot V_{Th}$$

$$V_L = 10.53\text{V}$$

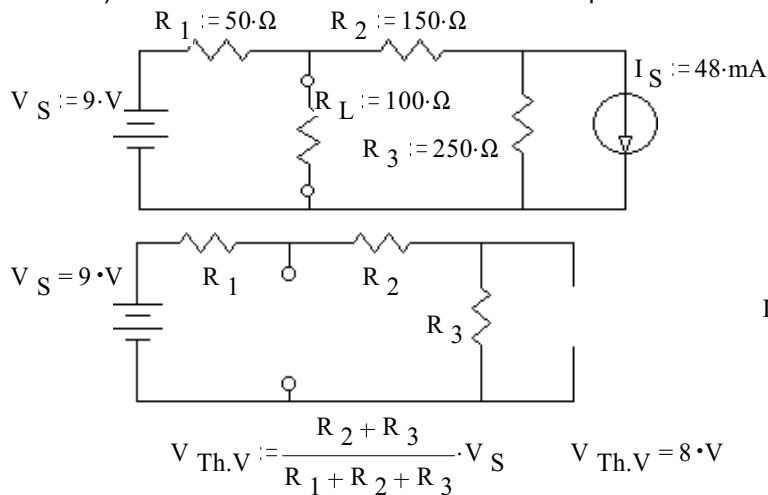Ex 3 a) Find and draw the Thevenin & Norton equivalent circuits.



Use superposition to find V_{Th} .

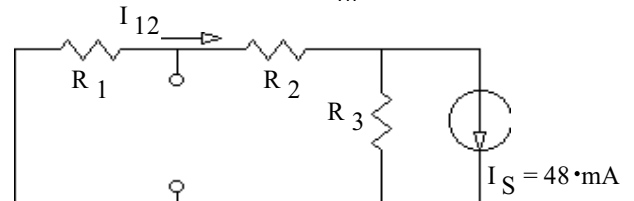

$$I_{12} = \frac{\frac{1}{R_1 + R_2}}{\frac{1}{R_1 + R_2} + \frac{1}{R_3}} \cdot I_S$$


$$I_{12} = 26.667\text{mA}$$

$$V_{Th,I} = -I_{12} \cdot R_1$$

$$V_{Th,I} = -1.333\text{V}$$


$$V_{Th} = V_{Th,V} + V_{Th,I}$$

$$V_{Th} = 6.667\text{V}$$

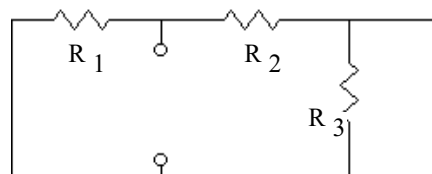

$$R_{Th} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2 + R_3}}$$

Thevenin equivalent circuit:

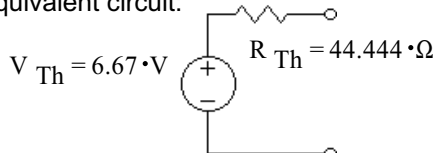

Norton equivalent circuit:

