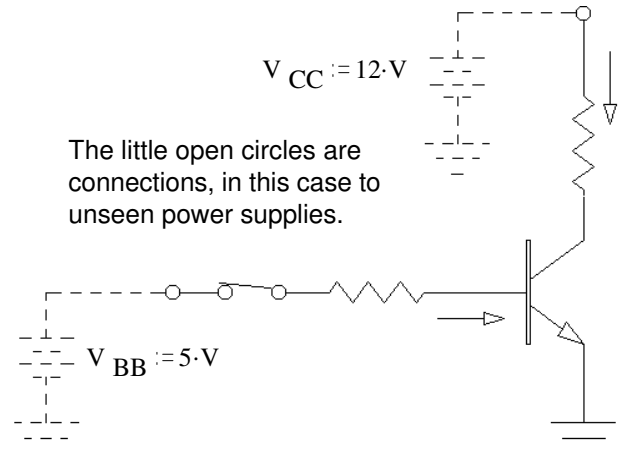
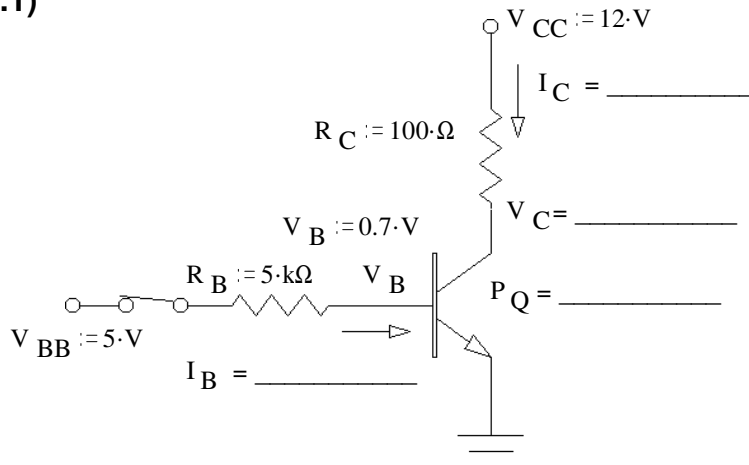


Ex.1)

$$\text{If: } \beta := 100 \quad I_B := \frac{V_{BB} - 0.7\text{V}}{R_B} \quad I_B = 0.86\text{mA}$$

$$I_C := \beta \cdot I_B \quad I_C = 86\text{mA}$$

$$V_C := V_{CC} - R_C \cdot I_C \quad V_C = 3.4\text{V}$$

$$P_Q := V_C \cdot I_C \quad P_Q = 292.4\text{mW}$$

$$\text{If: } \beta := 200 \quad I_B := \frac{V_{BB} - 0.7\text{V}}{R_B} \quad I_B = 0.86\text{mA}$$

$$I_C := \beta \cdot I_B \quad I_C = 172\text{mA}$$

$$V_C := V_{CC} - R_C \cdot I_C \quad V_C = -5.2\text{V}$$

$$\text{must be in saturation: } V_C := 0.2\text{V}$$

$$I_C := \frac{V_{CC} - V_C}{R_C} \quad I_C = 118\text{mA}$$

$$P_Q := V_C \cdot I_C \quad P_Q = 23.6\text{mW}$$

Since saturation can depend on β , You usually assume a small β when designing a circuit that should saturate (a switching circuit).

$$\text{If: } R_C := 50\Omega \quad I_C := \beta \cdot I_B \quad I_C = 172\text{mA}$$

$$\text{same } \beta := 200$$


$$V_C := V_{CC} - R_C \cdot I_C \quad V_C = 3.4\text{V}$$

$$P_Q := V_C \cdot I_C \quad P_Q = 584.8\text{mW}$$

Saturation also depends on R_C and V_{CC} .

What is the largest value that R_B could be and still keep the transistor in saturation?

$$I_{C\text{sat}} := \frac{V_{CC} - 0.2\text{V}}{R_C} \quad I_{C\text{sat}} = 236\text{mA} \quad I_B := \frac{I_{C\text{sat}}}{\beta} \quad I_B = 1.2\text{mA} \quad R_{B\text{max}} = \frac{5\text{V} - 0.7\text{V}}{I_B} = 4\text{k}\Omega$$

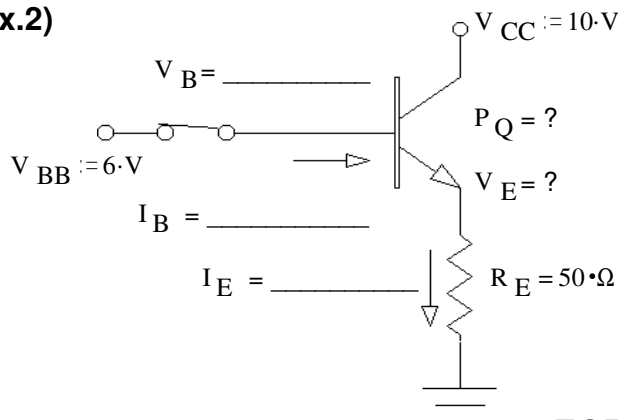Ex.2)

$$V_B := 6\text{V} \quad V_E := 5.3\text{V} \quad R_E := 50\Omega$$

$$I_E := \frac{V_E}{R_E} \quad I_E = 106\text{mA}$$

$$I_B := \frac{I_E}{\beta + 1} \quad I_B = 0.5\text{mA}$$


Almost independent of β , if β is big enough.

$$P_Q := (V_{CC} - V_E) \cdot I_E \quad P_Q = 0.498\text{W}$$

ECE 2210 Transistor switching circuit Examples, p2


Ex.3) Let's assume a small β . $\beta := 10$

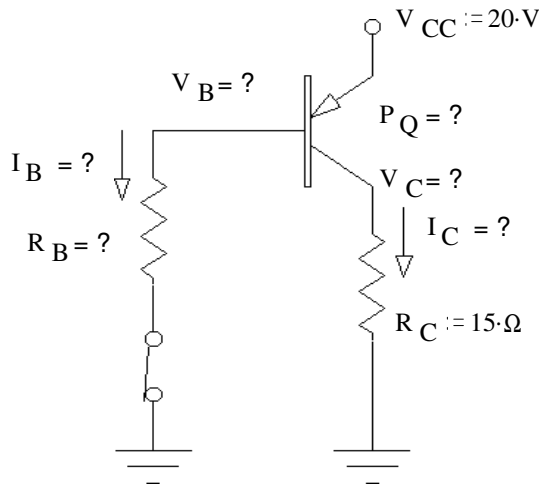Let's assume saturation and find the R_B necessary.



$$\begin{aligned}
 V_C &:= V_{CC} - 0.2 \cdot V & V_C &= 19.8 \cdot V \\
 R_C &:= 15 \cdot \Omega & I_{C\text{sat}} &:= \frac{V_C}{R_C} & I_{C\text{sat}} &= 1.32 \cdot A \\
 I_{C\text{sat}} &:= \frac{V_C}{R_C} & I_B &:= \frac{I_{C\text{sat}}}{\beta} & I_B &= 132 \cdot \text{mA} \\
 I_B &:= \frac{I_{C\text{sat}}}{\beta} & V_B &:= V_{CC} - 0.7 \cdot V & V_B &= 19.3 \cdot V \\
 V_B &:= V_{CC} - 0.7 \cdot V & R_B &:= \frac{V_B}{I_B} & R_B &= 146 \cdot \Omega \\
 R_B &:= \frac{V_B}{I_B} & P_Q &:= 0.2 \cdot V \cdot I_C & P_Q &= 34 \cdot \text{mW} \\
 P_Q &:= 0.2 \cdot V \cdot I_C & & & &
 \end{aligned}$$

Ex.4)

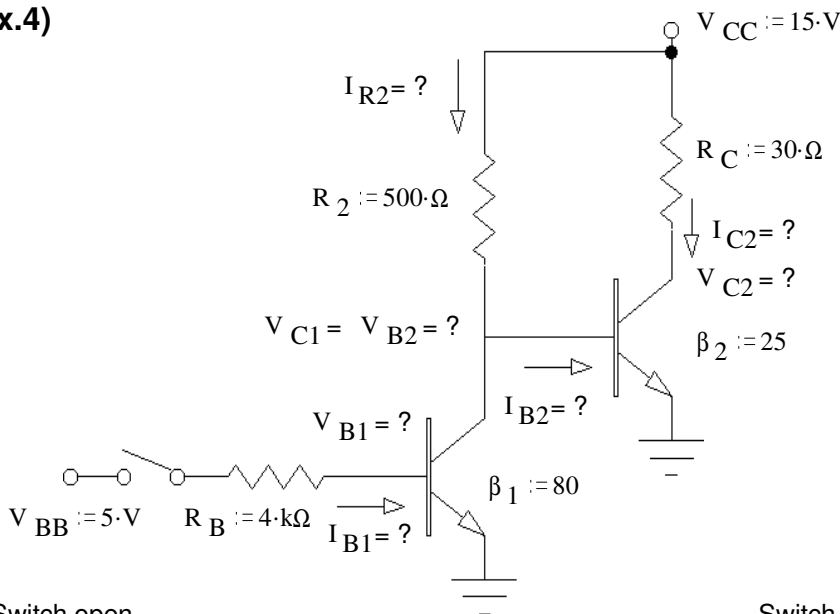

Switch open

$$\begin{aligned}
 I_{B1o} &:= 0 & V_{B1o} &:= 0 \cdot V \\
 V_{B2o} &:= 0.7 \cdot V & I_{B2o} &:= \frac{V_{CC} - 0.7 \cdot V}{R_2} & I_{B2o} &= 28.6 \cdot \text{mA} \\
 I_{B2o} &:= \frac{V_{CC} - 0.7 \cdot V}{R_2} & I_{R2o} &:= I_{B2o} & I_{R2o} &= 28.6 \cdot \text{mA} \\
 I_{R2o} &:= I_{B2o} & I_{C2o} &:= \beta_2 \cdot I_{B2o} & I_{C2o} &= 715 \cdot \text{mA} \\
 I_{C2o} &:= \beta_2 \cdot I_{B2o} & V_{C2o} &:= V_{CC} - R_C \cdot I_{C2o} & V_{C2o} &= -6.45 \cdot V \\
 V_{C2o} &:= V_{CC} - R_C \cdot I_{C2o} & Q_2 & \text{must be in saturation:} & V_{C2o} &:= 0.2 \cdot V \\
 Q_2 & \text{must be in saturation:} & I_{C2o} &:= \frac{V_{CC} - V_{C2o}}{R_C} & I_{C2o} &= 493.3 \cdot \text{mA} \\
 I_{C2o} &:= \frac{V_{CC} - V_{C2o}}{R_C} & & & &
 \end{aligned}$$

Switch closed

$$\begin{aligned}
 I_{B1c} &:= \frac{5 \cdot V - 0.7 \cdot V}{R_B} & I_{B1c} &= 1.08 \cdot \text{mA} \\
 I_{B1c} &:= \frac{5 \cdot V - 0.7 \cdot V}{R_B} & \text{assume } Q_1 \text{ is in saturation} & & V_{C1c} &:= 0.2 \cdot V \\
 \text{assume } Q_1 \text{ is in saturation} & & I_{C1c} &:= \frac{V_{CC} - V_{C1c}}{R_2} & I_{C1c} &= 29.6 \cdot \text{mA} \\
 I_{C1c} &:= \frac{V_{CC} - V_{C1c}}{R_2} & \beta_1 \cdot I_{B1c} &= 86 \cdot \text{mA} & I_{C1} & \text{is controlled by } R_2 \\
 \beta_1 \cdot I_{B1c} &= 86 \cdot \text{mA} & V_{B2c} &:= V_{C1c} & V_{B2c} &= 0.2 \cdot V \\
 V_{B2c} &:= V_{C1c} & I_{B2c} &:= 0 & I_{C2c} &:= 0 = I_{RCc} \\
 I_{B2c} &:= 0 & & & &
 \end{aligned}$$

When the switch is open, current flows in through the load resistor, R_C . When it is closed, no current flows through the load. This is an example of logical "inversion".