


## 1.5 First-order transient examples

1. a) What is the value of the voltage across C at  $t := 25 \cdot \mu\text{s}$  if the switch is closed at time  $t = 0$ ?

$$\tau := R \cdot C \quad \tau = 0.082 \cdot \text{ms}$$

$$v_C(0) = 0 \cdot \text{V} \quad v_C(\infty) = 9 \cdot \text{V}$$
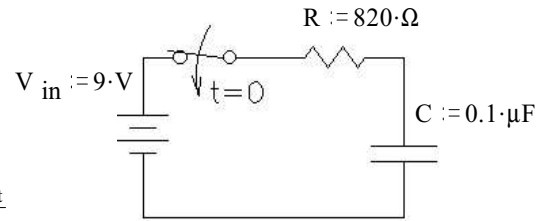
$$v_C(t) = v_C(\infty) + (v_C(0) - v_C(\infty)) \cdot e^{-\frac{t}{\tau}} = 9 \cdot \text{V} + (0 \cdot \text{V} - 9 \cdot \text{V}) \cdot e^{-\frac{t}{\tau}} = 2.365 \cdot \text{V}$$



- b) When will the current through the resistor be  $i_R := 5 \cdot \text{mA}$ ?

$$i_R(0) = \frac{V_{\text{in}}}{R} = 10.976 \cdot \text{mA} \quad i_R(\infty) = 0 \cdot \text{mA}$$

$$i_R(t) = i_R(\infty) + (i_R(0) - i_R(\infty)) \cdot e^{-\frac{t}{\tau}} = 0 \cdot \text{mA} + (10.976 \cdot \text{mA} - 0 \cdot \text{mA}) \cdot e^{-\frac{t}{\tau}} = 10.976 \cdot \text{mA} \cdot e^{-\frac{t}{\tau}} = 5 \cdot \text{mA}$$

$$\text{Rearrange the equation:} \quad t = -\tau \cdot \ln\left(\frac{5 \cdot \text{mA}}{10.976 \cdot \text{mA}}\right) = 64.5 \cdot \mu\text{s}$$

- c) When will the current through the resistor be  $i_R := 20 \cdot \text{mA}$ ?

Since the initial condition is 11mA and the final condition is 0mA,  $i_R$  will never be 20mA.

2. A  $1000 \mu\text{F}$  capacitor has an initial charge of 12 volts. A  $20 \Omega$  resistor is connected across the capacitor at time  $t = 0$ . Find the energy dissipated by the resistor in the first 5 time constants.

After 5 time constants nearly all of the energy initially stored in the capacitor will be dissipated by the resistor.

$$C := 1000 \cdot \mu\text{F} \quad V_C := 12 \cdot \text{V} \quad W_C := \frac{1}{2} \cdot C \cdot V_C^2 \quad W_C = 0.072 \cdot \text{joule}$$

You can get to this answer just by knowing a little about the exponential curve, but what if you want a more accurate answer? Then you'll have to find the remaining voltage across the capacitor at  $t = 5\tau$  and subtract off the energy left in the capacitor at that time.

$$v_C(0) = 12 \cdot \text{V} \quad v_C(\infty) = 0 \cdot \text{V} \quad v_C(t) = v_C(\infty) + (v_C(0) - v_C(\infty)) \cdot e^{-\frac{t}{\tau}} = 0 \cdot \text{V} + (12 \cdot \text{V} - 0 \cdot \text{V}) \cdot e^{-\frac{t}{\tau}} = 12 \cdot \text{V} \cdot e^{-\frac{t}{\tau}}$$

$$\text{at } t = 5\tau: \quad v_C(5\tau) = 12 \cdot \text{V} \cdot e^{-5} = 81 \cdot \text{mV} \quad \frac{1}{2} \cdot C \cdot (81 \cdot \text{mV})^2 = 3.281 \cdot 10^{-6} \cdot \text{joule}$$

$$\text{Not surprisingly, this makes no significant difference:} \quad W_R = W_C - \frac{1}{2} \cdot C \cdot (81 \cdot \text{mV})^2 = 0.072 \cdot \text{joule}$$


3. The capacitor is initially uncharged. The switch is in the upper position from 0 to 2ms and is switched down at time  $t = 2\text{ms}$ .

What is the capacitor voltage  $V_C(t)$ ?

$$\text{First interval } v_C(0) = 0 \cdot \text{V} \quad v_C(\infty) = 24 \cdot \text{V}$$

$$\tau := (R_1 + R_2 + R_3) \cdot C \quad \tau = 1.08 \cdot \text{ms}$$
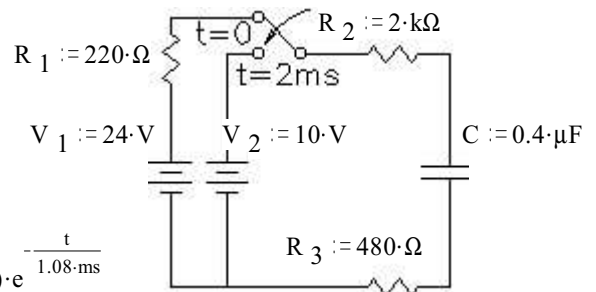
$$v_C(t) = v_C(\infty) + (v_C(0) - v_C(\infty)) \cdot e^{-\frac{t}{\tau}} = 24 \cdot \text{V} + (0 \cdot \text{V} - 24 \cdot \text{V}) \cdot e^{-\frac{t}{1.08 \cdot \text{ms}}}$$



$$\text{at } 2\text{ms} \quad 24 \cdot \text{V} - 24 \cdot \text{V} \cdot e^{-\frac{2 \cdot \text{ms}}{1.08 \cdot \text{ms}}} = 20.233 \cdot \text{V}$$


Second interval, define a new time,  $t_t = t - 2\text{ms}$

$$v_C(0) = 20.233 \cdot V \quad v_C(\infty) = 10 \cdot V$$

$$\tau := (R_2 + R_3) \cdot C \quad \tau = 0.992 \cdot \text{ms}$$

$$v_C(t_t) = v_C(\infty) + (v_C(0) - v_C(\infty)) \cdot e^{-\frac{t_t}{\tau}} = 10 \cdot V + (20.233 \cdot V - 10 \cdot V) \cdot e^{-\frac{t_t}{0.992 \cdot \text{ms}}} = 10 \cdot V + 10.233 \cdot V \cdot e^{-\frac{t - 2 \cdot \text{ms}}{0.992 \cdot \text{ms}}}$$

$$t := 0, .02 \dots 6 \text{ ms}$$

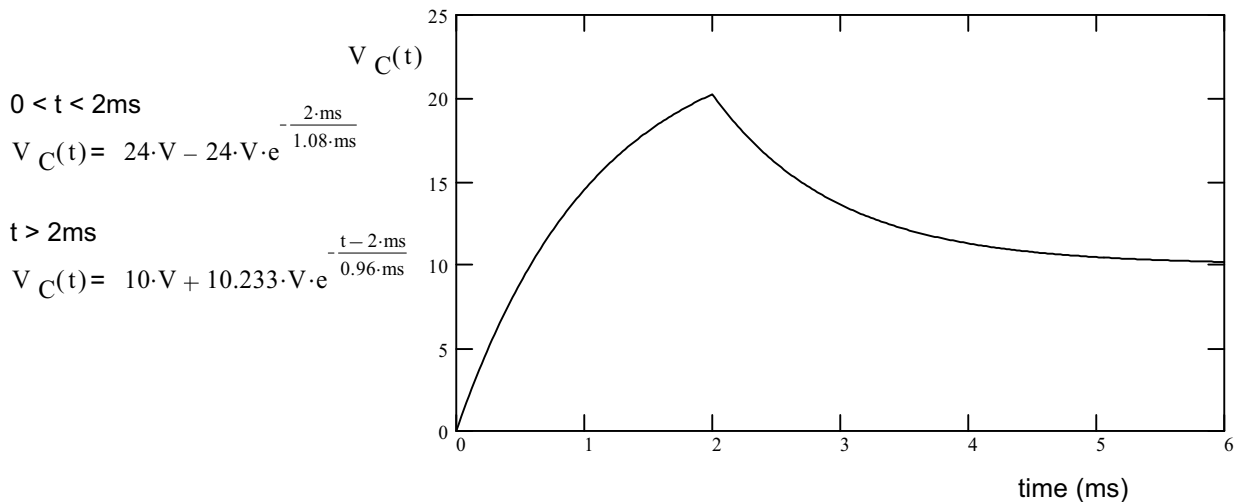

4. For the circuit at right, when is the voltage across  $R_2 = 10\text{V}$ ?

Taking  $L$  as the "load" and finding the Thevenin equivalent of the rest:

$$R_{Th} := \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} + R_3 \quad R_{Th} = 5.833 \cdot \Omega$$

$$\tau := \frac{L}{R_{Th}} \quad \tau = 85.714 \cdot \mu\text{s}$$

$$v_{R2}(0) = \frac{R_2}{R_1 + R_2} \cdot V_{in} = 13.75 \cdot V$$

$$R_{23} := \frac{1}{\frac{1}{R_2} + \frac{1}{R_3}}$$

$$v_{R2}(\infty) = \frac{R_{23}}{R_1 + R_{23}} \cdot V_{in} = 9.429 \cdot V$$

$$v_{R2}(t) = v_{R2}(\infty) + (v_{R2}(0) - v_{R2}(\infty)) \cdot e^{-\frac{t}{\tau}}$$

$$= 9.429 \cdot V + (13.75 \cdot V - 9.429 \cdot V) \cdot e^{-\frac{t}{85.714 \cdot \mu\text{s}}} = 10\text{V}$$

$$t = -\tau \cdot \ln\left(\frac{10 \cdot V - 9.429 \cdot V}{13.75 \cdot V - 9.429 \cdot V}\right) = 173 \cdot \mu\text{s}$$

