


# ECE 2210 First-Order Transient Examples

A. Stolp  
rev 12/19/15  
2/223/22

**Ex1** a) Find the expression for  $v_C(t)$  if the switch is closed at time  $t = 0$  and  $v_C(0) = 0$ .


$$v_C(t) = v_C(\infty) + (v_C(0) - v_C(\infty)) \cdot e^{-\frac{t}{\tau}}$$

redraw to find  $v_C(\infty)$

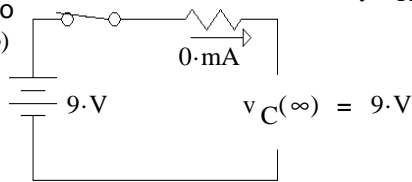


$$\tau := R \cdot C \quad \tau = 60 \cdot \mu s$$
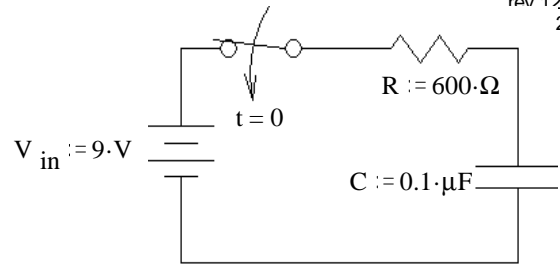
$$v_C(t) = 9 \cdot V + (0 \cdot V - 9 \cdot V) \cdot e^{-\frac{t}{60 \cdot \mu s}}$$



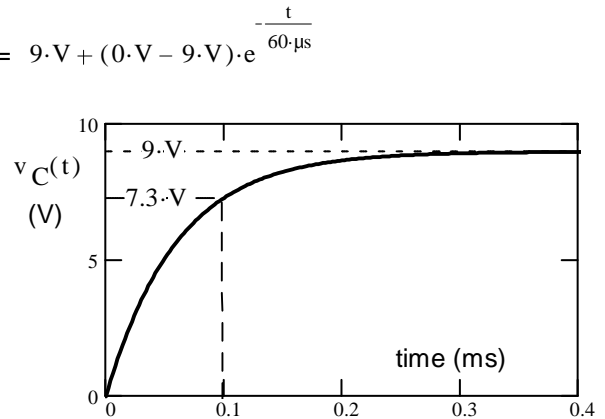b) What is the voltage across the capacitor,  $C$ , at  $t = 0.1 \text{ms}$  ?

$$v_C(25 \cdot \mu s) = 9 \cdot V - 9 \cdot V \cdot e^{-\frac{100 \cdot \mu s}{60 \cdot \mu s}} = 7.3 \cdot V$$



c) When will the current through the resistor be  $i_R := 5 \cdot \text{mA}$  ?



$$i_R(\infty) = 0 \cdot \text{mA} \quad i_R(0) = \frac{9 \cdot V}{R} = 15 \cdot \text{mA} \quad \text{found from drawing}$$

$$i_R(t) = i_R(\infty) + (i_R(0) - i_R(\infty)) \cdot e^{-\frac{t}{\tau}}$$

$$= 0 \cdot \text{mA} + (15 \cdot \text{mA} - 0 \cdot \text{mA}) \cdot e^{-\frac{t}{\tau}}$$

$$= 15 \cdot \text{mA} \cdot e^{-\frac{t}{60 \cdot \mu s}} = 5 \cdot \text{mA} \quad \text{at some time, } t$$
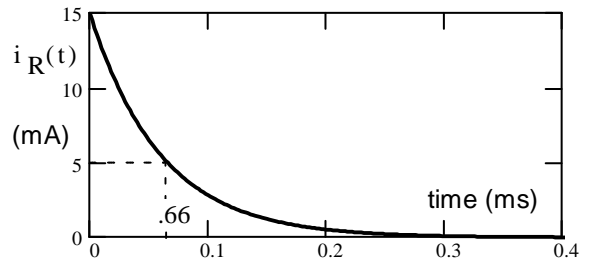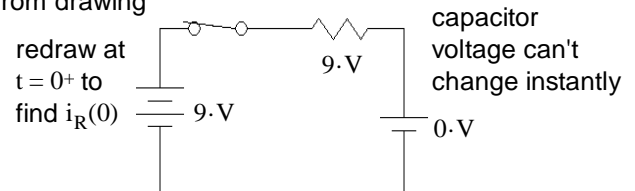
$$\text{Solve for } t = -\tau \cdot \ln\left(\frac{5 \cdot \text{mA}}{15 \cdot \text{mA}}\right) = 65.92 \cdot \mu s$$



d) When will the current through the resistor be  $i_R := 20 \cdot \text{mA}$  ?

Since the initial condition is about 15mA and the final condition is 0mA,  $i_R$  will never be 20mA.

**Ex2** A  $1000 \mu\text{F}$  capacitor has an initial charge of 12 volts. A  $20 \cdot \Omega$  resistor is connected across the capacitor at time  $t = 0$ . Find the energy dissipated by the resistor in the first 5 time constants.

After 5 time constants nearly all of the energy initially stored in the capacitor will be dissipated by the resistor.

$$C := 1000 \cdot \mu\text{F} \quad V_C := 12 \cdot V \quad W_C := \frac{1}{2} \cdot C \cdot V_C^2 \quad W_C = 0.072 \cdot \text{joule}$$

You can get to this answer just by knowing a little about the exponential curve, but what if you want a more accurate answer? Then you'll have to find the remaining voltage across the capacitor at  $t = 5t$  and subtract the energy left in the capacitor at that time.

$$v_C(0) = 12 \cdot V \quad v_C(\infty) = 0 \cdot V \quad v_C(t) = v_C(\infty) + (v_C(0) - v_C(\infty)) \cdot e^{-\frac{t}{\tau}} = 0 \cdot V + (12 \cdot V - 0 \cdot V) \cdot e^{-\frac{t}{\tau}} = 12 \cdot V \cdot e^{-\frac{t}{\tau}}$$

$$\text{at } t = 5\tau: \quad v_C(5 \cdot \tau) = 12 \cdot V \cdot e^{-5} = 81 \cdot \text{mV} \quad \frac{1}{2} \cdot C \cdot (81 \cdot \text{mV})^2 = 3.281 \cdot 10^{-6} \cdot \text{joule}$$




Not surprisingly, this makes no significant difference:

$$W_R = W_C - \frac{1}{2} \cdot C \cdot (81 \cdot \text{mV})^2 = 0.072 \cdot \text{joule}$$

**Ex3** The capacitor is initially uncharged. The switch is in the upper position from 0 to 2ms and is switched down at time  $t = 2\text{ms}$ .

a) What is the capacitor voltage,  $v_C(t)$



First interval  $v_C(0) = 0\text{V}$

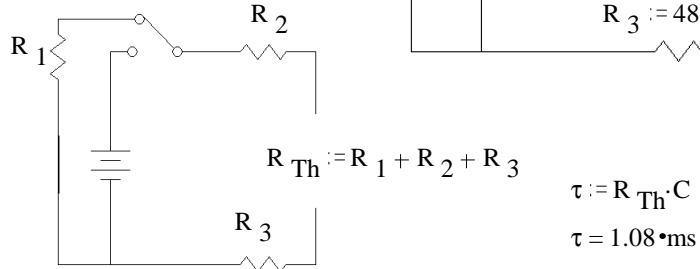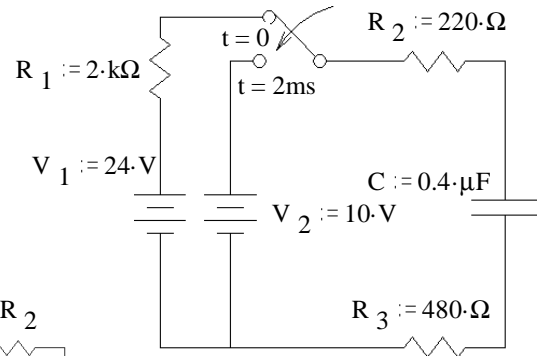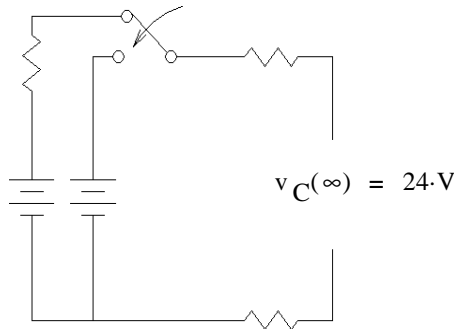

$$v_C(t) = v_C(\infty) + (v_C(0) - v_C(\infty)) \cdot e^{-\frac{t}{\tau}} = 24\text{V} + (0\text{V} - 24\text{V}) \cdot e^{-\frac{t}{1.08\text{ms}}}$$

at 2ms:  $24\text{V} - 24\text{V} \cdot e^{-\frac{2\text{ms}}{1.08\text{ms}}} = 20.23 \cdot \text{V}$

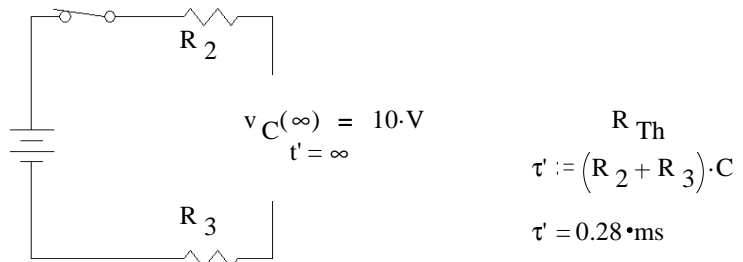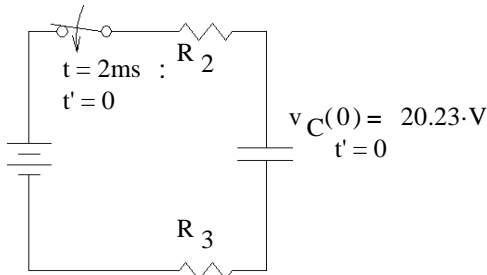Second interval, define a new time,  $t' = t - 2\text{ms}$




$$v_C(t') = v_C(\infty) + (v_C(0) - v_C(\infty)) \cdot e^{-\frac{t'}{\tau'}} = 10\text{V} + (20.23\text{V} - 10\text{V}) \cdot e^{-\frac{t'}{0.28\text{ms}}} = 10\text{V} + 10.23\text{V} \cdot e^{-\frac{t-2\text{ms}}{0.28\text{ms}}}$$

$0 < t < 2\text{ms}$

$$V_C(t) = 24\text{V} - 24\text{V} \cdot e^{-\frac{t}{1.08\text{ms}}}$$

$t > 2\text{ms}$
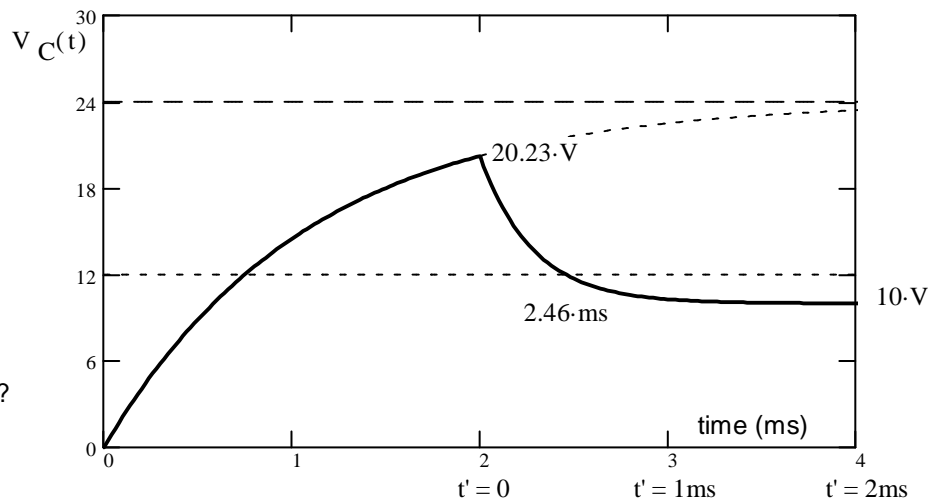
$$V_C(t) = 10\text{V} + 10.23\text{V} \cdot e^{-\frac{t-2\text{ms}}{0.28\text{ms}}}$$



b) When is voltage across the capacitor 12V AND getting smaller?

$$12\text{V} = 10\text{V} + 10.23\text{V} \cdot e^{-\frac{t_{12}}{0.28\text{ms}}}$$



$$\frac{12\text{V} - 10\text{V}}{10.23\text{V}} = e^{-\frac{t_{12}}{0.28\text{ms}}} \quad \ln\left(\frac{12\text{V} - 10\text{V}}{10.23\text{V}}\right) = -\left(\frac{t_{12}}{0.28\text{ms}}\right)$$

$$t_{12} = -0.28\text{ms} \cdot \ln\left(\frac{12\text{V} - 10\text{V}}{10.23\text{V}}\right) = 0.46 \cdot \text{ms}$$


$$2\text{ms} + 0.46\text{ms} = 2.46\text{ms}$$

Ex4 a) Find the complete expression for  $i_L(t)$ .

Before the switch closes,  $t = 0^-$

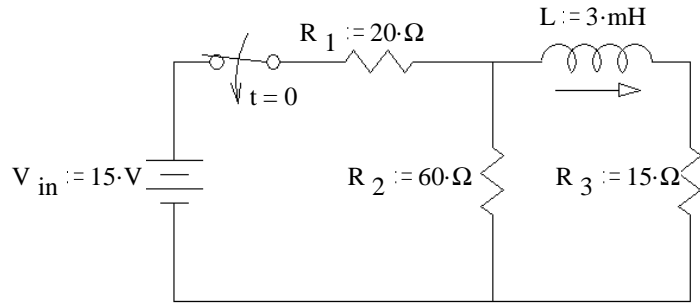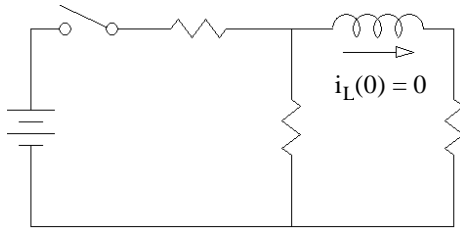

Final time,  $t = \infty$

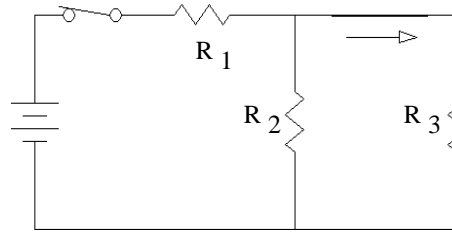

$$R_{23} := \frac{1}{\frac{1}{R_2} + \frac{1}{R_3}}$$


$$R_{23} = 12 \cdot \Omega$$

$$v_{R3}(\infty) = \frac{R_{23}}{R_1 + R_{23}} \cdot V_{in} = 5.625 \cdot V$$

$$i_L(\infty) = \frac{v_{R3}(\infty)}{R_3} = \frac{5.625 \cdot V}{15 \cdot \Omega} = 375 \cdot mA$$

$$R_{Th} := \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} + R_3$$

$$R_{Th} = 30 \cdot \Omega$$

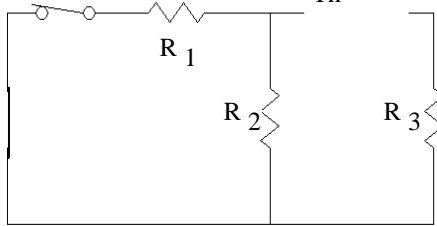


$$\tau := \frac{L}{R_{Th}}$$

$$\tau = 100 \cdot \mu s$$

$$i_L(t) = i_L(\infty) + (i_L(0) - i_L(\infty)) \cdot e^{-\frac{t}{\tau}} = 375 \cdot mA + (0 \cdot mA - 375 \cdot mA) \cdot e^{-\frac{t}{100 \cdot \mu s}} = 375 \cdot mA - 375 \cdot mA \cdot e^{-\frac{t}{100 \cdot \mu s}}$$

b) When is the voltage across  $R_2 = 10V$ ?

Before the switch closes,  $t = 0^-$

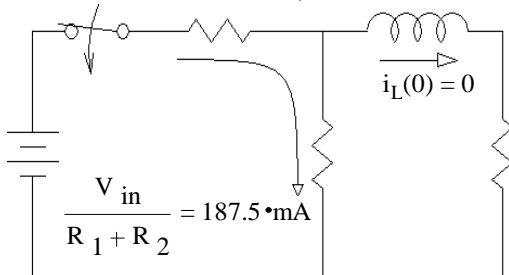

$$v_{R2}(0) = \frac{R_2}{R_1 + R_2} \cdot V_{in} = 11.25 \cdot V$$

From drawing above at  $t = \infty$

$$v_{R2}(\infty) = v_{R3}(\infty) = \frac{R_{23}}{R_1 + R_{23}} \cdot V_{in} = 5.625 \cdot V$$

$$v_{R2}(t) = v_{R2}(\infty) + (v_{R2}(0) - v_{R2}(\infty)) \cdot e^{-\frac{t}{\tau}}$$

$$= 5.625 \cdot V + (11.25 \cdot V - 5.625 \cdot V) \cdot e^{-\frac{t}{100 \cdot \mu s}}$$

$$= 10 \cdot V \text{ at some time, solving for that time...}$$

$$t = -\tau \cdot \ln\left(\frac{10 \cdot V - 5.625 \cdot V}{11.25 \cdot V - 5.625 \cdot V}\right) = 25 \cdot \mu s$$

Alternatively, when  $v_{R2}(t) = 10V$ , then  $v_{R1}(t) = 5V$  and  $i_L(t) = \frac{5 \cdot V}{R_1} - \frac{10 \cdot V}{R_2} = 83.333 \cdot mA$


$$t = -\tau \cdot \ln\left(\frac{83.333 \cdot mA - 375 \cdot mA}{-375 \cdot mA}\right) = 25 \cdot \mu s$$

c) What is the  $v_L(t)$  expression?


$$v_L(t) = v_L(\infty) + (v_L(0) - v_L(\infty)) \cdot e^{-\frac{t}{\tau}} = 0 \cdot V + (11.25 \cdot V - 0 \cdot V) \cdot e^{-\frac{t}{100 \cdot \mu s}}$$

**Ex5** The switch has been closed for a long time and is opened (as shown) at time  $t = 0$ .

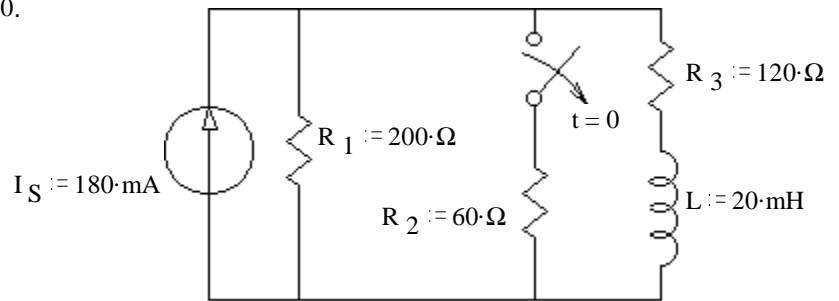a) Find the complete expression for  $i_L(t)$ .




Before the switch opens,  $t = 0^-$

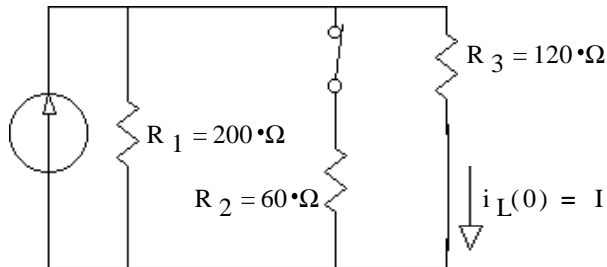


$$i_L(0) = I_S \cdot \frac{\frac{1}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = 50 \text{ mA}$$

Final time,  $t = \infty$

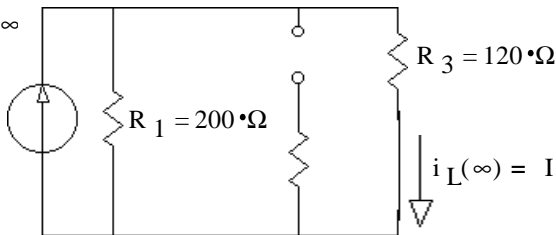
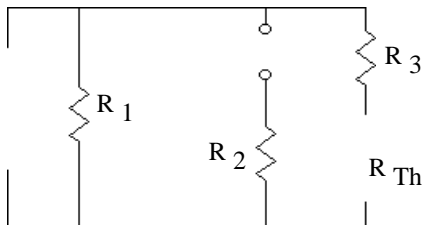
$$i_L(\infty) = I_S \cdot \frac{\frac{1}{R_3}}{\frac{1}{R_1} + \frac{1}{R_3}} = 112.5 \text{ mA}$$




$$R_{Th} := R_1 + R_3 \quad R_{Th} = 320 \cdot \Omega$$

$$\tau := \frac{L}{R_{Th}} \quad \tau = 62.5 \cdot \mu\text{s}$$

$$i_L(t) = i_L(\infty) + (i_L(0) - i_L(\infty)) \cdot e^{-\frac{t}{\tau}} = 112.5 \text{ mA} + (50 \text{ mA} - 112.5 \text{ mA}) \cdot e^{-\frac{t}{62.5 \cdot \mu\text{s}}} = 112.5 \text{ mA} - 62.5 \text{ mA} \cdot e^{-\frac{t}{62.5 \cdot \mu\text{s}}}$$

b) Find  $i_L$  at time  $t = 1.4\tau$ .  $i_L(1.4\tau) = 112.5 \text{ mA} - 62.5 \text{ mA} \cdot e^{-\frac{1.4\tau}{\tau}} = 112.5 \text{ mA} - 62.5 \text{ mA} \cdot e^{-1.4} = 97.088 \text{ mA}$

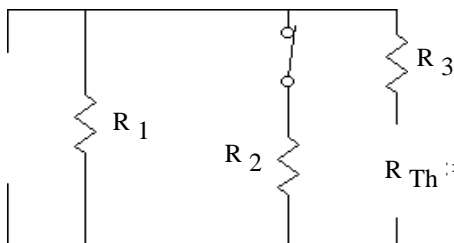c) At time  $t = 1.4\tau$  the switch is closed again. Find the complete expression for  $i_L(t')$ , where  $t'$  starts at  $t = 1.4\tau$ . Be sure to clearly show the time constant.



$$R_{Th} := \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} + R_3$$

$$R_{Th} = 166.2 \cdot \Omega$$

$$\tau := \frac{L}{R_{Th}} \quad \tau = 120.4 \cdot \mu\text{s}$$

$$i_L(0) = 97.1 \text{ mA} \quad \text{from part b)}$$

$$i_L(\infty) = 50 \text{ mA} \quad \text{initial value from part a)}$$

$$i_L(t) = i_L(\infty) + (i_L(0) - i_L(\infty)) \cdot e^{-\frac{t}{\tau}} = 50 \text{ mA} + (97.1 \text{ mA} - 50 \text{ mA}) \cdot e^{-\frac{t}{120.4 \cdot \mu\text{s}}} = 50 \text{ mA} + 47.1 \text{ mA} \cdot e^{-\frac{t}{120.4 \cdot \mu\text{s}}}$$