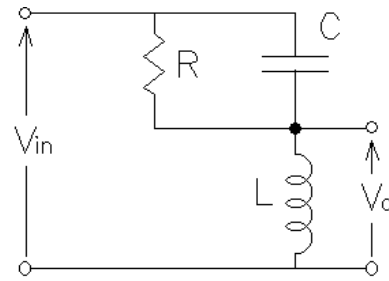


Ex. 1 a) Find the transfer function of the circuit shown. Write your equation in the form of one simple polynomial divided by another

$$H(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{L \cdot s}{\frac{1}{\frac{1}{R} + C \cdot s}} \cdot \left(\frac{1}{R} + C \cdot s \right) = \frac{L \cdot s}{1 + L \cdot s \cdot \left(\frac{1}{R} + C \cdot s \right)}$$

$$= \frac{\frac{L \cdot s}{R} + L \cdot C \cdot s^2}{1 + \frac{L \cdot s}{R} + L \cdot C \cdot s^2} = \frac{\frac{L \cdot s}{R} + L \cdot C \cdot s^2}{L \cdot C \cdot s^2 + \frac{L \cdot s}{R} + 1} \cdot \frac{1}{\frac{1}{L \cdot C}} = \frac{s^2 + \frac{1}{C \cdot R} \cdot s}{s^2 + \left(\frac{1}{C \cdot R} \right) \cdot s + \frac{1}{L \cdot C}}$$



b) Find the characteristic equation


$$0 = s^2 + \frac{1}{C \cdot R} \cdot s + \frac{1}{L \cdot C}$$

Ex. 2

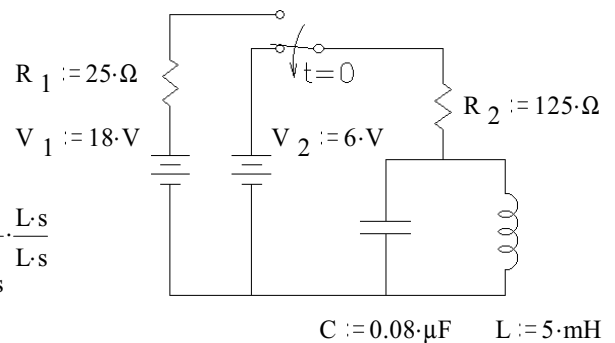a) Find the characteristic equation of the circuit shown (after the switch moves to the lower position at $t = 0$).

$$\frac{V_C(s)}{V_{in}(s)} = H(s) = \frac{\frac{1}{L \cdot s}}{\frac{1}{L \cdot s} + R_2} \cdot \left(\frac{1}{L \cdot s} + C \cdot s \right) = \frac{1}{1 + \frac{R_2}{L \cdot s} + R_2 \cdot C \cdot s} \cdot \frac{L \cdot s}{L \cdot s}$$

$$= \frac{L \cdot s}{L \cdot s + R_2 + R_2 \cdot C \cdot L \cdot s^2} \cdot \frac{1}{R_2 \cdot C \cdot L} = \frac{\frac{1}{R_2 \cdot C} \cdot s}{\frac{1}{R_2 \cdot C} \cdot s + \frac{1}{L \cdot C} + s^2}$$



Characteristic equation:

$$0 = s^2 + \frac{1}{R_2 \cdot C} \cdot s + \frac{1}{L \cdot C}$$

b) Find the solutions of the characteristic equation.

$$s_1 := \frac{-\frac{1}{R_2 \cdot C} + \sqrt{\left(\frac{1}{R_2 \cdot C} \right)^2 - \frac{4}{L \cdot C}}}{2}$$

$$s_1 = -5 \cdot 10^4 \cdot \frac{1}{\text{sec}}$$

$$s_2 := \frac{-\frac{1}{R_2 \cdot C} - \sqrt{\left(\frac{1}{R_2 \cdot C} \right)^2 - \frac{4}{L \cdot C}}}{2}$$

$$s_2 = -5 \cdot 10^4 \cdot \frac{1}{\text{sec}}$$

c) Find initial and final conditions for $v_C(t)$

before switch is moved: $v_L(\infty) = 0 = v_L(0^-) = v_C(0^-) = 0 = v_C(0^+)$

$s_1 = s_2$ so... critically damped

$$\frac{d}{dt} v_C(0) = \frac{i_C(0)}{C} \quad \text{before switch is moved: } i_{L0} := \frac{V_1 - 0 \cdot V}{R_1 + R_2} \quad \text{so... } i_{L0} = 120 \cdot \text{mA}$$

$$\text{after switch is moved: } i_{R0} := \frac{6 \cdot V - 0 \cdot V}{R_2} \quad i_{R0} = 48 \cdot \text{mA}$$

not all of the inductor's current comes through the resistor anymore, so the difference must come from the capacitor

$$i_{C0} := i_{R0} - i_{L0} \quad i_{C0} = -72 \cdot \text{mA} \quad \frac{d}{dt} v_C(0) = \frac{i_{C0}}{C} = -9 \cdot 10^5 \cdot \frac{V}{\text{sec}}$$

Second-Order Transient Examples, p.2

d) Find the full expression of $v_C(t)$.

Critically damped $b^2 - 4 \cdot k = 0$ $s_1 = s_2 = -\frac{b}{2} = s$ s_1 and s_2 are real, equal and negative

$$v_X(t) = v_X(\infty) + B \cdot e^{s_1 t} + D \cdot t \cdot e^{s_2 t}$$

$$v_X(0) = v_X(\infty) + B$$

$$\frac{d}{dt}v_X(0) = B \cdot s + D \quad \text{Solve simultaneously}$$


$$v_C(0) = v_C(\infty) + B$$

$$\frac{d}{dt}v_C(0) = B \cdot s + D$$

$$0 = 0 + B \quad B = 0$$

$$-9 \cdot 10^5 \cdot \frac{V}{\text{sec}} = 0 \cdot \left(-5 \cdot 10^4 \cdot \frac{1}{\text{sec}} \right) + D \quad D := -9 \cdot 10^5 \cdot \frac{V}{\text{sec}}$$


$$v_C(t) := -9 \cdot 10^5 \cdot \frac{V}{\text{sec}} \cdot t \cdot e^{s_1 t}$$

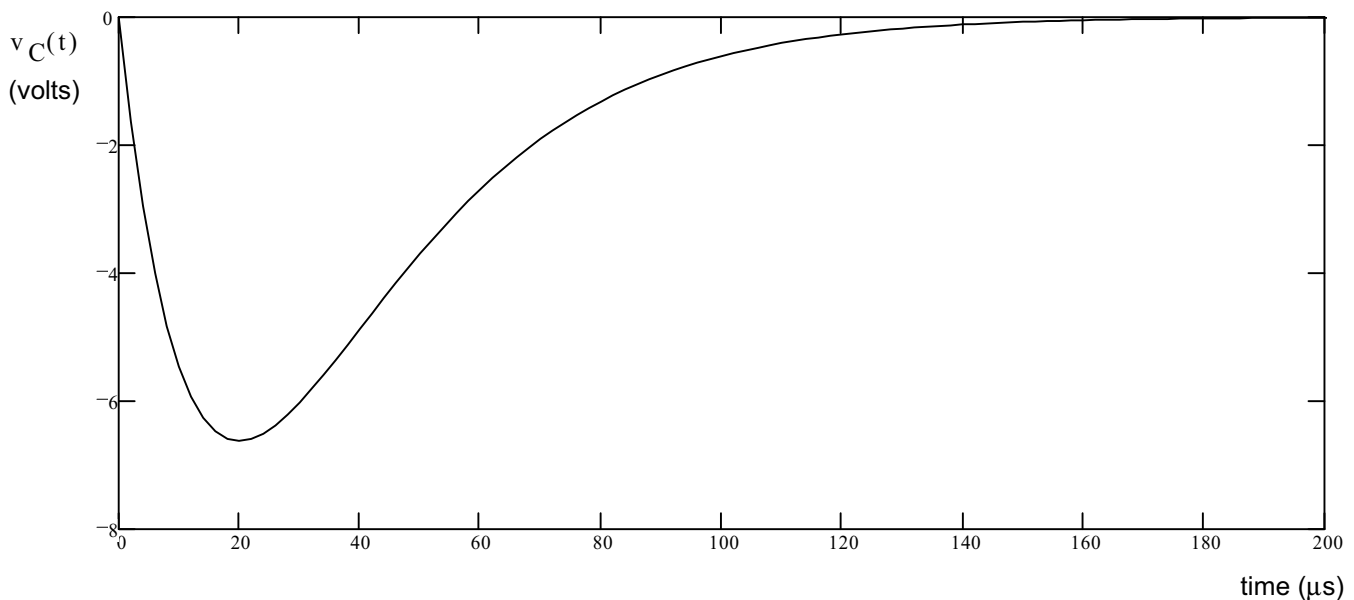

Ex. 3

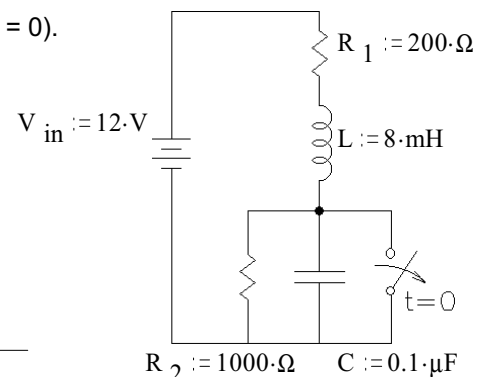a) Find the characteristic equation of the circuit shown. (after the switch opens at $t = 0$). Write your equation in the form of a simple polynomials.

$$\begin{aligned} H(s) &= \frac{I_T(s)}{V_{in}(s)} = \frac{1}{Z(s)} = \frac{1}{\frac{1}{\frac{1}{R_2} + C \cdot s} + L \cdot s + R_1} \cdot \left(\frac{1}{R_2} + C \cdot s \right) \\ &= \frac{\frac{1}{R_2} + C \cdot s}{1 + L \cdot s \cdot \left(\frac{1}{R_2} + C \cdot s \right) + R_1 \cdot \left(\frac{1}{R_2} + C \cdot s \right)} = \frac{\frac{1}{R_2} + C \cdot s}{1 + \frac{L \cdot s}{R_2} + L \cdot C \cdot s^2 + \frac{R_1}{R_2} + R_1 \cdot C \cdot s} \\ &= \frac{\frac{1}{R_2} + C \cdot s}{L \cdot C \cdot s^2 + \frac{L \cdot s}{R_2} + R_1 \cdot C \cdot s + 1 + \frac{R_1}{R_2} \cdot \frac{1}{L \cdot C}} = \frac{\frac{1}{R_2} + C \cdot s}{s^2 + \left(\frac{L}{L \cdot C \cdot R_2} + \frac{R_1 \cdot C}{L \cdot C} \right) \cdot s + \left(1 + \frac{R_1}{R_2} \right) \cdot \frac{1}{L \cdot C}} \\ &= \frac{1}{L} \cdot \frac{s + \frac{1}{C \cdot R_2}}{s^2 + \left(\frac{1}{C \cdot R_2} + \frac{R_1}{L} \right) \cdot s + \left(1 + \frac{R_1}{R_2} \right) \cdot \frac{1}{L \cdot C}} \end{aligned}$$



$$\text{Characteristic eq.: } 0 = s^2 + \left(\frac{1}{C \cdot R_2} + \frac{R_1}{L} \right) \cdot s + \left(1 + \frac{R_1}{R_2} \right) \cdot \frac{1}{L \cdot C}$$

b) Find the solutions (numbers) of the characteristic equation:

Second-Order Transient Examples, p.3

$$b := \frac{1}{C \cdot R_2} + \frac{R_1}{L}$$

$$b = 3.5 \cdot 10^4 \cdot \text{sec}^{-1}$$

$$k := \left(1 + \frac{R_1}{R_2}\right) \cdot \frac{1}{L \cdot C}$$

$$k = 1.5 \cdot 10^9 \cdot \text{sec}^{-2}$$

Underdamped

$$s_1 := \frac{-b + \sqrt{b^2 - 4 \cdot k}}{2}$$

$$s_1 = -1.75 \cdot 10^4 + 3.455 \cdot 10^4 j \quad \cdot \frac{1}{\text{sec}}$$

$$\alpha := -\frac{b}{2}$$

$$\alpha = -1.75 \cdot 10^4 \cdot \text{sec}^{-1}$$

$$s_2 := \frac{-b - \sqrt{b^2 - 4 \cdot k}}{2}$$

$$s_2 = -1.75 \cdot 10^4 - 3.455 \cdot 10^4 j \quad \cdot \frac{1}{\text{sec}}$$

$$\omega := \frac{1}{2} \cdot \sqrt{4 \cdot k - b^2}$$

$$\omega = 3.455 \cdot 10^4 \cdot \text{sec}^{-1}$$

c) Plot the poles and zeroes of the transfer function.

The poles are the s's where the denominator is zero, s_1 & s_2

The zero is the s where the numerator is zero: $-\frac{1}{C \cdot R_2} = -1 \cdot 10^4 \cdot \text{sec}^{-1}$

d) Initial and final conditions for $i_L(t)$

$$i_{L0} := \frac{V_{in}}{R_1} \quad i_{L0} = 60 \cdot \text{mA}$$

initial voltage across R_1 : $v_{R10} := i_{L0} \cdot R_1 \quad v_{R10} = 12 \cdot \text{V}$

capacitor was shorted before switch opened, so... $v_{C0} := 0 \cdot \text{V}$

initial voltage across the inductor: $v_{L0} := V_{in} - v_{R10} - v_{C0} \quad v_{L0} = 0 \cdot \text{V}$

$$\frac{d}{dt} i_L(0) = \frac{v_{L0}}{L} = 0 \cdot \frac{\text{A}}{\text{sec}}$$

e) Find the full expression of $i_L(t)$.

Underdamped $v_X(t) = v_X(\infty) + e^{\alpha t} \cdot (B \cdot \cos(\omega \cdot t) + D \cdot \sin(\omega \cdot t))$



$$i_L(t) = i_L(\infty) + e^{\alpha t} \cdot (B \cdot \cos(\omega \cdot t) + D \cdot \sin(\omega \cdot t))$$

$$i_L(\infty) = i_{Lfin} := \frac{V_{in}}{R_1 + R_2} \quad i_{Lfin} = 10 \cdot \text{mA}$$

$$i_L(0) = i_L(\infty) + B \quad \text{so.. } B = i_L(0) - i_L(\infty) \quad B := i_{L0} - i_{Lfin} \quad B = 50 \cdot \text{mA}$$

$$\frac{d}{dt} i_L(0) = B \cdot \alpha + D \cdot \omega \quad \text{so.. } D = \frac{\frac{d}{dt} i_L(0) - B \cdot \alpha}{\omega} \quad D := \frac{0 \cdot \frac{\text{A}}{\text{sec}} - B \cdot \alpha}{\omega} \quad D = 25.325 \cdot \text{mA}$$
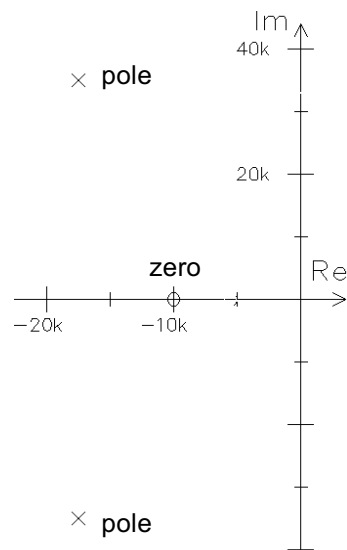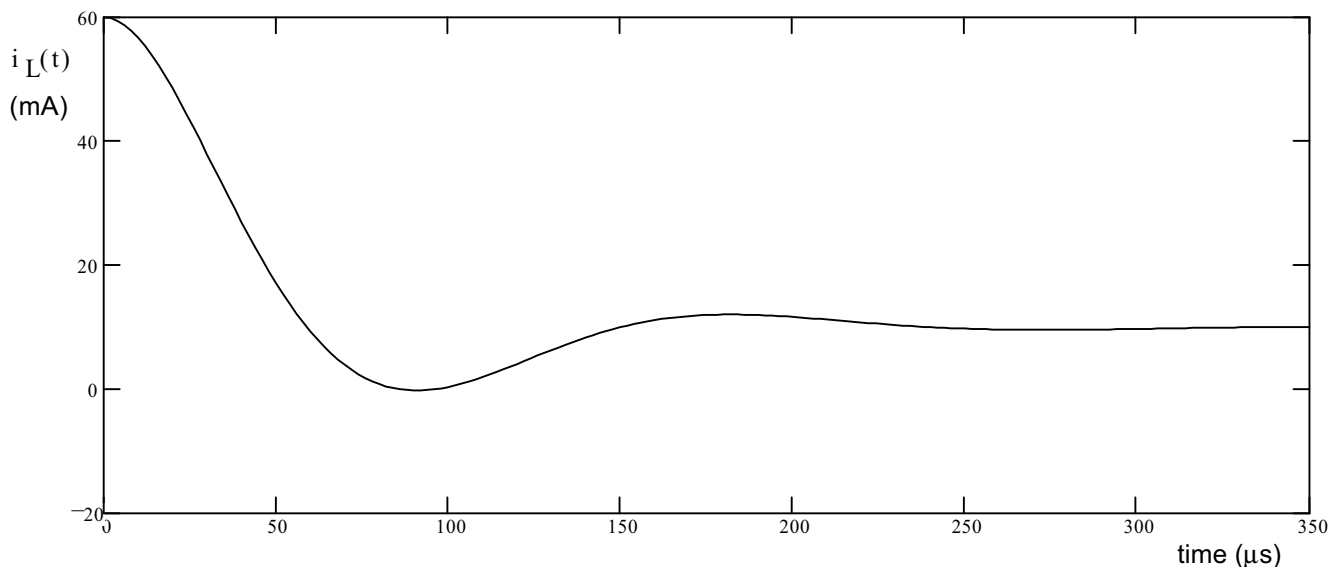
$$i_L(t) := 10 \cdot \text{mA} + e^{\frac{17500}{\text{sec}} t} \cdot \left(50 \cdot \text{mA} \cdot \cos\left(\frac{34550}{\text{sec}} \cdot t\right) + 25.325 \cdot \text{mA} \cdot \sin\left(\frac{34550}{\text{sec}} \cdot t\right) \right)$$



Second-Order Transient Examples, p.4

f) Initial and final conditions for $v_C(t)$

$$v_{C0} = 0 \cdot V$$

$$i_{R20} := \frac{0 \cdot V}{R_2}$$

$$i_{R20} = 0 \cdot \text{mA}$$

$$i_{L0} = 60 \cdot \text{mA}$$

$$i_{C0} := i_{L0} - i_{R20}$$

$$i_{C0} = 60 \cdot \text{mA}$$

$$\frac{d}{dt}v_C(0) = \frac{i(0)}{C} = \frac{i_{C0}}{C} = 6 \cdot 10^5 \cdot \frac{V}{\text{sec}}$$

$$V_{C\text{fin}} := \frac{R_2}{R_1 + R_2} \cdot V_{\text{in}}$$

$$V_{C\text{fin}} = 10 \cdot V$$

g) Find the full expression of $v_C(t)$.

$$B := v_{C0} - V_{C\text{fin}}$$


$$B = -10 \cdot V$$

$$D := \frac{6 \cdot 10^5 \cdot \frac{V}{\text{sec}} - B \cdot \alpha}{\omega}$$

$$D = 12.301 \cdot V$$

$$v_C(t) = v_C(\infty) + e^{\alpha t} \cdot (B \cdot \cos(\omega t) + D \cdot \sin(\omega t))$$
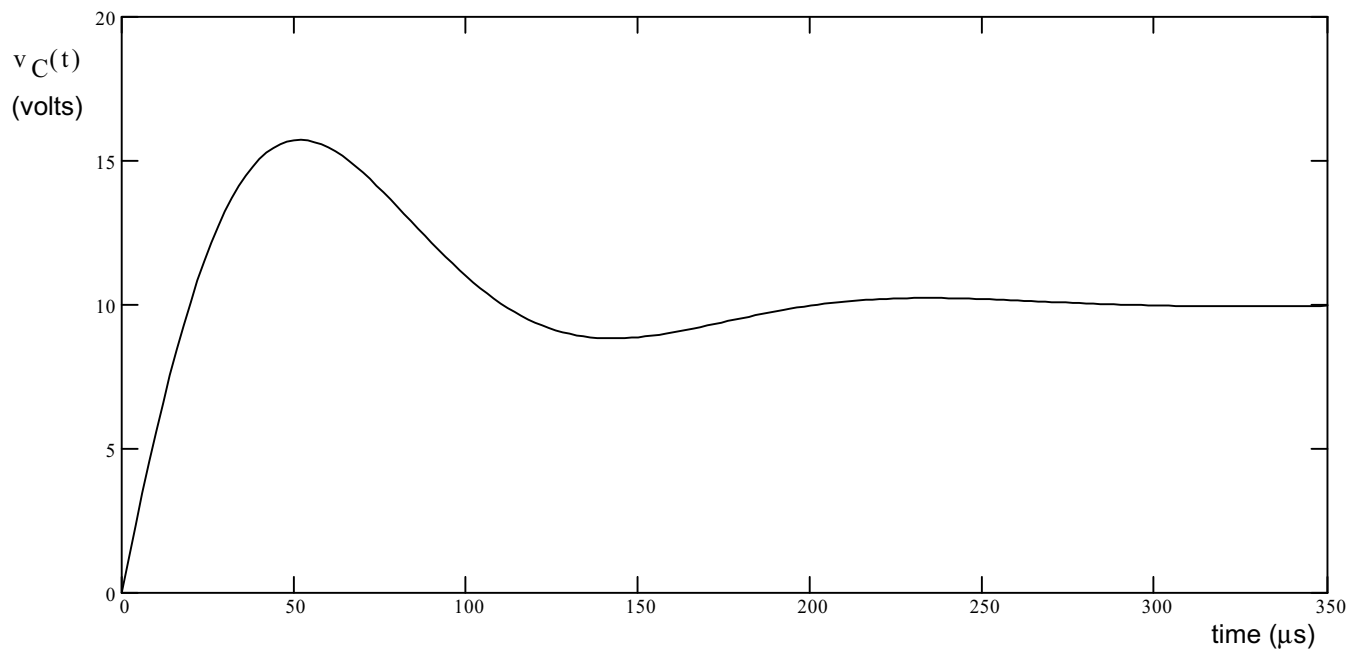
$$v_C(t) := 10 \cdot V + e^{\frac{-17500}{\text{sec}} t} \cdot \left(-10 \cdot V \cdot \cos\left(\frac{34550}{\text{sec}} \cdot t\right) + 12.301 \cdot V \cdot \sin\left(\frac{34550}{\text{sec}} \cdot t\right) \right)$$



Second-Order Transient Examples, p.5

h) What value of R_1 would make this system critically damped?

$$\left(\frac{1}{C \cdot R_2} + \frac{R_1}{L}\right)^2 = 4 \cdot \left(1 + \frac{R_1}{R_2}\right) \cdot \frac{1}{L \cdot C}$$

$$\frac{1}{C^2 \cdot R_2^2} + \frac{2}{C \cdot R_2} \cdot \frac{R_1}{L} + \frac{R_1^2}{L^2} = \frac{4}{L \cdot C} + \frac{4}{C \cdot R_2} \cdot \frac{R_1}{L}$$

$$\frac{1}{L^2} \cdot R_1^2 - \frac{2}{L \cdot C \cdot R_2} \cdot R_1 + \left(\frac{1}{C^2 \cdot R_2^2} - \frac{4}{L \cdot C}\right) = 0$$

$$R_1^2 - \frac{2 \cdot L}{C \cdot R_2} \cdot R_1 + \left(\frac{L^2}{C^2 \cdot R_2^2} - \frac{4 \cdot L}{C}\right) = 0$$

Solve for R_1 with quadratic equation:

$$R_1 = \frac{\frac{2 \cdot L}{C \cdot R_2} + \sqrt{\left(\frac{2 \cdot L}{C \cdot R_2}\right)^2 - 4 \cdot \left(\frac{L^2}{C^2 \cdot R_2^2} - \frac{4 \cdot L}{C}\right)}}{2} = 645.685 \cdot \Omega$$

this must be
the only solution

Quadratic equation can be reduced to:

$$\frac{L}{C \cdot R_2} - \frac{4}{2} \cdot \sqrt{\frac{L}{C}} = -485.685 \cdot \Omega \text{ this solution can't be}$$

Ex. 2 with bigger R_2

a) Find the characteristic equation of the circuit shown (after the switch moves to the lower position at $t = 0$).

$$\frac{V_C(s)}{V_{in}(s)} = H(s) = \frac{\frac{1}{\frac{1}{L \cdot s} + C \cdot s}}{\frac{1}{\frac{1}{L \cdot s} + C \cdot s} + R_2} \cdot \left(\frac{1}{L \cdot s} + C \cdot s\right) = \frac{1}{1 + \frac{R_2}{L \cdot s} + R_2 \cdot C \cdot s} \cdot \frac{L \cdot s}{L \cdot s}$$

$$= \frac{L \cdot s}{L \cdot s + R_2 + R_2 \cdot C \cdot L \cdot s^2} \cdot \frac{\frac{1}{R_2 \cdot C \cdot L}}{\frac{1}{R_2 \cdot C \cdot L}} = \frac{\frac{1}{R_2 \cdot C} \cdot s}{\frac{1}{R_2 \cdot C} \cdot s + \frac{1}{L \cdot C} + s^2}$$

Characteristic equation:

$$0 = s^2 + \frac{1}{R_2 \cdot C} \cdot s + \frac{1}{L \cdot C}$$

b) Find the solutions of the characteristic equation.

$$\frac{1}{R_2 \cdot C} = 1.25 \cdot 10^4 \cdot \text{sec}^{-1}$$

$$\frac{4}{L \cdot C} = 1 \cdot 10^{10} \cdot \text{sec}^{-2}$$

$$s_1 := \frac{-\frac{1}{R_2 \cdot C} + \sqrt{\left(\frac{1}{R_2 \cdot C}\right)^2 - \frac{4}{L \cdot C}}}{2}$$

$$s_2 := \frac{-\frac{1}{R_2 \cdot C} - \sqrt{\left(\frac{1}{R_2 \cdot C}\right)^2 - \frac{4}{L \cdot C}}}{2}$$

$$s_1 = -6.25 \cdot 10^3 + 4.961 \cdot 10^4 j \quad \cdot \frac{1}{\text{sec}}$$

$$s_2 = -6.25 \cdot 10^3 - 4.961 \cdot 10^4 j \quad \cdot \frac{1}{\text{sec}}$$

s_1 & s_2 complex,
so underdamped

$$\alpha := \text{Re}(s_1) \quad \alpha = -6.25 \cdot 10^3 \cdot \text{sec}^{-1}$$

$$\omega := \text{Im}(s_1) \quad \omega = 4.961 \cdot 10^4 \cdot \text{sec}^{-1}$$

Second-Order Transient Examples, p.5

Second-Order Transient Examples, p.6

c) Find initial and final conditions for $v_C(t)$

before switch is moved: $v_L(\infty) = 0 = v_L(0^-) = v_C(0^-) = 0 = v_C(0^+)$

$$\frac{d}{dt}v_C(0) = \frac{i_C(0)}{C} \quad \text{before switch is moved:} \quad i_{L0} := \frac{V_1 - 0 \cdot V}{R_1 + R_2} \quad \text{so...} \quad i_{L0} = 17.561 \text{ mA}$$

$$\text{after switch is moved:} \quad i_{R0} := \frac{6 \cdot V - 0 \cdot V}{R_2} \quad i_{R0} = 6 \text{ mA}$$

not all of the inductor's current comes through the resistor anymore, so the difference must come from the capacitor

$$i_{C0} := i_{R0} - i_{L0} \quad i_{C0} = -11.561 \text{ mA} \quad \frac{d}{dt}v_C(0) = \frac{i_{C0}}{C} = -1.445 \cdot 10^5 \cdot \frac{V}{\text{sec}}$$

d) Find the full expression of $v_C(t)$.

Underdamped $b^2 - 4 \cdot k < 0$ $s_1 = \alpha + j \cdot \omega$ $s_2 = \alpha - j \cdot \omega$ α is negative

$$v_X(t) = v_X(\infty) + e^{\alpha t} \cdot (B \cdot \cos(\omega \cdot t) + D \cdot \sin(\omega \cdot t))$$

$$v_X(0) = v_X(\infty) + B$$

$$\text{so.. } B = v_X(0) - v_X(\infty)$$

$$B := 0 \cdot V - 0 \cdot V$$

$$B = 0 \cdot V$$

$$\frac{d}{dt}v_X(0) = B \cdot \alpha + D \cdot \omega \quad \text{so.. } D = \frac{\frac{d}{dt}v_X(0) - B \cdot \alpha}{\omega}$$

$$D := \frac{-1.445 \cdot 10^5 \cdot \frac{V}{\text{sec}} - B \cdot \alpha}{\omega}$$

$$D = -2.913 \cdot V$$

$$v_C(t) = v_C(\infty) + e^{\alpha t} \cdot (B \cdot \cos(\omega \cdot t) + D \cdot \sin(\omega \cdot t))$$

$$v_C(t) := 0 \cdot V + e^{\alpha t} \cdot (B \cdot \cos(\omega \cdot t) + D \cdot \sin(\omega \cdot t)) = -2.913 \cdot V \cdot e^{\frac{-6250}{\text{sec}} t} \cdot \sin\left(\frac{49610}{\text{sec}} \cdot t\right)$$

