
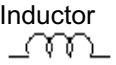



# Notes, Second Order Transients

ECE 2210 A.Stolp 4/6/00, 10/24/05

			Laplace impedance	initial conditions	final conditions	
					DC	AC
Capacitor		$i_C = C \cdot \frac{d}{dt} v_C$ $v_C = \frac{1}{C} \cdot \int_{-\infty}^t i_C dt$	$\frac{1}{C \cdot s}$	short, or $v_C(0+) = v_C(0-)$	open	$\frac{1}{j \cdot \omega \cdot C}$
Inductor		$v_L = L \cdot \frac{d}{dt} i_L$ $i_L = \frac{1}{L} \cdot \int_{-\infty}^t v_L dt$	$L \cdot s$	open, or $i_L(0+) = i_L(0-)$	short	$j \cdot \omega \cdot L$
Resistor		$v_R = i_R \cdot R$ $i_R = \frac{v_R}{R}$	$R$	$R$	$R$	$R$

## Characteristic equation

Use Laplace impedances, manipulate your circuit equation(s) into one equation of this form:

$$\left( a_1 \cdot s^2 + b_1 \cdot s + k_1 \right) \cdot \overset{\text{May be } I_{in} \text{ or any forcing function}}{V_{in}(s)} = \left( s^2 + b \cdot s + k \right) \cdot \overset{\text{May be } I_X \text{ or any desired variable}}{V_X(s)}$$

Coefficients may be zero      NO denominator s terms       $s^2 + b \cdot s + k = 0$  = Characteristic equation

## Differential equation

$$a_1 \cdot \frac{d^2}{dt^2} v_{in}(t) + b_1 \cdot \frac{d}{dt} v_{in}(t) + k_1 \cdot v_{in}(t) = \frac{d^2}{dt^2} v_X(t) + b \cdot \frac{d}{dt} v_X(t) + k \cdot v_X(t)$$

## Transfer function

Rearrange circuit equation to:  $H(s) = \frac{\overset{\text{May be } I_X \text{ or any desired variable}}{V_X(s)}}{\overset{\text{May be } I_{in} \text{ or any forcing function}}{V_{in}(s)}} = \frac{a_1 \cdot s^2 + b_1 \cdot s + k_1}{s^2 + b \cdot s + k}$  = transfer function

## Complete solution

Solutions to the characteristic equation:  $s_1 = -\frac{b}{2} + \frac{\sqrt{b^2 - 4 \cdot k}}{2}$      $s_2 = -\frac{b}{2} - \frac{\sqrt{b^2 - 4 \cdot k}}{2}$

### Find initial Conditions ( $v_C$ and/or $i_L$ )

Find conditions of just before time  $t = 0$ ,  $v_C(0-)$  and  $i_L(0-)$ . These will be the same just after time  $t = 0$ ,  $v_C(0+)$  and  $i_L(0+)$  and will be your initial conditions.

Use normal circuit analysis to find your desired variable:  $v_X(0)$  or  $i_X(0)$

Also find:  $\frac{d}{dt} v_X(0)$  or  $\frac{d}{dt} i_X(0)$  The trick to finding these is to see that:  $\frac{d}{dt} v_C(0) = \frac{i_C(0)}{C}$  and  $\frac{d}{dt} i_L(0) = \frac{v_L(0)}{L}$

### Find final conditions ("steady-state" or "forced" solution)

DC inputs: Inductors are shorts Capacitors are opens Solve by DC analysis  $v_X(\infty)$  or  $i_X(\infty)$


AC inputs: Solve by AC steady-state analysis using  $\omega$

$v_X(t)$  may be replaced by  $i_X(t)$  or any desired variable in the equations below

Overdamped  $b^2 - 4 \cdot k > 0$      $s_1$  and  $s_2$  are real and negative

$$v_X(t) = v_X(\infty) + B \cdot e^{s_1 \cdot t} + D \cdot e^{s_2 \cdot t}$$
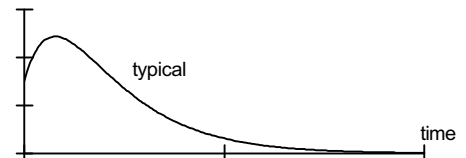
$$v_X(0) = v_X(\infty) + B + D \quad \frac{d}{dt} v_X(0) = B \cdot s_1 + D \cdot s_2 \quad \text{Solve simultaneously for B and D}$$




Critically damped  $b^2 - 4 \cdot k = 0$      $s_1 = s_2 = -\frac{b}{2} = s$      $s_1$  and  $s_2$  are real, equal and negative

$$v_X(t) = v_X(\infty) + B \cdot e^{s \cdot t} + D \cdot t \cdot e^{s \cdot t}$$

$$v_X(0) = v_X(\infty) + B \quad \frac{d}{dt} v_X(0) = B \cdot s + D \quad \text{so.. } D = \frac{d}{dt} v_X(0) - B \cdot s$$
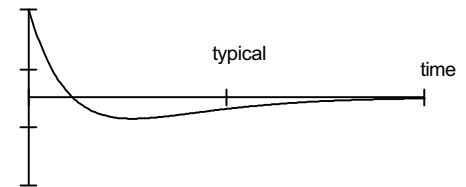
$$\text{so.. } B = v_X(0) - v_X(\infty)$$



Underdamped  $b^2 - 4 \cdot k < 0$      $s_1 = \alpha + j \cdot \omega$      $s_2 = \alpha - j \cdot \omega$      $\alpha$  is negative

$$v_X(t) = v_X(\infty) + e^{\alpha \cdot t} \cdot (B \cdot \cos(\omega \cdot t) + D \cdot \sin(\omega \cdot t))$$

$$v_X(0) = v_X(\infty) + B \quad \frac{d}{dt} v_X(0) = B \cdot \alpha + D \cdot \omega \quad \text{so.. } D = \frac{\frac{d}{dt} v_X(0) - B \cdot \alpha}{\omega}$$

$$\text{so.. } B = v_X(0) - v_X(\infty)$$

