
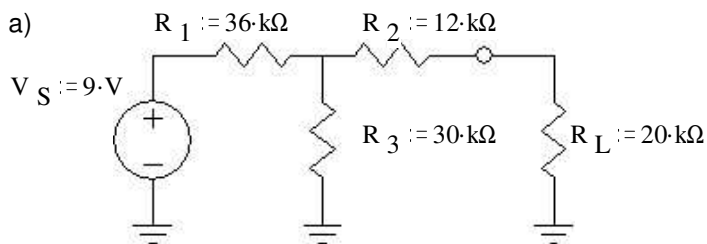


Thevenin & Norton equivalent circuits

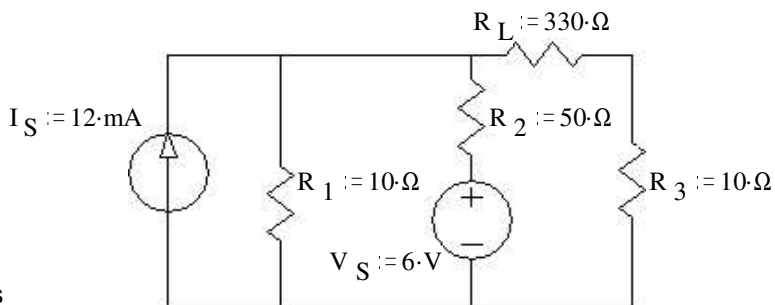1. For each of the circuits below, find and draw the Thevenin equivalent circuit.



b) The load resistor is R_L , and is in a strange place in this circuit.
Hint: use superposition to find V_{Th} .




2nd hint: Nodal analysis is even easier.

2. For the circuit of problem 1a, find the voltage across R_L (V_L) and the current through R_L (I_L) using your Thevenin equivalent circuit.


3. For each of the circuits in problem 1, find and draw the Norton equivalent circuit.

4. For the circuit of problem 1b, find V_L and I_L using your Norton equivalent circuit.

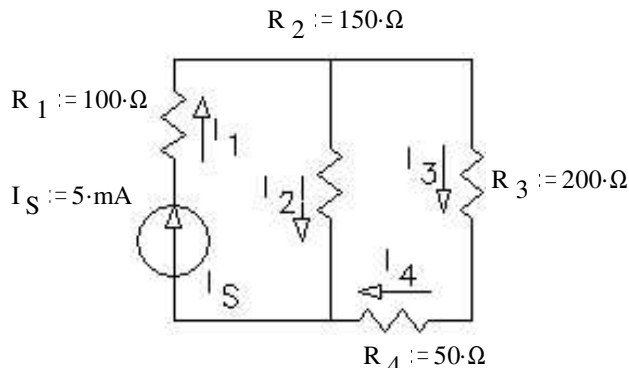5. For the circuit shown at right, use Thevenin's theorem to find the current through the 50 Ω resistor R_4 .



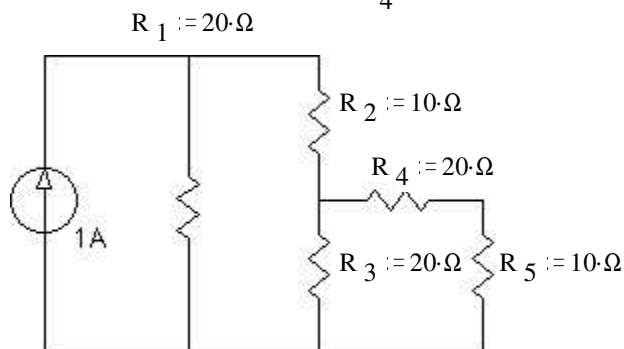6. For the circuit shown, use Norton's theorem to find the value of the current in R_5 . Hint: You can find I_N either by calculation of the open circuit voltage (V_{OC}) and R_N or by direct calculation of the short-circuit current (I_{SC}), however, there is something about the values of the resistors which makes the second method easier than it would at first appear.



Source resistance

7. The terminal voltage of a car's battery drops from 12.5 V to 8.5 volts when starting. The starter motor draws 60 A of current.

- Draw the voltage-source model (Thevenin equivalent) of this battery. Include the values of V_S and R_S .
- Draw the current-source model (Norton equivalent) of this battery. Include the values of I_S and R_S .
- Which of these two models is more appropriate for the car battery?
- What terminal voltage would you expect if this battery were being charged at 20 A?

Answers

- | | | |
|--------------------------|-----------------------------------------|---------------------|
| 1. a) 4.091·V , 28.4·kΩ | b) 1.1·V , 18.3·Ω | 2. 1.69·V , 84.6·μA |
| 3. a) 0.144·mA , 28.4·kΩ | b) 60·mA , 18.3·Ω | 4. 3.16·mA, 1.042·V |
| 6. 0.19·A | 7. a) $V_S = 12.5·V$, $R_S = 0.0667·Ω$ | 5. 1.88·mA |
| | b) $I_S = 187.5·A$, $R_S = 0.0667·Ω$ | c) Thevenin |
| | | d) 13.83·V |