

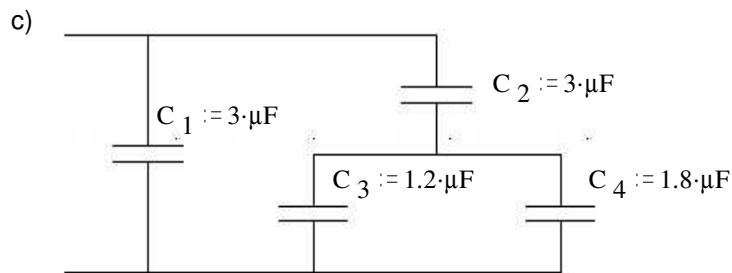
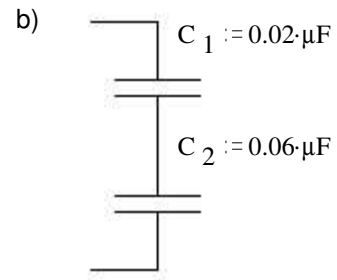
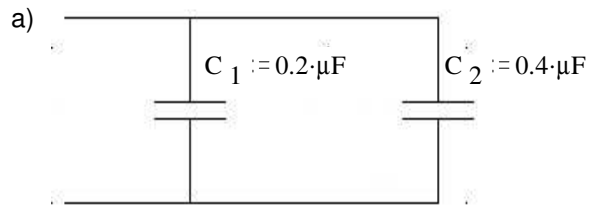
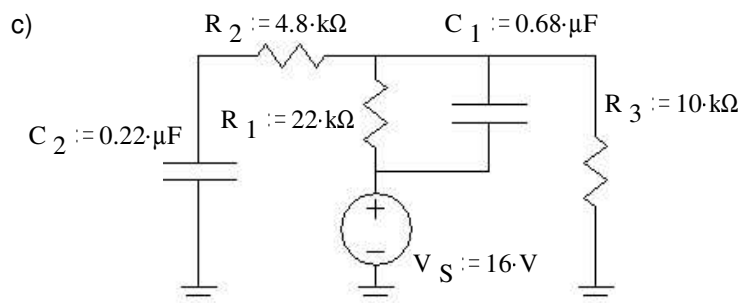


You will probably need more paper for your calculations, but problems 3 & 4 require waveform drawings and you may want to hand this sheet in with your drawings.


1) Find C_{eq} in each case

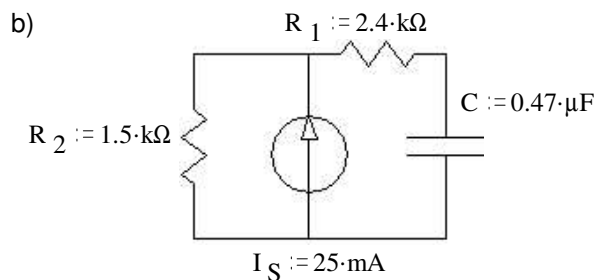

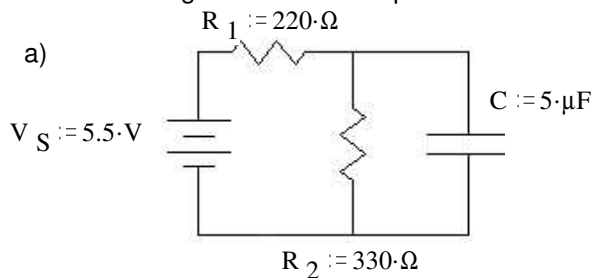
2. Each of the following circuits have been connected as shown for a long time. Find the voltage across each capacitor and the energy stored in each.



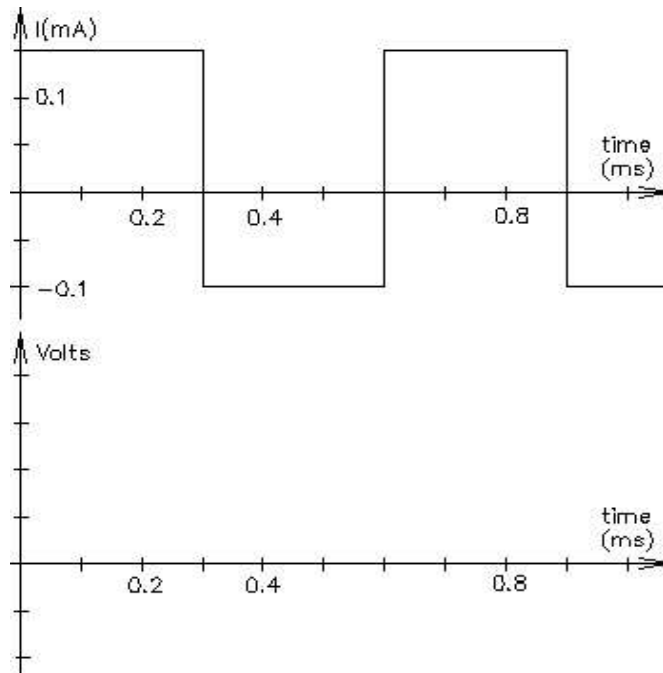3. The current waveform shown below flows through a $0.025 \mu\text{F}$ capacitor. Make an accurate drawing of the voltage across it. Label your graph. Assume the initial voltage across the capacitor is 0 V .



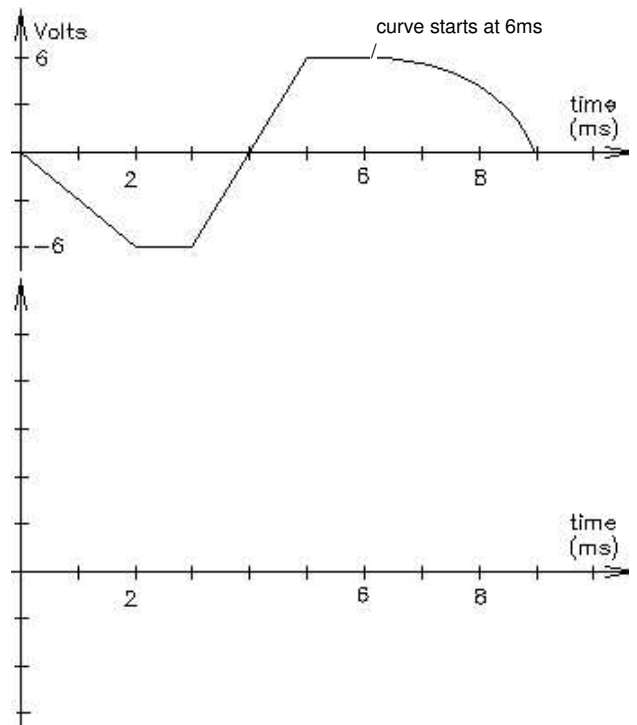
4. The voltage across a $2 \mu\text{F}$ capacitor is shown below. Make an accurate drawing of the capacitor current. Label your graph.



5. The voltage across a $0.68 \mu\text{F}$ capacitor is $v_c = 6 \cdot V \cdot \cos\left(200 \cdot t + \frac{\pi}{2}\right)$ find i_c .

6. The current through a $0.0047 \mu\text{F}$ capacitor is $i_c = 18 \cdot \mu\text{A} \cdot \cos\left(628 \cdot t - \frac{\pi}{4}\right)$ find v_c .

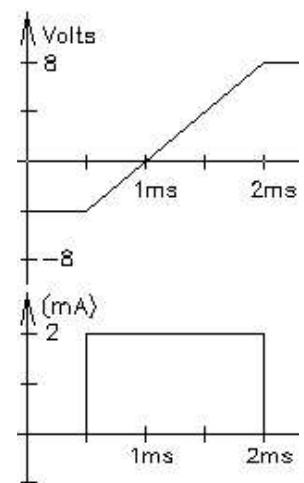7. A capacitor voltage and current are shown at right. What value is the capacitor?



Answers

1. a) $0.6 \mu\text{F}$ b) $0.015 \mu\text{F}$ c) $4.5 \mu\text{F}$
 2. a) 3.3 V 0.027 mJ b) 37.5 V 0.33 mJ c) 11 V 0.0411 mJ 5 V $2.75 \mu\text{J}$
 3. 1.8 V 0.6 V 2.4 V 4. -6 mA 12 mA ramp to -8 mA
 5. $i_c = -0.816 \text{ mA} \cdot \cos(200 \cdot t)$ 6. $v_c = -6.1 \text{ V} \cdot \cos\left(628 \cdot t + \frac{\pi}{4}\right)$ 7. $0.25 \mu\text{F}$