

If you have the textbook, read pages 128 to 147. If not, find the section in your book that covers first-order transient responses of RC and RL circuits and read that.


1. An FE style problem

A 10-microfarad capacitor has been charged to a potential of 150 volts. A resistor of $25\ \Omega$ is then connected across the capacitor through a switch. When the switch has been closed for 10 time constants the total energy dissipated by the resistor is most nearly



- (A) 1.0×10^{-7} joules
 (B) 1.1×10^{-1} joules
 (C) 9.0×10^1 joules
 (D) 9.0×10^3 joules

2. a) The switch is closed at time $t = 0$ and $v_C(0) = 0\text{V}$, find $v_C(t)$.


b) What is the value of the voltage across C at $t := 40\ \mu\text{s}$

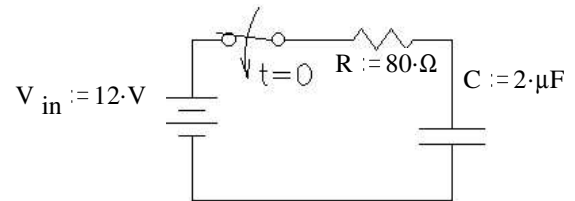3. In the circuit below, the switch has been in the upper position for a long time and is switched down at time $t = 0$.

What is the capacitor voltage (V_C) at $t := 4\ \text{ms}$

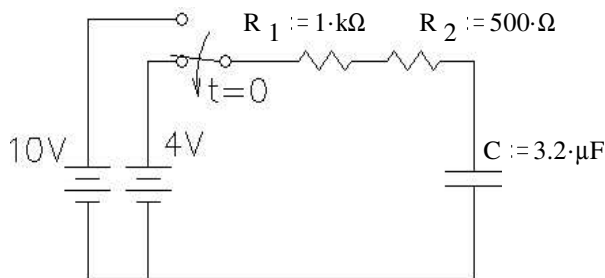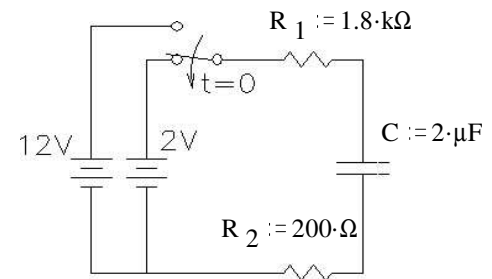4. The switch below has been in the upper position for a long time and is switched down at time $t = 0$. At what time is $v_C = 4\text{V}$?5. a) What is the time constant of this circuit?
Hint: Use a Thevenin equivalent circuit.


b) What will be the final value of v_C ?
(After the switch has been closed for a long time)

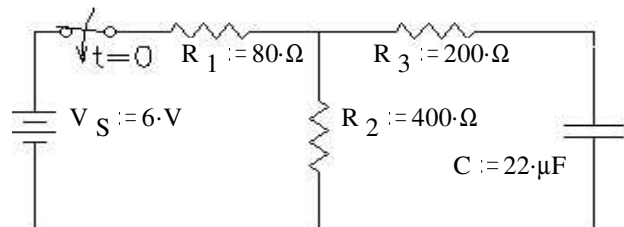6. In a circuit with two capacitors (C_1), the left capacitor (C_2) has an initial charge and the right one does not. When the switch is closed at time $t = 0$, current $i(t)$ flows, discharging C_1 and charging C_2 .

a) Derive the differential equation for $i(t)$. Hint: write an equation in terms of i and integrals of i , then differentiate the whole equation.

Write your DE in this form: $\text{Constant} = x(t) + \tau \frac{d}{dt}x(t)$

What is the time constant (τ)?

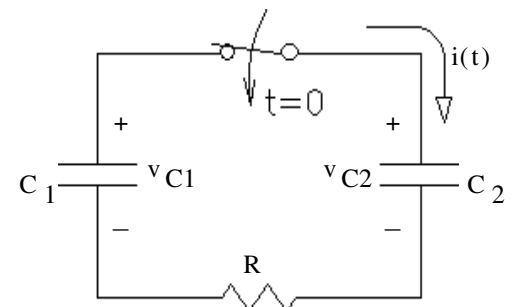

b) Find $i(t)$ given $C_1 := 24\ \mu\text{F}$ $C_2 := 12\ \mu\text{F}$ $R := 400\ \Omega$ $v_{C1}(0) = 18\ \text{V}$ $v_{C2}(0) = 0\ \text{V}$

c) Find $v_{C2}(t)$ for the same values. Hint: The trick here will be finding the final condition. Realize that charge will be conserved. If C_1 discharges x coulombs, then C_2 will charge x coulombs. Charges will stop flowing when $v_{C1} = v_{C2}$. It may help to think of two water tanks, one with half the cross-sectional area of the other. $V = \frac{Q}{C}$

d) Find the initial and final stored energy of the system ($W_{C1} + W_{C2}$) to find the total "loss". What happened to that energy?

Answers 1. B 2.a) $12\ \text{V} - 12\ \text{V} \cdot e^{-\frac{t}{0.16\ \text{ms}}}$ 3. $6.61\ \text{V}$ 4. $6.44\ \text{ms}$ 5. a) $5.87\ \text{ms}$ 6.a) $\tau = R \cdot \left(\frac{1}{C_1} + \frac{1}{C_2} \right)$
 b) $5\ \text{V}$

6.b) $i(t) = 45\ \text{mA} \cdot e^{-\frac{t}{3.2\ \text{ms}}}$

c) $12\ \text{V} - 12\ \text{V} \cdot e^{-\frac{t}{3.2\ \text{ms}}}$

d) $1.3\ \text{mJ}$ dissipated in resistor