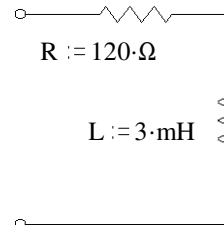


The 2nd exam will include this material


1. For the circuit shown, find the following:

- a) At what frequency would the magnitude of the total impedance be 240Ω ?
- b) At this frequency, what is the phase angle of the impedance?
- c) At this frequency, you want to add a capacitor in series to make the circuit appear purely resistive (the impedance has no imaginary component). Find the value of the capacitor.





2. You need to design a circuit in which the current $i(t)$ leads the voltage $v_S(t)$ by 36° of phase.

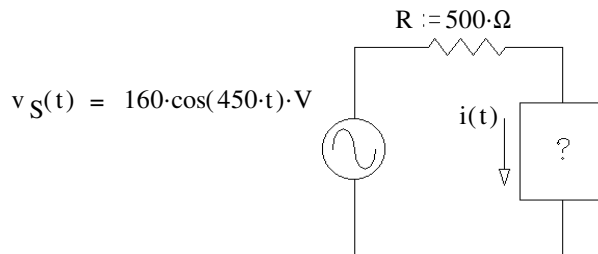- a) What should go in the box: R, L, C?
- b) Find its value.




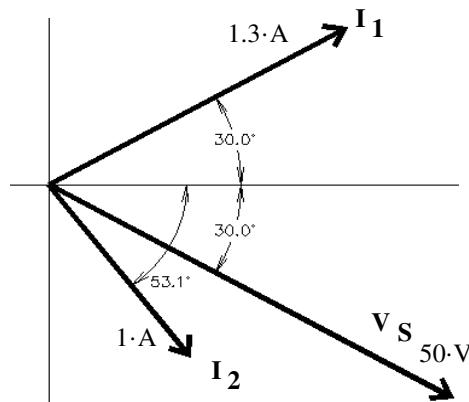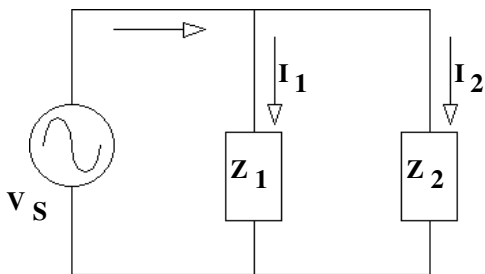3. The phasor diagram at right shows the source voltage and two branch currents of a parallel circuit. Find the impedance of each of the two branches.



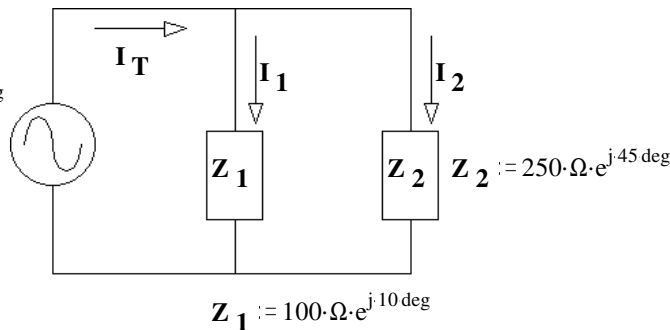4. a) Find all the currents, I_1 , I_2 , and I_T .

$v_S := 24 \cdot V \cdot e^{j \cdot 45 \text{ deg}}$




b) Draw a phasor diagram showing I_1 , I_2 , and I_T to scale so that you can show that they obey KCL.

5. a) Find the AC current source, I_{in} in polar form.

b) Find V_T .


c) Choose one:

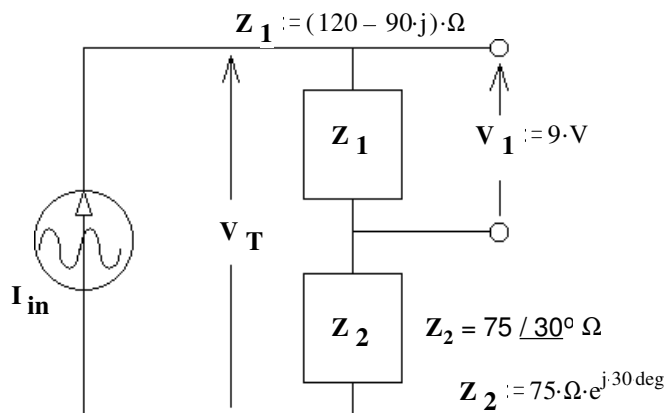- i) The source current leads the source voltage.
- ii) The source current lags the source voltage.



ECE 2210 homework # 13 p.2

6. a) Find Z_1 .

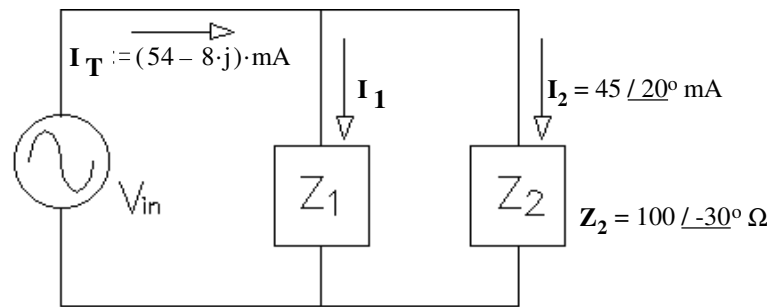


b) To make Z_1 in the simplest way, what part(s) would you need? Just determine the needed part(s) from the list below and state why you made that choice, don't find the values.

- | | | | | |
|-------------------|-------------------|-----------|--------------|----------------|
| resistor | capacitor | inductor | power supply | current source |
| Thevenin resistor | Ideal transformer | voltmeter | ammeter | scope |


- c) Choose one: i) I_2 leads the source voltage (V_{in}) ii) I_2 lags the source voltage (V_{in})
- d) Choose one: i) I_1 leads I_2 ii) I_1 lags I_2

7. Find Z .

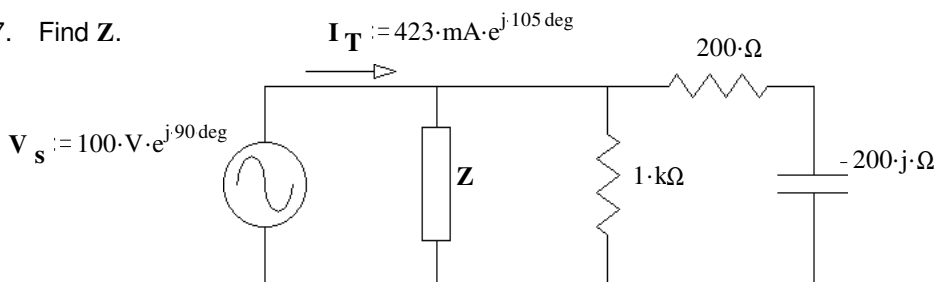


8. a) Find the total impedance of the circuit.

b) Find I_T .

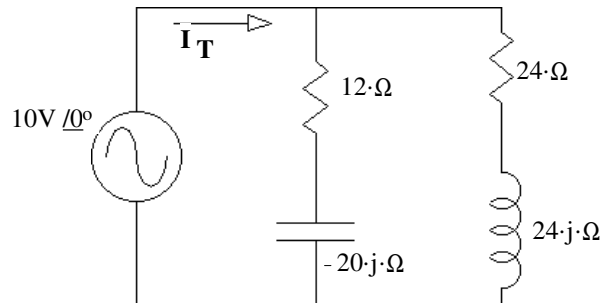

9. Find Z_{eq} in simple polar form.

$f := 8000 \text{ Hz}$

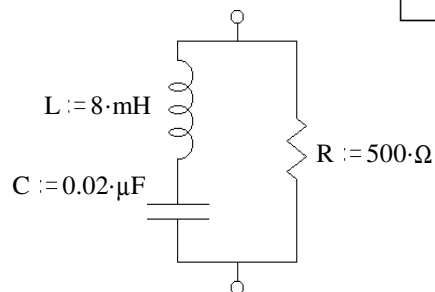

Answers

1. a) 11 kHz b) 60° c) 0.0694 μF
2. a) C b) 6.12 μF
3. $Z_1 = (19.2 - 33.3j) \cdot \Omega$ $Z_2 = (46.0 + 19.6j) \cdot \Omega$
4. a) $(0.197 + 0.138j) \cdot A + 0.096 \cdot A = 0.293 + 0.138j \cdot A$
5. a) 60 / 36.87° mA b) 11.54 / 21° V c) i)
6. a) 172 / 53.4° Ω b) phase angle > 0, resistor and inductor
c) i) d) ii)
7. 657 Ω / 67.4° 8. a) 21.86 Ω / -20.38° b) 0.457 A / 20.38°
9. 382 Ω / -40.2°

