


ECE 2210 homework PA1

d

Note: In the following problems, you may assume voltages and currents are RMS unless stated otherwise or given as a function of time.

- Read the AC power notes and examples.
- Compute the power factor for an inductive load consisting of $L := 20\text{mH}$ and $R := 6\text{-}\Omega$ in series. $\omega := 377\frac{\text{rad}}{\text{s}}$
- The complex power consumed by a load is $620 \angle 29^\circ$ VA. Find:
 - Apparent power (as always, give the correct units).
 - Real power.
 - Reactive power.
 - Power factor.
 - Is the power factor leading or lagging?
 - Draw a phasor diagram.
- In the circuit shown, the voltmeter measures 120V, the ammeter measures 6.3A and the wattmeter measures 560W. The load consists of a resistor and an inductor. The frequency is 60Hz. Find the following:

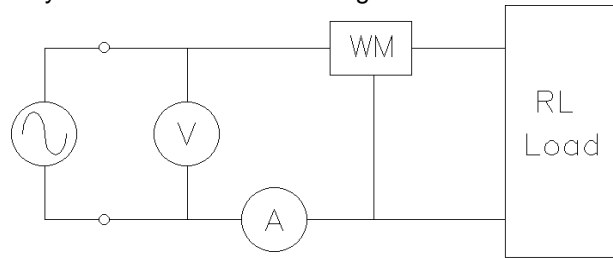
- Power factor
- Leading or lagging?
- Real power.
- Apparent power.
- Reactive power.
- Draw a phasor diagram.



- The load is in a box which cannot be opened. Add another component to the circuit above to correct the power factor (make $\text{pf} = 1$). Draw the correct component in the correct place and find its value. This component should not affect the real power consumption of the load.

- For the circuit shown, find the following: (as always, give the correct units)

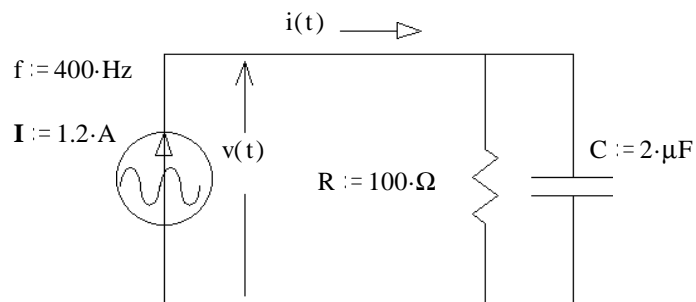- The complex power.
- Real power.
- Reactive power.
- Apparent power.
- Draw a power phasor diagram.




- A load draws 12kVA at 0.8 pf, lagging when hooked to 480V. A capacitance is hooked in parallel with the load and the power factor is corrected to 0.9, lagging.


- Find the reactive power (VAR) of the capacitor. Draw a phasor diagram as part of the solution.
- Find the value of the capacitor assuming $f = 60\text{Hz}$.

- Consider the circuit at right. The resistor and capacitor together make up the load.

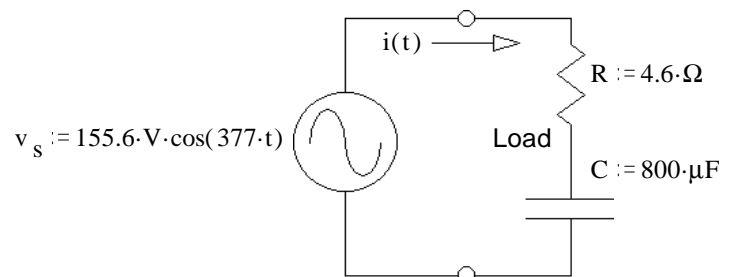- Find the load impedance of the circuit.
- Compute the average power dissipated by the load.




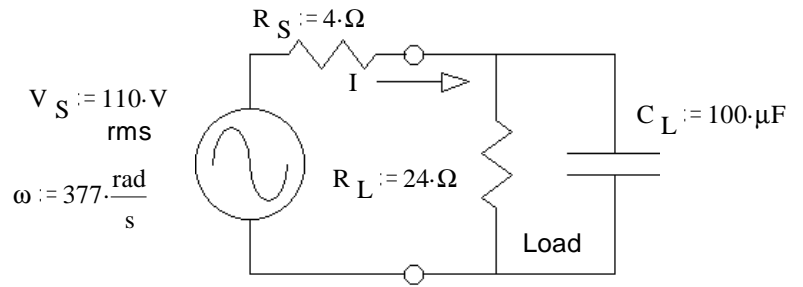8. a) Compute the average power dissipated by the load (R_L and C_L taken together).
 b) Compute the power dissipated by the internal source resistance (R_S) in this circuit.




Answers



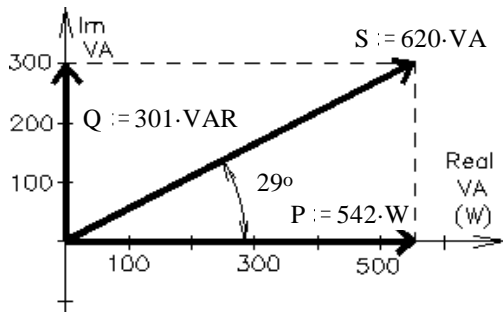
2. pf := 0.623
 3. a) 620·VA
 b) 542·W
 c) 301·VAR
 d) 0.875
 e) lagging
 f) ----->



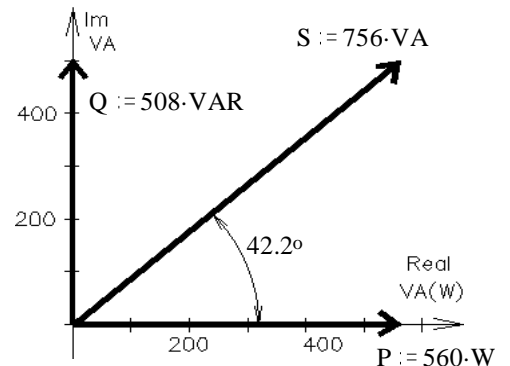4. a) 0.741
 b) lagging
 c) 560·W
 d) 756·VA
 e) 508·VAR
 f) ----->
 g) 93.6·μF capacitor in parallel with load



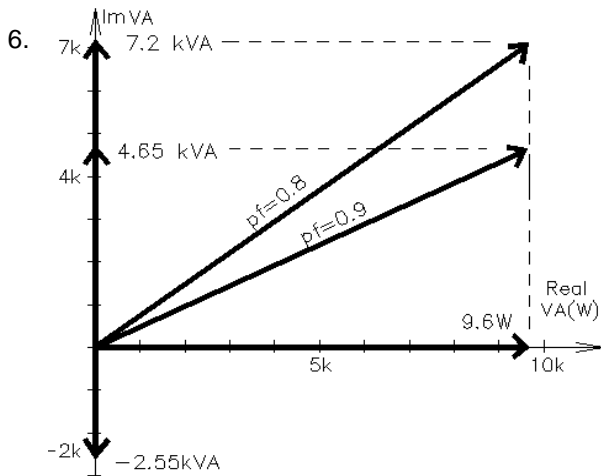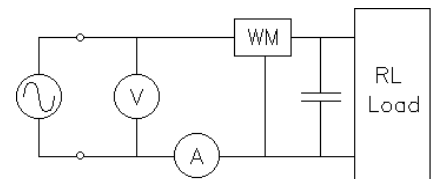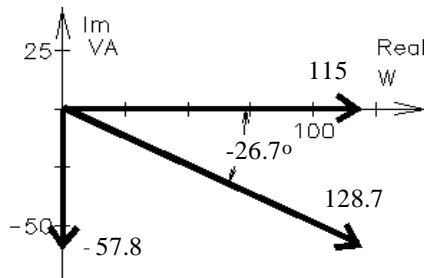5. a) $(115 - 57.8j) \cdot VA$
 b) 115·W
 c) -57.8·VAR
 d) 128.7·VA
 e) ----->



a) -2.55·kVA

b) 29.4·μF

7. a) $Z := 5.67 \cdot \Omega \cdot e^{-j35.8 \text{ deg}}$ b) $P_{av} := 1.73 \cdot kW$

8. a) $P_{av} := 364 \cdot W$ b) 110·W