

ECE 2210 homework PA2


Note: In the following problems, you may assume voltages and currents are RMS unless stated otherwise or given as a function of time. Transformers are ideal unless stated otherwise.

1. A load draws 12kVA at 0.8 pf, lagging when hooked to 480V. A capacitance is hooked in parallel with the load and the power factor is corrected to 0.9, lagging.

- a) Find the reactive power (VAR) of the capacitor. Draw a phasor diagram as part of the solution.
- b) Find the value of the capacitor assuming $f = 60\text{Hz}$.


2. Consider the circuit at right. The resistor and capacitor together make up the load.

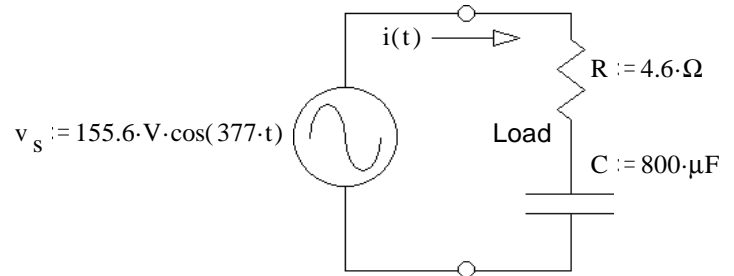- a) Find the load impedance of the circuit.
- b) Compute the average power dissipated by the load.



3. a) Compute the average power dissipated by the load (R_L and C_L taken together).

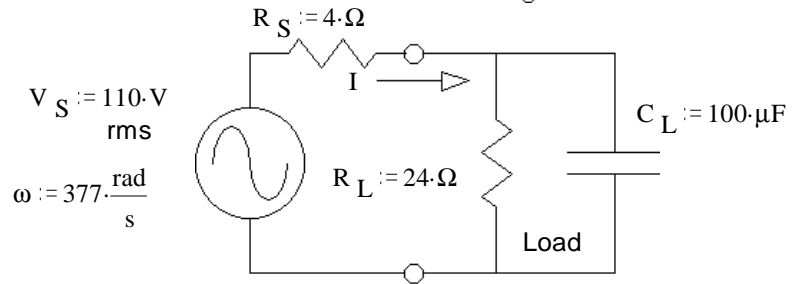- b) Compute the power dissipated by the internal source resistance (R_S) in this circuit.



4. Read sections 2.28, 3.8, & 7.1 in your textbook.

5. An ideal transformer has 330 turns on the primary winding and 36 turns on the secondary. If the primary is connected across a 110 V (rms) generator, what is the rms output voltage?

6. A transformer has $N_1 = 320$ turns and $N_2 = 1000$ turns. If the input voltage is $v(t) = (255 \text{ V})\cos(\omega t)$, what rms voltage is developed across the secondary coil?

7. A step-up transformer is designed to have an output voltage of 2200 V (rms) when the primary is connected across a 240 V (rms) source.


- a) If there are 150 turns on the primary winding, how many turns are required on the secondary?
- b) If a load resistor across the secondary draws a current of 1.2 A, what is the current in the primary, assuming ideal conditions?

8. The primary current of an ideal transformer is 8.5 A and the primary voltage is 80 V. 1.0 A is delivered to a load resistor connected to the secondary. Calculate the voltage across the secondary.

9. An ideal transformer has a turns ratio ($N = N_1/N_2$) of 1.5. It is desired to operate a 200Ω resistive load at 150 V (rms).

- a) Find the secondary and primary currents.
- b) Find the source voltage (V_1).
- c) Find the power dissipated in the load resistor and the power delivered to the primary from the source.
- d) Find the impedance the source sees looking into the primary winding by calculating $Z_{eq} = N^2 Z_L$ and again by calculating V_1 / I_1 .

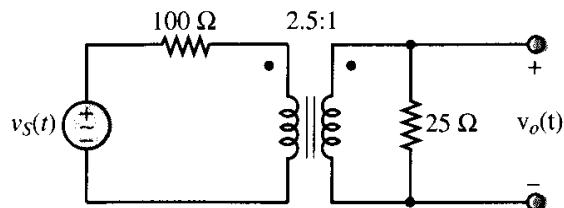
10. For the ideal transformer shown in the figure, find $v_o(t)$ if $v_s(t)$ is $320\text{V}\cos(377t)$.



ECE 2210 Homework PA2 p2


11. The transformer shown in the circuit below is ideal. It is rated at 120/30 V, 80 VA, 60 Hz
Find the following:

- a) $I_1 = ?$
- b) $V_2 = ?$

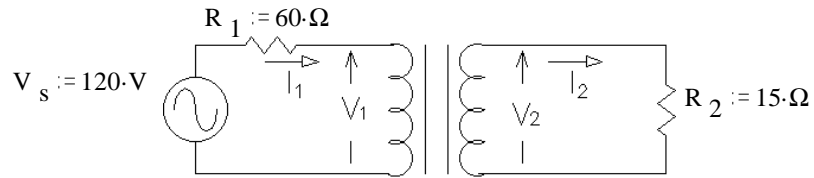

12. A transformer is rated at 13,800/480 V, 60 kVA, 60 Hz. (Note: kVA stands for kilo-Volt-Amp, in this case it is the transformer's voltage rating times its current rating.) Find the allowable primary and secondary currents at a supply voltage of 12,000 V at 100% power factor. Repeat for a power factor of 50%.
13. An ideal transformer has a rating of 500/125 V, 10 kVA, 60 Hz. It is loaded with an impedance of 5Ω at 80% pf (0.80). The source voltage applied to the primary winding is 440 V (rms). Find:
- a) the load voltage
 - b) the load current
 - c) the kVA delivered to load
 - d) the power delivered to load
 - e) the primary current
 - f) the power factor of primary
 - g) the impedance the source sees looking into primary.
14. An ideal transformer is rated to deliver 400 kVA at 460 V to a customer.
- a) How much current can the transformer supply to the customer?
 - b) If the customer's load is purely resistive (i.e. if the $pf = 1$), what is the maximum power the customer can receive?
 - c) If the customer's power factor is 0.8 (lagging), what is the maximum usable power the customer can receive?
 - d) What is the maximum power if the power factor is 0.7 (lagging)?
 - e) If the customer requires 300 kW to operate, what is the minimum allowable power factor given the rating of this transformer?

Answers

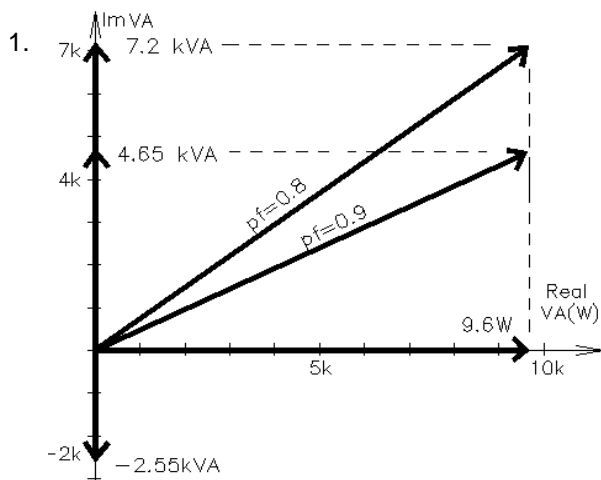

- a) -2.55 kVA
- b) 29.4 μ F
- 2. a) $Z := 5.67 \cdot \Omega \cdot e^{-j \cdot 35.8 \cdot \text{deg}}$
- b) $P_{av} := 1.73 \cdot \text{kW}$
- 3. a) $P_{av} := 364 \cdot \text{W}$
- b) 110 W
- 5. 12 V
- 6. 563 V
- 7. a) 1375 turns
- b) 11 A
- 8. 680 V

9. a) 0.75 A, 0.50 A b) 225 V c) 112.5 W d) 450 Ω

10. $78V \cos(377t)$

11. a) 0.4 A b) 24 V

12. 4.35 A, 125 A any pf, (Using the transformer at a lower voltage does not increase its current rating.)

13. a) 110 V b) 22 A c) 2.42 kVA d) 1.94 kW e) 5.5 A f) 0.80 g) $80\Omega / \underline{36.9^\circ} \Omega$

14. a) 870 A b) 400 kW c) 320 kW d) 280 kW e) 0.75