


ECE 2210 homework PA2

d

Note: In the following problems, you may assume voltages and currents are RMS unless stated otherwise or given as a function of time. Transformers are ideal unless stated otherwise.


- Read sections 2.28, & 3.8 in your textbook. Note: His secondary windings and currents are backwards.
- An ideal transformer has 330 turns on the primary winding and 36 turns on the secondary. If the primary is connected across a 110 V (rms) generator, what is the rms output voltage?
- A transformer has $N_1 = 320$ turns and $N_2 = 1000$ turns. If the input voltage is $v(t) = (255 \text{ V})\cos(\omega t)$, what rms voltage is developed across the secondary coil?
- A step-up transformer is designed to have an output voltage of 2200 V (rms) when the primary is connected across a 240 V (rms) source.
 - If there are 150 turns on the primary winding, how many turns are required on the secondary?
 - If a load resistor across the secondary draws a current of 1.2 A, what is the current in the primary, assuming ideal conditions?
- The primary current of an ideal transformer is 8.5 A and the primary voltage is 80 V. 1.0 A is delivered to a load resistor connected to the secondary. Calculate the voltage across the secondary.
- An ideal transformer has a turns ratio ($N = N_1/N_2$) of 1.5. It is desired to operate a 200Ω resistive load at 150 V (rms).
 - Find the secondary and primary currents.
 - Find the source voltage (V_1).
 - Find the power dissipated in the load resistor and the power delivered to the primary from the source.
 - Find the impedance the source sees looking into the primary winding by calculating $Z_{eq} = N^2 Z_L$ and again by calculating V_1 / I_1 .

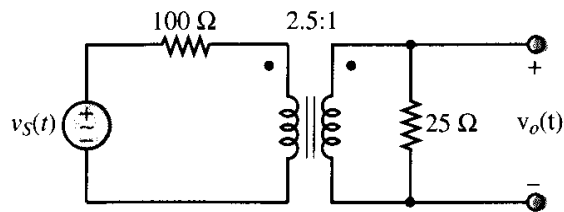- For the ideal transformer shown in the figure, find $v_o(t)$ if $v_s(t)$ is $320V\cos(377t)$.



- The transformer shown in the circuit below is ideal. It is rated at 120/30 V, 80 VA, 60 Hz. Find the following:

- $I_1 = ?$
- $V_2 = ?$

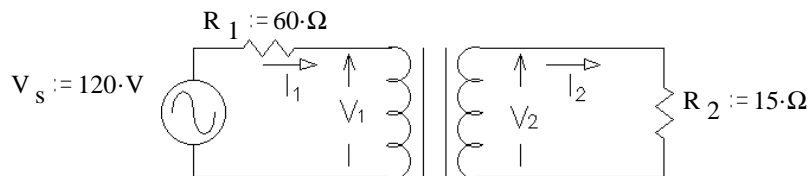

- A transformer is rated at 13,800/480 V, 60 kVA, 60 Hz. (Note: kVA stands for kilo-Volt-Amp, in this case it is the transformer's voltage rating times its current rating.) Find the allowable primary and secondary currents at a supply voltage of 12,000 V at 100% power factor. Repeat for a power factor of 50%.
- An ideal transformer has a rating of 500/125 V, 10 kVA, 60 Hz. It is loaded with an impedance of 5Ω at 80% pf (0.80). The source voltage applied to the primary winding is 440 V (rms). Find:
 - the load voltage
 - the load current
 - the kVA delivered to load
 - the power delivered to load
 - the primary current
 - the power factor of primary
 - the impedance the source sees looking into primary.

11. An ideal transformer is rated to deliver 400 kVA at 460 V to a customer.
- How much current can the transformer supply to the customer?
 - If the customer's load is purely resistive (i.e. if the $\text{pf} = 1$), what is the maximum power the customer can receive?
 - If the customer's power factor is 0.8 (lagging), what is the maximum usable power the customer can receive?
 - What is the maximum power if the power factor is 0.7 (lagging)?
 - If the customer requires 300 kW to operate, what is the minimum allowable power factor given the rating of this transformer?

Answers

2. 12 V 3. 563 V 4. a) 1375 turns 5. 680 V b) 11 A
6. a) 0.75 A, 0.50 A b) 225 V c) 112.5 W d) 450 Ω
7. $78V\cos(377t)$ 8. a) 0.4 A b) 24V
9. 4.35 A, 125 A any pf, (Using the transformer at a lower voltage does not increase its current rating.)
10. a) 110 V b) 22 A c) 2.42 kVA d) 1.94 kW e) 5.5 A f) 0.80 g) $80\Omega / 36.9^\circ \Omega$
11. a) 870 A b) 400 kW c) 320 kW d) 280 kW e) 0.75