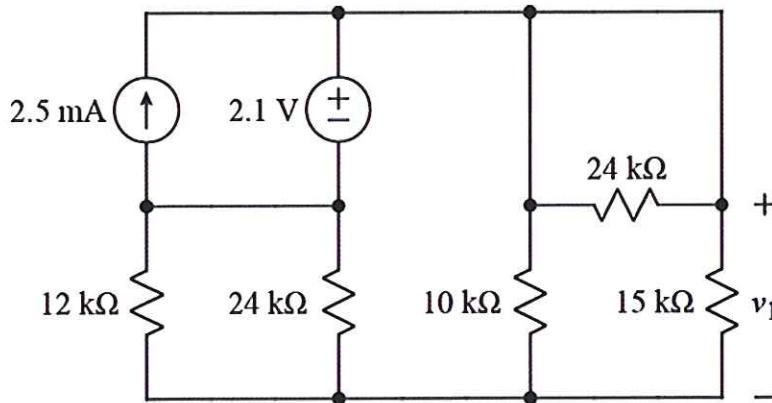




Ex:


Calculate v_1 .

Sol'n: The lower left $12\text{ k}\Omega$ and $24\text{ k}\Omega$ R's are in parallel. The upper right wire and $24\text{ k}\Omega$ are in parallel, as well.

$$12\text{ k}\Omega \parallel 24\text{ k}\Omega = 12\text{ k}\Omega \cdot 1 \parallel 2 = 12\text{ k}\Omega \cdot \frac{2}{3} = 8\text{ k}\Omega$$

$$0\text{ }\Omega \parallel 24\text{ k}\Omega \approx 0\text{ }\Omega \text{ (wire)}$$

circuit:

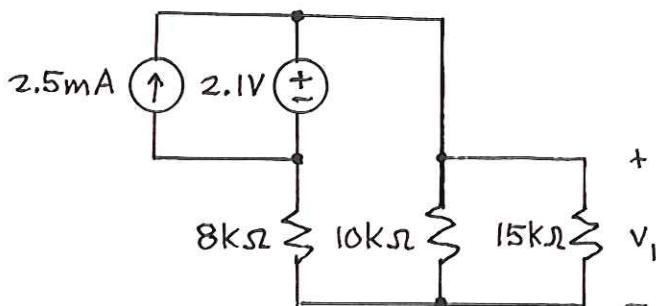


We see that the $10\text{ k}\Omega$ is in parallel with the $15\text{ k}\Omega$.

$$10\text{ k}\Omega \parallel 15\text{ k}\Omega = 5\text{ k}\Omega \cdot 2 \parallel 3 = 5\text{ k}\Omega \cdot \frac{6}{5} = 6\text{ k}\Omega$$

We have two separate circuits across the 2.1V source: one circuit is the 2.5mA source, and the other circuit is all the R's. We may solve these circuits separately, meaning we may ignore the 2.1V source.

circuit for finding V_1 :

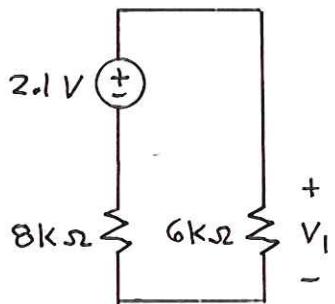

This is a V-divider:

$$V_1 = 2.1V \cdot \frac{6\text{k}\Omega}{6\text{k}\Omega + 8\text{k}\Omega} = 2.1V \cdot \frac{6}{14} = 2.1V \left(\frac{3}{7}\right)$$

or

$$V_1 = 0.9V$$