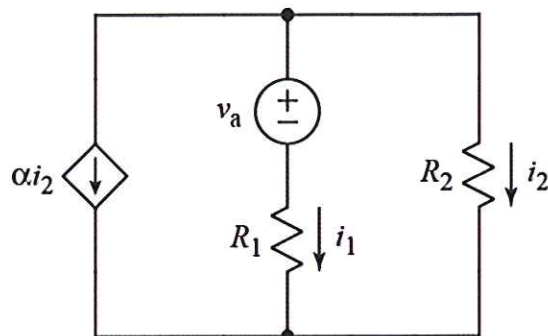


Ex:




Derive an expression for i_1 . The expression must not contain more than the circuit parameters v_a , R_1 , R_2 , and α . Note: $\alpha > 0$.

sol'n: We use Kirchhoff's laws.

have
We have no R 's in series having the same i ,
so we move on to a current sum at the
top node.

$$\alpha i_2 + i_1 + i_2 = 0 \text{ A}$$

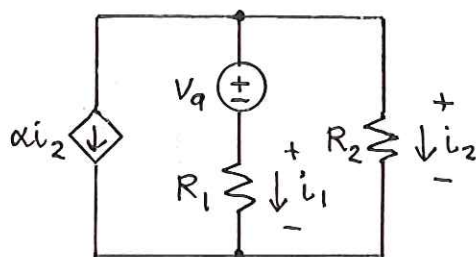We have one v -loop that doesn't pass
thru a current source. It is on the right.



The voltage drops are $v_1 = i_1 R_1$ and $v_2 = i_2 R_2$.

$$i_1 R_1 + v_a - i_2 R_2 = 0 \text{ V}$$

The current sum for the top node gives a second equation.

$$\alpha i_2 + i_1 + i_2 = 0 \text{ A}$$

We eliminate i_2 by using the second eq'n and substituting for i_2 in the first eq'n.

$$i_2(1 + \alpha) = -i_1$$

or

$$i_2 = \frac{-i_1}{1 + \alpha}$$

Substituting into the first eq'n, we have

$$i_1 R_1 + V_a - \frac{-i_1}{1 + \alpha} R_2 = 0 \text{ V}$$

or

$$i_1 \left(R_1 + \frac{R_2}{1 + \alpha} \right) = -V_a$$

or

$$i_1 = \frac{-V_a}{R_1 + \frac{R_2}{1 + \alpha}}$$