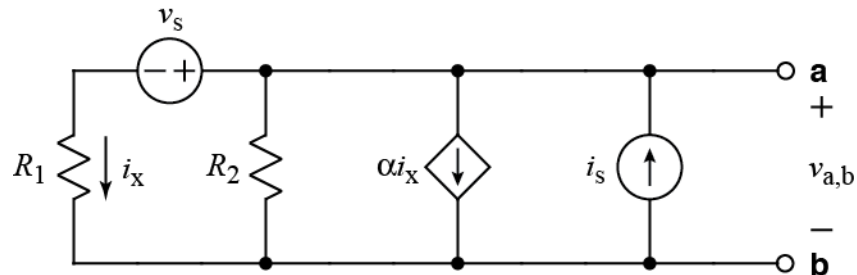


Ex:



- Using superposition, derive an expression for $v_{a,b}$ that contains no circuit quantities other than i_s , v_s , R_1 , R_2 , and α . Current i_x must not appear in your solution. **Note:** $\alpha \geq 0$.
- Make a consistency check on your expression for $v_{a,b}$ by setting resistors and sources to numerical values for which the value of $v_{a,b}$ is obvious. State the values of resistors and sources for your consistency check, and show that your expression for $v_{a,b}$ is satisfied for these values. (In other words, plug the values into your expression from part (a) and show that it agrees with the value from your consistency check.)
- Find the Thevenin equivalent circuit at terminals **a** and **b**. Express the Thevenin voltage, v_{Th} , and Thevenin resistance, R_{Th} in terms of no circuit quantities other than i_s , v_s , R_1 , R_2 , and α . i_x must not appear in your solution. **Note:** $\alpha \geq 0$.
- Determine the value of R_L connected from **a** to **b** that would absorb maximum power. Your answer must be written in terms of no circuit quantities other than i_s , v_s , R_1 , R_2 , and α .

SOL'N: a) In superposition, we turn on one independent source at a time, and we keep dependent sources on all the time.

Case I: Turn on v_s and turn off i_s (which becomes an open circuit).

Using the node-voltage method, we label the entire top wire to the right of v_s as $v_{a,b}$ and we label the bottom wire as reference. We then write an expression for i_x in terms of node-voltage $v_{a,b}$ and write an equation for the sum of currents out of the $v_{a,b}$ node.

$$i_x = \frac{v_{a,b1} - v_s}{R_1}$$

Now the sum-of-currents equation:

$$\frac{v_{a,b1} - v_s}{R_1} + \frac{v_{a,b1}}{R_2} + \alpha \frac{v_{a,b1} - v_s}{R_1} = 0 \text{ A}$$

We factor out $v_{a,b}$ and move constants to the other side of the equation:

$$v_{a,b1} \left(\frac{1}{R_1} + \frac{1}{R_2} + \alpha \frac{1}{R_1} \right) = v_s \left(\frac{1}{R_1} + \alpha \frac{1}{R_1} \right)$$

or

$$v_{a,b1} = v_s \frac{\frac{1+\alpha}{R_1}}{\frac{1+\alpha}{R_1} + \frac{1}{R_2}} = v_s \frac{(1+\alpha)R_2}{(1+\alpha)R_2 + R_1}$$

An alternative approach is to model the dependent source as a resistor, R_{eq} . We observe that $v_{a,b}$ may then be computed by using a voltage divider:

$$v_{a,b1} = v_s \frac{R_2 \parallel R_{Eq}}{R_1 + R_2 \parallel R_{Eq}}$$

To find the equivalent resistance of the dependent source, we observe that current i_x flows through R_2 in parallel with R_{eq} , so we have a current divider with currents $(1 + \alpha)i_x$ in R_2 and $-\alpha i_x$ in R_{eq} . The ratio of the currents is the inverse of the ratio of the resistances:

$$\frac{(1 + \alpha)i_x}{-\alpha i_x} = \frac{R_{eq}}{R_2}$$

or

$$R_{eq} = -R_2 \frac{1 + \alpha}{\alpha}$$

Now we can compute the parallel resistance of R_2 and R_{eq} .

$$R_2 \parallel R_{\text{eq}} = R_2 \parallel -\frac{R_2(1+\alpha)}{\alpha} = R_2 \cdot 1 \parallel -\frac{1+\alpha}{\alpha} = R_2 \frac{-\frac{1+\alpha}{\alpha}}{1-\frac{1+\alpha}{\alpha}}$$

or

$$R_2 \parallel R_{\text{eq}} = R_2 \frac{-(1+\alpha)}{\alpha - (1+\alpha)} = R_2(1+\alpha)$$

We use this result in the voltage divider, obtaining the same result as before:

$$v_{a,b1} = v_s \frac{R_2 \parallel R_{\text{Eq}}}{R_1 + R_2 \parallel R_{\text{Eq}}} = v_s \frac{R_2(1+\alpha)}{R_1 + R_2(1+\alpha)}$$

Case II: Turn off v_s (which becomes a wire) and turn on i_s .

Using node voltage, we proceed as in Case I but have simpler equations because v_s is off.

$$i_{x2} = \frac{v_{a,b2}}{R_1}$$

Now the sum-of-currents equation:

$$\frac{v_{a,b2}}{R_1} + \frac{v_{a,b2}}{R_2} + \alpha \frac{v_{a,b2}}{R_1} - i_s = 0 \text{ A}$$

We factor out $v_{a,b}$ and move constants to the other side of the equation:

$$v_{a,b2} \left(\frac{1}{R_1} + \frac{1}{R_2} + \alpha \frac{1}{R_1} \right) = i_s$$

or

$$v_{a,b2} [R_2(1+\alpha) + R_1] = i_s R_1 R_2$$

or

$$v_{a,b2} = i_s \frac{R_1 R_2}{(1+\alpha)R_2 + R_1}$$

An alternative approach is to model the dependent source as a resistor. We have the dependent source in parallel with R_1 , and we may calculate

the voltage across R_1 as $i_x R_1$. This voltage is also across the dependent source, allowing us to define an equivalent resistance for the dependent source using Ohm's law:

$$R_{Eq2} = \frac{i_x R_1}{\alpha i_x} = \frac{R_1}{\alpha}$$

It is interesting to note that this equivalent resistance is different than the equivalent resistance from Case I.

Now we have current source i_s in parallel with three resistors that we can combine into one resistance, and Ohm's law gives $v_{a,b2}$ in terms of current times resistance:

$$v_{a,b2} = i_s \cdot R_1 \parallel R_2 \parallel R_{Eq2} = i_s \cdot R_1 \parallel R_2 \parallel \frac{R_1}{\alpha}$$

or

$$v_{a,b2} = i_s \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{\alpha}{R_1}} = i_s \frac{R_1 R_2}{(1 + \alpha) R_2 + R_1}$$

Now we sum the two $v_{a,b}$'s to get the total $v_{a,b}$:

$$v_{a,b} = v_{a,b1} + v_{a,b2} = v_s \frac{R_2(1 + \alpha)}{R_1 + R_2(1 + \alpha)} + i_s \frac{R_1 R_2}{(1 + \alpha) R_2 + R_1}$$

- b) One consistency check is to set $v_s = 0$ V and set $\alpha = 1$, causing R_1 and the dependent source to be in parallel and have the same current, implying that they are the same resistance. In parallel, they have resistance $R_1/2$.

In this case, our circuit will have the following output voltage:

$$v_{a,b} = i_s \cdot \frac{R_1}{2} \parallel R_2 = i_s \cdot \frac{\frac{R_1}{2} R_2}{\frac{R_1}{2} + R_2} = i_s \cdot \frac{R_1 R_2}{R_1 + 2 R_2}$$

Now we check what value our formula from part (a) gives:

$$v_{a,b} = 0 \cdot \frac{R_2(1+1)}{R_1 + R_2(1+1)} + i_s \frac{R_1 R_2}{(1+1) R_2 + R_1} = i_s \frac{R_1 R_2}{2 R_2 + R_1}$$

This agrees with what we expect, so the consistency check is satisfied. Many other checks are possible.

- c) The voltage $v_{a,b}$ found in part (a) is the Thevenin equivalent voltage, so all we need now is R_{Th} . Perhaps the simplest way to find R_{Th} is to turn off the independent sources and connect a current source to the output. We then determine $v_{a,b}$ across the current source and use Ohm's law to find R_{Th} . For the source, we could use a value of i_s , in which case we have exactly Case II of the superposition from part (a). Our voltage will then be $v_{a,b2}$. Thus, we have the following value for R_{Th} :

$$R_{Th} = \frac{v_{a,b2}}{i_s} = \frac{i_s \frac{R_1 R_2}{(1 + \alpha)R_2 + R_1}}{i_s} = \frac{R_1 R_2}{(1 + \alpha)R_2 + R_1}$$

An alternative approach to finding R_{Th} is to use the short-circuit current, i_{sc} , that flows from **a** to **b** when a wire is connected across those terminals. In that case, the voltage on the top and bottom rails is zero. This means there is no voltage drop across R_2 , and we may ignore R_2 . Also, we have voltage $-v_s$ on the top end of R_1 , giving the current for i_x directly:

$$i_x = -\frac{v_s}{R_1}$$

Now we can write a current summation for the top rail:

$$-\frac{v_s}{R_1} + \alpha \left(-\frac{v_s}{R_1} \right) - i_s + i_{sc} = 0 \text{ A}$$

or

$$i_{sc} = \frac{v_s}{R_1} - \alpha \left(-\frac{v_s}{R_1} \right) + i_s = v_s \frac{1 + \alpha}{R_1} + i_s$$

Using this current, we find R_{Th} :

$$R_{Th} = \frac{v_{a,b}}{i_{sc}} = \frac{v_s \frac{R_2(1 + \alpha)}{R_1 + R_2(1 + \alpha)} + i_s \frac{R_1 R_2}{(1 + \alpha)R_2 + R_1}}{v_s \frac{1 + \alpha}{R_1} + i_s}$$

or

$$R_{\text{Th}} = \frac{v_{\text{a,b}}}{i_{\text{sc}}} = \frac{R_1 R_2}{R_1 + R_2(1 + \alpha)}$$

d) Maximum power is obtained by setting $R_L = R_{\text{Th}}$:

$$R_L = R_{\text{Th}} = \frac{R_1 R_2}{(1 + \alpha)R_2 + R_1}$$