
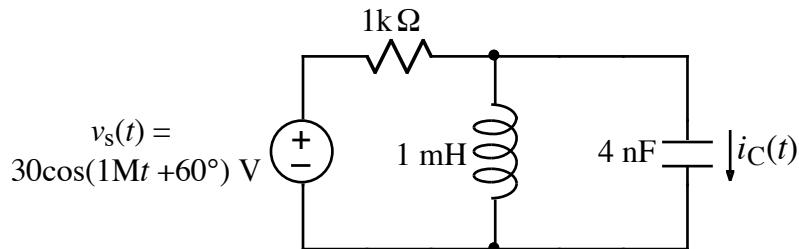


1.

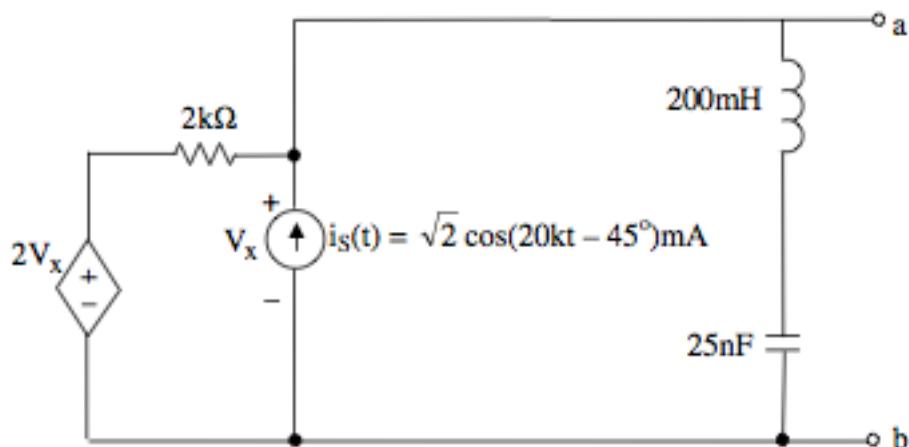


- a) Find the phasor value for $v_s(t)$.
- b) Draw the frequency-domain circuit diagram, including the phasor value for $v_s(t)$ and impedance values for components.
- 2. Find the phasor value for $i_C(t)$.
- 3.



- Draw a frequency-domain equivalent of the above circuit. Show a numerical phasor value for $i_s(t)$, and show numerical impedance values for R , L , and C . Label the dependent source appropriately.
- 4. Find the Thevenin equivalent (in the frequency domain) for the above circuit. Give the numerical phasor value for \mathbf{V}_{Th} and the numerical value for the impedance value of z_{Th} .

5.

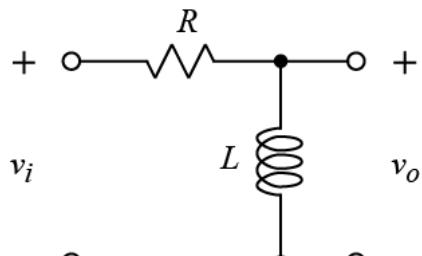

$$R = 20 \text{ k}\Omega \quad L = 200 \text{ nH}$$

- Determine the transfer function V_o/V_i .
- Plot $|H(j\omega)| \equiv |V_o / V_i|$ versus ω .
- Find the value of ω where $|\operatorname{Re}(H(j\omega))| = |\operatorname{Im}(H(j\omega))|$.