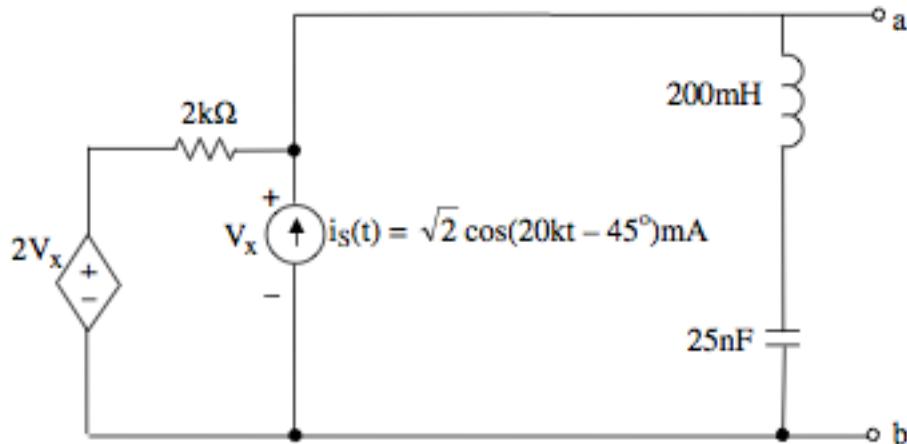





Ex:



- Draw a frequency-domain equivalent of the above circuit. Show a numerical phasor value for $i_s(t)$, and show numerical impedance values for R , L , and C . Label the dependent source appropriately.
- Find the Thevenin equivalent (in the frequency domain) for the above circuit. Give the numerical phasor value for \mathbf{V}_{Th} and the numerical value for the impedance value of z_{Th} .

SOL'N: a)

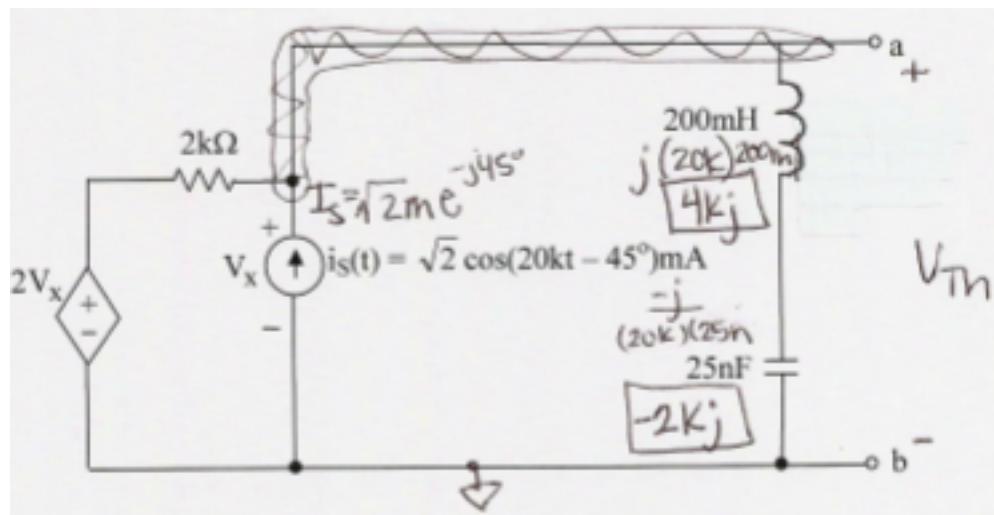

b)

$$\textcircled{1} \text{ Find } V_{Th}: \quad V_{Th} = V_x$$

Using node-voltage:


$$V_{Th} - \frac{2V_{Th}}{2k} + \frac{V_{Th}}{(4k-j-2k)} - \sqrt{2}me^{-j45^\circ} = 0$$

$$V_{Th} \left(\frac{j}{2k} - \frac{2j}{2k} + \frac{1}{2k} \right) = \sqrt{2}me^{-j45^\circ}$$

$$V_{Th} \left(\frac{1-j}{2k} \right) = \frac{\sqrt{2}me^{-j45^\circ} \cdot (2ke^{j90^\circ})}{(1-j)} = \frac{\sqrt{2}m(2k)e^{j45^\circ}}{\sqrt{2}e^{-j45^\circ}}$$

$$\boxed{V_{Th} = 2e^{j90^\circ}}$$

\textcircled{2} Find Z_{Th} :

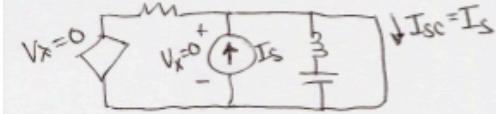

$$Z_{Th} = \frac{V_{Th}}{I_{Sc}} = \frac{2e^{j90^\circ}}{\sqrt{2}me^{-j45^\circ}}$$

$$\boxed{Z_{Th} = \frac{2k}{\sqrt{2}} e^{j135^\circ}}$$

$$V_{Th} = 2e^{j90^\circ} \text{ V}$$

$$z_{Th} = \frac{2k\Omega}{\sqrt{2}} e^{j135^\circ}$$